
EE40
Lecture 4
Josh Hug

6/28/2010

For those of you watching the webcast...

- We started today with a bunch of blackboard problems
- Hopefully they are legible online, let me know if they're not
- Scanned copies of my notes will be available online within a day or so

iClicker Logistics

- Everyone should go register their iClicker at iClicker.com
- Directions will be posted on the website, but it's pretty easy
- Your student ID is just the first letter of your first name, and then your entire last name, example:
 - John Quincy Onahal-Menchura would have ID “JONAHAL-MENCHURA”
 - Just to be safe, enter your ID in all capital letters

Late HW Logistics

- Reminder: You get 1 late homework with no penalty, and 1 dropped homework
- If you want to turn in a HW late, you must email the readers (CC the email to me as well)
 - Make sure “Late Homework” is in the title
- This will help us with book keeping of who has turned in a late homework
- Late homeworks are due by the next homework deadline
- If you don't email us, no late credit!

Midterm

- We still have 11 days until the first midterm (July 9th)
- Will cover everything up to and including what we do this Friday (July 2nd)
- You will be allowed one 8.5" x 11" sheet of paper with anything you want to write on it
 - Must be handwritten
 - You can keep it after the exam
- Each midterm you will be allowed to augment your equation collection by 1 additional sheet of paper

Lunch and Webcasts

- If you signed up for lunch, just come up at the end of class and we'll head out together after the post-lecture question battery
- A couple of lunch spots left if you didn't sign up
- Webcasts now available for lectures 1-3, should be linked in the same directory as the actual lectures
- Lecture 2 debugging ("in parallel" vs. "in parallel") coming after class

Important Dates this Week

- Lab #1 on Tuesday
 - Do pre-lab before lab (available on line)
 - Submit prelab in lab
- Lab #2 on Wednesday
- Make up lab to be scheduled if there is a need, most likely on Thursday
- HW2 posted, due Friday at 5 PM
 - It is long, get started early

Secret Office Hours

- By request, holding an extra office hour today
 - 477 Cory, 3:15PM-4:15 PM
- If you're behind and you can come, please do

iClicker HW1



- For those that turned in HW1, approximately how much time did you spend on homework 1?
 - A. 0-3 hours
 - B. 3-6 hours
 - C. 6-9 hours
 - D. 9-12 hours
 - E. More than 12 hours

iClicker HW1

- Did you guys work on the homework solo or with others?
 - A. I did the homework completely solo
 - B. I had some, but not much, interaction with others
 - C. Mostly alone, but then worked in Cory 240 with the impromptu last minute study group
 - D. Did homework solo, but then went over homework with a group that I'll probably work with again
 - E. Worked with a group that I'll probably work with again (this is ok!)

The Need for Dependent Sources

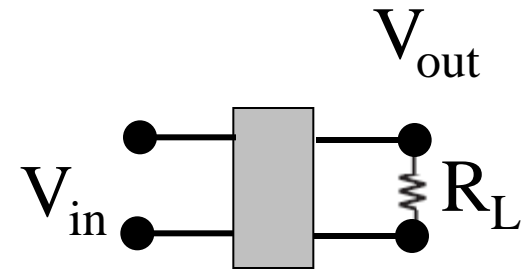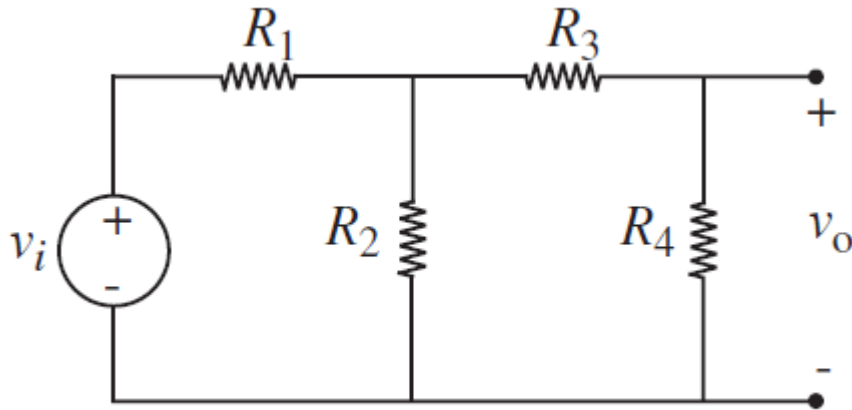- Suppose you build a circuit such that $v_o = v_i/1000$, to be used as a power supply



- E.g. $R_1 = 332.667\Omega$, $R_2 = R_3 = R_4 = 1\Omega$
- Consider what happens when you attach a load to the power supply, say a resistor

- $$V_{out} = \frac{R_L}{666.333 + 1000R_L} V_{in}$$



Doesn't work for:

A. Very high R_L


B. Very low R_L

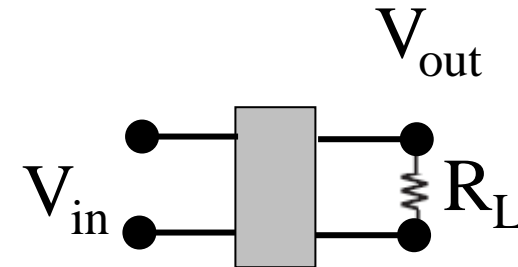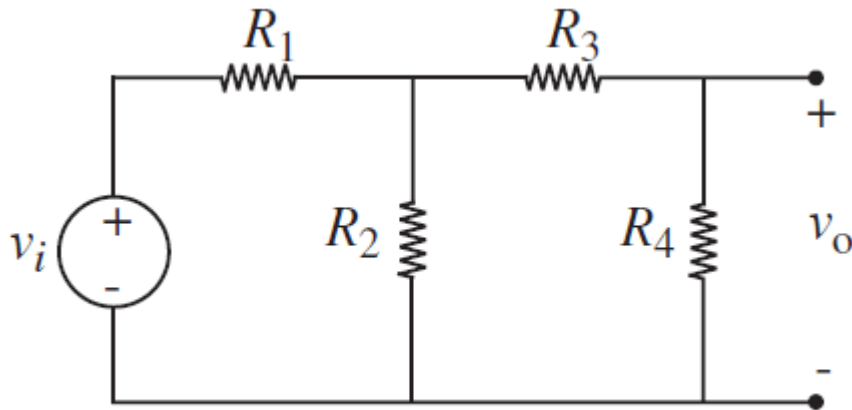C. Very high or low R_L

- $R_1=332.667 \Omega$, $R_2=R_3=R_4=1\Omega$



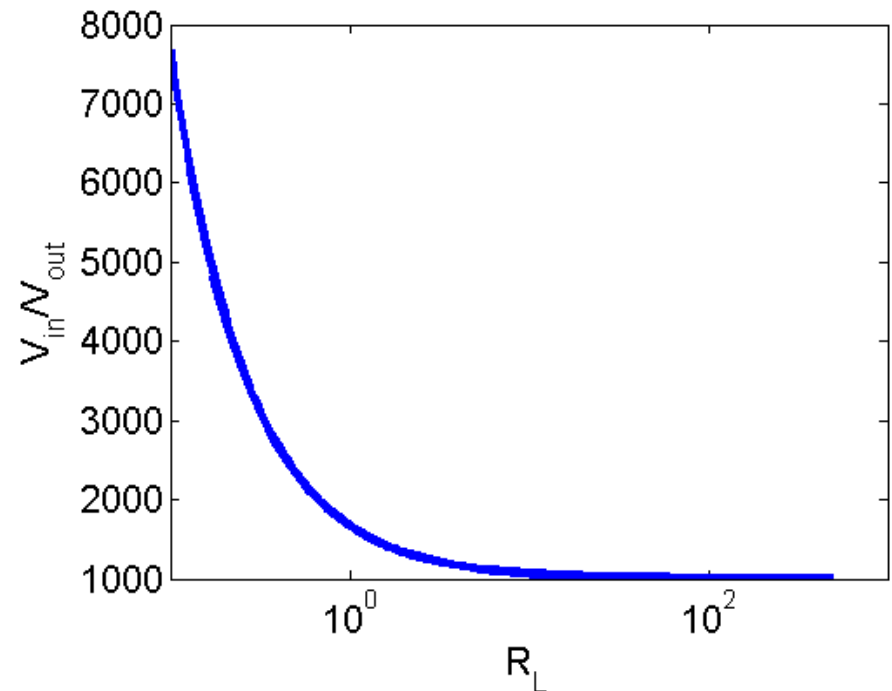- For $R_L < 10\Omega$ or so, we have distortion
- Can mitigate this distortion with different resistor values, but there's a better way



Building a Better Attenuator



- Using any ideal basic circuit element that we've discussed, what's the best possible circuit we can design so that $V_{\text{out}} = V_{\text{in}}/1000$?

Dependent Sources





- Dependent sources are great for decoupling circuits!
- Only one problem:
 - They don't exist

Operational Amplifiers

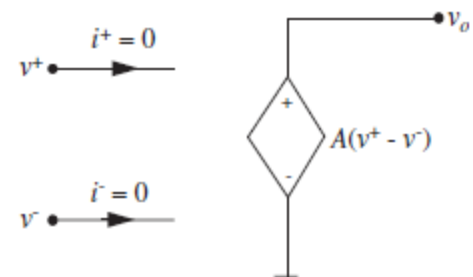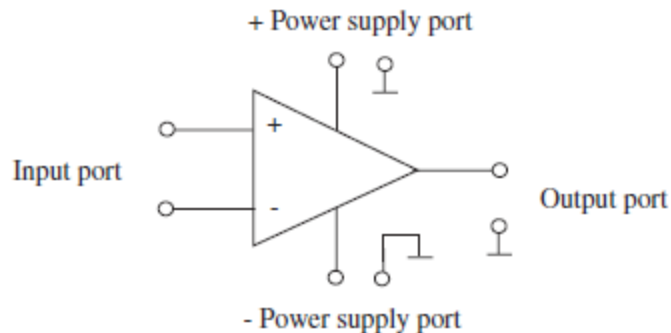- Dependent Sources are handy
 - Allows for decoupling
- Only one problem:
 - They don't exist
- The “Operational Amplifier” approximates an ideal voltage dependent voltage source
 - Very very cool circuits
 - Analog IC design is hard



Most Obvious Op-Amp Circuit

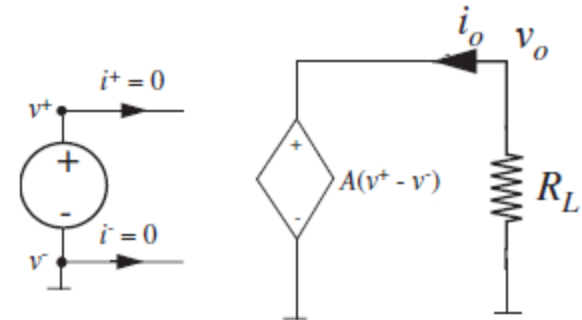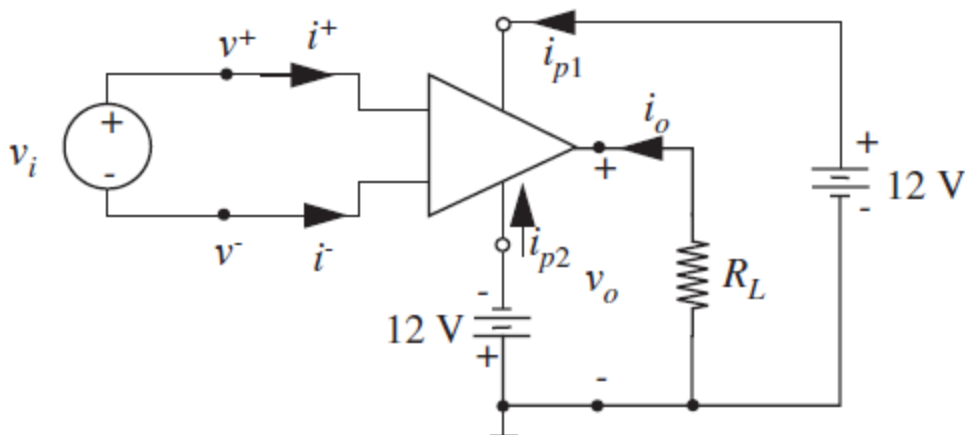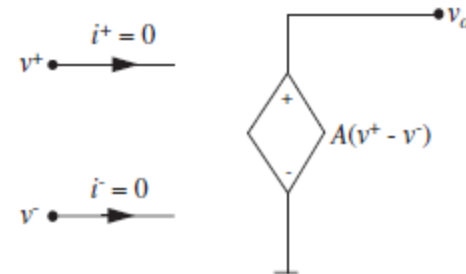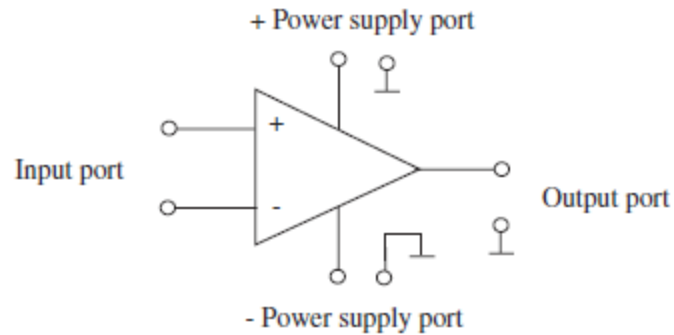


$$v_o = Av_i$$

One Problem


- The “open loop gain” A is:
 - Hard to reliably control during manufacturing
 - Typically very large ($A > 1,000,000$)
 - Fixed for a single device
- For example, if you needed $V_o = V_{in}/1000$ within 2%, you’d need a high quality op-amp with $A = 1/1000$
- Could spend a lot of time and money addressing these, but there is a better way

$$v_o = Av_i$$

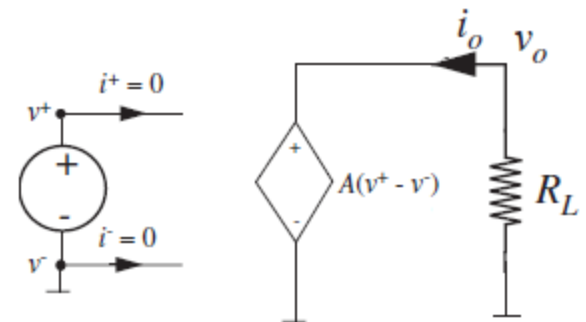


Feedback

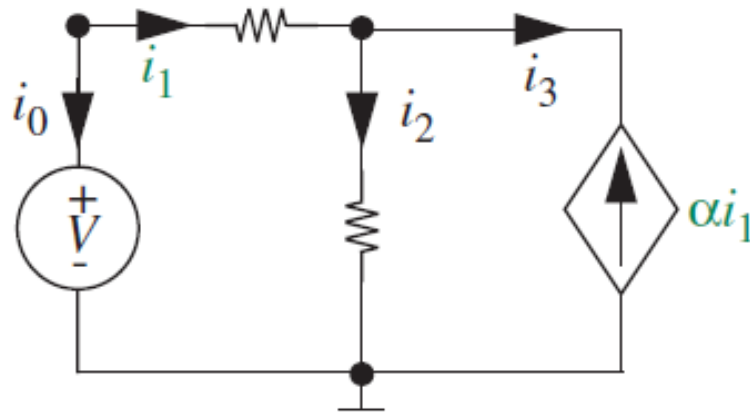- Recall before that I mentioned that dependent sources can provide feedback to their controlling input, e.g.:




- Remember also that these can be a little tricky to analyze

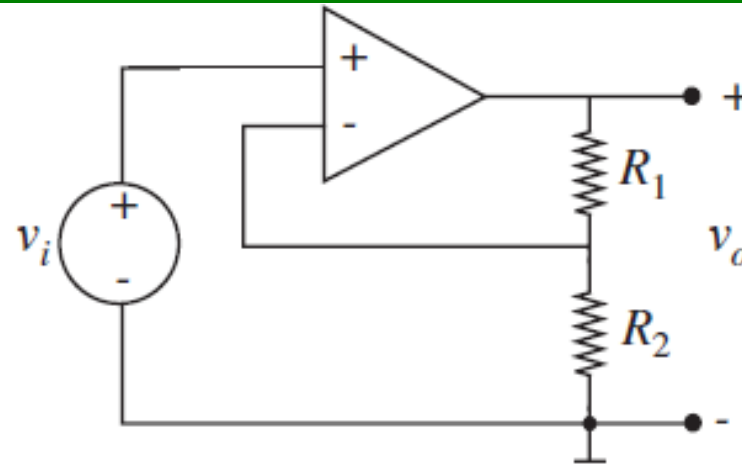Simple Op-Amp Circuit with Negative Feedback



(a)

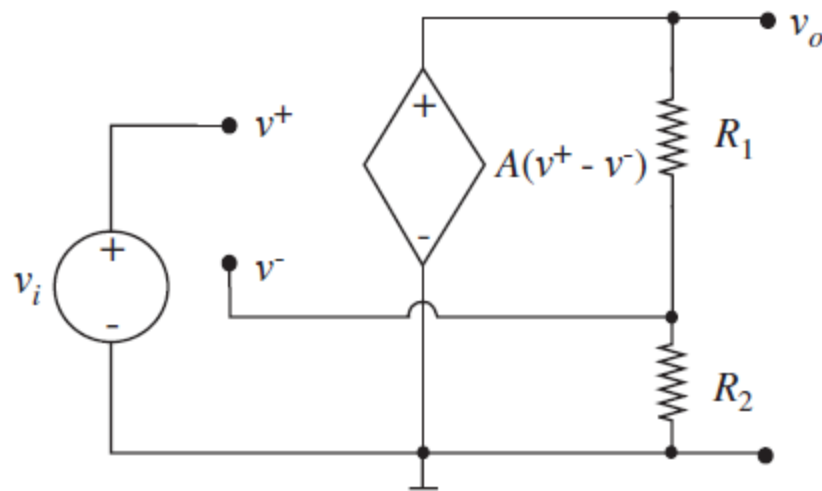

On the board:

$$v_o = \frac{Av_i}{1 + A \frac{R_2}{R_1 + R_2}}$$

Negative Feedback Op-Amp Circuit


$$v_o \equiv \frac{Av_i}{1 + A \frac{R_2}{R_1 + R_2}}$$

Assuming A is very big...

$$v_o \approx \frac{Av_i}{A \frac{R_2}{R_1 + R_2}}$$



$$v_o \approx \frac{v_i}{\frac{R_2}{R_1 + R_2}}$$
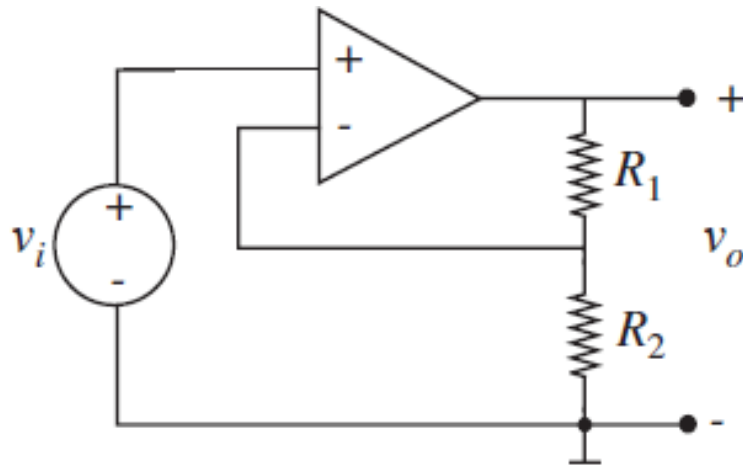
$$v_o \approx v_i \frac{R_1 + R_2}{R_2}$$



(a)


Op-Amp Circuit

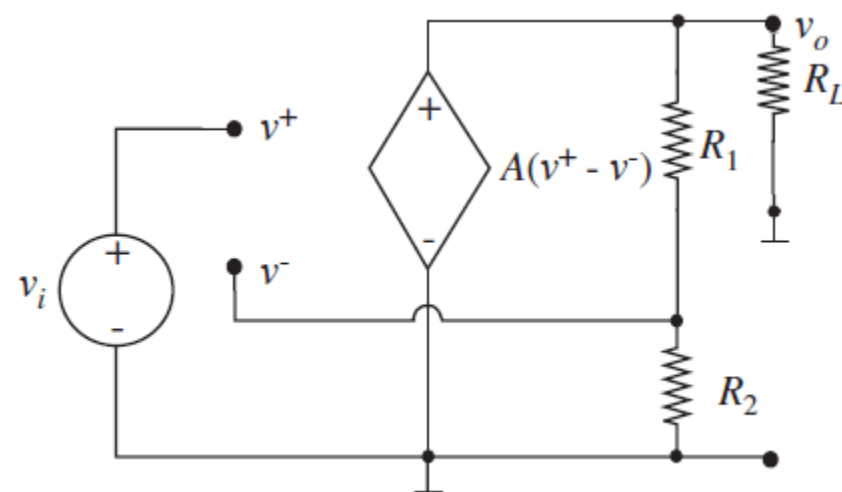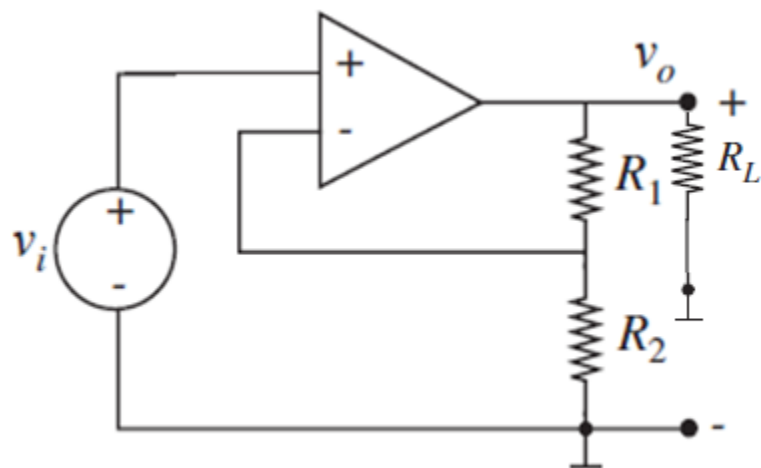

- Output voltage is independent of load!
- One op-amp fits all, just tweak your resistors!
- Output is independent of A !

$$v_o = v_i \frac{R_1 + R_2}{R_2}$$

Wait, so whoa, how did that happen?

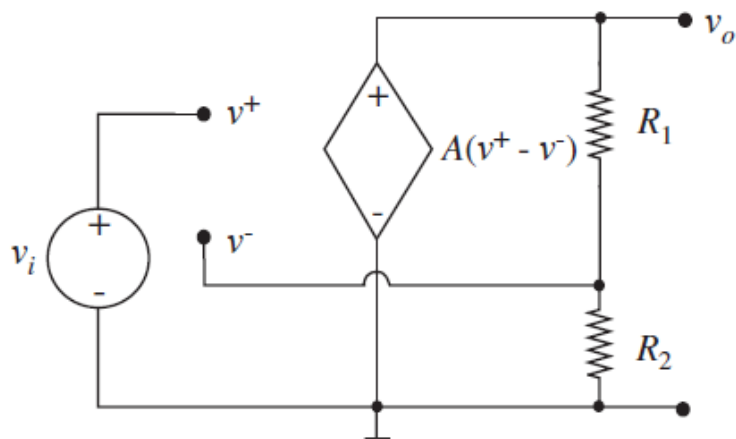

$$v_o = \frac{Av_i}{1 + A \frac{R_2}{R_1 + R_2}}$$

- Let's consider what happened to v^- :

$$v^- = \frac{Av_i}{1 + A \frac{R_2}{R_1 + R_2}} \times \frac{R_2}{R_1 + R_2}$$


$$v^- = v^+ \frac{AR_2}{R_1 + R_2 + AR_2}$$

and for large A ...

$$v^- = v^+ (1 + \varepsilon)$$

Where ε represents
some tiny number

The Voodoo of Analog Circuit Design

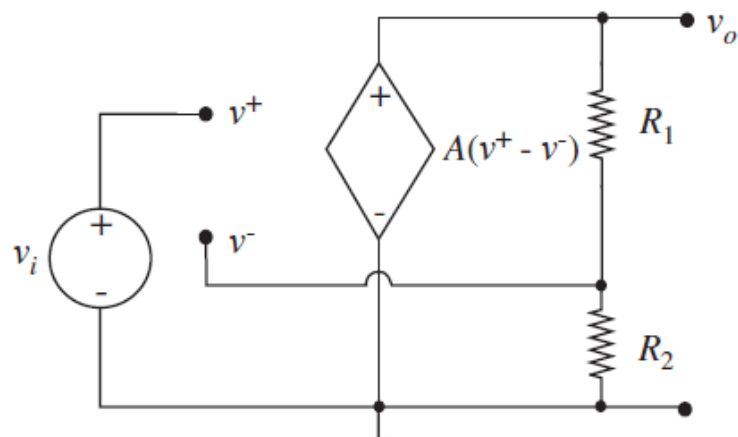

$$v_o = \frac{Av_i}{1 + A \frac{R_2}{R_1 + R_2}}$$

For large A:

$$v_o = v_i \frac{R_1 + R_2}{R_2}$$

$$v^- = v^+ (1 + \varepsilon)$$


- The “negative feedback” forces v^- to be extremely close to v^+
- This very tiny difference between v^- and v^+ gives us v_o

Consequence of Negative Feedback

- In any circuit where v_o is connected back to v^- (and not to v^+), we have the property that $v^- = v^+(1 + \varepsilon)$
- We'll approximate this by assuming that $v^- = v^+$
 - Of course it's not actually equal, otherwise the op-amp would not do anything
 - However with $A > 1,000,000$, this approximation is incredibly accurate
 - Less error from this approximation than component variation, temperature variation, etc.


Approach to Op-Amp Circuits

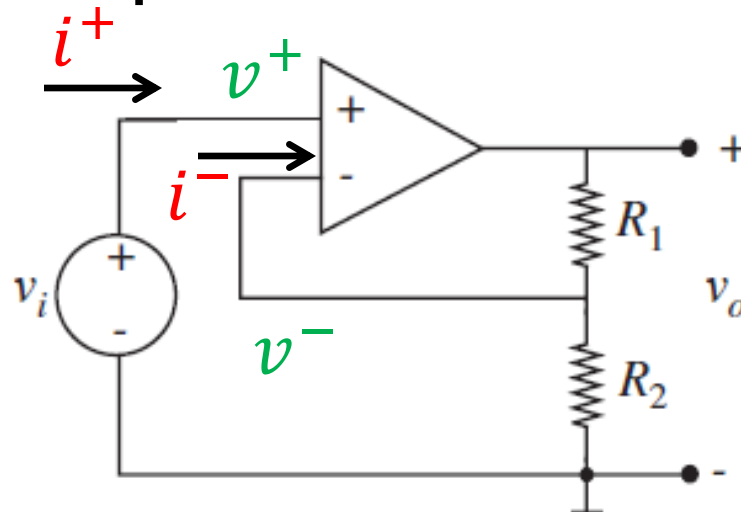- If there's only negative feedback:
 - Assume $v^+ = v^-$
 - Assume $i^+ = 0$ and $i^- = 0$ } “Summing-point constraint”
- If there's no feedback or positive feedback, replace the op-amp with equivalent dependent source and solve



(a)

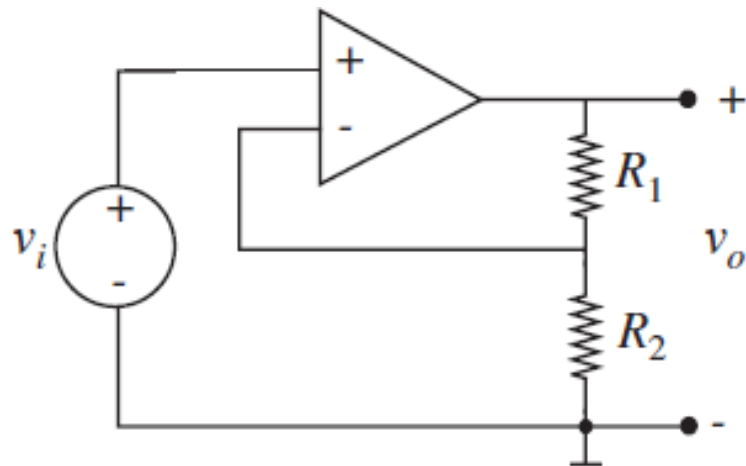Example using the Summing-Point Constraint



(a)

$$v^- = v^+ = v_i$$

$$i^- = 0, i^+ = 0$$

$$i_{R_2} = \frac{v^-}{R_2} = \frac{v_i}{R_2}$$

$$\begin{aligned} i_{R_1} &= i^- + i_{R_2} \\ &= i_{R_2} \\ &= \frac{v_i}{R_2} \end{aligned}$$

$$\begin{aligned} v_o &= v_i + i_{R_1} R_1 \\ &= v_i + v_i R_1 / R_2 \\ &= v_i \frac{R_1 + R_2}{R_2} \end{aligned}$$


Summing-Point Constraint

- You don't have to use the summing-point constraint
- However, it is **much** faster, albeit trickier
- This is where building your intuition helps, so you can see where to go next


Op-Amp Circuits

- There are a bunch of archetypical circuits, the one we've studied today is the “non-inverting amplifier”

Inverting amplifier

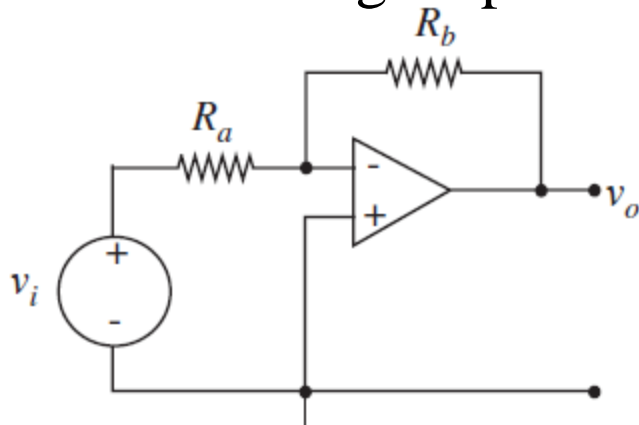


$$v_o = -\frac{R_b}{R_a} v_i$$

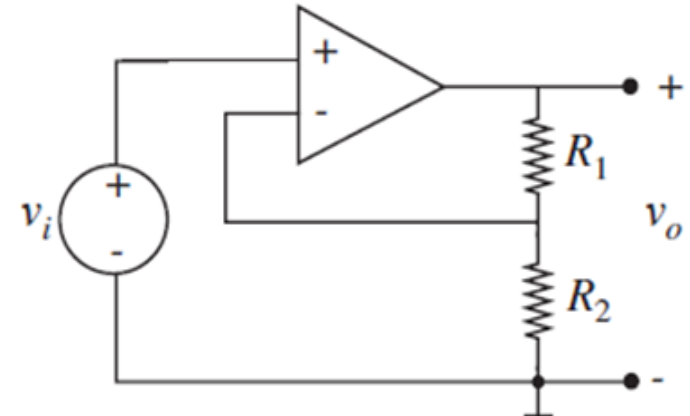

$$v_o = v_i \frac{R_1 + R_2}{R_2}$$

Voltage follower

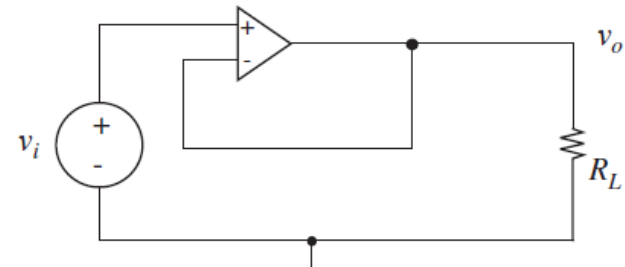

$$v_o = v_i$$

For Next Time

- Lots more op-amp circuits
- Useful for abstractions for analyzing and designing op-amp circuits
- Before we go, a couple of questions

Pacing

- Class Pacing
 - A. Way too slow
 - B. Too slow
 - C. Just right
 - D. Too fast
 - E. Way too fast


Blackboard

- PowerPoint vs. chalkboard
 - A. Almost always prefer PowerPoint
 - B. PowerPoint is slightly preferable
 - C. Whatever is fine
 - D. Chalkboard is a bit better
 - E. I'd prefer little to no PowerPoint

Extra Slides


Voltage Sources and the Node Voltage Method

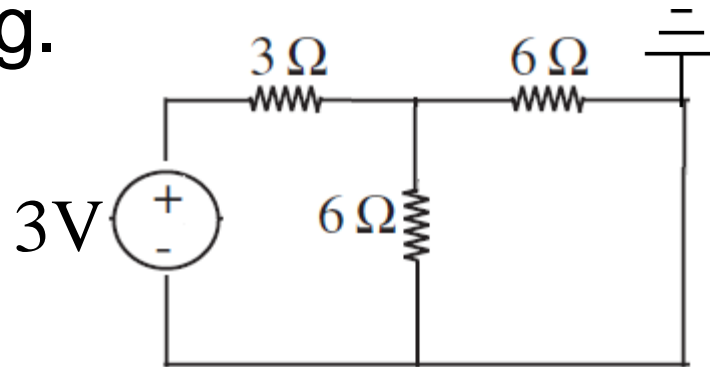- I didn't point this out explicitly, but whenever you have a voltage source that connects two nodes, and neither of those nodes are ground, e.g.



- Then you have to write KCL for the surface enclosing the two nodes (the book calls these surfaces “supernodes”)
- If a node has N voltage sources, the surface will include N nodes

Supernode Example

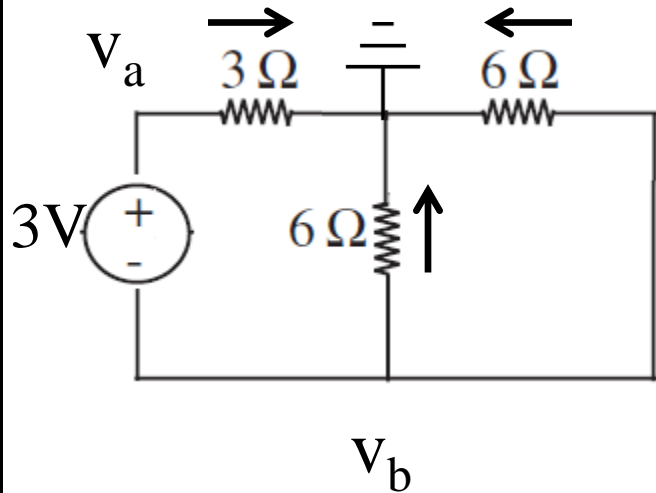

$$v_a = v_b + 3$$

Treat a and b together as one node, giving KCL:

$$\frac{v_a}{3} + \frac{v_b}{6} + \frac{v_a}{6} = 0$$

If you try to write KCL for node a or b alone, you'll get stuck when you try to write the current from a to b.

Note to Non-Native Speakers

- I try my hardest to make sure the language on homework problems and on tests is clear
- Please don't hesitate to ask me if something seems confusing