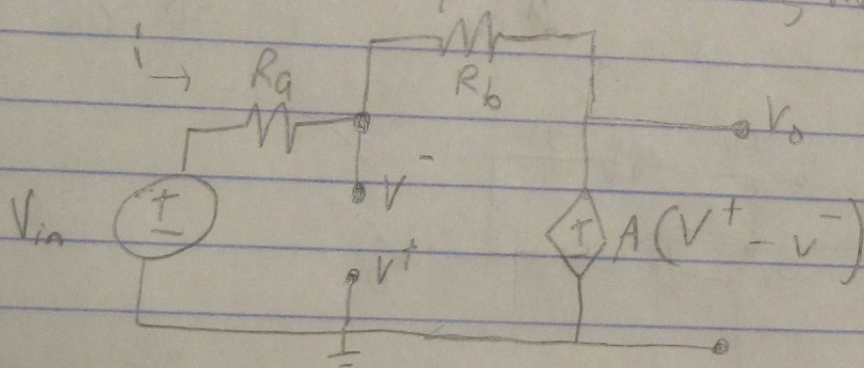


Goal, find $\frac{V_o}{V_{in}}$.

Two approaches:

(slower approach, but familiar)

#1: Replace w/ dependent source, and use node voltage!



where $A > 1,000,000$

Get V^+ for free, is ground, $V^+ = 0$.

Get V_o for free, source connected to ground, $V_o = A(V^+ - V^-) = -AV^-$

or $V^- = -V_o/A$

Node V^- :

$$\frac{V^- - V_{in}}{R_a} + \frac{V^- - V_o}{R_b} = 0$$

Substitute

$$\frac{-V_o/A - V_{in}}{R_a} + \frac{-V_o/A - V_o}{R_b} = 0$$

$$\frac{-V_o \cdot R_b}{A} - R_b \cdot V_{in} - \frac{V_o \cdot R_a}{A} - V_o \cdot R_a = 0$$

if A very large, then:


$$V_o \left(\frac{R_b}{A} + \frac{R_a}{A} + R_a \right) = -R_b \cdot V_{in}$$

$$V_o = \frac{R_b V_{in}}{\frac{R_b}{A} + \frac{R_a}{A} + R_a}$$

$$V_o = -\frac{R_b}{R_a} V_{in}$$

Approach


#2: Or with summing point constraint:

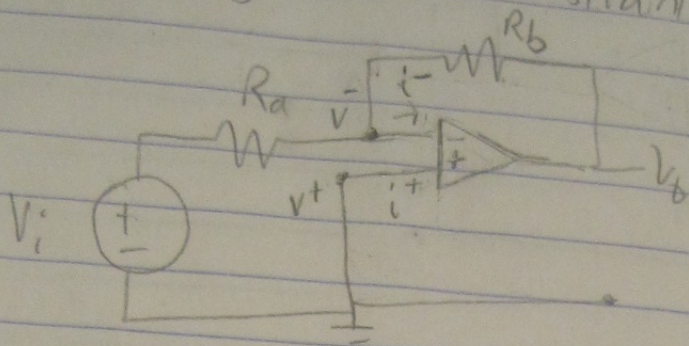

Summing point constraint gives us:

$$v^- = v^+ \\ \text{and } v^+ \text{ is ground, so } v^- = v^+ = 0.$$

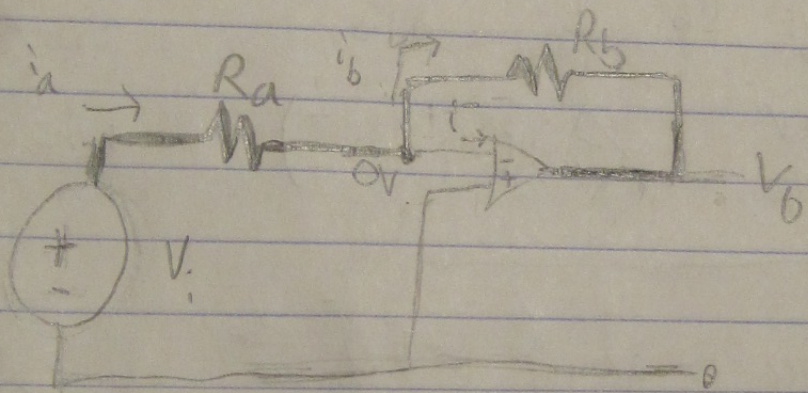Further, we also know $i^- = 0$ and $i^+ = 0$



Drew
op-amp
lightly here
to emphasize
that all it
does is force
 v^- to zero
and i^- and
 i^+ to zero.

$$i_a = i_b = \frac{V_i}{R_a}$$

$$V_o = 0 - i_b \cdot R_b = -\frac{R_b}{R_a} V_i$$

$$V_o = -\frac{R_b}{R_a} V_i$$

Done in 2 lines
No algebra.

Also, $i_b = i_a$
because
 i^- is zero
in case you
were confused.


That was a lot easier, right?

God bless you, Harold Stephen Black.

Another Summary

Point Constraint Example:

Find V_o

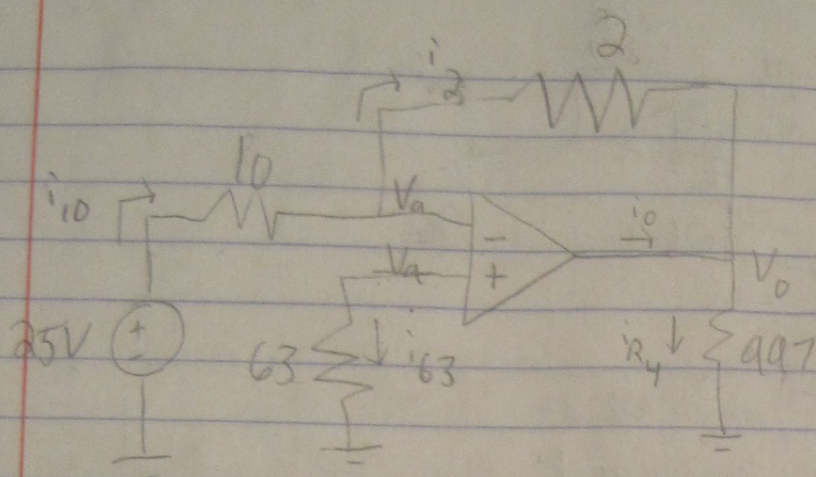

First, set

$$V^- = V^+ = V_a$$

Second, note that

$$i_{10} = i_2 \quad \text{and} \quad i_{63} = 0$$

Now can use node voltage if you don't want to think anymore, which will give you:

$$V^-: \frac{V_a - 25}{10} + \frac{V_a - V_o}{2} = 0$$

$$V^+: \frac{V_a}{63} = 0$$

Enough to solve, giving

$$V_a = 0$$

$$V_o = -5V$$

$$V_o: \frac{V_o - V_a}{2} + \frac{V_o}{997} + i_o = 0$$

just gives i_o which we don't need.

Note, i_o is usually not zero! Function of the load!

Faster way:


Just realize immediately that i_{63} is zero and so V_a must be zero.

Then realize that $i_{10} = i_2 = \frac{25V}{10\Omega} = 2.5A$, regardless of the 997Ω resistor or 2Ω resistor.

$$\text{Then, } V_o = 0 - 2.25 = -5V.$$

This is pretty much what we did on the previous page.

Composition of Op-Amps.

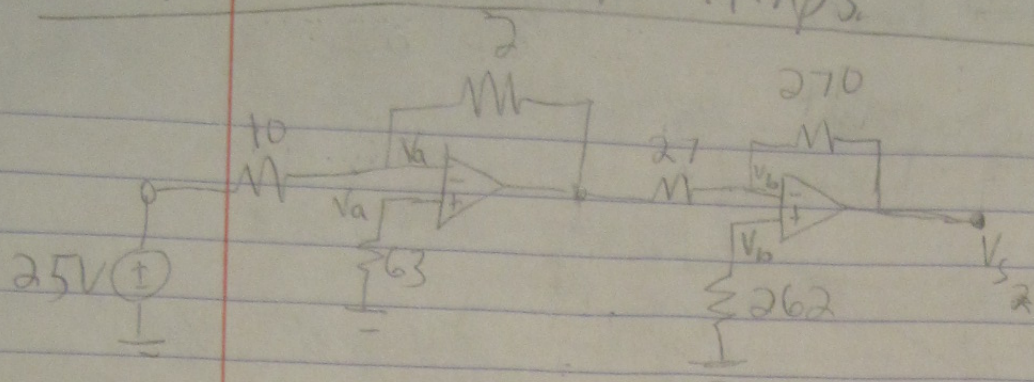

stage 1 stage 2
Summing point constraint:

$$V_{\text{stage}_2}^- = V_{\text{stage}_1}^+ = V_a = 0$$

because no current through 63Ω

$V_{\text{stage}_1}^-$ is

$$i_{10} = i_2 = \frac{25V}{10\Omega} = 2.5A$$

Just the - terminal of the op-amp in Stage 1

$$V_{s_1} = -2.5A \cdot 2\Omega = -5V$$

Seem familiar? Op-amps provide isolation. Doesn't matter what you connect them to!


Continuing w/ stage 2:

no current through 262Ω

$$V_{\text{stage}_2}^- = V_{\text{stage}_2}^+ = V_b = 0$$

$$i_{27} = \frac{V_{s_1} - 0}{27} = \frac{-5V}{27\Omega}$$
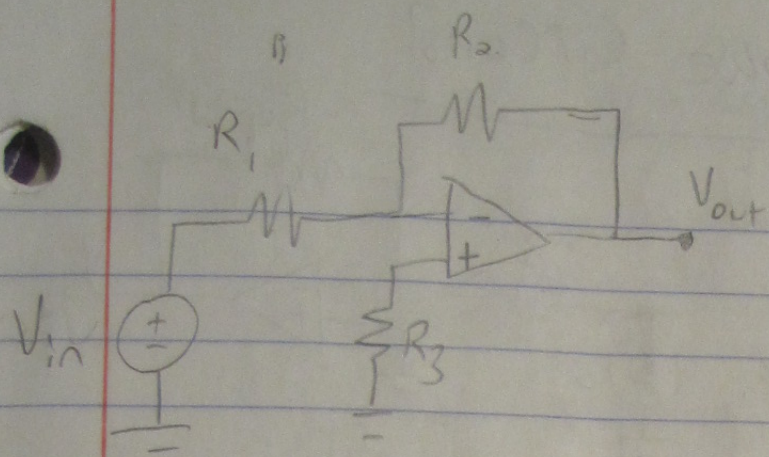
$$V_{s_2} = 0 - \frac{-5V}{27\Omega} \cdot 270\Omega = 50V$$




Earlier, we showed


$$V_{out} = -\frac{R_2}{R_1} \cdot V_{in}$$

It doesn't matter what kind of load we put at V_{out} , except that we shouldn't "cross the streams", i.e. connect a voltage source from V_{out} to ground.

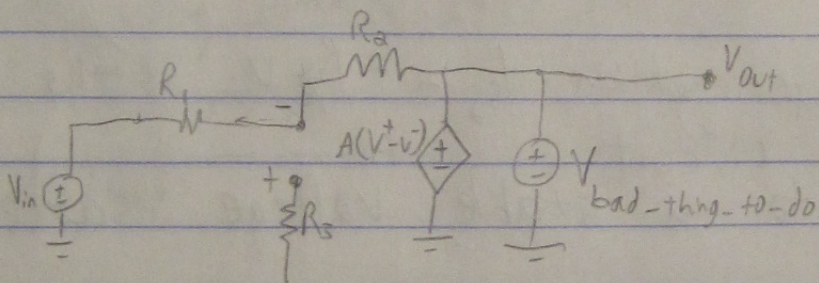Why? - because \rightarrow is a voltage source, and that would be 2 voltage sources in parallel:



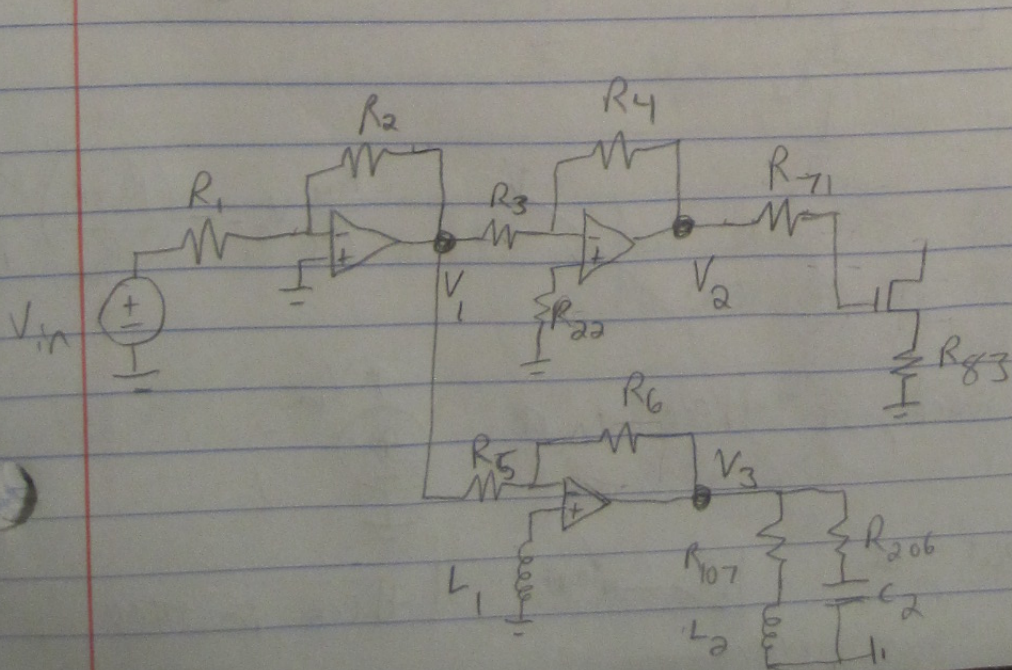So what this means is we can analyze each stage individually, and that loads don't matter, i.e.:




$$V_1 = -\frac{R_2}{R_1} \cdot V_{in}$$

$$V_2 = \frac{R_4 \cdot R_2}{R_1 \cdot R_3} V_{in}$$

$$V_3 = \frac{R_6 \cdot R_2}{R_5 \cdot R_1} V_{in}$$

When is it safe to compose circuits?

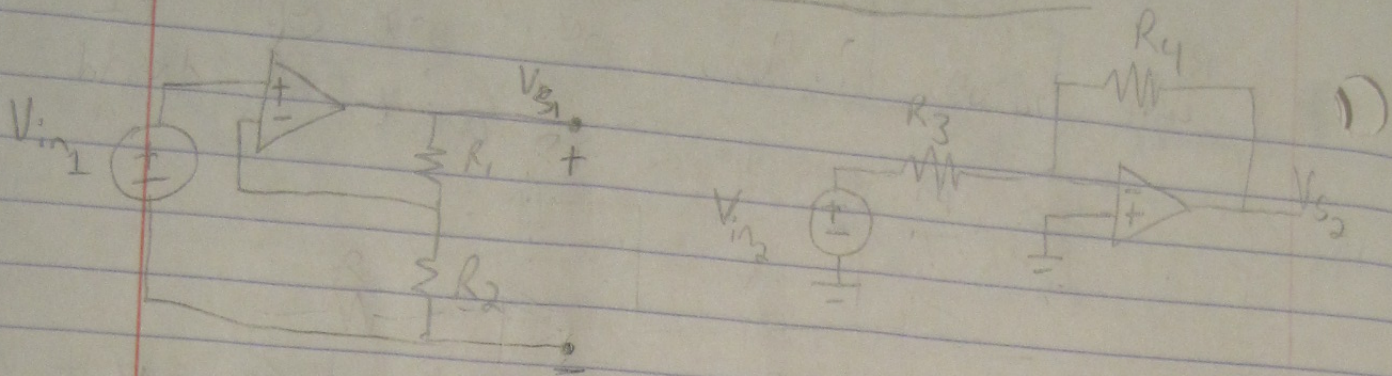


$$V_{s1} = V_{in1} \left(\frac{R_2 + R_1}{R_2} \right)$$

$$V_{s2} = -\frac{R_4}{R_3} V_{in2}$$

How do we know it's safe to compose these circuits?


Well our equation $V_{s2} = -\frac{R_4}{R_3} V_{in2}$ tells us how the circuit reacts to a stable voltage source.

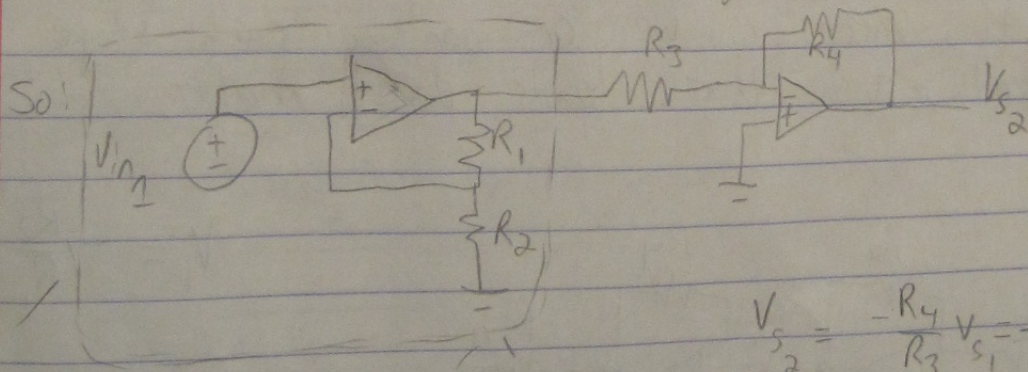
And what does our circuit on the left do? Provide a stable voltage source!




Acts like V_{in2}

$$V_{s2} = -\frac{R_4}{R_3} V_{s1} = -\left(\frac{R_2 + R_1}{R_2} \right) \frac{R_4}{R_3} V_{in}$$

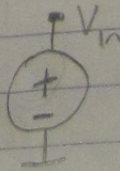In other words, if there's a 

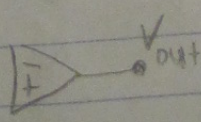you can put a  there instead if V_{out} is a known voltage

Multi-Source op-amp example

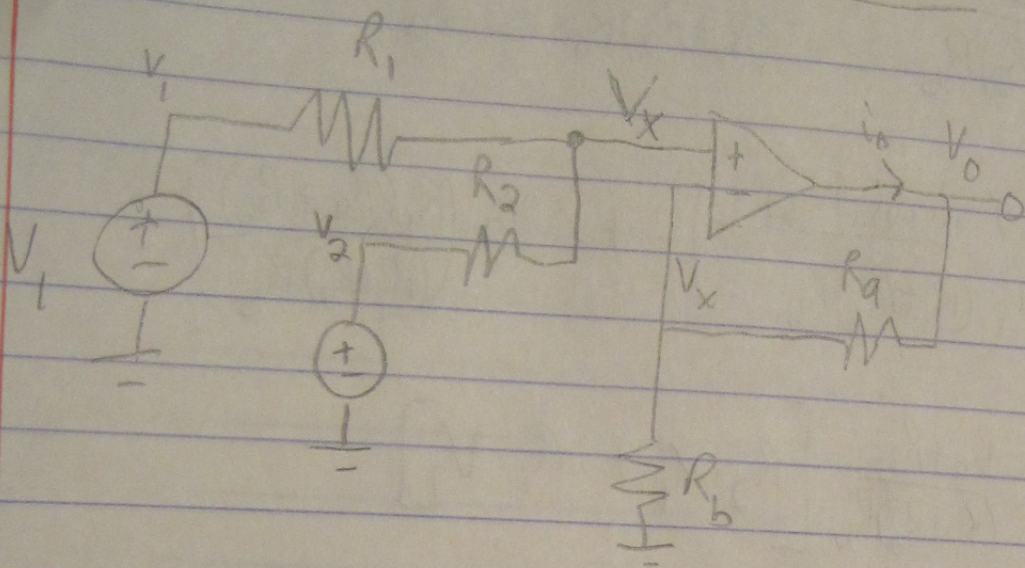

Goal: Find V_0
as function of V_1, V_2

Complicated enough that I'd suggest just using node voltage

First, using summing point and get that $V^+ = V^- = V_x$
and $i^+ = i^- = 0$.

Node Voltage:

$$V^+: \frac{V_x - V_1}{R_1} + \frac{V_x - V_2}{R_2} = 0 \quad V^-: \frac{V_x}{R_b} + \frac{V_x - V_0}{R_a} = 0$$

Again, you might be tempted to write KCL for V_0 , giving:

$$V_0: \frac{V_0 - V_x}{R_a} - i_o = 0$$

but all this gives you is i_o .
No need to do this!

KCL

$$\text{From KCL @ } V^+: V_x R_2 - V_1 R_2 + V_x R_1 - V_2 R_1 = 0$$

$$V_x = \frac{V_1 R_2 + V_2 R_1}{R_1 + R_2}$$

From KCL @ V^- :

$$\frac{V_1 R_2 + V_2 R_1}{(R_1 + R_2) R_b} + \frac{V_1 R_2 + V_2 R_1}{(R_1 + R_2) R_b} = \frac{V_o}{R_a}$$


$$V_o = V_1 \left(\frac{R_2 (R_a + R_b)}{(R_1 + R_2) R_b} \right) + V_2 \left(\frac{R_1 (R_a + R_b)}{(R_1 + R_2) R_b} \right)$$

$$= \frac{R_a + R_b}{(R_1 + R_2) R_b} [R_2 \cdot V_1 + R_1 \cdot V_2]$$

Performs weighted sums of voltages.

Provides a reliable way to add 2 voltages.
Can also make a subtractor.

iClicker Question:

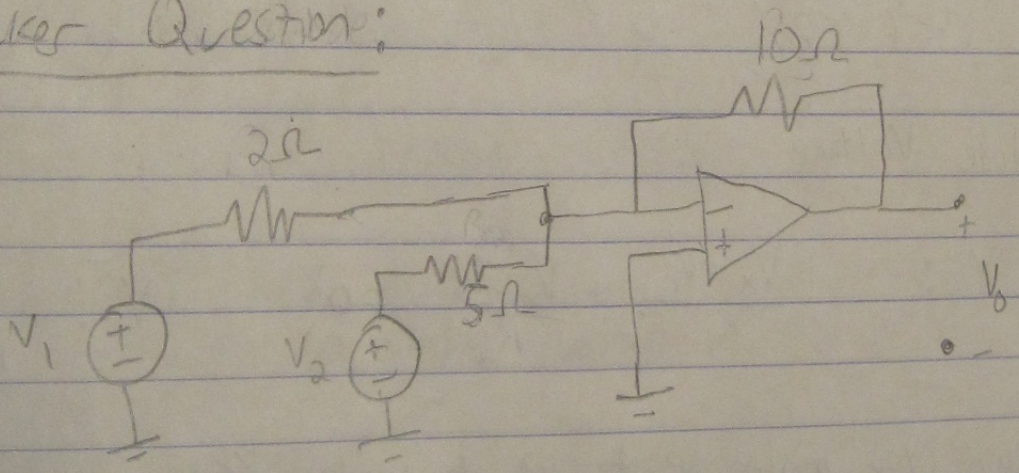

- A. $5V_1 + 2V_2$
- B. $2V_1 + 5V_2$
- C. $-5V_1 - 2V_2$
- D. $-2V_1 - 5V_2$
- E. $2V_1 - 5V_2$

$i_2 = \frac{V_1}{2}$ $i_5 = \frac{V_2}{5}$ $i_{10} = i_2 + i_5$ $V_o = -i_{10} \cdot 10 = -5V_1 - 2V_2$