
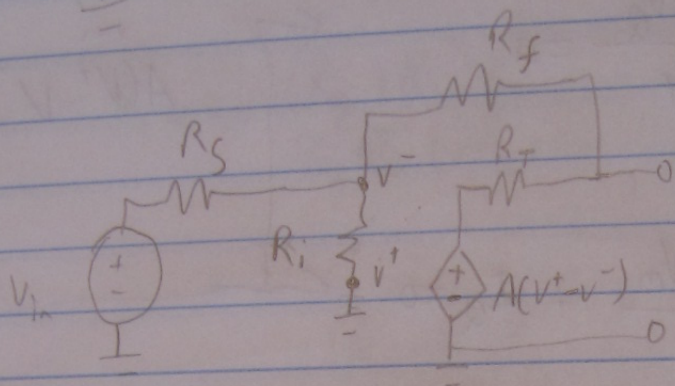


This is very dry stuff. Sorry!

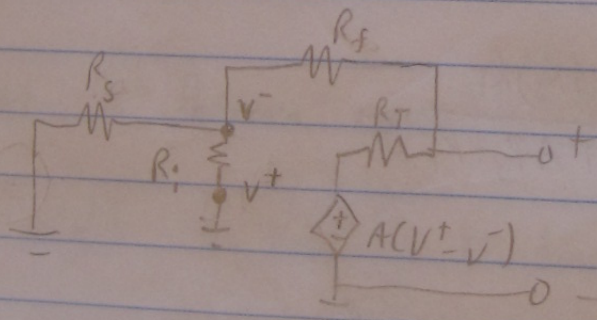


To find resistance looking into output terminals, we eliminate the INDEPENDENT voltage source.

Why? Well, output resistance is supposed to represent the resistance that a load is competing with, i.e. the Thevenin resistance of the Thevenin equivalent circuit



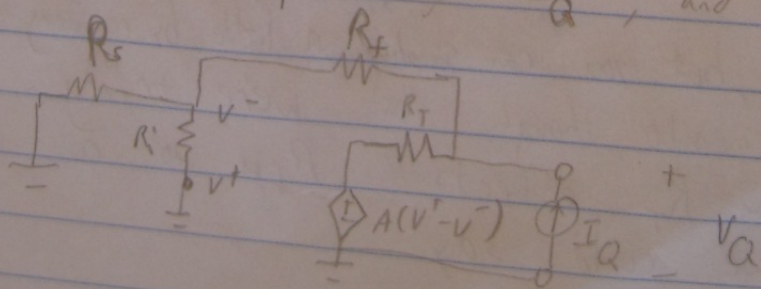Apply a made up source  $I_Q$ , and find  $V_Q$



For clarity,  $V^- = V_m$

$V^+ = V_p$

Node voltage:

$$\frac{V_m}{R_S} + \frac{V_m}{R_i} + \frac{V_m - V_Q}{R_f} = 0$$

$$A(V^+ - V^-) = -AV_m$$

$$\frac{V_Q + AV_m}{R_T} + \frac{V_Q - V_m}{R_f} + I_Q = 0$$

Goal: Find  $\frac{V_Q}{I_Q} = R_{TH}$

Can we use summing point constraint?  
No! Node voltage equations get stupid since  $V_m = 0$   
- Intuitively: We care about the minor deviation when computing their resistance.

In practical circuits,  $R_i$  is tiny compared to  $R_f$  and  $R_S$ .  
 $R_i \sim 10^{12} \Omega$ , so unless you're using resistors made of glass, you're good. Thus we can set  $V_m/R_i = 0$ .

Lots of Algebra:

$$V_Q = \frac{I_Q (R_S + R_S) R_T}{R_f + R_S + A R_S R_T}$$

$$R_{TH} = \frac{(R_S + R_S) R_T}{R_f + R_S + A R_S R_T}$$

This answer is fine, but you can simplify a little by considering what happens as  $A$  gets large. Remember, though, that we're trying to understand how  $R_T$  affects  $R_{TH}$ . So as  $A$  gets large, we could say

$$\frac{(R_S + R_S) R_T}{R_f + R_S + A R_S R_T} \rightarrow 0$$

, but that's boring and just means that strong enough amplification can overcome  $R_T$ .

So, let's instead consider what happens as  $A$  is *big*, but not *too* big, enough.

$$R_{TH} = \frac{(R_f + R_s) R_T}{R_s + R_s + A R_s + R_T}$$

$$R_f + R_s + A R_s + R_T \approx A R_s$$

$$R_{TH} \approx \frac{(R_f + R_s) R_T}{A R_s} = \frac{R_T}{A \frac{R_s}{R_f + R_s}}$$


Typical  $R_T$  is  $1,000 \Omega$ . For  $A = 10^6$ ,  $R_s = 10^5$ ,  $R_f = 10^4$

$$R_{TH} = \frac{1,000}{10^6 \cdot \frac{10^4}{10^5 + 10^4}} \approx 10^{-2} = 0.01 \Omega$$

Not too shabby

What is Thevenin equivalent circuit?

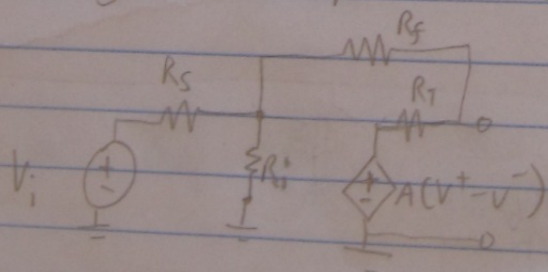You might be tempted to find  $V_{oc}$  of:



And you could, giving the most accurate answer:


$$V_{oc} = \frac{-(A R_s - R_T) V_i}{R_s + R_s + A R_s + R_T}$$

which in the large  $A$  limit, gives our summing point constraint answer:


$$V_{oc} = -\frac{R_f}{R_s} V_i$$

Thus our Thevenin circuit, assuming very large  $R_i$  and  $A$  is:
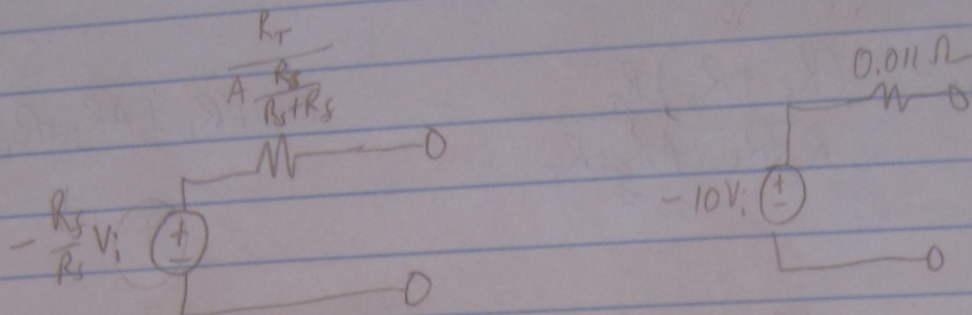
$$A = 10^6 \quad R_f = 10^5 \quad R_s = 10^4 \quad R_T = 10^3$$




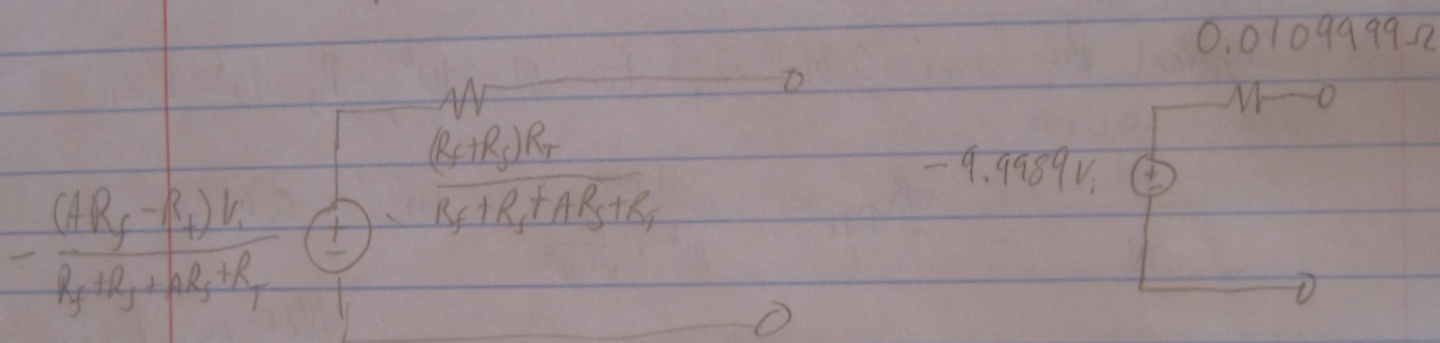Or if we want to be really accurate and consider what happens if  $A$  isn't "big enough":




Unless a problem specifically says otherwise, assume your op-amp is ideal.

Input Resistance

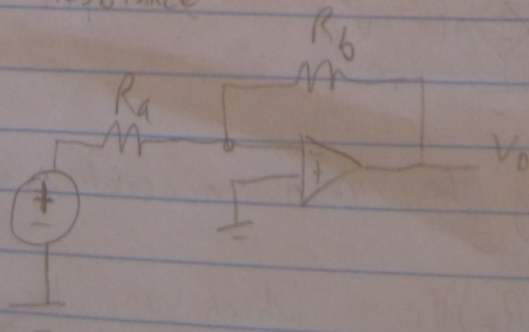


Find input resistance of ideal op-amp.

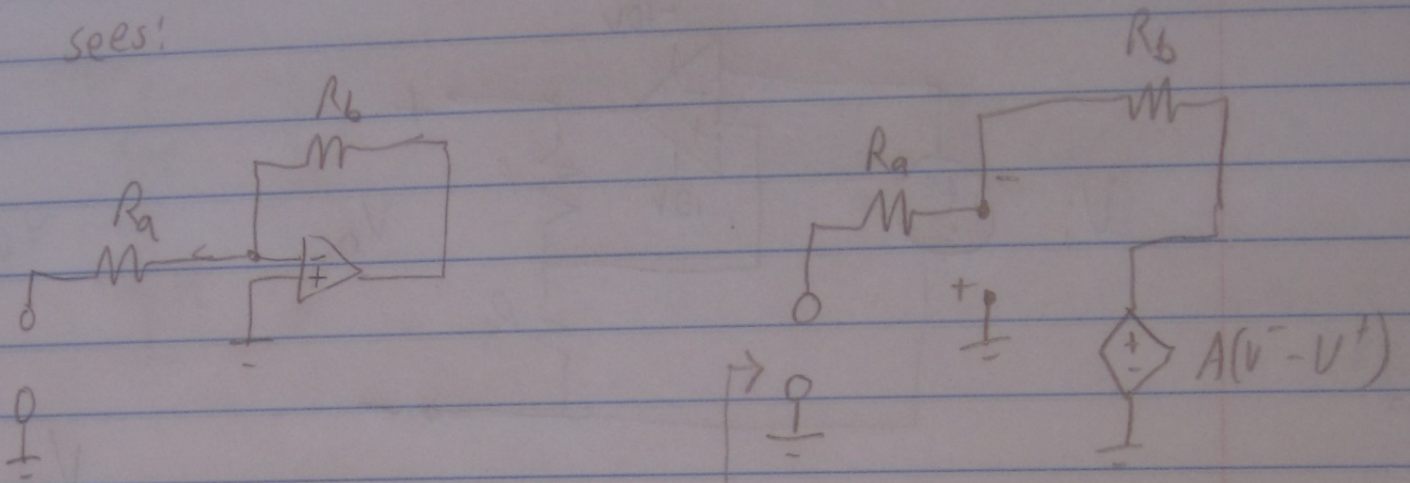We're interested in the resistance that the input voltage source sees!



Want  $R_{eq}$

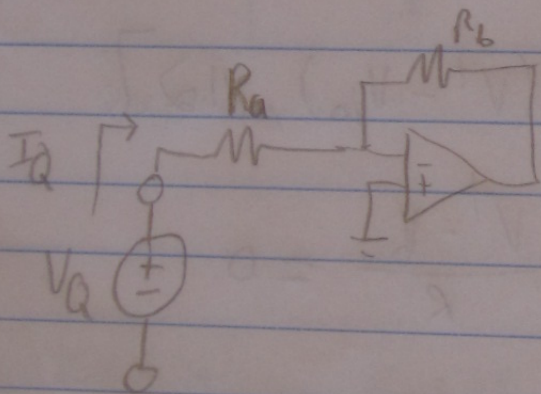Keep in mind that finding  $R_{eq}$  is the same as applying a made up voltage  $V_a$  and finding  $I_a$ , i.e.




which for ideal op-amp is just  $I_a = \frac{V_a}{R_a}$

$$\text{So } R_{eq} = \frac{V_a}{I_a} = \frac{V_a}{V_a/R_a} = \boxed{R_a} \quad \text{Easy!}$$

Can repeat for non-ideal op-amp, but I won't. See Sec. 15.42 for the non-ideal case.


# Positive Feedback:

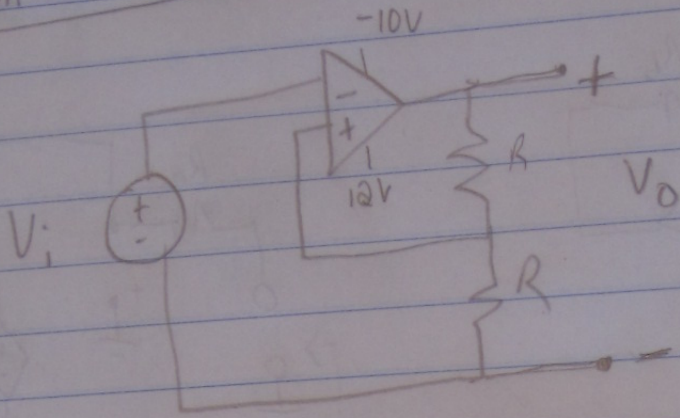

F  
-10, 12

$$V_{min} = -10V$$


$$V_{max} = 12V$$

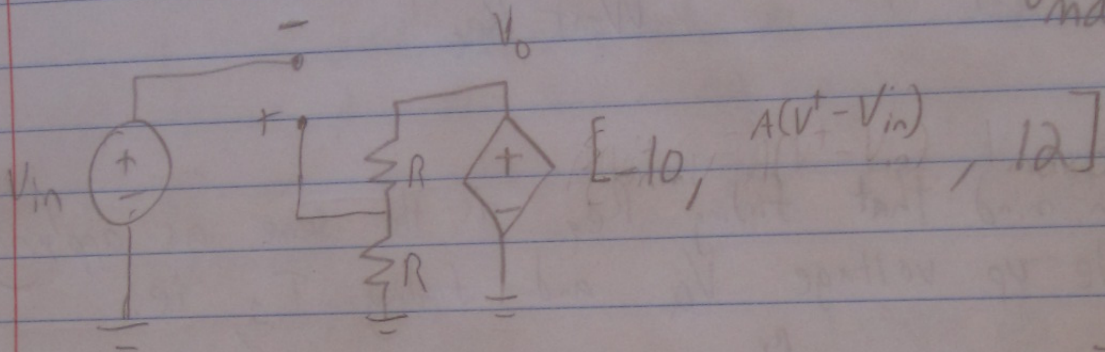

$$V_o = [-10, A(V^+ - V_{in}), 12]$$

$$V^+ \text{ node: } \frac{V^+}{R} + \frac{V^+ - V_o}{R} = 0$$
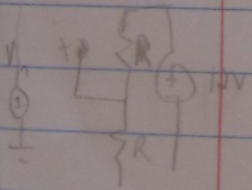
$$\frac{V^+}{R} + \frac{V^+ - [-10, A(V^+ - V_{in}), 12]}{R} = 0$$




$$V^+ (2 - A) = [-10, A(V^+ - V_{in}), 12]$$


$$V^+ = \frac{[-10, A(V^+ - V_{in}), 12]}{2 - A}$$

Step back and think!

Consider  $V_{in} = 0$ :

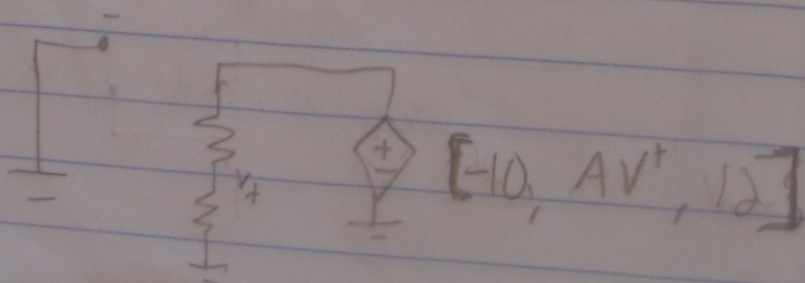

If  $V^+ = +5V$

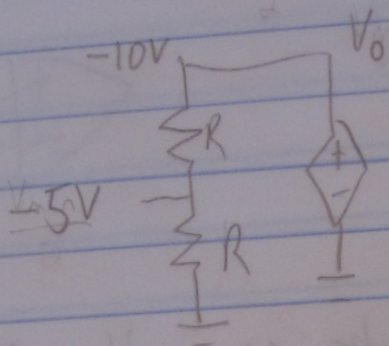


Voltage divider says  $V_0 = -10V$   
 Op-amp says:

$$V_0 = [-10V, -5A, 12V] = 10V$$

gain not amps!

Everything is consistent!

If  $V^+ = -6V$

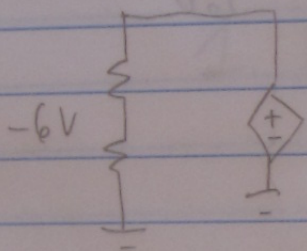


Voltage divider says  $V_0 = -12V$

Op-amp says:


$$V_0 = [-10V, -6A, 12V] = -10V$$

disagreement

Interestingly, if we have:

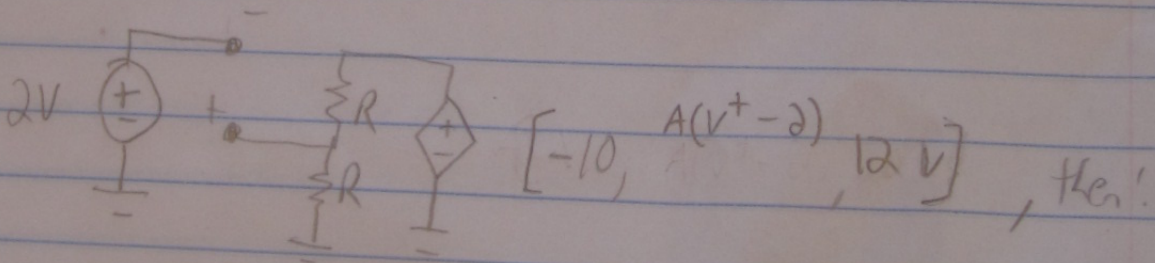

If  $V^+ = -5V$

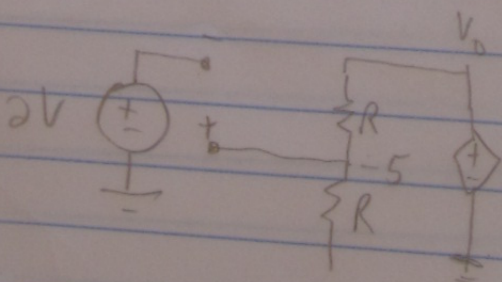


Current divider says  $V_0 = -10V$

Op-amp says:

$$[-10, A(-7), 10V] = -10V$$

OK!

And if we assume  $V^+ = 6V$

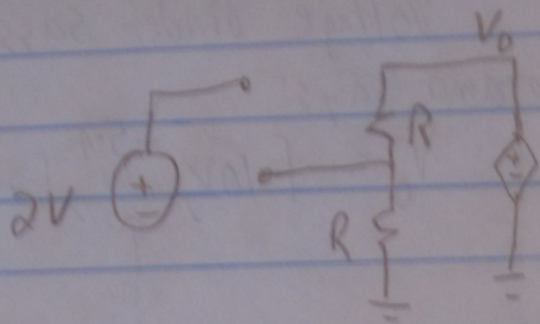

Current divider says  $V_0 = 12V$   
op amp says:

$$[-10, A \cdot (3V), 12] = 12V$$

Consistent!  $V^+$  can be  $-5V$  or  $6V$ .

