
EE40
Lecture 6
Josh Hug

7/2/2010

General Info

- HW2 due today at 5PM
- HW3 out, due TUESDAY at 2PM
- There will be an optional pre-midterm HW available Tuesday
- No lecture Monday
- Labs as usual on Tuesday
- No lab Wednesday
- Midterm next Friday in class
 - **12:10-1:30 [be on time!]**
 - No electronic devices
 - One 8.5"x11" (or A4) sheet of paper
 - Handwritten anything you want, both sides

Op-Amps – How Good Are They Exactly?


- We've been studying ideal op-amps
- Of course, real Op-Amps aren't perfect
 - For example, you can't drive every device in the universe from a real op-amp
- How do we precisely state the quality of a voltage source?
 - Look at its Thevenin equivalent
 - Lower Thevenin resistance is better

Example: Batteries

- Real voltage sources, like batteries, have a limit to how much current they can draw
 - Called “internal resistance”
 - This internal resistance often varies with charge status, load attached, temperature, and more
 - Just like Thevenin resistance

e.g., a car battery supplies 12 Volts, and can supply at most 200 amps, what is its internal resistance?

$$12\text{V}/200\text{A}=0.06\Omega$$

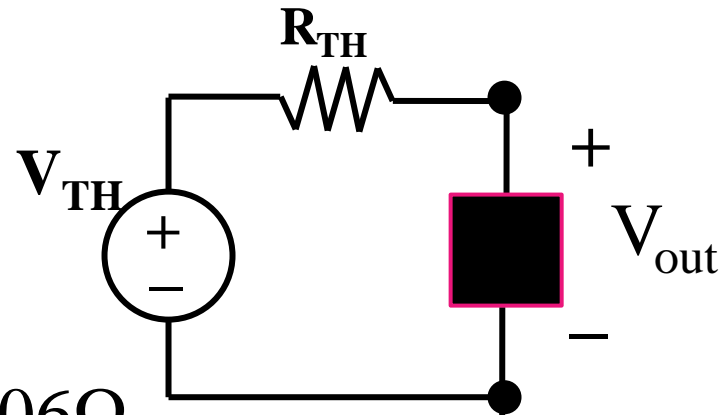

Measuring the Quality of a Source


- If you attach a resistive load, then the output voltage is:

$$- V_{out} = \frac{R_L}{R_L + R_{TH}} V_{TH}$$

- If you want V_{out} to be 99% of V_{TH} , then:

$$- \frac{99}{100} V_{TH} = \frac{R_L}{R_L + R_{TH}} V_{TH}$$

$$- R_L = 99R_{TH}$$


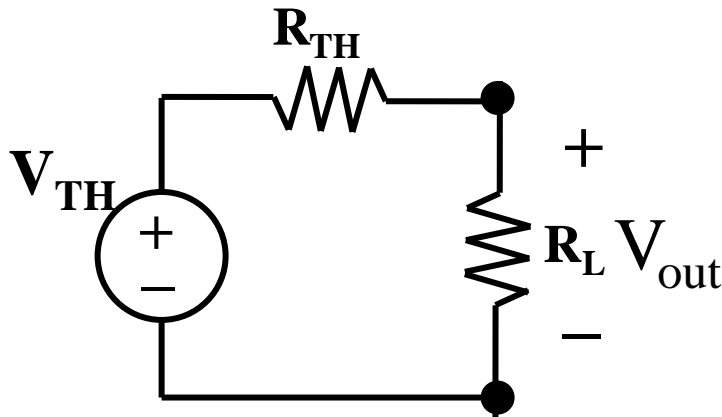


So basically, for loads which are more than 99 times the Thevenin resistance, you get >99% of the Thevenin voltage



Lower R_{TH} is better, can handle smaller loads

Source Quality Example

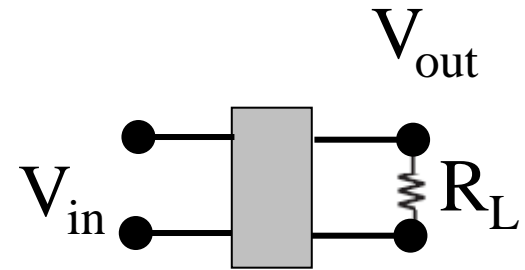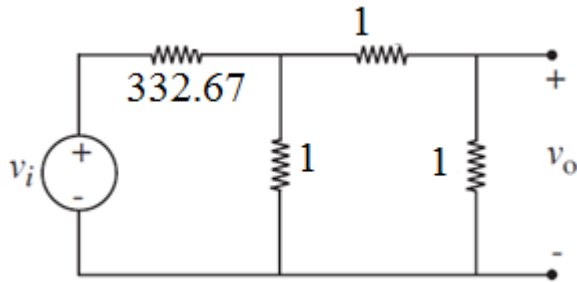- Everyone's favorite resistive power supply again, $v_o = v_i / 1000$



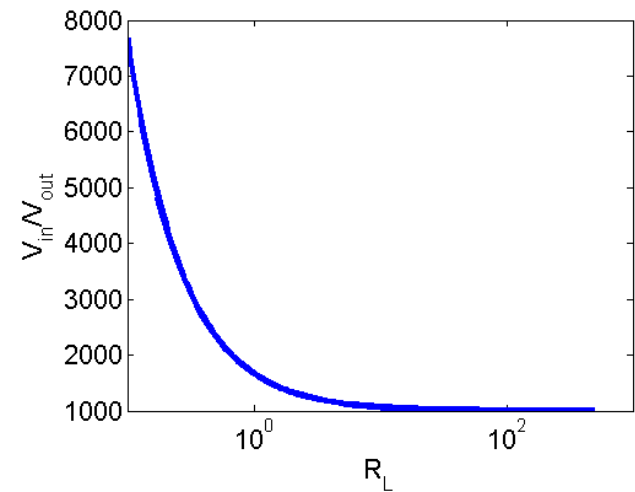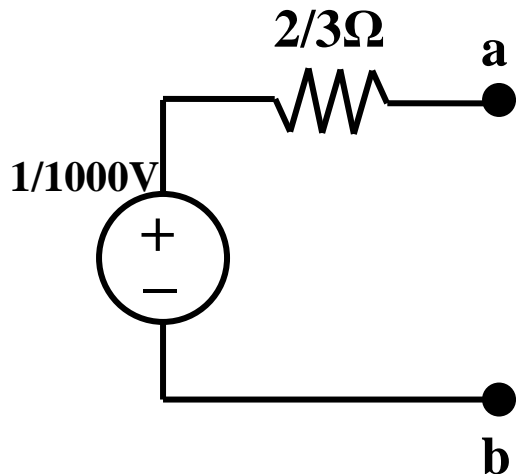- $$V_{out} = \frac{R_L}{666.333 + 1000R_L} V_{in}$$




$$R_L = 99 * 2/3 \Omega = 66 \Omega$$


66Ω load gets 99% of V_{TH}

Thevenin Equivalents of Op-Amp circuits

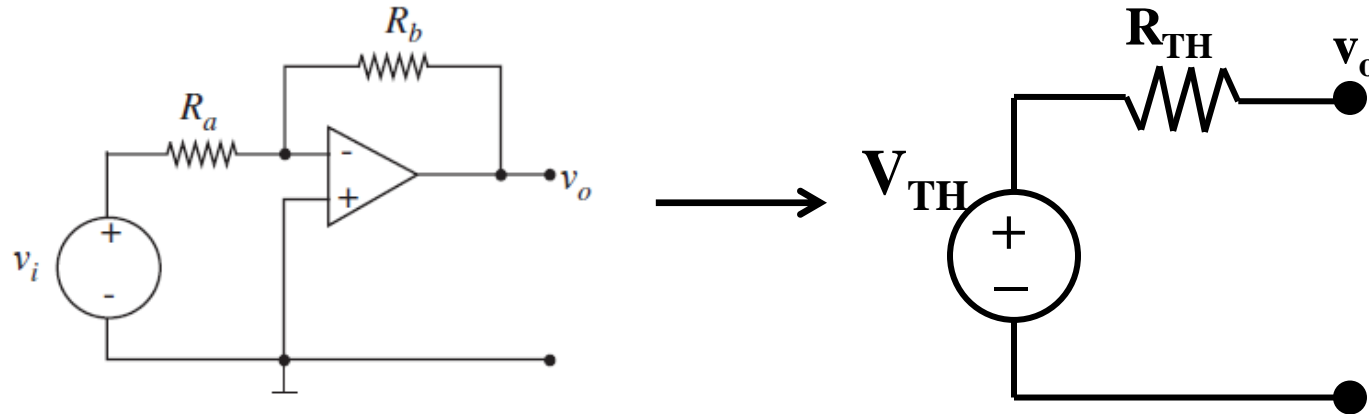
- Can find Thevenin equivalent of an op-amp circuit at its output terminals:



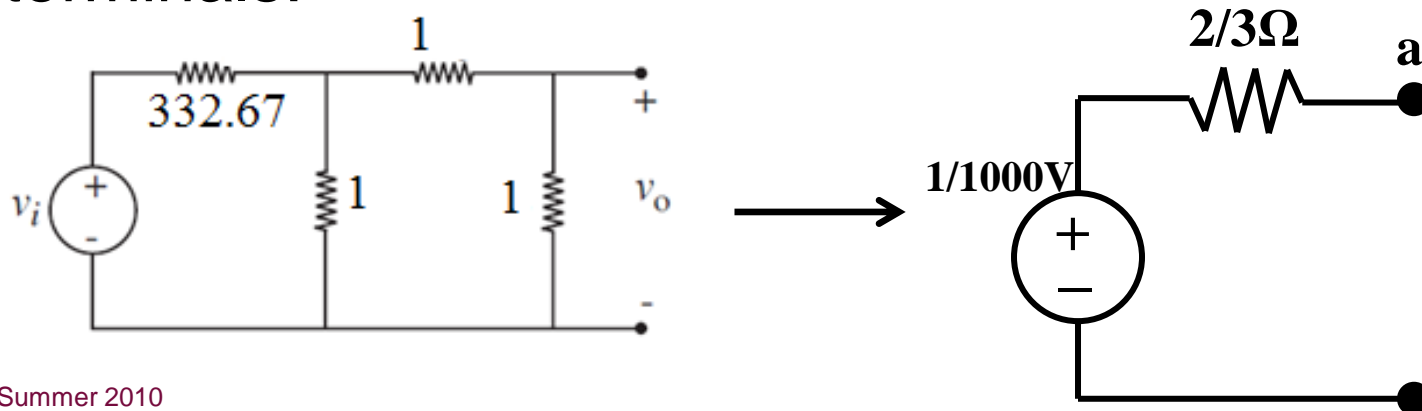- Just like finding Thevenin equivalent of a simple resistor based voltage attenuator at its output terminals:




Thevenin of Inverting Amplifier

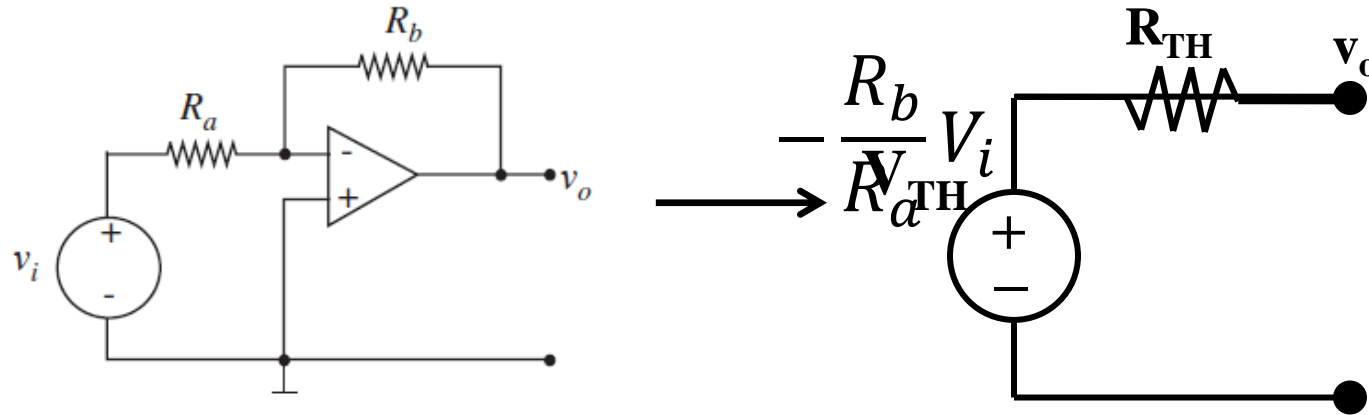


- Assuming that the op-amp here is IDEAL, what's the best way to find the Thevenin equivalent circuit?
 - We've already derived that it's a perfect voltage source!

But if you really want to...

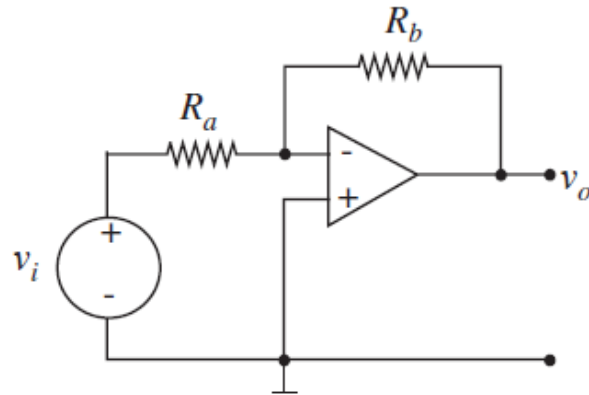

$$V_{OC} = -\frac{R_b}{R_a} V_{in}$$

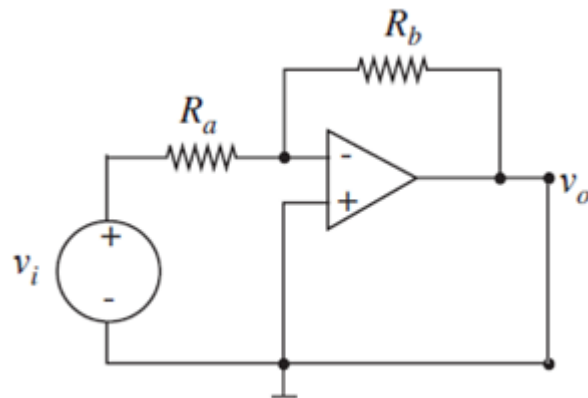



$$I_{SC} = \frac{V_{out}}{0} = \infty$$

$$R_{TH} = \frac{V_{OC}}{\infty} = 0$$


Technically you should take limits here but we are lazy...

What's wrong?

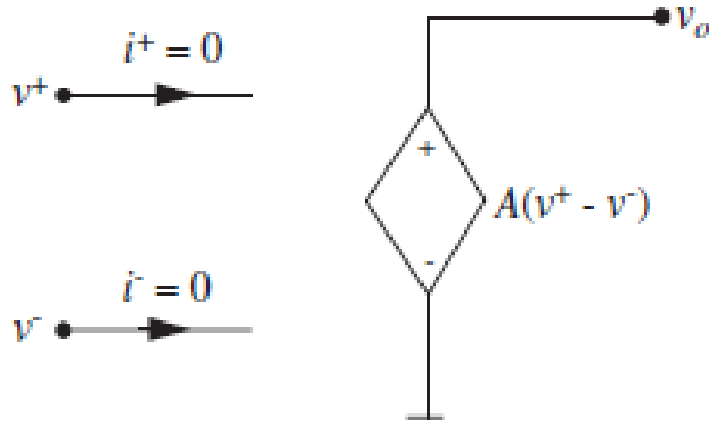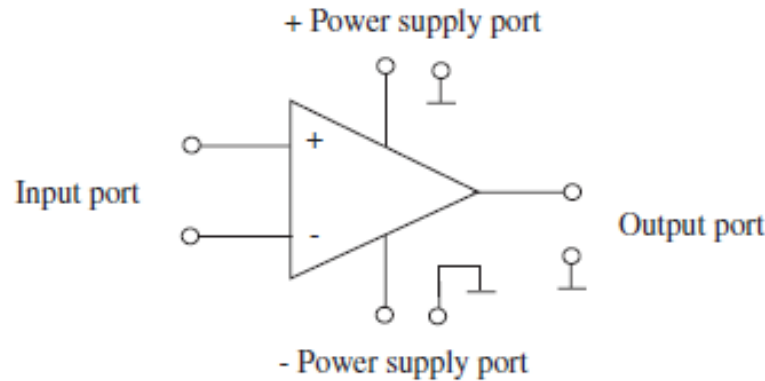- Our op-amp model is missing something
 - That's why it's the "ideal" op-amp model
 - We'll now introduce the "resistive" op-amp model




Ideal

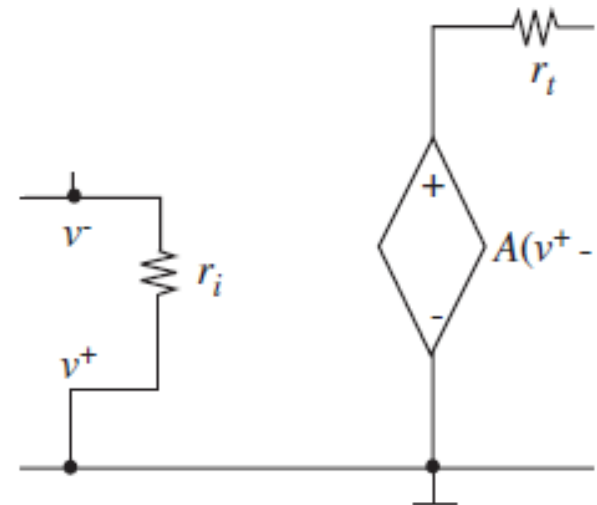

Resistive Op-Amp Model


Resistive Op-Amp model

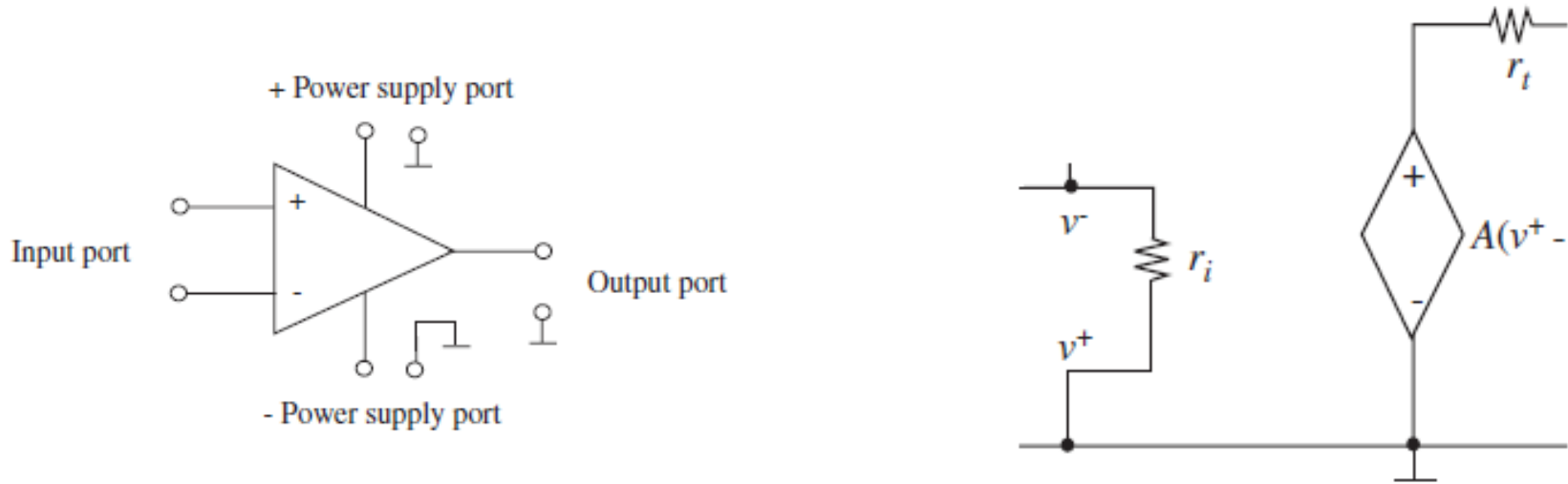

- Takes in to account the fact that
 - Some current flows into the input terminals
 - The op-amp cannot source all device in the universe (output resistance is non-zero)

Output Resistance of Inverting Op-Amp

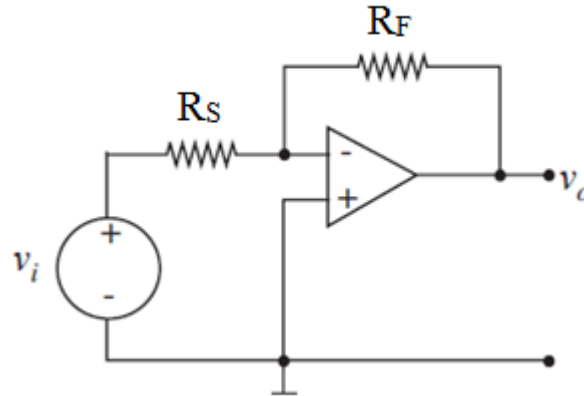- On board (using resistive model of op-amp)




$$R_{out} \cong \frac{R_t}{A \frac{R_s}{R_s + R_f}}$$

- Output Resistance
 - Tells us how small our load can be before we start losing signal fidelity

Input Resistance

- Resistance at the input terminals of a device
- Tells us how much current will be generated for a fixed input voltage
 - Useful, for example, to find power needed to power a device (at that input)


$$R_{in} = R_S$$

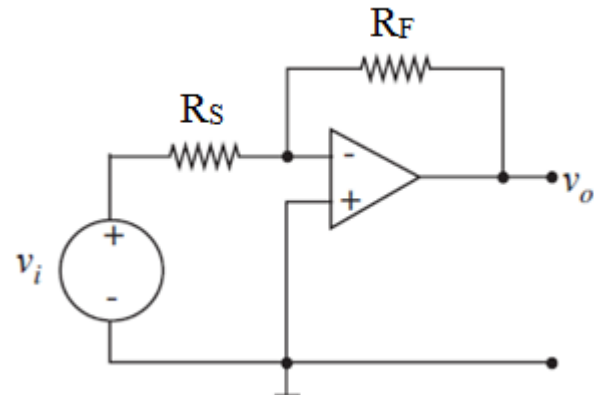

Input Resistance of Inverting Amplifier

- What is the input resistance of an inverting amplifier using ideal op-amp model?

$$R_{in} = R_S$$

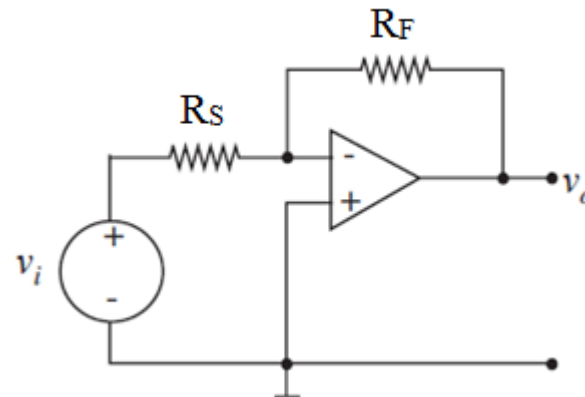


- What is the input resistance of an inverting amplifier using resistive op-amp model?

$$R_i = r_i \parallel (R_f + r_t) \parallel \left(\frac{R_f + r_t}{A} \right) \quad (\text{See sec 15.42 in book})$$

$$R_{in} \cong R_S$$

Why are these quantities useful?

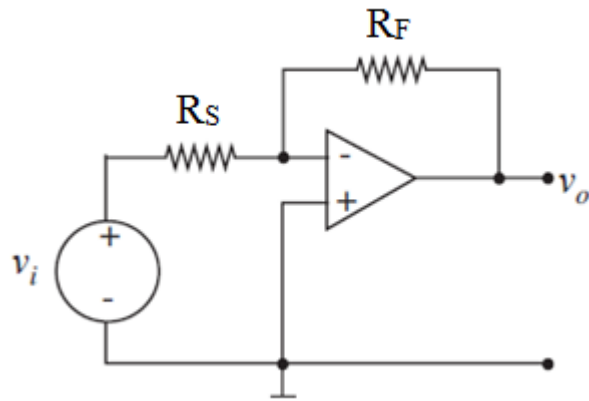

$$R_{in} \cong R_s$$

$$R_{out} \cong \frac{R_t}{A \frac{R_s}{R_s + R_f}}$$

- Input resistance tells us how much current (power) our input signal needs to provide
- Output resistance says how small of a load we can drive

Why are these quantities useful?




- An iPod provides roughly 1V signal output with 20Ω internal resistance
- Speakers might be 4Ω resistance
- Connect iPod directly to such speakers
 - Internal resistance dominates

$$V_{speaker} = \frac{4}{20 + 4} \times 1V = 0.17V$$



$$P_{speaker} = 0.17^2 / 4\Omega = 0.0072 \text{ Watts}$$

Why are these quantities useful?

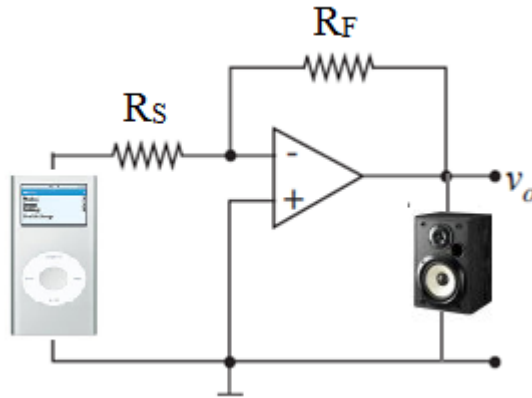


$$R_{in} \cong R_s$$
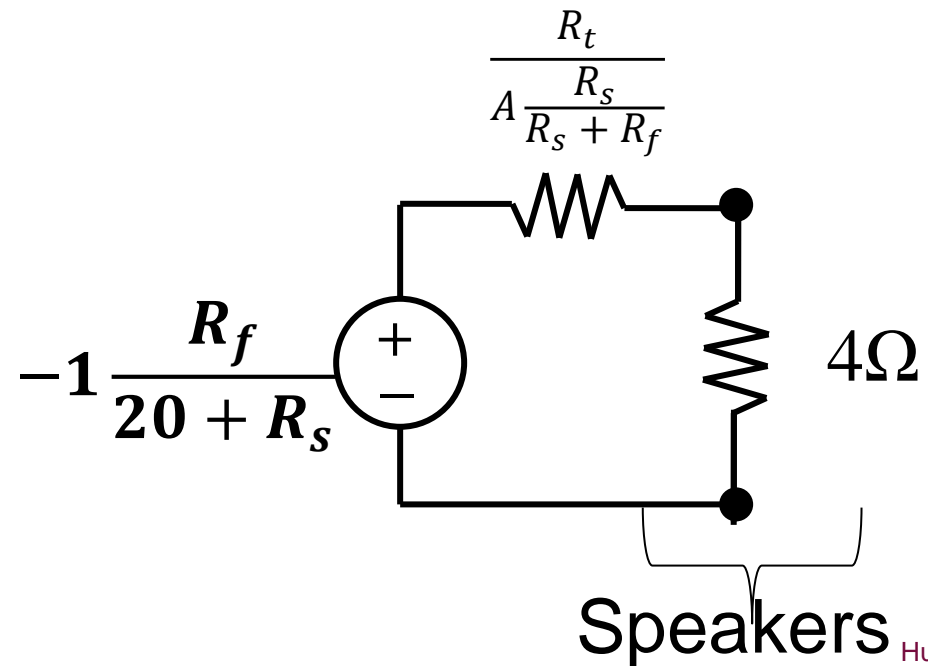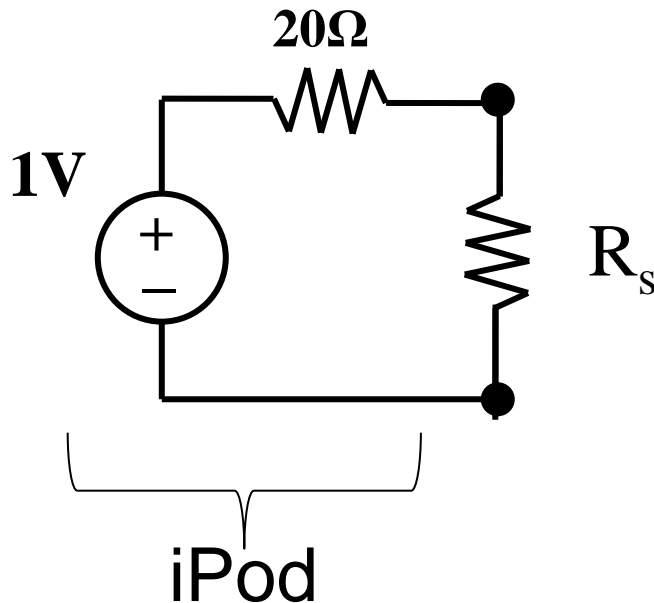
$$R_{out} \cong \frac{R_t}{A \frac{R_s}{R_s + R_f}}$$




Bad Amplifier (Small R_s)

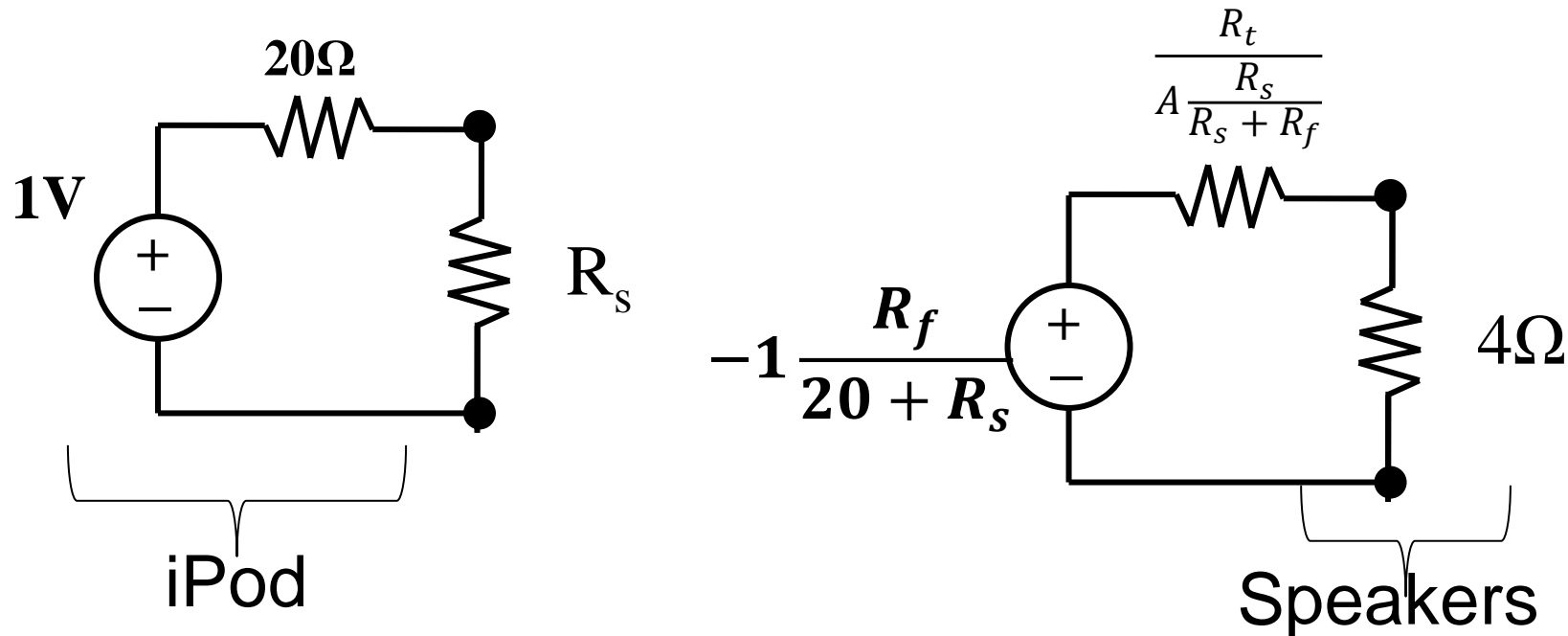

- Very small R_s
 - iPod must supply 50mW
 - Output resistance is large (can't drive speakers)

Good Amplifier

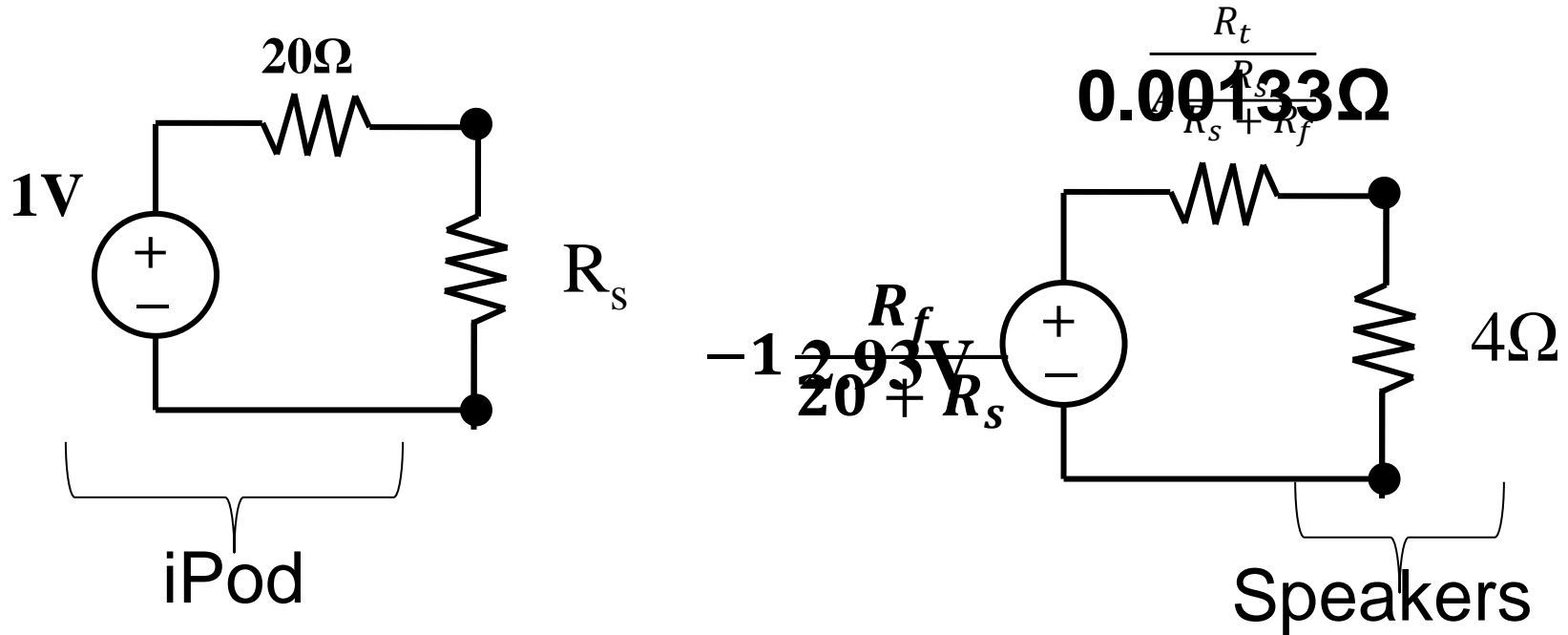


Must provide 1 mW

- $R_s=1000$, $R_f=3000$, $A=10^6$, $R_t=1000$





Op-Amp Saturation

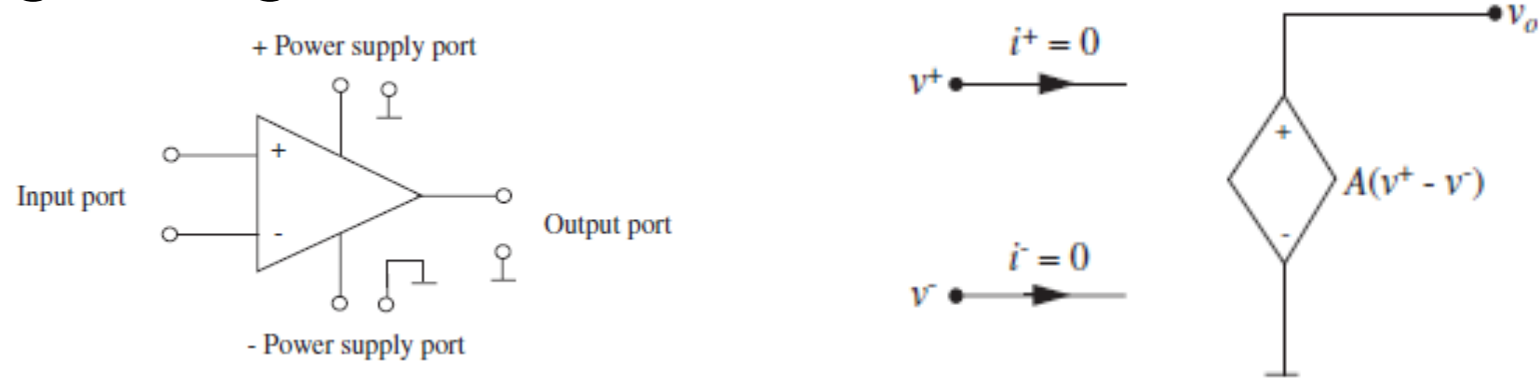- Remember those power ports we've been ignoring?




- They specify the maximum and minimum voltage that our op-amp can deliver
 - If $v_{\min} < A(v^+ - v^-) < v_{\max}$
 - Op-Amp output is $A(v^+ - v^-)$
 - If $A > v_{\max}$,
 - Op-Amp output is v_{\max}
 - If $A < v_{\min}$,
 - Op-Amp output is v_{\min}

Op-Amp Saturation Example

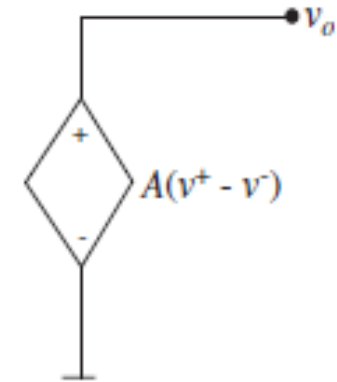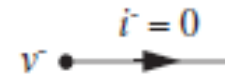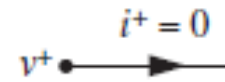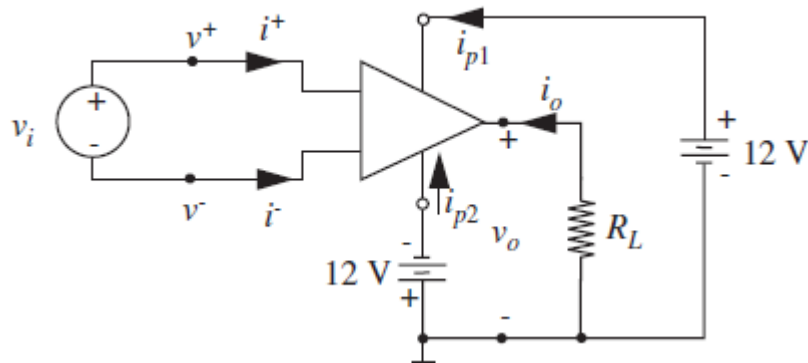


- $v_{max} = 12V, v_{min} = -12V$
- If $A=3$:

V_{in}	V_o
-5 V	-12V
-1V	-3V
2V	6V
1,512,312V	12V

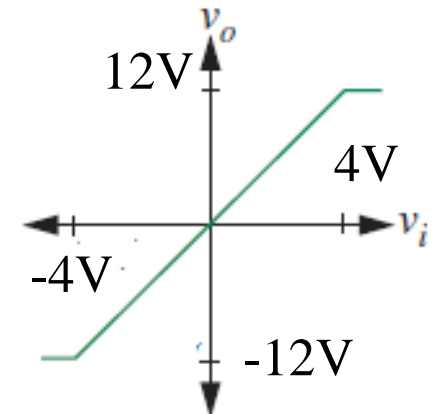

Positive Feedback

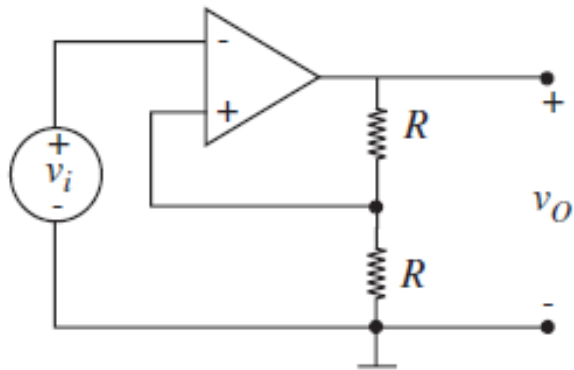

On the board

That's all for Op-Amps

- No class Monday
- Enjoy weekend (doing op-amp problems)