

---

**7/12/2010**

**Lecture 8**

**Capacitors and Inductors**



**Congratulations to  
Paul the Octopus  
on getting 8/8  
world cup  
predictions correct**

## So far...

---

- All circuits we've dealt with have reacted instantaneously
  - Change a resistance, voltage, or current, and everything else reacts instantly
- Obviously this isn't a complete model for electronic device. Why?

## For the next 2 weeks

---

- We'll be talking about elements with memory
  - Capacitors
  - Inductors
- Our first 6 lectures taught us how we can take a circuit schematic containing memoryless elements and convert them into algebraic equations
- In the next 2 lectures we'll talk about how to convert circuits with memory into differential equations
- The next 3 after that will be about how we can use algebraic equations for circuits with memory if we have AC sources

# Announcements


---

- Midterm #2 will be on the 28<sup>th</sup>
  - Elements with memory
- Make sure you do pre-lab before lab tomorrow
  - Who has finished it?
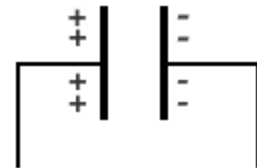
# The Capacitor

---


- The basic idea is pretty simple
  - Imagine you have two parallel metal plates, both of which have equal and opposite excess charges
  - Plates are separated by an insulating layer (air, glass, wood, etc)



- The charges would love to balance out
- Insulator blocks them (just as the ground blocks you from falling into the center of the earth)
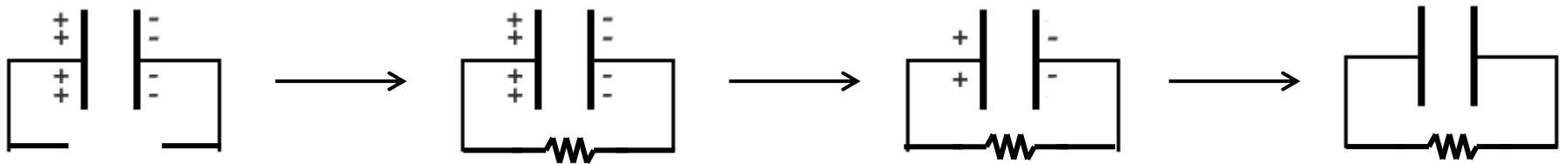
# The Capacitor


- If you were to connect a resistive wire to the plates
  - Charges would flow through the wire
    - Charge flow is current
    - $P = I^2 R$
    - Energy is released as heat


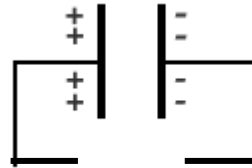
# The Capacitor

---

- Remember that a voltage is the electrical potential between two points in space



- Here, we have an imbalance of charge, and thus an electric field, and thus a voltage


$$V = EL$$

- Field strength is dependent on number and distribution of charges as well as material properties
- Field length is dependent on size of capacitor
- Capacitor size and material properties lumped into single “capacitance”  $C$

- $V = Q/C$
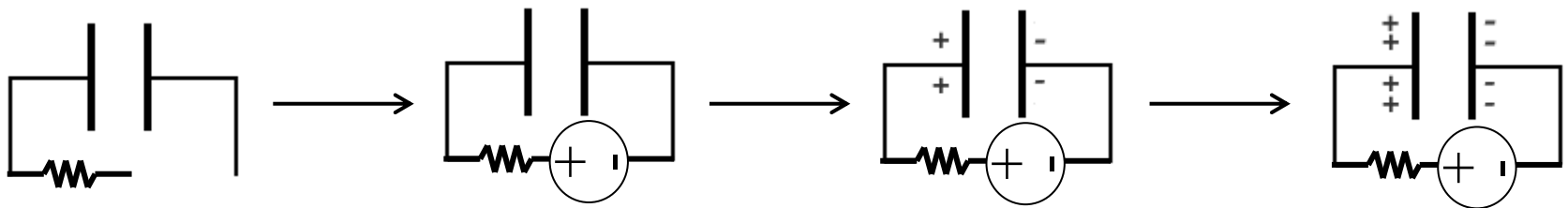
# The Capacitor

- Thus, if you connect a voltage source to the plates
  - Like charges will move to get away from the source
    - Charge flow is current
    - Current will stop once charges reach equilibrium with voltage source, i.e.  $V_C = V_S$
    - Energy has been stored






# The Capacitor

Lots of current

Zero current

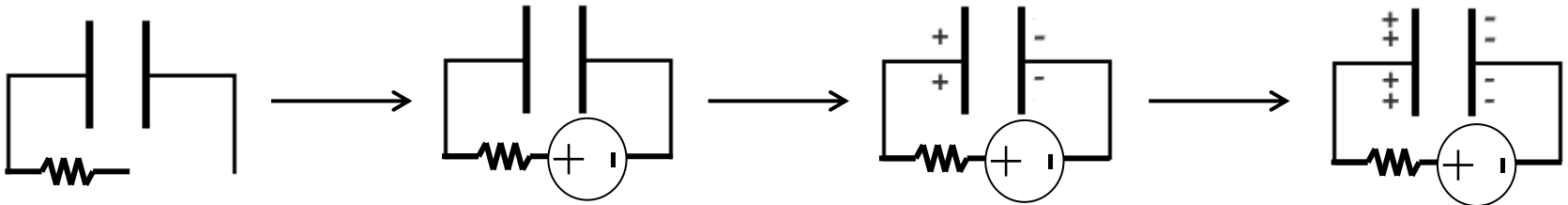


Zero  $V_C$

$V_C = V_S$

$$I = C \frac{dV}{dt}$$

Lots of current  
[the other way]


Zero current

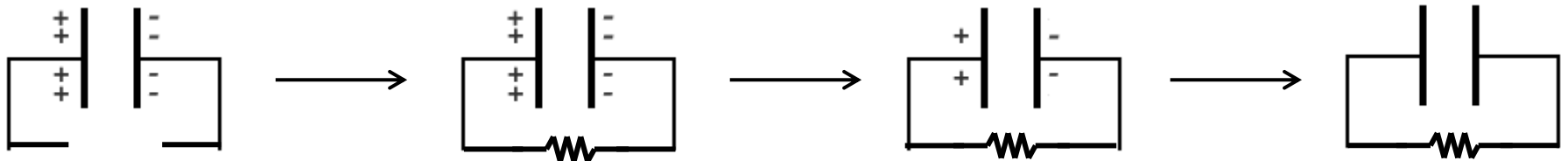


$V_C = V_S$

Zero  $V_C$

# iClicker

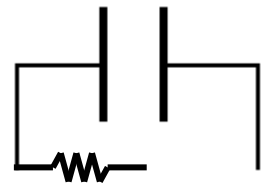


Lots of current

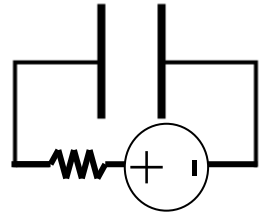

Zero  $V_C$

Zero current

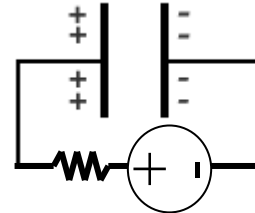

$V_C = V_S$

Acts like a:

A. Short circuit


B. Open circuit

C. Resistor

D. Voltage source


E. Current source

Lots of current

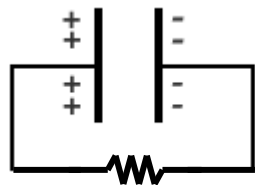

High  $V_C$


Zero current

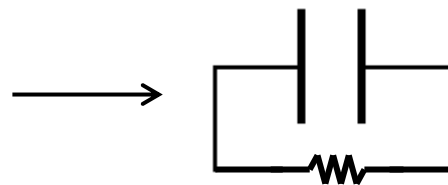

Zero  $V_C$
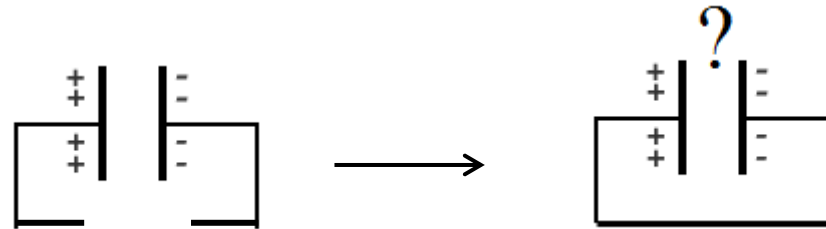
# Extreme Corner Case

- What happens if we short a charged capacitor?



- Think of it is as the limit as resistance goes to zero:
  - Infinite current
  - Lasts only a very short time ( $P = V(t)I(t)$ ) until energy is released
- Mathematically poorly behaved
  - Don't do this

# How much energy is stored?


---

- $P(t) = V(t)I(t)$
- $P(t) = V_C(t)C \frac{dV_C(t)}{dt}$
- $E = \int_0^t P(t)dt$   
 $= \frac{1}{2} CV_C(t)^2$

Strictly speaking we shouldn't use  $t$  as our integration variable and also the limit that we're integrating to, but you know what I mean...
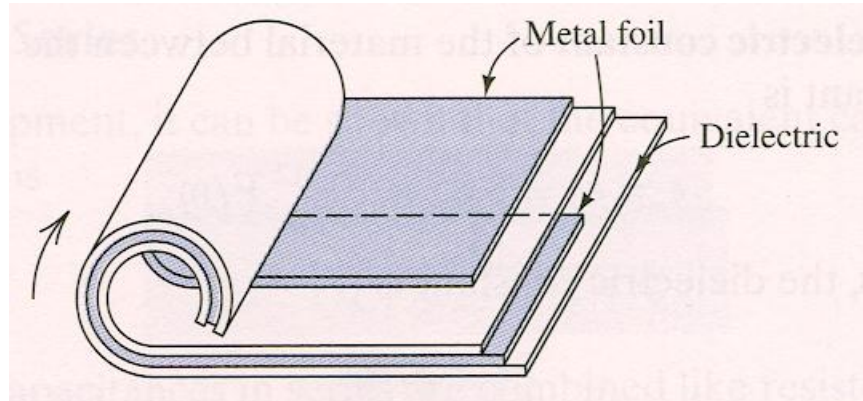
# Practical Capacitors

- A capacitor can be constructed by interleaving the plates with two dielectric layers and rolling them up, to achieve a compact size.




- To achieve a small volume, a very thin dielectric with a high dielectric constant is desirable. However, dielectric materials break down and become conductors when the electric field (units:  $V/cm$ ) is too high.
  - Real capacitors have maximum voltage ratings
  - An engineering trade-off exists between compact size and high voltage rating

# Capacitors

---

- Useful for
  - Storing Energy
  - Filtering
  - Modeling unwanted capacitive effects, particularly delay


# Capacitor

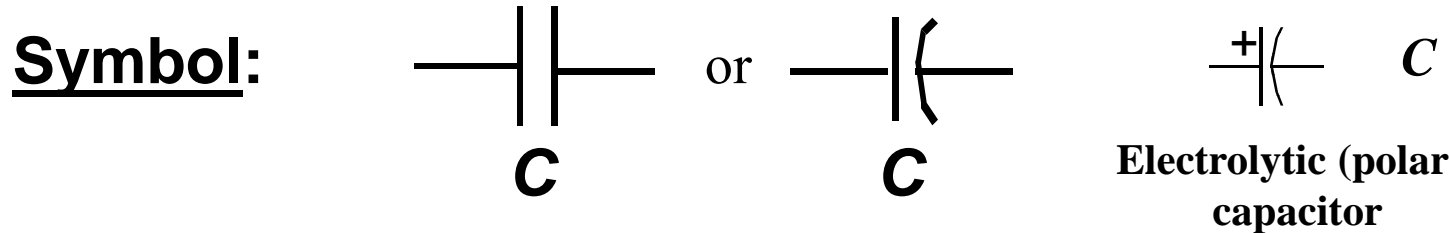

**Units:** Farads (Coulombs/Volt) These have high capacitance and cannot support voltage drops of the wrong polarity  
(typical range of values: 1 pF to 1 μF; for “supercapacitors” up to a few F!)

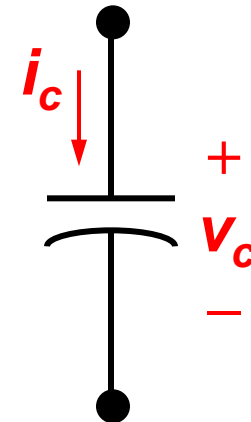
**Current-Voltage relationship:**

$$i_c = \frac{dQ}{dt} = C \frac{dv_c}{dt}$$




**Note:**  $v_c$  must be a continuous function of time since the charge stored on each plate cannot change suddenly

# Node Voltage with Capacitors

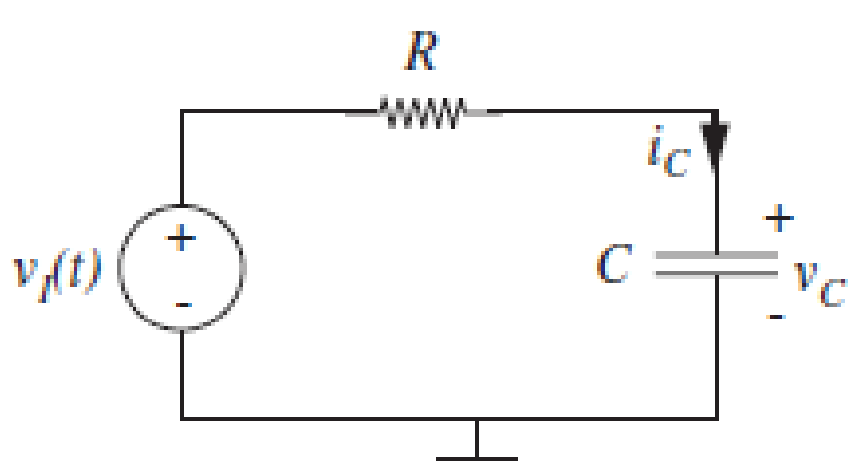
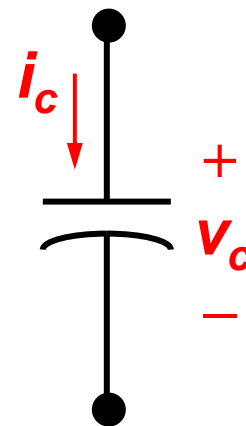
$$i_c = \frac{dQ}{dt} = C \frac{dv_c}{dt}$$




- At the top right node, we write KCL
  - Current to the left through resistor:
  - Current down through the capacitor

$$\frac{V_C(t) - V_I(t)}{R}$$


$$C \frac{dV_C(t)}{dt}$$



# Node Voltage with Capacitors

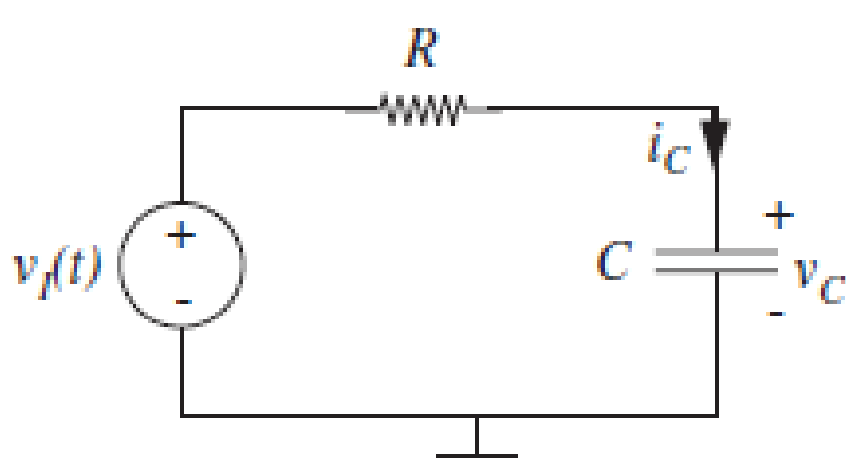
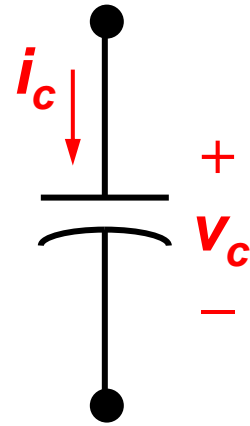
$$i_c = \frac{dQ}{dt} = C \frac{dv_c}{dt}$$



- Or in other words

$$\frac{V_C(t) - V_I(t)}{R} + C \frac{dV_C(t)}{dt} = 0$$

- Or more compactly:

$$\frac{V_C - V_I}{R} + CV'_C = 0$$

# ODEs

---

$$\frac{V_C - V_I}{R} + CV_C' = 0$$

- Later today, we'll talk about how to solve ODEs...
- For now, let's talk about inductors

# Inductors

---



- Capacitors are a piece of cake to understand, just rely on Coulomb's Law

$$F = k_e \frac{q_1 q_2}{d^2}$$

- Inductors, by contrast, involve magnetic fields, and rely instead on Faraday's Law
  - Comprehension comes with greater difficulty
- Thus, we'll treat inductors as mathematical objects and leave the derivation to Physics 7B (or page 467 of the book)

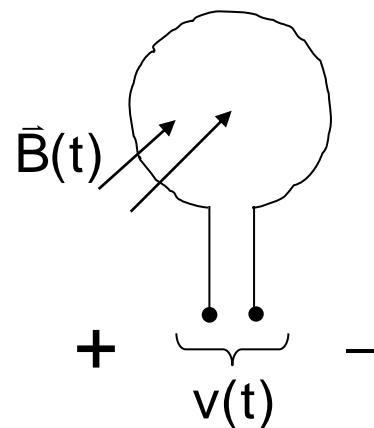
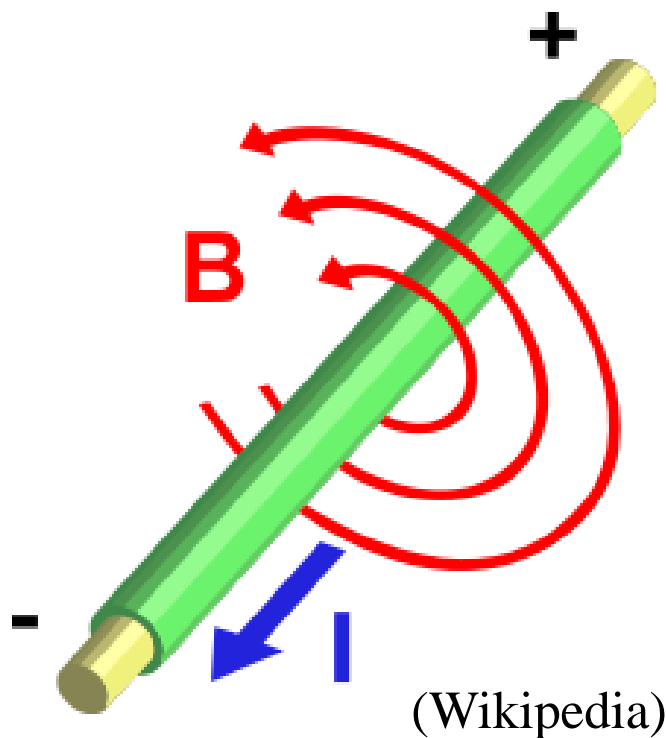
# Two Fundamental Principles

- The flow of current induces a magnetic field (Ampere's Law)
- A change in magnetic field through a loop of wire induces a voltage (Faraday's Law)




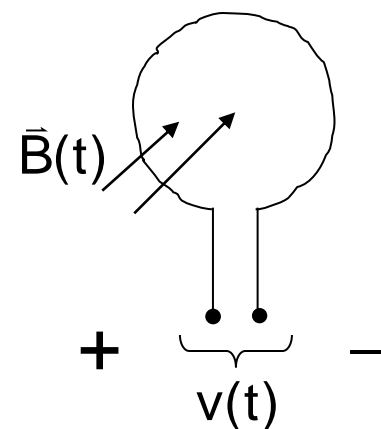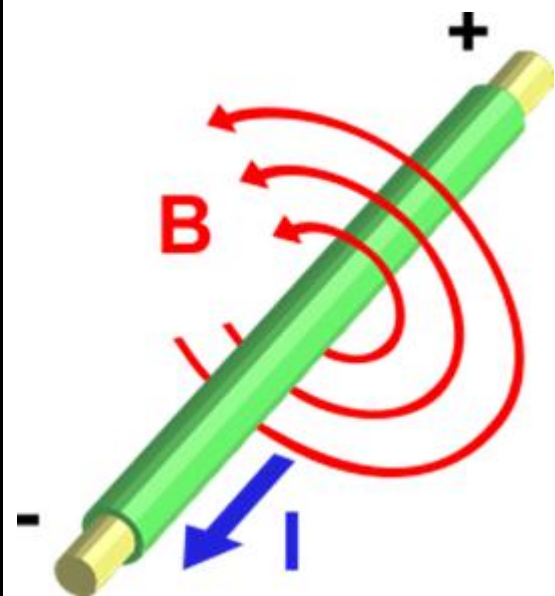
# Inductor Basics (1)

- When we connect a voltage source to a wire, current clearly takes a little time to get moving
- Thus, the magnetic field builds to some maximum strength over time




# Inductor Basics (2)

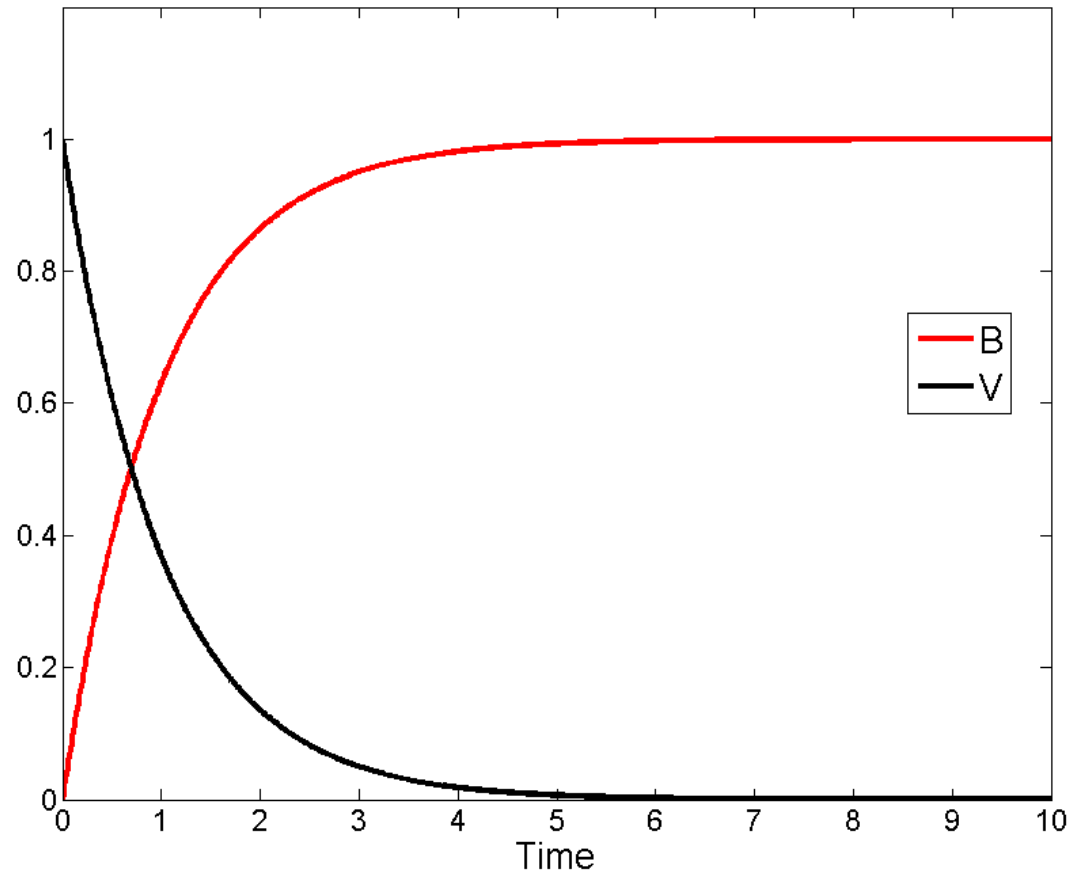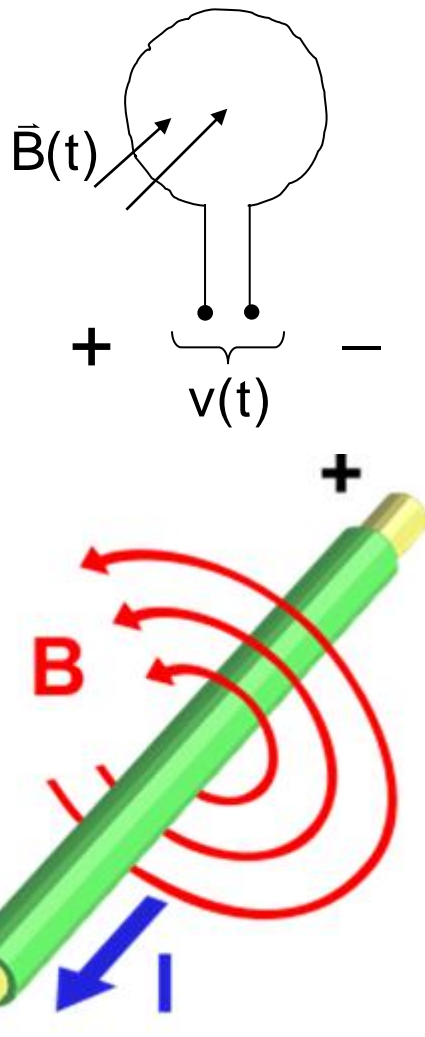

Current in a wire ~~causes~~ induces a voltage in any nearby circuit
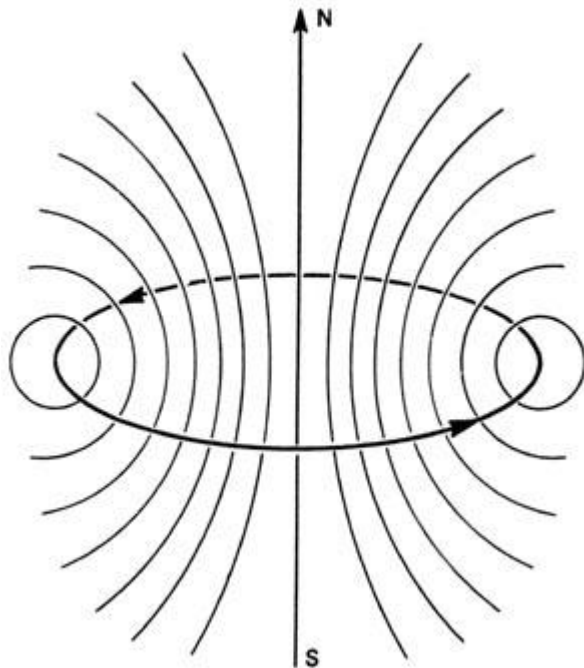
## Inductors Basics (3)

- If we make a loop, the entire loop of wire will all contribute to the magnetic field through the loop
- What's more, this field will go through the loop producing the current!
  - Self induced voltage
  - **Self inductance**



From: Dr. Richard F.W.  
Bader Professor of  
Chemistry / McMaster  
University

# Inductors Basics (4)

---

- More loops
  - More magnetic field generated
  - More circuit to receive magnetic field



- Inductors are literally just loops of wire
- Just like capacitors are just two conductors separated by an insulator (or a gap)
- Just like resistors are just stuff with wires stuck to the ends




# Inductors

---

- Capacitors hold a voltage in the form of stored charge
- Inductors hold a current in the form of stored magnetic field [dude...]
  
- For webcast viewers, see drawings on board/notes for more comparison to capacitor

---

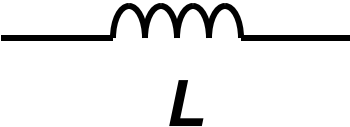**Symbol:** 


**Units:** Henrys (Volts • second / Ampere)

(typical range of values:  $\mu\text{H}$  to 10 H)

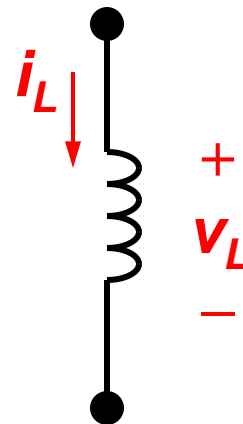**Current in terms of voltage:**

$$di_L = \frac{1}{L} v_L(t) dt$$

$$i_L(t) = \frac{1}{L} \int_{t_0}^t v_L(\tau) d\tau + i(t_0)$$



**Note:**  $i_L$  must be a continuous function of time

# Summary

## Capacitor

$$i = C \frac{dv}{dt}; w = \frac{1}{2} C v^2$$

**v** cannot change **instantaneously**

**i** can change instantaneously

Do not short-circuit a charged capacitor (-> infinite current!)

**In steady state (not time-varying), a capacitor behaves like an open circuit.**

## Inductor

$$v = L \frac{di}{dt}; w = \frac{1}{2} L i^2$$

**i** cannot change **instantaneously**

**v** can change instantaneously

Do not open-circuit an inductor with current (-> infinite voltage!)


**In steady state, an inductor behaves like a short circuit.**

# Ordinary Differential Equations

---

- Inductors, too, give us a simple 1<sup>st</sup> order relationship between voltage and current
- Node Voltage with memoryless circuits gave us algebraic equations
- Node voltage with elements with memory will give us Ordinary Differential Equations (ODEs)
- Next week will be a bunch of setting up and solving 1<sup>st</sup> and 2<sup>nd</sup> order linear ODEs
- Higher order and especially nonlinear ODEs are tough to solve. For example...

# Chua's Circuit

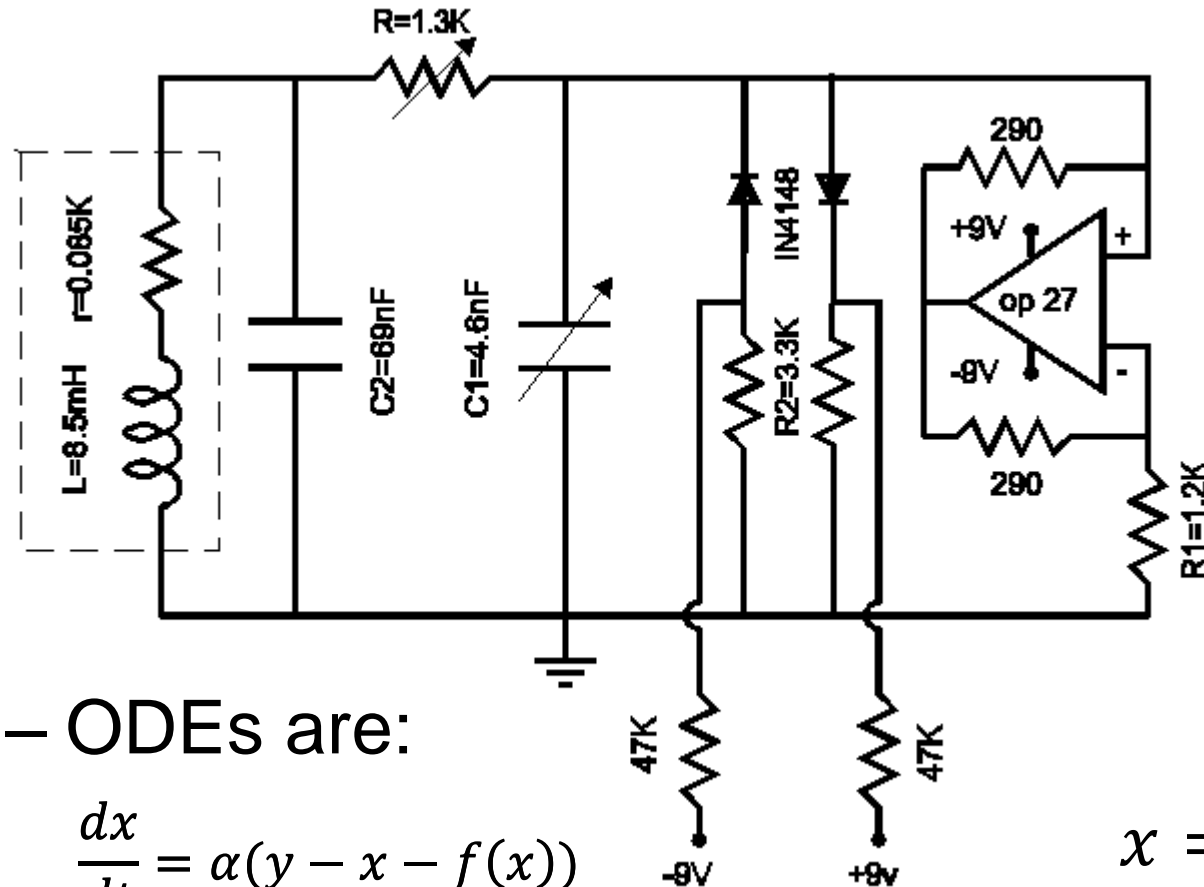

$f(x)$  –  
response  
of diodes  
and  
resistor  
block

– ODEs are:

$$\frac{dx}{dt} = \alpha(y - x - f(x))$$

$$\frac{dy}{dt} = x - y + z$$

$$\frac{dz}{dt} = -\beta y$$

$$x = v_{C1}$$

$$y = v_{C2}$$

$$z = i_L$$

# Chua's Circuit

- Despite simplicity of ODEs

$$\frac{dx}{dt} = \alpha(y - x - f(x))$$

$$\frac{dy}{dt} = x - y + z$$

$$\frac{dz}{dt} = -\beta y$$

- Exhibits chaos!

Invented by current  
UC Berkeley EECS  
professor Leon  
Chua in 1983

