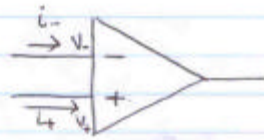



Ideal op-amp



The ideal op-amp operates on the following principles:

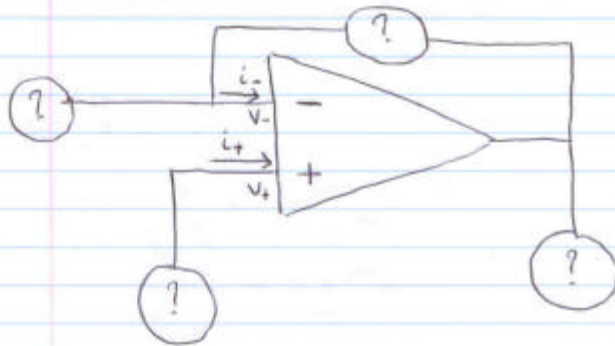- 1) $i_+ = 0$
- 2) $i_- = 0$
- 3) $v_+ = v_-$


So even if we connect other elements on the amplifier's terminals, these rules still apply:



$$\begin{aligned} i_+ &= 0 \\ i_- &= 0 \\ v_+ &= v_- \end{aligned}$$

Examples

①

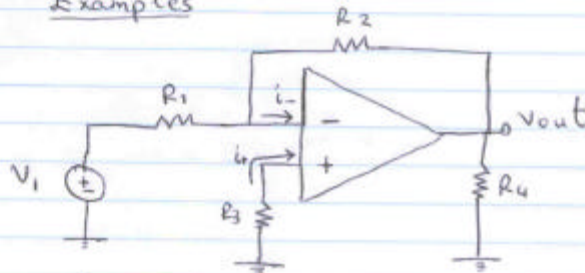

Find $\frac{V_{out}}{V_1}$

Step 1


$i_+ = 0 \Rightarrow$ The voltage across $R_3 = 0 \Rightarrow V_+ = 0$

Step 2

$V_+ = V_- \Rightarrow V_- = 0$

Step 3

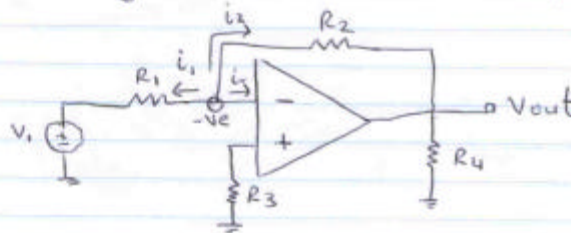
Use the fact that $i_- = 0$ and do nodal analysis on the -ve node:



The voltage at the -ve terminal is $V_- = 0$ (We will need this)

$$\text{So: } i_1 + i_2 + i_- = 0 \Rightarrow \frac{0 - V_1}{R_1} + \frac{0 - V_{out}}{R_2} + 0 = 0$$
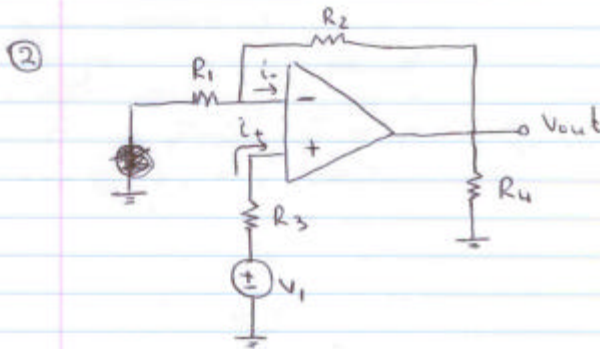
$$\Rightarrow -\frac{V_1}{R_1} - \frac{V_{out}}{R_2} = 0 \Rightarrow \boxed{\frac{V_{out}}{V_1} = -\frac{R_2}{R_1}}$$



Find $\frac{v_{out}}{v_1}$

Step 1


$i_+ = 0 \Rightarrow$ The voltage across $R_3 = 0 \Rightarrow V_+ = V_1$

Step 2

$V_+ = V_- \Rightarrow V_- = V_1$

Step 3

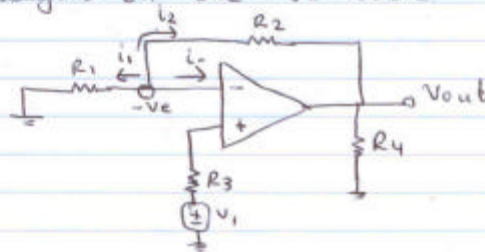Use the fact that $i_- = 0$ and do nodal analysis on the -ve node




The voltage at the -ve node is $V_- = V_1$

$$i_1 + i_2 + i_- = 0 \Rightarrow \frac{V_1 - 0}{R_1} + \frac{V_1 - v_{out}}{R_2} + 0 \Rightarrow \boxed{\frac{v_{out}}{V_1} = 1 + \frac{R_2}{R_1}}$$

Notes

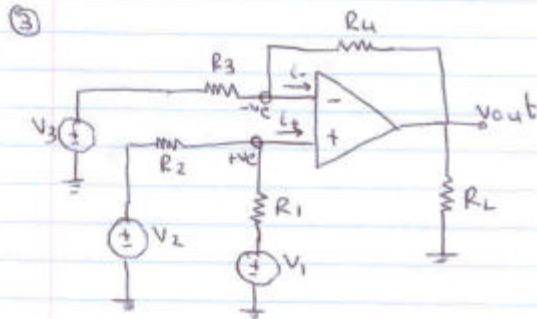- 1) Example ① has a negative gain, so it is called the inverting configuration. Example ② has a positive gain so it is called the non-inverting configuration



Find V_{out} in terms of $V_1, V_2, V_3, R_1, R_2, R_3, R_4$

Step 1

$$i_+ = 0 \Rightarrow \frac{V_{+ve} - V_1}{R_1} + \frac{V_{+ve} - V_2}{R_2} = 0 \Rightarrow V_{+ve} = \left(\frac{R_2 \cdot V_1 + R_1 \cdot V_2}{R_1 + R_2} \right)$$

All I did was nodal analysis at the +ve terminal

$$V_+ = V_{+ve} = \left(\frac{R_2 \cdot V_1 + R_1 \cdot V_2}{R_1 + R_2} \right)$$

Step 2

$$\text{Use } V_+ = V_- \Rightarrow V_- = \frac{R_2 \cdot V_1 + R_1 \cdot V_2}{R_1 + R_2}$$

Step 3


Nodal analysis at the -ve node: (Remember: $i_- = 0$)

$$\frac{V_- - V_3}{R_3} + \frac{V_- - V_{out}}{R_4} = 0 \Rightarrow V_{out} = \left(-\frac{R_4}{R_3} \right) \cdot V_3 + \left(1 + \frac{R_4}{R_3} \right) \cdot V_-$$

↑ inverting ↑ non-inverting

Now finally, if we substitute $V_- = \frac{R_2 \cdot V_1 + R_1 \cdot V_2}{R_1 + R_2}$ we get:
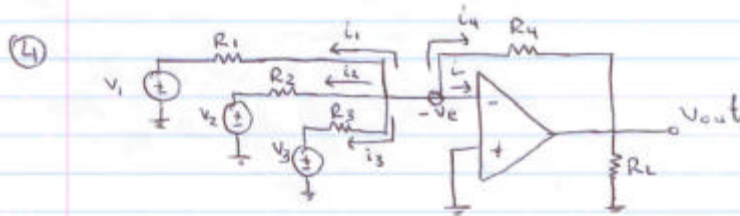
$$V_{out} = \left(-\frac{R_4}{R_3} \right) V_3 + \left(1 + \frac{R_4}{R_3} \right) \left(\frac{R_2 \cdot V_1 + R_1 \cdot V_2}{R_1 + R_2} \right)$$



Find V_{out} in terms of $V_1, V_2, V_3, R_1, R_2, R_3$

Again: $V_+ = 0 \Rightarrow V_- = 0$

So $V_{-ve} = 0$

And by doing nodal analysis:

$$\sum i_1 + i_2 + i_3 + i_4 + i_- = 0 \Rightarrow i_1 + i_2 + i_3 + i_4 = 0 \text{ since } i_- = 0$$

$$\Rightarrow \frac{0 - V_1}{R_1} + \frac{0 - V_2}{R_2} + \frac{0 - V_3}{R_3} + \frac{0 - V_{out}}{R_4} = 0$$


$$\Rightarrow V_{out} = \underbrace{-\frac{R_4}{R_1} \cdot V_1}_{\text{inverting}} + \underbrace{-\frac{R_4}{R_2} \cdot V_2}_{\text{inverting}} + \underbrace{-\frac{R_4}{R_3} \cdot V_3}_{\text{inverting}}$$

Note

In all of the above examples we were able to find V_{out} without ever considering ~~about~~ the value of R_L . That is the good thing about ideal op-amps: The load resistor (R_L) does not affect the output voltage.

Cascading op-amps


Consider:

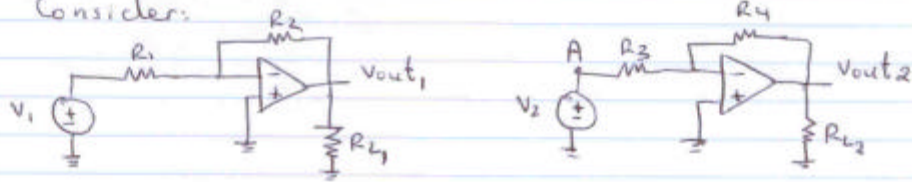

We have shown in example ① that:

$$V_{out1} = V_1 \cdot \left(-\frac{R_2}{R_1}\right) \quad \text{and} \quad V_{out2} = V_2 \cdot \left(-\frac{R_4}{R_3}\right)$$

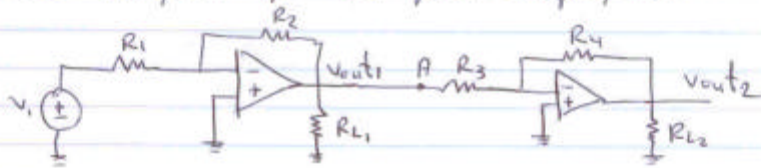What is going to happen if instead of using the voltage source V_2 , I connect point A to the output of the first amplifier?



Well, for the first amplifier: $V_{out1} = V_1 \cdot \left(-\frac{R_2}{R_1}\right)$
Remember that whatever we decide to connect on the output is not going to affect the value of V_{out1} .

Now for the second amplifier:

$$V_+ = 0 \Rightarrow V_- = 0$$

And by using $i_- = 0$ and doing nodal analysis on the -ve node: $\frac{0 - V_A}{R_3} + \frac{0 - V_{out2}}{R_4} + 0 = 0 \Rightarrow V_{out2} = \left(-\frac{R_4}{R_3}\right) V_A$

What is V_A though? $V_A = V_{out1} = V_1 \cdot \left(-\frac{R_2}{R_1}\right)$

$$\Rightarrow V_{out2} = \left(-\frac{R_4}{R_3}\right) V_1 \cdot \left(-\frac{R_2}{R_1}\right) \Rightarrow V_{out2} = \left(\frac{R_2 R_4}{R_1 R_3}\right) V_1$$

↑ gain of 2nd amplifier
↑ gain of 1st amplifier