09/22/03

EE 42 – Introduction to Electronics for Computer Science

Fall 2003, Dept. EECS, 510 Cory UC Berkeley Course Web Site Prof. A. R. Neureuther neureuth@eecs.berkeley.edu 642 - 4590 Office Hours M1, Tu, Th 10:30-11:30, F 11 http://www - inst.eecs.berkeley.edu/~ee42/

Problem Set # 5 Due: 1 PM Oct 1st, 2003 in box outside 240 Cory

Announcements:

Midterm in class on Thursday, 10/2/03 Covers lectures 1-9, closed book and notes, bring calculator, paper provided Reading Week #5: Review Schwarz and Oldham 2.3, 2.4, 3.1, 4.1, 8.1 Review Sessions for Midterm: Tuesday, Sept 30th and Wed, Oct 1st

5.1 Super-node Use the circuit to the right.

a) Find Va and Vb if $R1=R2=R3=R4=10k\Omega$, and V1 = V4 =1.5V with VLL = 1V b) Check your answers using KCL



a) Use KCL, find V_E

5.2 Dependent Sources Use the circuit to the right.

- b) Find the voltage across the AA' terminal, Vtest
- c) Find the resistance seen looking into AA'

5.3 Thevenin and Norton Equivalents Use the circuit to the right

- a) Find RN
- b) Find RTH
- c) Find the Thevenin equivalent circuit

d) Find the Norton equivalent circuit

5.4 Review of Transients Use the circuit to the right

The switch in the circuit closes at t = 0. Just before switching, the capacitor is charged to 2V

a) Find the voltage on the capacitor Vc (t) for t > 0b) Find dVc(t)/dt just before the switch closes at t = 0



