

thrust

#1

$$E_T = \int P_T = \int IV dt$$

$$= V \int_0^\infty I dt$$

$$= V E_{c\infty}$$

$$E_{c\infty} = CV$$

$$E_T = \underline{CV^2}$$

$$E_C = \int P_C = \int C V_C \frac{dV_C}{dt} dt \quad P_C = I_C V_C = \left(C \frac{dV_C}{dt} \right) V_C$$

$$= C \int_0^\infty V_C \frac{dV_C}{dt} dt$$


$$= C \int_0^V V_C dV_C$$

$$E_C = \frac{C}{2} V_C^2 \Big|_0^V = \underline{\frac{1}{2} CV^2}$$

$$E_R = E_T - E_C = CV^2 - \frac{1}{2} CV^2 = \underline{\frac{1}{2} CV^2}$$

→ NOTICE THIS ENERGY IS NOT DEPENDENT ON R.

#2

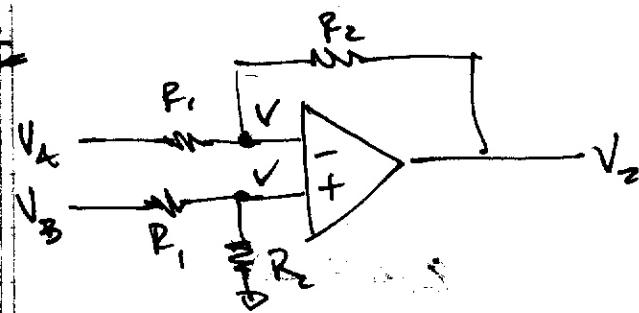Assuming Ideal Amp

$$\textcircled{1} \quad \frac{V_A - V}{R_1} = \frac{V - V_2}{R_2} \Rightarrow V = \frac{R_2 V_A + R_1 V_2}{R_1 + R_2}$$

$$\textcircled{2} \quad \frac{V_B - V}{R_1} = \frac{V}{R_2} \Rightarrow V = \frac{R_2 V_B}{R_1 + R_2}$$

$$\frac{R_2}{R_1 + R_2} V_B = \frac{R_2 V_A + R_1 V_2}{R_1 + R_2}$$

$$\Rightarrow \frac{R_2}{R_1} (V_B - V_A) = V_2 \Rightarrow$$

$$K = \frac{R_2}{R_1}$$

#3

$$A + B = \overline{(A \cdot \bar{B})}$$

A	B	$A + B$	\bar{A}	\bar{B}	$\bar{A}\bar{B}$	$(\bar{A} \cdot \bar{B})$
0	0	0	1	1	1	0
0	1	1	1	0	0	1
1	0	1	0	1	0	1
1	1	1	0	0	0	0

~~24~~

D	K	w ₁	w ₂	w ₃	A
0	0	0	0	0	1
0	0	0	0	1	1
0	0	0	1	0	1
0	0	1	1	1	1
0	1	0	0	0	1
0	1	0	1	1	1
0	1	1	1	1	1
1	0	0	0	0	0
1	0	0	0	1	0
1	0	1	0	0	0
1	0	1	1	1	0
1	1	0	0	0	0
1	1	0	1	1	0
1	1	1	1	1	0
1	0	0	0	0	1
1	0	0	0	1	1
0	0	0	1	1	1
0	0	1	0	0	1
0	1	0	0	1	1
1	0	0	0	0	0
1	0	0	1	0	0
1	0	1	1	1	0
1	1	0	0	0	0
1	1	0	1	1	0
1	1	1	0	0	0
1	1	1	1	1	0

$$A = \bar{K}(\bar{D} + \bar{w}_1 + \bar{w}_2 + \bar{w}_3)$$