

EECS 42 Introduction to Electronics for Computer Science Andrew R. Neureuther

Lecture #4

- Capacitors and Inductors
- Energy Stored in C and L
- Equivalent Circuits
 - Thevenin
 - Norton

<http://inst.EECS.Berkeley.EDU/~ee42/>

Game Plan 02/03/03

Monday 02/03/03

- Capacitors and Inductors; Equivalent Sources
Schwarz and Oldham: 5.1-5.2, 3.1

Wednesday 02/05/03

- N-L Elements; Graphical Solutions; Power
Schwarz and Oldham: 3.2-3.4

Next (4th) Week

- RC Transient
Schwarz and Oldham: 8.1 plus Handouts


Problem Set #2 – Out 1/27/03 - Due 2/5/03 2:30 in box near 275 Cory

2.1 Flow; 2.2 KCL; 2.3 KVL; 2.4 resistor circuit; 2.5 Power

Problem Set #3 – Out 2/2/03 - Due 2/12/03 2:30 in box near 275 Cory

3.1 and 3.2 charging capacitors; 3.3 –3.5; Equivalent Circuits;

What Goes In the Circuit Element Boxes?

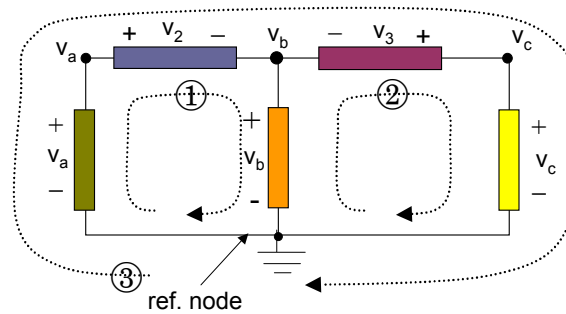

Copyright 2001, Regents of University of California

BASIC CIRCUIT ELEMENTS

- Voltage Source (always supplies some constant given voltage - like ideal battery)
- Current Source (always supplies some constant given current)
- Resistor (Ohm's law)
- Wire ("short" – no voltage drop)
- Capacitor (capacitor law – based on energy storage in electric field of a dielectric S&O 5.1)
- Inductor (inductor law – based on energy storage in magnetic field in space S&O 5.1)


Copyright 2001, Regents of University of California

CAPACITOR

Version Date 02/02/03

Any two conductors a and b separated by an insulator with a difference in voltage V_{ab} will have an equal and opposite charge on their surfaces whose value is given by $Q = CV_{ab}$, where C is the **capacitance** of the structure, and the + charge is on the more positive electrode.

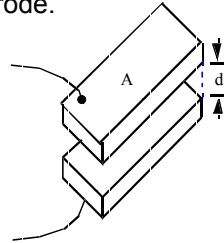
A simple *parallel-plate capacitor* is shown. If the area of the plate is A , the separation d , and the *dielectric constant* of the insulator is ϵ , the capacitance equals $C = A \epsilon / d$.



Symbol or

Constitutive relationship: $Q = C (V_a - V_b)$.

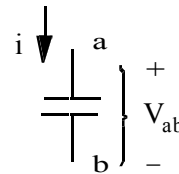(Q is positive on plate a if $V_a > V_b$)



But $i = \frac{dQ_a}{dt}$ so $i = C \frac{dv}{dt}$ equivalent to $Q = C v$

where we use the *associated reference directions*.

Copyright 2001, Regents of University of California

Version Date 02/02/03

ENERGY STORED IN A CAPACITOR


You might think the energy (in Joules) is QV , which has the dimension of joules. But during charging the average voltage was only half the final value of V .

Thus, energy is $\frac{1}{2} QV = \frac{1}{2} CV^2$.

Copyright 2001, Regents of University of California

ENERGY STORED IN A CAPACITOR (cont.)


More rigorous derivation: During charging, the power flow is $v \cdot i$ into the capacitor, where i is into + terminal. We integrate the power from $t = 0$ ($v = 0$) to $t = \text{end}$ ($v = V$). The integrated power is the energy
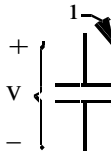
$$E = \int_{t = t_{\text{Initial}}}^{t = t_{\text{Final}}} v \cdot i \, dt = \int_{v = V_{\text{Initial}}}^{v = V_{\text{Final}}} v \frac{dq}{dt} \, dt = \int_{v = V_{\text{Initial}}}^{v = V_{\text{Final}}} v \, dq$$


but $dq = C \, dv$. (We are using small q instead of Q to remind us that it is time varying. Most texts use Q .)

$$E = \int_{v = V_{\text{Initial}}}^{v = V_{\text{Final}}} C v \, dv = \frac{1}{2} C V_{\text{Final}}^2 - \frac{1}{2} C V_{\text{Initial}}^2$$

CAPACITORS IN PARALLEL

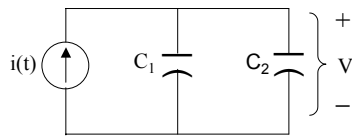


Add Currents


$$i(t) = C_1 \frac{dV}{dt} + C_2 \frac{dV}{dt}$$

Equivalent capacitance defined by

$$i = C_{\text{eq}} \, dV$$

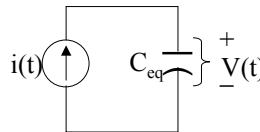

Clearly, $C_{\text{eq}} = C_1 + C_2$ CAPACITORS IN PARALLEL

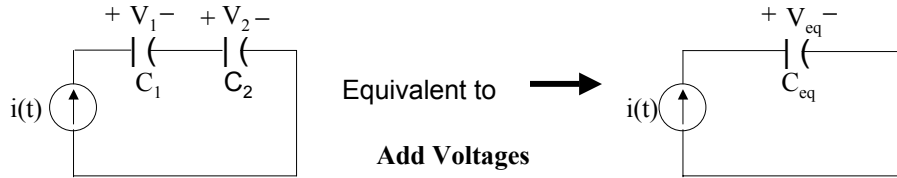CAPACITORS IN SERIES

Equivalent capacitance defined by

$$V_{eq} = V_1 + V_2 \quad \text{and} \quad i = C_{eq} \frac{dV_{eq}}{dt} = C_{eq} \frac{d(V_1 + V_2)}{dt}$$

$$i = C_1 \frac{dV_1}{dt} = C_2 \frac{dV_2}{dt}$$

$$\text{So } \frac{dV_1}{dt} = \frac{i}{C_1}, \quad \frac{dV_2}{dt} = \frac{i}{C_2}, \quad \text{so } \frac{dV_{eq}}{dt} = i \left(\frac{1}{C_1} + \frac{1}{C_2} \right) \equiv \frac{i}{C_{eq}}$$

$$\text{Clearly, } C_{eq} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2}} = \frac{C_1 C_2}{C_1 + C_2} \quad \text{CAPACITORS IN SERIES}$$

Capacitance and Inductance

- Capacitors: two plate example; Store energy in the electric field $Q = CV$, $I = C dV/dt$ and $V = (1/C)$ integral of voltage
- Computer example 1 mA current charging 1 pF
 $V(t) = (I/C)t = (10^{-3} \text{ A}/10^{-12} \text{ F}) t = 10^9 \text{ V/s } t$
- At D.C. time derivatives are zero $\Rightarrow C$ is open circuit
- C in parallel add; series $1/C = \text{sum}(1/C_i)$; short together (infinite current but conserve charge)
- Inductors: coil example; Store energy in the magnetic field; Flux = LI , $V = L dI/dt$ and $I = (1/L)$ (integral of voltage)
- At D.C. time derivatives are zero $\Rightarrow L$ is short circuit
- L in parallel $1/L = \text{sum}(1/L_i)$; series add; connect in series when have different currents $\Rightarrow L_1 I_1 + L_2 I_2 = (L_1 + L_2) I_{NEW}$

Example of I-V Graphs


Version Date 02/02/03

Resistors in Series

If two resistors are in series the current is the same; clearly the total voltage will be the sum of the two IR values i.e. $I(R_1+R_2)$.

Thus the equivalent resistance is R_1+R_2 and the I-V graph of the series pair is the same as that of the equivalent resistance.

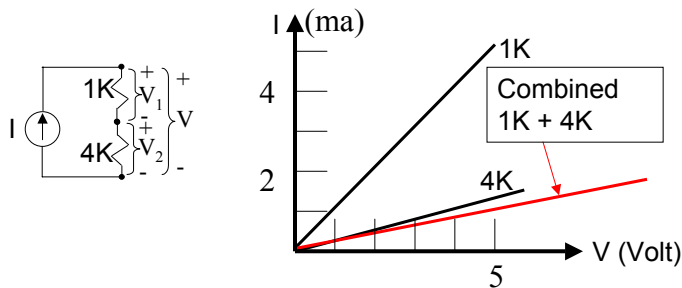Of course we can also find the I-V graph of the combination by adding the voltages directly on the I-V axes. Lets do an example for 1K + 4K resistors



Copyright 2001, Regents of University of California

Example of I-V Graphs


Version Date 02/02/03

Simple Circuit, e.g. voltage source + resistor.

If two circuit elements are in series the current is the same; clearly the total voltage will be the sum of the voltages i.e. $V_S + IR$.



We can graph this on the I-V plane. We find the I-V graph of the combination by adding the voltages V_S and IR at each current I .

Lets do an example for $V_S=2V$, $R=2K$

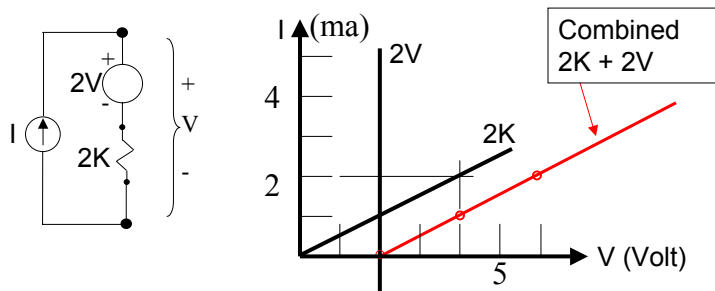


Copyright 2001, Regents of University of California

Simplest Equivalent Circuits

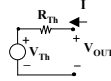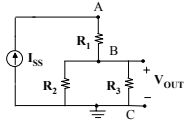


Thevenin

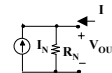

Norton

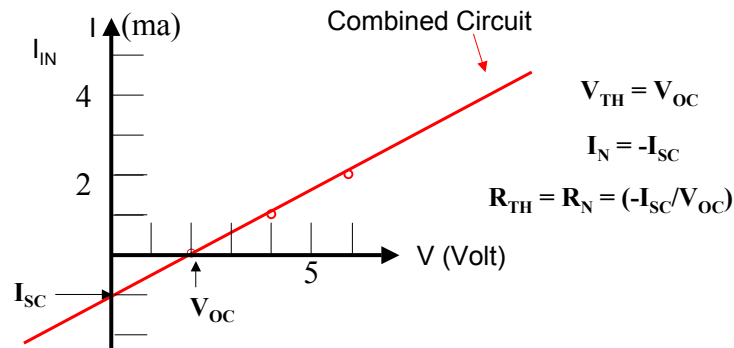An adequately equivalent circuit is one that has an I vs. V graph that is identical to that of the original circuit.



Copyright 2001, Regents of University of California

I vs. V and Equivalent Circuits

- I vs. V for ideal voltage source is a vertical line at $V = V_{SV}$
- I vs. V for ideal current source is a horizontal line at $I = I_{SC}$
- I vs. V for a circuit made up of ideal independent sources and resistors is a straight line.
- The simplest circuit for a straight line is an ideal voltage source and a resistor (Thevenin) or a current source and a parallel resistor (Norton)
- The easiest way to find the I vs. V line is to find the intercepts where $I = 0$ (open circuit voltage V_T) and where $V = 0$ (Short circuit current I_N)
- The short-cut for finding the $(\text{slope})^{-1} = R_T = R_N$ is to turn off all of the dependent sources to zero and find the remaining equivalent resistance between the terminals of the elements.

Copyright 2001, Regents of University of California