

EECS 42 Intro. electronics for CS Spring 2003 Lecture 4: 02/03/03 A.R. Neureuther
Version Date 02/02/03

EECS 42 Introduction to Electronics for Computer Science

Andrew R. Neureuther

Lecture #4

- Capacitors and Inductors
- Energy Stored in C and L
- Equivalent Circuits
 - Thevenin
 - Norton

<http://inst.EECS.Berkeley.EDU/~ee42/>

Copyright 2001, Regents of University of California

EECS 42 Intro. electronics for CS Spring 2003 Lecture 4: 02/03/03 A.R. Neureuther
Version Date 02/02/03

BASIC CIRCUIT ELEMENTS

- Voltage Source (always supplies some constant given voltage - like ideal battery)
- Current Source (always supplies some constant given current)
- Resistor (Ohm's law)
- Wire ("short" - no voltage drop)
- Capacitor (capacitor law - based on energy storage in electric field of a dielectric S&O 5.1)
- Inductor (inductor law - based on energy storage in magnetic field in space S&O 5.1)

Copyright 2001, Regents of University of California

EECS 42 Intro. electronics for CS Spring 2003 Lecture 4: 02/03/03 A.R. Neureuther
Version Date 02/02/03

Game Plan 02/03/03

Monday 02/03/03

- Capacitors and Inductors; Equivalent Sources
Schwarz and Oldham: 5.1-5.2, 3.1

Wednesday 02/05/03

- N-L Elements; Graphical Solutions; Power
Schwarz and Oldham: 3.2-3.4

Next (4th) Week

- RC Transient
Schwarz and Oldham: 8.1 plus Handouts

Problem Set #2 - Out 1/27/03 - Due 2/5/03 2:30 in box near 275 Cory
2.1 Flow; 2.2 KCL; 2.3 KVL; 2.4 resistor circuit; 2.5 Power

Problem Set #3 - Out 2/2/03 - Due 2/12/03 2:30 in box near 275 Cory
3.1 and 3.2 charging capacitors; 3.3-3.5; Equivalent Circuits;


Copyright 2001, Regents of University of California



EECS 42 Intro. electronics for CS Spring 2003 Lecture 4: 02/03/03 A.R. Neureuther
Version Date 02/02/03

CAPACITOR

Any two conductors a and b separated by an insulator with a difference in voltage V_{ab} will have an equal and opposite charge on their surfaces whose value is given by $Q = CV_{ab}$, where C is the **capacitance** of the structure, and the + charge is on the more positive electrode.

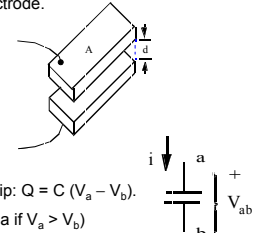A simple *parallel-plate capacitor* is shown. If the area of the plate is A, the separation d, and the *dielectric constant* of the insulator is ϵ , the capacitance equals $C = A \epsilon / d$.



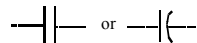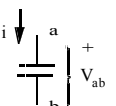Symbol  or 


Constitutive relationship: $Q = C (V_a - V_b)$.
(Q is positive on plate a if $V_a > V_b$)

But $i = \frac{dQ}{dt}$ so $i = C \frac{dv}{dt}$ equivalent to $Q = C v$
where we use the **associated reference directions**.

Copyright 2001, Regents of University of California

EECS 42 Intro. electronics for CS Spring 2003 Lecture 4: 02/03/03 A.R. Neureuther
Version Date 02/02/03

What Goes In the Circuit Element Boxes?

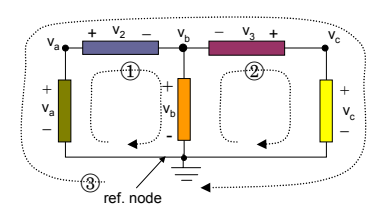

Copyright 2001, Regents of University of California

EECS 42 Intro. electronics for CS Spring 2003 Lecture 4: 02/03/03 A.R. Neureuther
Version Date 02/02/03

ENERGY STORED IN A CAPACITOR

You might think the energy (in Joules) is QV , which has the dimension of joules. But during charging the average voltage was only half the final value of V .


Thus, energy is $\int QV = \int CV^2$.

Copyright 2001, Regents of University of California

EECS 42 Intro. electronics for CS Spring 2003 Lecture 4: 02/03/03 A.R. Neureuther
Version Date 02/02/03

ENERGY STORED IN A CAPACITOR (cont.)

More rigorous derivation: During charging, the power flow is $v \cdot i$ into the capacitor, where i is into + terminal. We integrate the power from $t = 0$ ($v = 0$) to $t = \text{end}$ ($v = V$). The integrated power is the energy
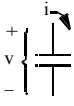
$$E = \int_{t = t_{\text{Initial}}}^{t = t_{\text{Final}}} v \cdot i \, dt = \int_{v = V_{\text{Initial}}}^{v = V_{\text{Final}}} v \frac{dq}{dt} dt = \int_{v = V_{\text{Initial}}}^{v = V_{\text{Final}}} v \, dq$$


but $dq = C \, dv$. (We are using small q instead of Q to remind us that it is time varying. Most texts use Q .)

$$E = \int_{v = V_{\text{Initial}}}^{v = V_{\text{Final}}} C v \, dv = \frac{1}{2} C V_{\text{Final}}^2 - \frac{1}{2} C V_{\text{Initial}}^2$$

Copyright 2001, Regents of University of California

EECS 42 Intro. electronics for CS Spring 2003 Lecture 4: 02/03/03 A.R. Neureuther
Version Date 02/02/03


Capacitance and Inductance

- Capacitors: two plate example; Store energy in the electric field $Q = CV$, $I = C \, dV/dt$ and $V = (1/C)$ integral of voltage
- Computer example 1 mA current charging 1 pF
 $V(t) = (I/C)t = (10^{-3} \text{ A}/10^{-12} \text{ F}) t = 10^9 \text{ V/s } t$
- At D.C. time derivatives are zero $\Rightarrow C$ is open circuit
- C in parallel add; series $1/C = \text{sum}(1/C_i)$; short together (infinite current but conserve charge)
- Inductors: coil example; Store energy in the magnetic field; Flux $= LI$, $V = L \, dI/dt$ and $I = (1/L)$ (integral of voltage)
- At D.C. time derivatives are zero $\Rightarrow L$ is short circuit
- L in parallel $1/L = \text{sum}(1/L_i)$; series add; connect in series when have different currents $\Rightarrow L_1 I_1 + L_2 I_2 = (L_1 + L_2) I_{\text{NEW}}$

Copyright 2001, Regents of University of California

EECS 42 Intro. electronics for CS Spring 2003 Lecture 4: 02/03/03 A.R. Neureuther
Version Date 02/02/03


CAPACITORS IN PARALLEL

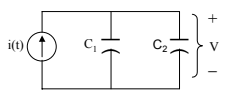

Add Currents

$$i(t) = C_1 \, d^v + C_2 \, d^v$$

Equivalent capacitance defined by
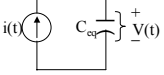
$$i = C_{\text{eq}} \, d^v$$


Clearly, $\frac{1}{C_{\text{eq}}} = \frac{1}{C_1} + \frac{1}{C_2}$ CAPACITORS IN PARALLEL

Copyright 2001, Regents of University of California

EECS 42 Intro. electronics for CS Spring 2003 Lecture 4: 02/03/03 A.R. Neureuther
Version Date 02/02/03


Example of I-V Graphs

Resistors in Series

If two resistors are in series the current is the same; clearly the total voltage will be the sum of the two IR values i.e. $I(R_1 + R_2)$.

Thus the equivalent resistance is $R_1 + R_2$ and the I-V graph of the series pair is the same as that of the equivalent resistance.

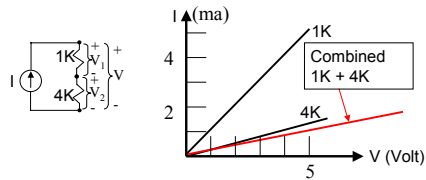
Of course we can also find the I-V graph of the combination by adding the voltages directly on the I-V axes. Lets do an example for 1K + 4K resistors



Copyright 2001, Regents of University of California

EECS 42 Intro. electronics for CS Spring 2003 Lecture 4: 02/03/03 A.R. Neureuther
Version Date 02/02/03

CAPACITORS IN SERIES

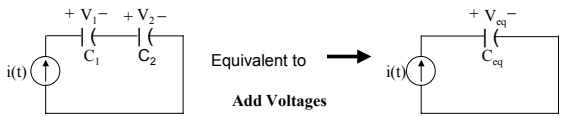

Add Voltages

Equivalent capacitance defined by

$$i = C_1 \, d^v_1 = C_2 \, d^v_2 \quad V_{\text{eq}} = V_1 + V_2 \text{ and } i = C_{\text{eq}} \, d^v_{\text{eq}} = C_{\text{eq}} \, d^v(V_1 + V_2)$$

So $\frac{d^v_1}{d^v_2} = \frac{C_2}{C_1}$, $\frac{d^v_2}{d^v_1} = \frac{C_1}{C_2}$, so $\frac{d^v_{\text{eq}}}{d^v} = i \left(\frac{1}{C_1} + \frac{1}{C_2} \right) \equiv \frac{1}{C_{\text{eq}}}$

Clearly, $\frac{1}{C_{\text{eq}}} = \frac{1}{C_1} + \frac{1}{C_2}$ CAPACITORS IN SERIES

Copyright 2001, Regents of University of California

EECS 42 Intro. electronics for CS Spring 2003 Lecture 4: 02/03/03 A.R. Neureuther
Version Date 02/02/03


Example of I-V Graphs

Simple Circuit, e.g. voltage source + resistor.

If two circuit elements are in series the current is the same; clearly the total voltage will be the sum of the voltages i.e. $V_S + IR$.


We can graph this on the I-V plane. We find the I-V graph of the combination by adding the voltages V_S and IR at each current I .

Lets do an example for $=2V$, $R=2K$

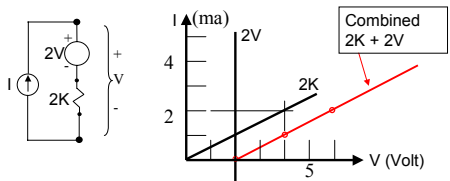


Copyright 2001, Regents of University of California

Simplest Equivalent Circuits

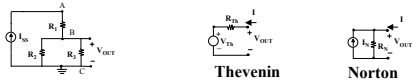

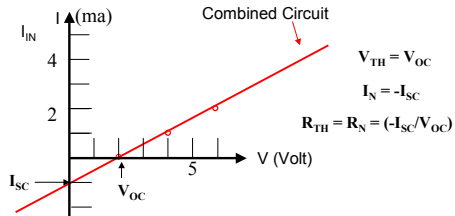An adequately equivalent circuit is one that has an I vs. V graph that is identical to that of the original circuit.



Copyright 2001, Regents of University of California

I vs. V and Equivalent Circuits

- I vs. V for ideal voltage source is a vertical line at $V = V_{SV}$
- I vs. V for ideal current source is a horizontal line at $I = I_{SC}$
- I vs. V for a circuit made up of ideal independent sources and resistors is a straight line.
- The simplest circuit for a straight line is an ideal voltage source and a resistor (Thevenin) or a current source and a parallel resistor (Norton)
- The easiest way to find the I vs. V line is to find the intercepts where $I = 0$ (open circuit voltage V_T) and where $V = 0$ (Short circuit current I_N)
- The short-cut for finding the (slope)⁻¹ = $R_T = R_N$ is to turn off all of the dependent sources to zero and find the remaining equivalent resistance between the terminals of the elements.

Copyright 2001, Regents of University of California