

EECS 42 Introduction to Electronics for Computer Science

Andrew R. Neureuther

Lecture #7

RC Circuits: For **viewgraphs handed out in class**
2/10/03 and on class web site under Lectures and
then **EECS42_Handout_RC** “Charging and
Discharging RC Circuits”

- **Easy Method**
- **Examples including Pulse Shape**

<http://inst.EECS.Berkeley.EDU/~ee42/>

Game Plan 02/05/03

Monday 02/10/03

- EC Response: Sketch/Trend, Exponential Solution**
Schwarz and Oldham: 8.1, Handout_RC VG 1-18

Wednesday 02/12/03

- Easy Method; Examples including Pulse Shape**
Handout_RC VG 19-28

Next (5th) Week

- Monday 2/17/03 is a UC Holiday (President's Day)**
- Nodal Analysis**
Schwarz and Oldham: pp. 53-58; 2.5- 2.6

Problem Set #4 – Out 2/10/03 - Due 2/19/03 2:30 in box in 240 Cory

RC Circuits: 4.1 sketch/trend; 4.2 exp form; 4.3 3-R's; 4.4 pulse shape