

**EECS 42 Introduction to Electronics for  
Computer Science  
Andrew R. Neureuther**

**Lecture # 14 Op-Amp Circuits and  
Comparators 4.3-4.4 (light on non-ideal)**

- A) Cascade Op-Amps**
- B) Integration/Differentiation Op-Amps**
- C) I vs. V of Op-Amps – Source Limits**
- D) Comparator Circuits**
- E) D to A Converters**

**<http://inst.EECS.Berkeley.EDU/~ee42/>**

**Game Plan 03/19/03**

**Monday 03/17/04**

- Monday: Circuit analysis with dependent sources  
(4.1-4.2)**

**Wednesday 03/19/03:**

- Comparators and op-amps (Comparator handout)**

**Next (10<sup>th</sup>) Week: After Spring Recess**

- Monday: 3/31/03 Logic with State Dependent Device  
593-595, 604-605**
- Wednesday: 4/02/03 Logic Static: Voltage Transfer  
Characteristic 606, Handout**

**Problem set #8: Half-Set - out Monday 3/17 and due at 2:30 4/02 in box in  
240 Cory – input/output impedance, comparators**

## NEGATIVE FEEDBACK

Familiar examples of negative feedback:

- Thermostat controlling room temperature
- Driver controlling direction of automobile
- Photochromic lenses in eyeglasses


Fundamentally  
pushes toward  
stability

Familiar examples of positive feedback:

- Microphone "squawk" in room sound system
- Mechanical bi-stability in light switches
- Thermonuclear reaction in H-bomb

Fundamentally  
pushes toward  
instability or  
bi-stability

## CASCADE OP-AMP CIRCUITS

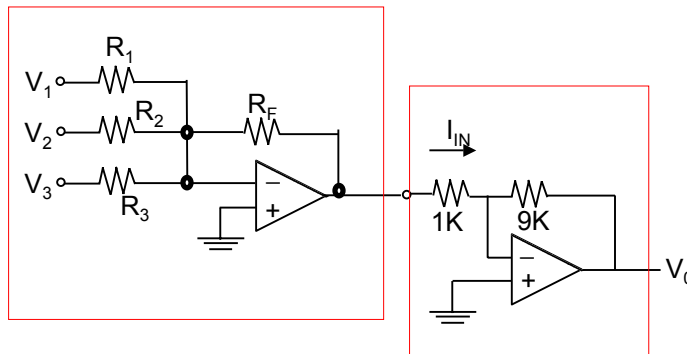


How do you get started on finding  $V_0$ ?

**Hint: Identify Stages**

**Hint:  $I_{IN}$  does not affect  $V_{O1}$**

See the further examples of op-amp circuits in the reader

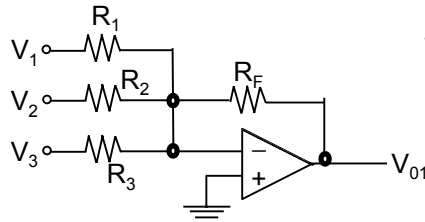
**CASCADE OP-AMP SOLUTION****FIRST STAGE IS "SUMMING JUNCTION" AMPLIFIER**

Solution:

$$i_{IN} \cong 0 \text{ and } V_{(-)} \cong V_{+} = 0$$


$$\text{KCL: } \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} + \frac{V_0}{R_F} = 0$$

$$\Rightarrow V_{01} = -\frac{R_F}{R_1} V_1 - \frac{R_F}{R_2} V_2 - \frac{R_F}{R_3} V_3$$

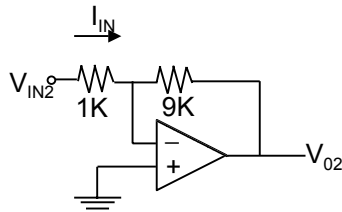**SECOND STAGE IS "INVERTING" AMPLIFIER**

$$V_{02} \cong -\frac{R_2}{R_1} V_{IN2}$$

Copyright 2001, Regents of University of California

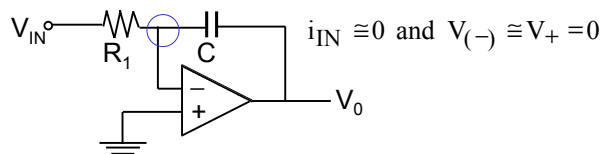
**INTEGRATING OP-AMP**

$$i_{IN} \cong 0 \text{ and } V_{(-)} \cong V_{+} = 0$$

**How do you get started on finding  $V_0$ ?****Hint:**  $i_{IN} \cong 0$  and  $V_{(-)} \cong V_{+} = 0$ **Hint:** KCL at  $V_{-}$  node with  $I_{IN} = 0$ 

Copyright 2001, Regents of University of California

### INTEGRATING OP-AMP

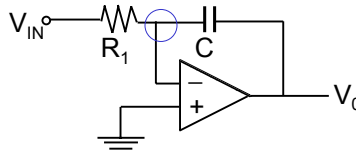


$$\frac{0 - V_{IN}}{R_1} + C \frac{\partial(0 - V_O)}{\partial t} = 0$$

Integrate from  $t_0$  to  $t$  to get  $V_O(t)$


$$V_O(t) = \frac{-1}{R_1 C} \int_{t_0}^t V_{IN}(t') dt'$$
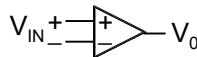
### OP-AMP I-V CHARACTERISTICS WITH RAILS




- Circuit model (ideal op-amp) gives the essential linear part
- But  $V_0$  cannot rise above some physical voltage related to the positive power supply  $V_{CC}$  ("upper rail")  $V_0 < V_{+RAIL}$
- And  $V_0$  cannot go below most negative power supply,  $V_{EE}$  i.e., limited by lower "rail"  $V_0 > V_{-RAIL}$

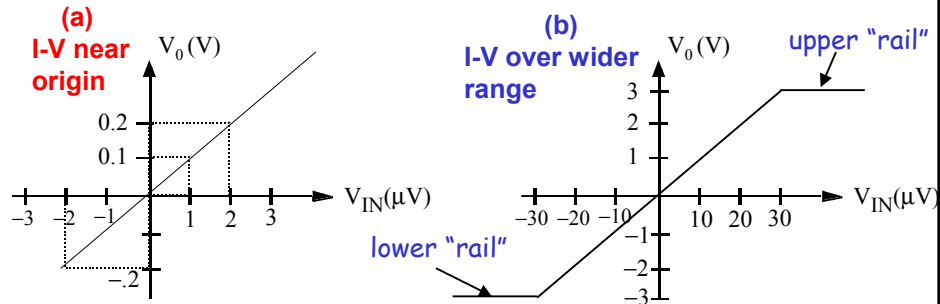Example: Amplifier with gain of  $10^5$ , with max  $V_0$  of 3V and min  $V_0$  of -3V.



## OP-AMP I-V CHARACTERISTICS WITH RAILS (cont.)

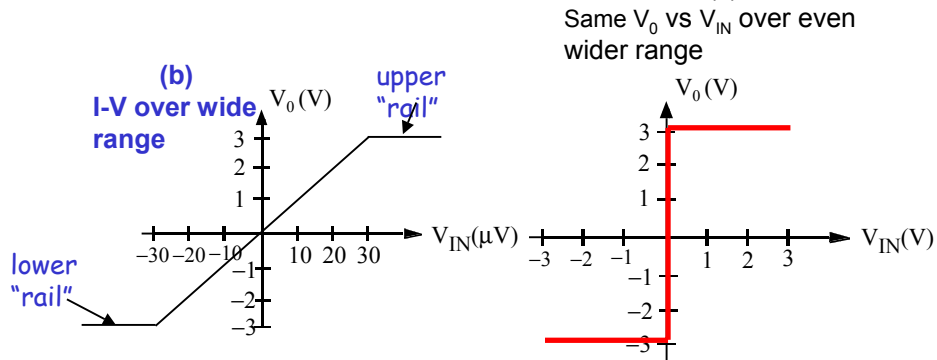
Example: Amplifier with gain of  $10^5$ , with upper rail of 3V and lower rail of -3V. We plot the  $V_0$  vs  $V_{IN}$  characteristics on two different scales



Copyright 2001, Regents of University of California

## SIMPLE A/D CONVERTER

I-V with equal X and Y axes

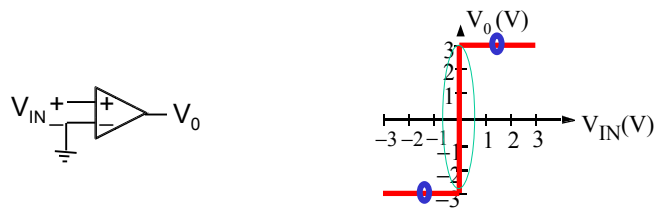



Note:

- (a) displays linear amplifier behavior ( $|V_{IN}| < 30 \mu\text{V}$ ) and stops at rails
- (b) shows comparator decision function (1 bit A/D converter centered at  $V_{IN} = 0$ ) where lower rail = logic "0" and upper rail = logic "1"


Copyright 2001, Regents of University of California
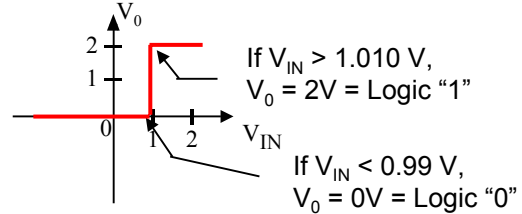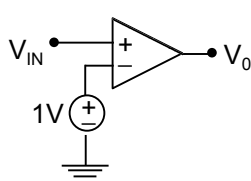
### OP-AMP USE AS COMPARATOR (A/D) MODE


Simple comparator with threshold at 1V. Design lower rail at 0V and upper rail at 2V (logic "1"). A = large (e.g.  $10^2$  to  $10^5$ )



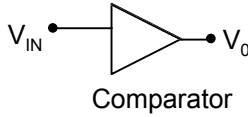NOTE: The actual diagram of a comparator would not show an amplifier with "offset" power supply as above. It would be a simple triangle, perhaps with the threshold level (here 1V) specified.



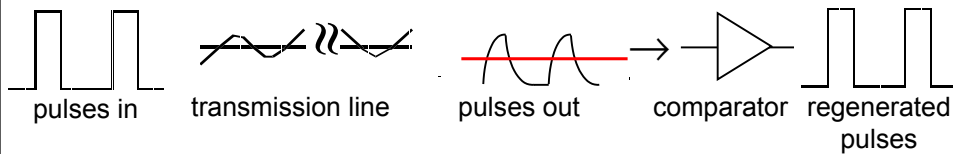
### ONE-BIT A/D CONVERSION REQUIRED IN DIGITAL SYSTEMS



As we saw, we set comparator **threshold** at a suitable value (e.g., halfway between rails) and comparator output goes to +rail if  $V_{IN} > V_{THRESHOLD}$  and to -rail if  $V_{IN} < V_{THRESHOLD}$ .

What would this circuit do?

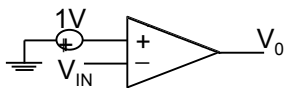


The **inverse** pulse shaped function is generated by applying the input voltage to V- and setting V+ to the threshold voltage.

### D/A CONVERSION

Version Date 03/16/03

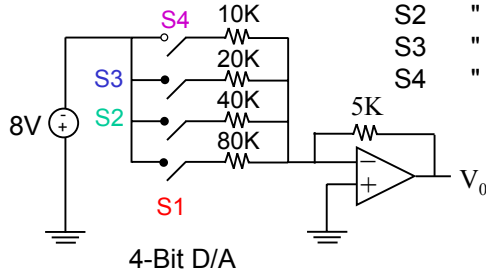Example: Digital representation of sound to analog  
(so you can hear it!) → D/A conversion

The summing junction op-amp provides a simple means of D/A conversion via **weighted-adder D/A converter**



- S1 closed if LSB = 1
- S2 " if next bit = 1
- S3 " if " " = 1
- S4 " if MSB = 1

Binary number	Analog output (volts)
0 0 0 0	0
0 0 0 1	.5
0 0 1 0	1
0 0 1 1	1.5
0 1 0 0	2
0 1 0 1	2.5
0 1 1 0	3
0 1 1 1	3.5
1 0 0 0	4
1 0 0 1	4.5
1 0 1 0	5
1 0 1 1	5.5
1 1 0 0	6
1 1 0 1	6.5
1 1 1 0	7
1 1 1 1	7.5

↑ MSB    ↑ LSB

Another way (not shown) is to sum **charges** instead of current with capacitor networks

Version Date 03/16/03

### CHARACTERISTIC OF A 4-BIT DAC

