

## EECS 42 Introduction to Electronics for Computer Science

### Andrew R. Neureuther

#### Lecture # 16 Logic with a State Dependent Device

S&O pp. 593-595, 604-606 (read for graphs and not physics or equations), plus Handout of these viewgraphs.

**A) State Dependent Device  $I_{OUT}$  vs.  $V_{OUT}$**

**B) Load Line Analysis for Logic Levels**

**C) Voltage Transfer Characteristics**

**VTC = plot of  $V_{OUT}$  vs.  $V_{IN}$**

**D) 42S\_NMOS Pull-Down Device and Logic**

**<http://inst.EECS.Berkeley.EDU/~ee42/>**

## Game Plan 03/31/03

#### Monday 03/31/04

- Welcome back plus HW#8 coaching
- State Dependent Devices (Transistors)
- Load Line, VTC, Pull Down Device (42S\_NMOS)

#### Wednesday 04/02/03:

- Pull-Up Device (42S\_PMOS)
- VTC and  $V_{MID}$


#### Next (11<sup>th</sup>) Week:

- Monday: 4/7/03 Logic Dynamic via Switched Resistor
- Wednesday: 4/09/03 Quiz; Complementary Gates

**Problem set #8: Half-Set - out Monday 3/17 and due at 2:30 4/02 in box in 240 Cory – input/output impedance, comparators**

**Problem set #9: Monday 3/31 and due at 2:30 4/09 in box in 240 Cory – Static Analysis of an Inverter with simplified EE 42 Device Models**
 
### EXAMPLE CIRCUIT: INCREASED INPUT RESISTANCE



Analysis: apply  $i_{TEST}$  and evaluate  $v_{TEST}$

$$v_{IN} = R_{IN} i_{TEST} \quad v_{TEST} = R_{IN} i_{TEST} + v_E$$

**KCL**  $\frac{v_E}{R_E} + \frac{v_E}{R_O} - i_{TEST} - G_m R_{IN} i_{TEST} = 0$



Check for special case for  $R_O$  infinite  $\frac{v_{TEST}}{i_{TEST}} = R_{IN} + (1 + G_m R_{IN}) R_E$

Similar to the homework


**Intuitive Explanation:**  $R_E$  puts  $R_{IN}$  on a node whose voltage increases in response to current in  $R_{IN}$ .
  
### OP-AMP USE AS COMPARATOR (A/D) MODE


Simple comparator with threshold at 1V. Design lower rail at 0V and upper rail at 2V (logic "1"). A = large (e.g.  $10^2$  to  $10^5$ )



 NOTE: The actual diagram of a comparator would not show an amplifier with "offset" power supply as above. It would be a simple triangle, perhaps with the threshold level (here 1V) specified.


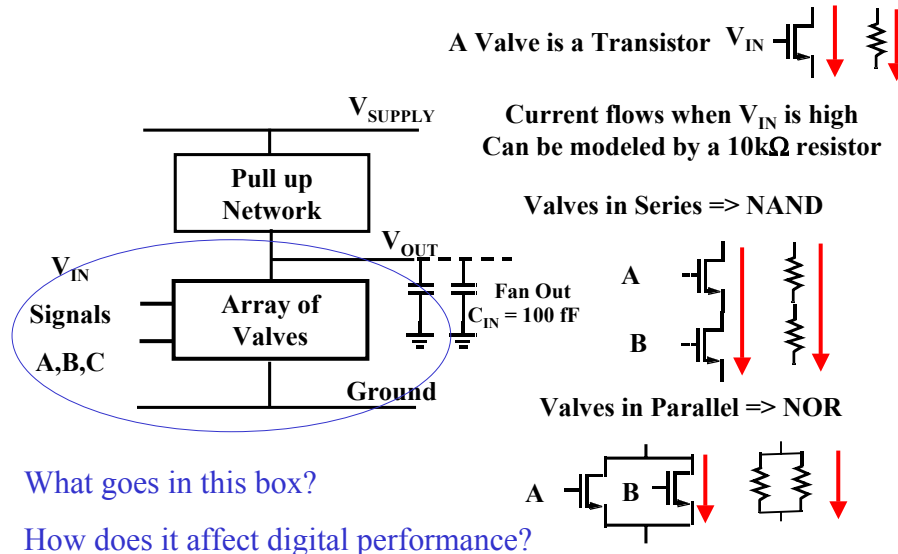
## Logic Gates – How are they built in practice?



Copyright 2001, Regents of University of California

## Digital Logic from State-Dependent Three-Terminal Devices


Three-terminal devices such as MOS transistors have characteristics (such as  $I_{OUT}$  vs.  $V_{OUT}$  curves) on the output side that can be programmed by changing signals on the input side (such as the input voltage).

The input can thus be viewed as changing or programming the ‘State’ of the output of the device.

Three-terminal devices whose ‘State’ can be programmed can be used to make digital logic devices for computers that respond to input signals.


Copyright 2001, Regents of University of California
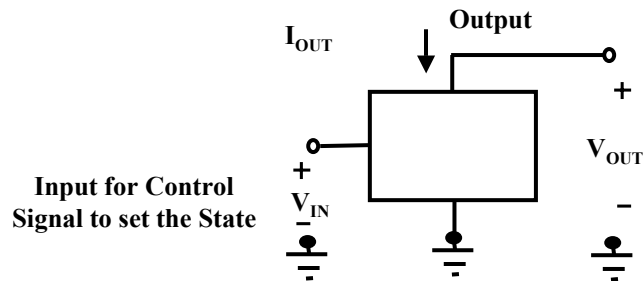
## State-Dependent Three-Terminal Device Element




Copyright 2001, Regents of University of California
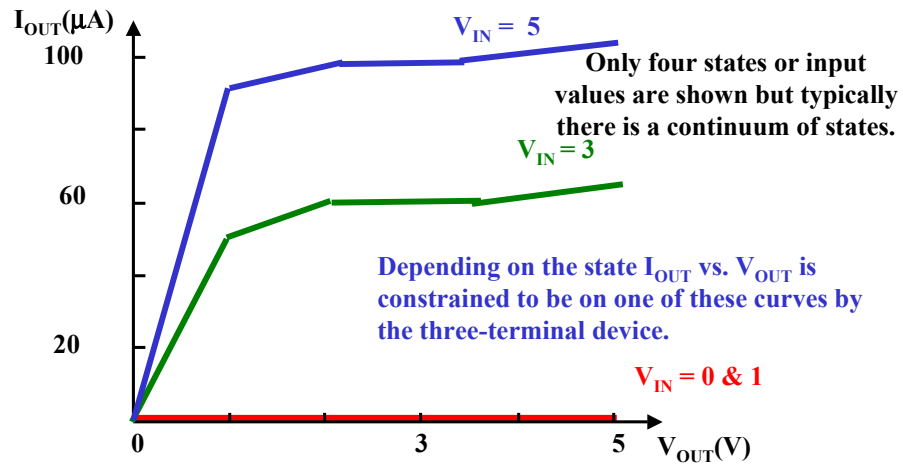
## State-Dependent Device $I_{OUT}$ vs. $V_{OUT}$



Copyright 2001, Regents of University of California

## Terminology for a Logic Circuit

 

$V_{DD}$  = Power supply voltage (D is from Drain)

**Pull-Down Network** = Set of devices used to carry current from the output node to ground to discharge the output node to ground.

**Pull-Up Network** = Set of devices used to carry current from the power supply to the output node to charge the output node to the power supply voltage.


$I_{OUT}$  = Current for the device under study.

$V_{TD}$  = Threshold Voltage value of  $V_{IN}$  at which the Pull-Down (NMOS transistor) begins to conduct.

$V_{OUT-SAT-D}$  = Value of  $V_{OUT}$  beyond which the current  $I_{OUT-D}$  saturates at the (drain) current saturation value  $I_{OUT-SAT-D}$ .

Copyright 2001, Regents of University of California

## Thevenin Model For Pull-Up Device

 

$$V_{THEVENIN} = V_{DD}$$

$$I_{OUT \text{ SHORT CIRCUIT}} = (V_{DD}/R_{PULL \text{ UP}})$$

Example:

$$V_{DD} = 5V \text{ and } R_{PULL \text{ UP}} = 100k\Omega$$


$$V_{THEVENIN} = 5V$$

$$I_{OUT \text{ SHORT CIRCUIT}} = 50 \mu A$$

Copyright 2001, Regents of University of California
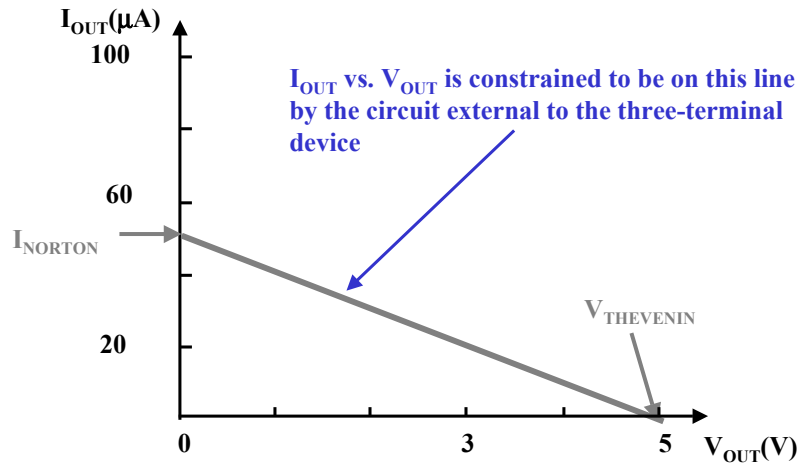
## Thevenin Model For Pull-Up Device


$I_{OUT}$  vs.  $V_{OUT}$   
For the Pull-Up Resistor and  $V_{DD}$



Copyright 2001, Regents of University of California

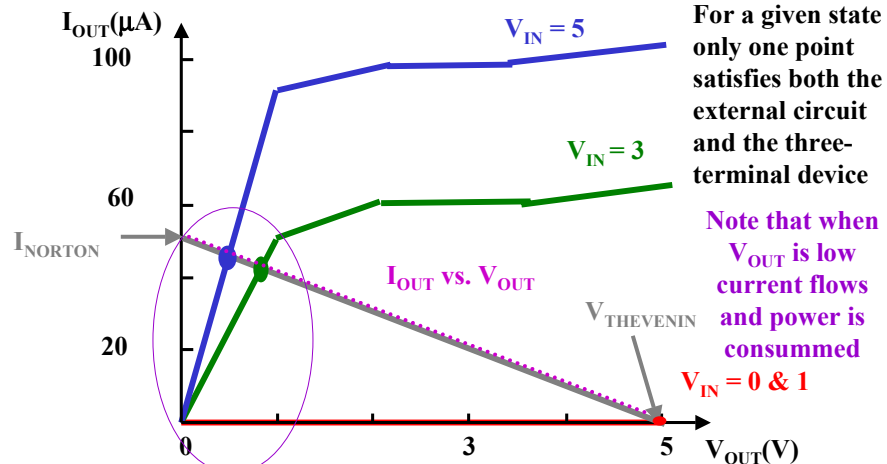
## Composite Current Plot for the Logic Circuit

Three-Terminal Device  
Plus Load Line for the Pull-Up Device



Copyright 2001, Regents of University of California

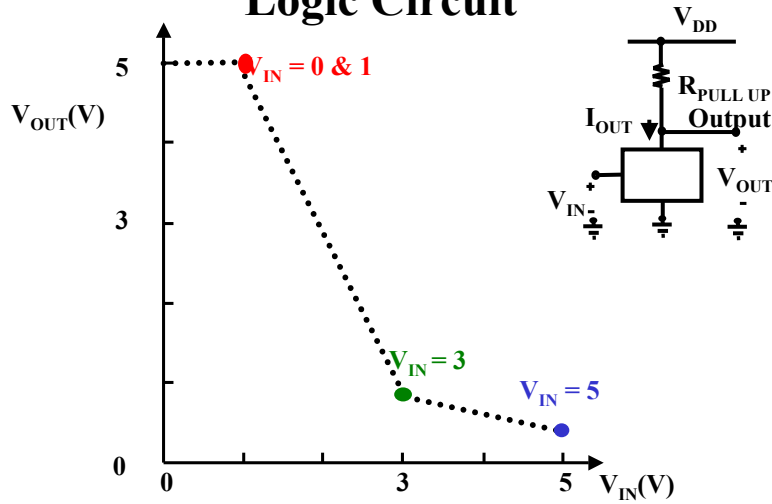
## Voltage Transfer Function for the Logic Circuit



Copyright 2001, Regents of University of California
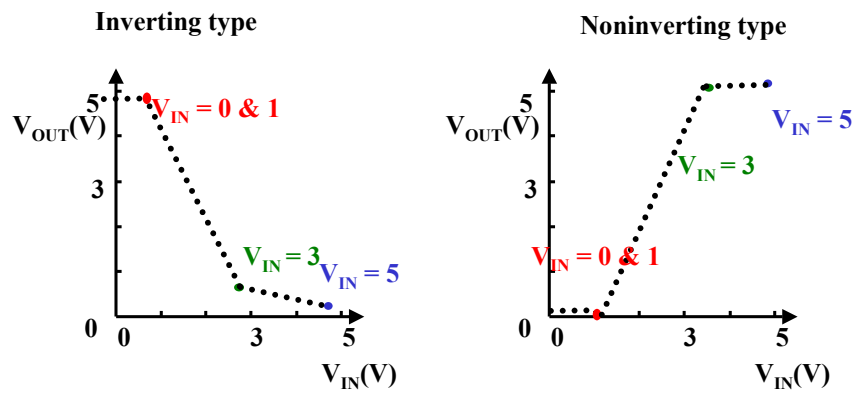
## Voltage Transfer Function: $V_{OUT}$ vs. $V_{IN}$

The  $V_{OUT}$  vs.  $V_{IN}$  characteristic is another view of the logic gate that is used to determine the inverting and noninverting nature of a gate.



Copyright 2001, Regents of University of California

## Saturation Current 42S\_NMOS Model

Current  $I_{OUT}$  only flows when  $V_{IN}$  is larger than the threshold value  $V_{TD}$  and the current is proportional to  $V_{OUT}$  up to  $V_{OUT-SAT-D}$  where it reaches the saturation current


$$I_{OUT-SAT-D} = k_D (V_{IN} - V_{TD}) V_{OUT-SAT-D}$$

Note that we have added an extra parameter to distinguish between threshold ( $V_{TD}$ ) and saturation ( $V_{OUT-SAT-D}$ ).

 Example:

$k_D = 25 \mu A/V^2$     Use these  
 $V_{TD} = 1V$         values in the  
 $V_{OUT-SAT-D} = 1V$     homework.

$$I_{OUT-SAT-PD} = 25 \frac{\mu A}{V^2} (3V - 1V) 1V = 50 \mu A$$




Copyright 2001, Regents of University of California

## Drawing $I_{OUT}$ as function of $V_{IN}$ and $V_{OUT}$ for the 42S\_NMOS Pull-Down Device

The equations are expressly designed for EE42 to make it very simple to draw  $I_{OUT}$  vs.  $V_{OUT}$

 
- 1) For  $V_{IN} < V_{TD}$ , the current is zero.
- 2) For  $V_{IN} > V_{TD}$ , first evaluate the current  $I_{OUT}$  at  $V_{OUT} = V_{TD}$  and plot the single point  $(I_{OUT}, V_{OUT})$
- 3) Draw a line from this point to the origin to create the linear region.
- 4) Draw a horizontal line from this point to create the saturation region



Copyright 2001, Regents of University of California



 
### States of 42S\_NMOS are Voltage Levels of $V_{IN}$




Copyright 2001, Regents of University of California
 
### Composite Current Plot for the 42S\_NMOS Logic Circuit



Copyright 2001, Regents of University of California
 
## Composite Current Plot for the 42S\_NMOS Circuit with 200kΩ Load to Ground



## Voltage Transfer Function for the 42S\_NMOS Logic Circuit w/wo Load

