

**EECS 42 Introduction to Electronics for
Computer Science
Andrew R. Neureuther**

Lecture # 19 Logic Transients

Handout of Wed Lecture.

A) Quiz

B) Worst Case CMOS Delay

C) Delay in CMOS Cascade

<http://inst.EECS.Berkeley.EDU/~ee42/>

Game Plan 04/07/03

Last Week: Static Logic: NMOS, CMOS; Graphical Solution and VTC) {All of this will be on 2nd Midterm)

Monday 4/07/03:

- Discharging Capacitors with NMOS and Eq. Resistance
- CMOS Logic and Propagation delay


Wednesday 04/09/03:

- QUIZ: Digital Blocks including timing diagrams and Dependent sources including Op-Amps
- Worst Case CMOS delay, Cascade and CMOS Latch

Next (11th) Week: Diodes and MOS Operation

No Problem set for 4/16 as Midterm 4/16: Lectures 1-17 with emphasis on Lectures 10-17; Review Session Monday 5:30-7PM

 $\frac{3}{4} V_{DD}/I_{SAT}$ Physical Interpretation



$\frac{3}{4} V_{DD}$ is the average value of V_{OUT}

Approximate the NMOS device curve by a straight line from (0,0) to $(I_{OUT-SAT-D}, \frac{3}{4} V_{DD})$.

Interpret the straight line as a resistor with

$$\text{slope} = 1/R = \frac{3}{4} V_{DD}/I_{SAT}$$

Copyright 2001, Regents of University of California

Switched Equivalent Resistance Values

The resistor values depend on the properties of silicon, geometrical layout, design style and technology node.

n-type silicon has a carrier mobility that is 2 to 3 times higher than p-type.

The resistance is inversely proportion to the gate width/length in the geometrical layout.

Design styles may restrict all NMOS and PMOS to be of a predetermined fixed size.


The current per unit width of the gate increases nearly inversely with the linewidth.

For convenience in EE 42 we assume $R_D = R_U = 10 \text{ k}\Omega$

Copyright 2001, Regents of University of California

CMOS Logic Gate: Example Inputs

A = 0
B = 1
C = 1

 

PMOS A conducts; B and C Open

Output is High


= 0

NMOS B and C conduct; A open

Logic is Complementary and produces F = 0

Copyright 2001, Regents of University of California

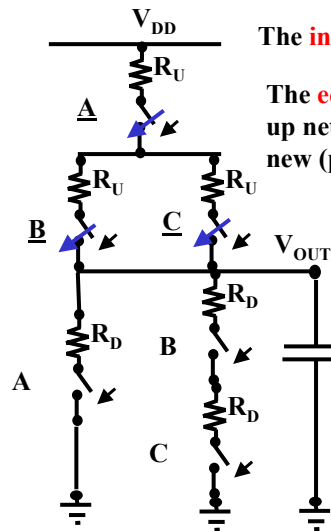Logic Gate Propagation Delay: Initial State



The **initial state** depends on the old (previous) inputs.

The **equivalent resistance** of the pull-down or pull-up network for the transient phase depends on the new (present) input state.


Example: A=0, B=0, C=0 for a long time.

These inputs provided a path to V_{DD} for a long time and the capacitor has precharged up to $V_{DD} = 5V$.

$C_{OUT} = 50 \text{ fF}$


Copyright 2001, Regents of University of California

Logic Gate Propagation Delay: Transient

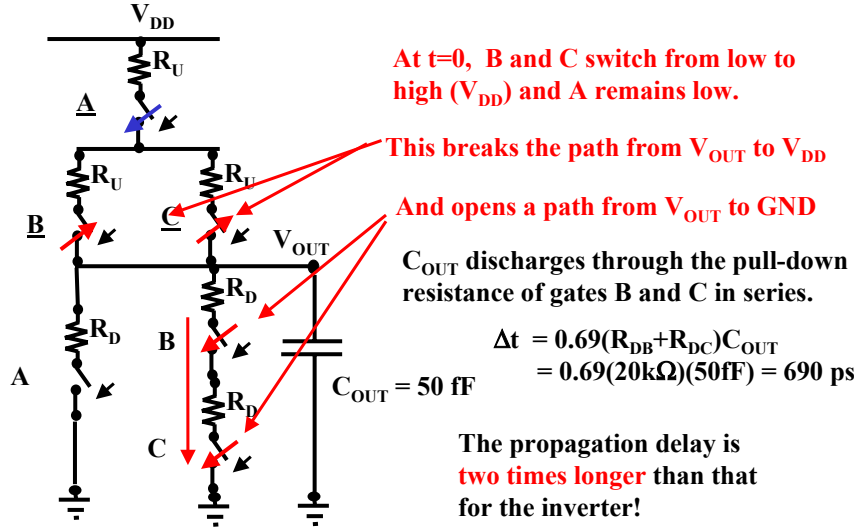

Copyright 2001, Regents of University of California


Logic Gate: Worst Case Scenarios

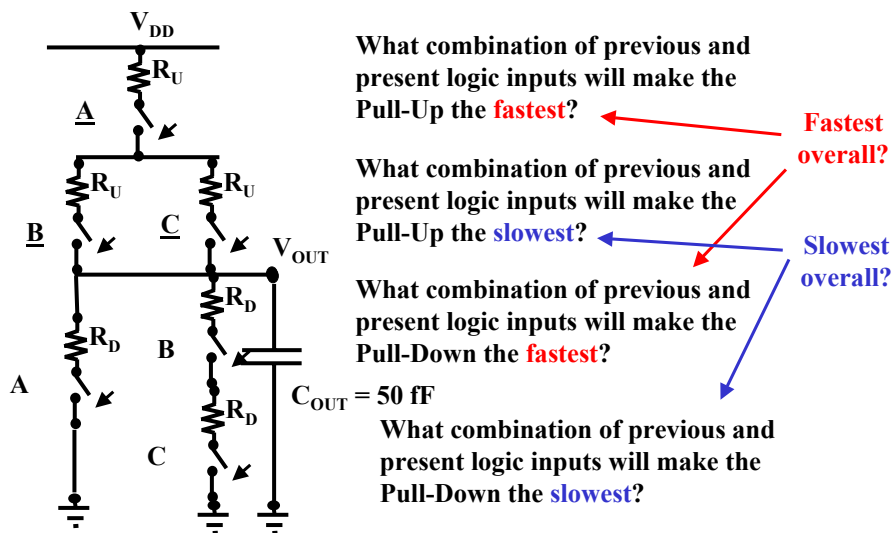

Copyright 2001, Regents of University of California

Logic Gate Cascade

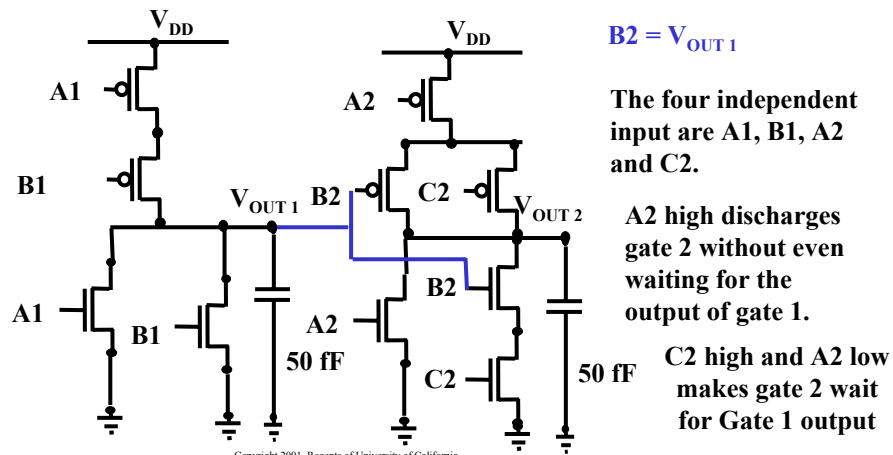
To avoid large resistance due to many gates in series, logic functions with 4 or more inputs are usually made from cascading two or more 2-4 input blocks.



Data Synchronization problem

- Combinatorial logic gates can give incorrect answers prematurely and may take several gate propagation delays produce an answer.
- Clocks (signals as to when to proceed) and latches (which capture and hold the correct outputs) can provide synchronization.

Latch Controlled by a Clock

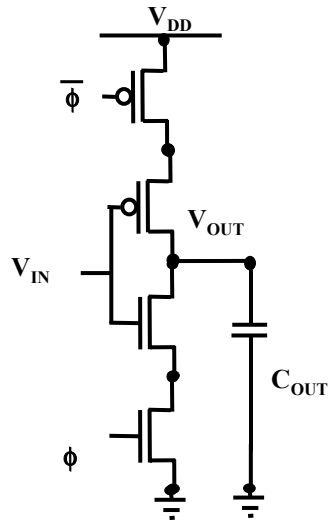


An inverter with clocked devices in series can form a latch.

When the clock ϕ is high its complement $\bar{\phi}$ is low and the inverter operates.

To synchronize the data the clock remains low until the data is correct at all locations on the chip. When the clock goes high the inverse of the data is passed.

Copyright 2001, Regents of University of California

Latch Work Best In Pairs

 

The first stage operates while the clock is low and inverts and amplifies the arriving signal and charges or discharges C_{L1} .

The second stage operates while the clock is high and inverts the signal on C_{L1} to charge or discharge C_{L2} and downstream logic gate inputs.

Copyright 2001, Regents of University of California