

EECS 42 Introduction to Electronics for Computer Science

Andrew R. Neureuther

Lecture # 27 Review For Final

Coverage and Emphasis Handout.


- A) Diodes with circuits and MOS Resistance
 - B) Static NMOS and CMOS
 - C) CMOS resistor model and Delay
 - D) Worst Case Delay, Timing, Latches
 - E) Op-Amps and Dependent Sources
- <http://inst.EECS.Berkeley.EDU/~ee42/>

Copyright 2001, Regents of University of California

Lecture 7

PULSE: Output is Rising exponential
then Falling exponential

 Example: Switch rises at $t=0$, falls at $t = 0.1, 1$ or $10\mu\text{sec}$ (Do $1\mu\text{sec}$ case)




Solution: for $RC = 1\mu\text{sec}$:
during the first rise V obeys:

$$V = 5 \left[1 - e^{-\frac{t}{10^{-6}}} \right]$$

Thus at $t = 1\mu\text{sec}$, rising voltage reaches

$$5 \left[1 - e^{-1} \right] = 3.16\text{V}$$

 
Now starting at $1\mu\text{sec}$ we are discharging the capacitor so the form is a falling exponential with initial value 3.16V :



Copyright 2001, Regents of University of California


EXAMPLE WITH BOTH SPECIAL CASES

Lecture 8

 

Copyright 2001, Regents of University of California

CASCADE OP-AMP CIRCUITS

 

How do you get started on finding V_0 ?

Hint: Identify Stages

Hint: I_{IN} does not affect V_{O1}


See the further examples of op-amp circuits in the reader

Copyright 2001, Regents of University of California

EXAMPLE CIRCUIT: INCREASED INPUT RESISTANCE

Lecture 20

Add resistor R_E

 

The output has been assumed to be shorted

Analysis: apply i_{TEST} and evaluate v_{TEST}

$$v_{IN} = R_{IN} i_{TEST} \quad v_{TEST} = R_{IN} i_{TEST} + v_E$$

KCL
$$\frac{v_E}{R_E} + \frac{v_E}{R_O} - i_{TEST} - G_m R_{IN} i_{TEST} = 0$$

Check for special case for R_O infinite
$$\frac{v_{TEST}}{i_{TEST}} = R_{IN} + (1 + G_m R_{IN}) R_E$$


Similar to the homework

Intuitive Explanation:
 R_E puts R_{IN} on a node whose voltage increases in response to current in R_{IN} .

Lecture 12

TIMING DIAGRAMS

Show transitions of variables vs time

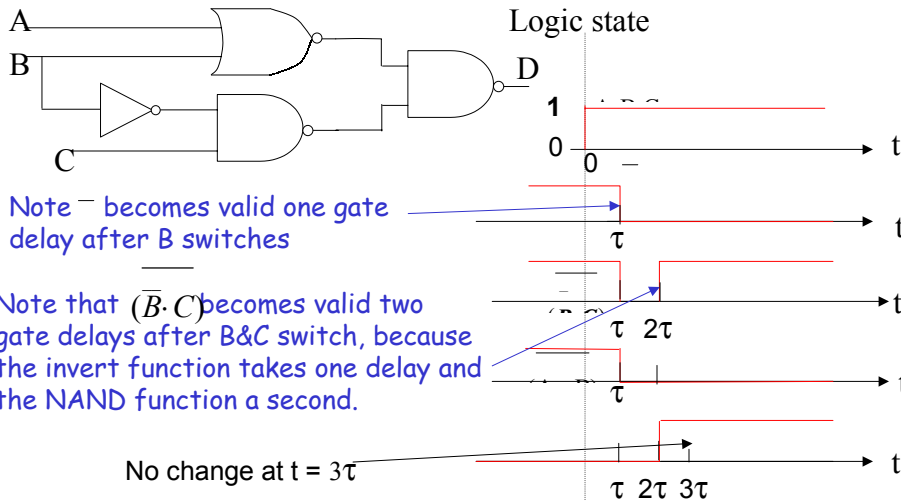


Note \bar{B} becomes valid one gate delay after B switches

Note that $(\bar{B} \cdot C)$ becomes valid two gate delays after B & C switch, because the invert function takes one delay and the NAND function a second.


No change at $t = 3\tau$

Lecture 23 DIODE I-V CHARACTERISTICS AND MODELS

 The equation $I = I_0 \exp(qV/kT - 1)$ is graphed below for $I_0 = 10^{-15}$ A



 
The characteristic is described as a “rectifier” – that is, a device that permits current to pass in only one direction. (The hydraulic analog is a “check valve”.) Hence the symbol:



Copyright 2001, Regents of University of California


Simple “Perfect Rectifier” Model

 If we can ignore the small forward-bias voltage drop of a diode, a simple effective model is the “perfect rectifier,” whose I-V characteristic is given below:



Physics of Current Flow, Resistance, Resistivity

Lecture 24

 

$E = V/L$.
 $I = V/R$
 $R = \rho L/A = (1/q \mu N) L/W t = (L/W) / \mu(qNt)$

But $q N t$ has the dimensions of charge per unit area and represents the charge per unit area in a film of thickness t when the film has N carriers/cm³ and is t units thick. Thus we call $q N t$ the “ Q ” and

$R = (L/W) / \mu Q = L/W R_{\square}$

Where R_{\square} is the resistance of a “square” of the film. Clearly if L is four times W , then $R = 4 R_{\square}$.

Copyright 2001, Regents of University of California

Lecture 17

Version Date 5/10/03

Saturation Current NMOS Model

Current I_{OUT} only flows when V_{IN} is larger than the threshold value V_{TD} and the current is proportional to V_{OUT} up to $V_{OUT-SAT-D}$ where it reaches the saturation current


$$I_{OUT-SAT-D} = k_D (V_{IN} - V_{TD}) V_{OUT-SAT-D}$$

Note that we have added an extra parameter to distinguish between threshold (V_{TD}) and saturation ($V_{OUT-SAT-D}$).

 Example:

$k_D = 25 \mu A/V^2$ Use these values in the homework.
 $V_{TD} = 1V$
 $V_{OUT-SAT-D} = 1V$

$$I_{OUT-SAT-PD} = 25 \frac{\mu A}{V^2} (3V - 1V) 1V = 50 \mu A$$




Copyright 2001, Regents of University of California

Version Date 5/10/03

Composite Current Plot for the 42PD Circuit with 200k Ω Load to Ground


Lecture 16

 

Copyright 2001, Regents of University of California

Voltage Transfer Function for the 42PD Logic Circuit w/wo Load

Lecture 16

 


Copyright 2001, Regents of University of California

Lecture 17

Transistor Inverter Example

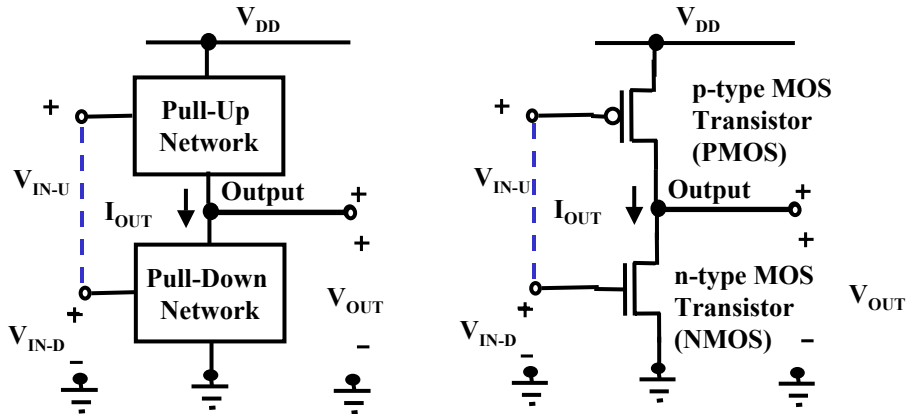
It may be simpler to just think of PMOS and NMOS transistors instead of a general 3 terminal pull-up or pull-down devices or networks.



Copyright 2001, Regents of University of California

Composite I_{OUT} vs. V_{OUT} for CMOS


Lecture 17

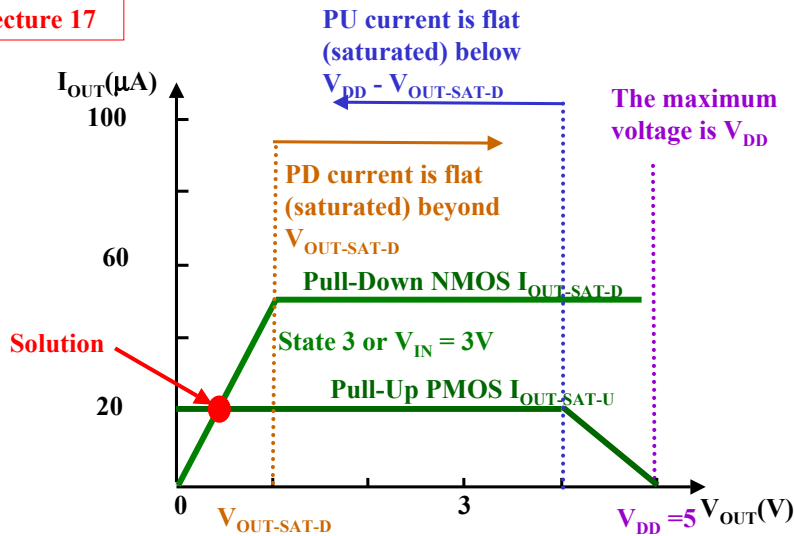

Copyright 2001, Regents of University of California

Voltage Transfer Function for the Complementary Logic Circuit


Lecture 17

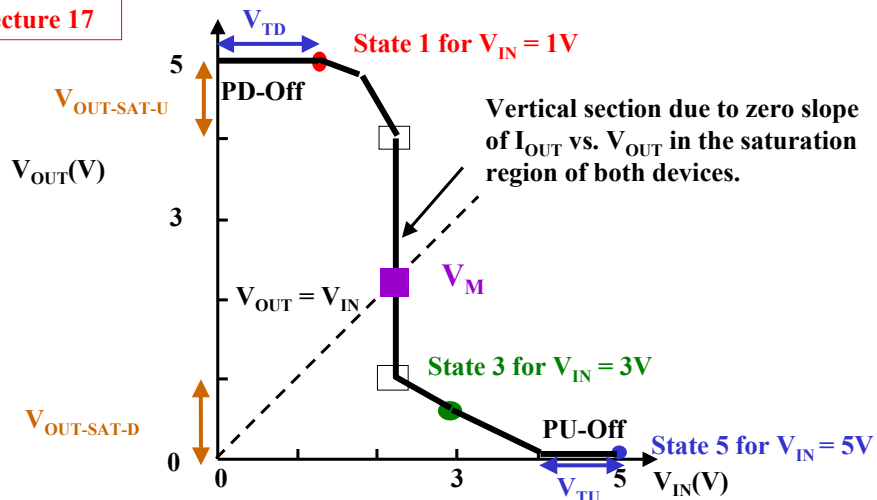

Copyright 2001, Regents of University of California

$\frac{3}{4} V_{DD}/I_{SAT}$ Physical Interpretation

Lecture 18

 

$\frac{3}{4} V_{DD}$ is the average value of V_{OUT}

Approximate the NMOS device curve by a straight line from (0,0) to ($I_{OUT-SAT-D}, \frac{3}{4} V_{DD}$).

Interpret the straight line as a resistor with


$$\text{slope} = 1/R = \frac{3}{4} V_{DD}/I_{SAT}$$

Copyright 2001, Regents of University of California

Lecture 18

Inverter Propagation Delay

Discharge (pull-down)

 

$$\Delta t = 0.69R_D C_{OUT} = 0.69(10k\Omega)(50fF) = 345 \text{ ps}$$

Discharge (pull-up)


$$\Delta t = 0.69R_U C_{OUT} = 0.69(10k\Omega)(50fF) = 345 \text{ ps}$$

Copyright 2001, Regents of University of California

CMOS Logic Gate: Example Inputs

Lecture 18

A = 0
B = 1
C = 1

 

PMOS A conducts; B and C Open

Output is High

= 0


NMOS B and C conduct; A open

Logic is Complementary and produces F = 0

Copyright 2001, Regents of University of California

Lecture 19

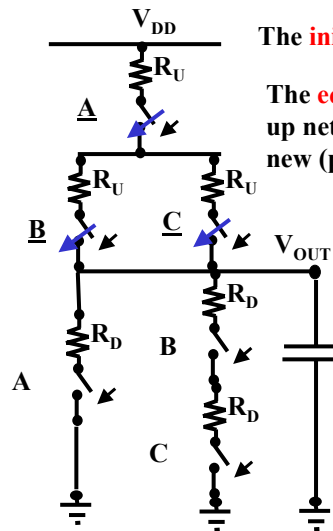Logic Gate Propagation Delay: Initial State



The **initial state** depends on the old (previous) inputs.

The **equivalent resistance** of the pull-down or pull-up network for the transient phase depends on the new (present) input state.

Example: A=0, B=0, C=0 for a long time.

These inputs provided a path to V_{DD} for a long time and the capacitor has precharged up to $V_{DD} = 5V$.


$C_{OUT} = 50 \text{ fF}$

Copyright 2001, Regents of University of California

Lecture 20

Logic Gate Cascade

 To avoid large resistance due to many gates in series, logic functions with 4 or more inputs are usually made from cascading two or more 2-4 input blocks.



$B2 = V_{OUT1}$


The four independent input are A1, B1, A2 and C2.

A2 high discharges gate 2 without even waiting for the output of gate 1.

C2 high and A2 low makes gate 2 wait for Gate 1 output


Lecture 21

Latch Work Best In Pairs

 


The first stage operates while the clock is low and inverts and amplifies the arriving signal and charges or discharges C_{L1} .

The second stage operates while the clock is high and inverts the signal on C_{L1} to charge or discharge C_{L2} and downstream logic gate inputs.

 

Lecture 22


Latch Operation: Pipelined

 

Lecture 22

Latch Timing Diagram

A1 = 0
B2 = 1
C2 = 0
B1 = 1 => 0

 

Latency 32 inverter delays

Throughput = $1/(20 \times 345\text{ps}) = 0.145 \text{ GHz}$

Lecture 22

Latency and Throughput

Latency L is the delay between the rising edge of the clock on L0 and the data being valid internally in the last latch.

$$\begin{aligned} L_{\text{LUMPED}} &= \tau_{L_EXT} + \tau_{\text{GATE1}} + \tau_{\text{GATE2}} + \tau_{L_INT} \\ &= 2\tau_{\text{INV}} + 2\tau_{\text{INV}} + 2\tau_{\text{INV}} + 2\tau_{\text{INV}} = 8\tau_{\text{INV}} \end{aligned}$$

$$\begin{aligned} L_{\text{PIPELINED}} &= \tau_{L_EXT} + \tau_{\text{GATE1}} + \tau_{L_INT} + \tau_{L_EXT} + \tau_{\text{GATE2}} + \tau_{L_INT} \\ &= 2\tau_{\text{INV}} + 2\tau_{\text{INV}} + 2\tau_{\text{INV}} + 2\tau_{\text{INV}} + 2\tau_{\text{INV}} + 2\tau_{\text{INV}} = 12\tau_{\text{INV}} \end{aligned}$$

Throughput T is the bits per second through the latches and is the maximum clock frequency.

$$\begin{aligned} P_{\text{LUMPED}} &= \tau_{L_EXT} + \tau_{\text{GATE1}} + \tau_{\text{GATE2}} + \tau_{L_INT} \\ &= 2\tau_{\text{INV}} + 2\tau_{\text{INV}} + 2\tau_{\text{INV}} + 2\tau_{\text{INV}} = 8\tau_{\text{INV}} \\ F_{\text{LUMPED}} &= 1/8(345\text{ps}) = 0.36 \text{ GHz} \end{aligned}$$

$$\begin{aligned} P_{\text{PIPELINED}} &= \tau_{L_EXT} + \text{MAX}(\tau_{\text{GATE1}}, \tau_{\text{GATE2}}) + \tau_{L_INT} \\ &= 2\tau_{\text{INV}} + 2\tau_{\text{INV}} + 2\tau_{\text{INV}} = 6\tau_{\text{INV}} \quad F_{\text{PIPELINED}} = 1/6(345\text{ps}) = 0.48 \text{ GHz} \end{aligned}$$

Copyright 2001, Regents of University of California

Lecture 25: on blackboard

Limitations of Power Consumption

- The resistive load of NMOS results in D.C. current and hence static power consumption given by the product of current times voltage.
- CMOS avoids this static loss as the pull-up device shuts off the current completely.
- CMOS still suffers a.c. power consumption that is proportional to the switching frequency.
- The energy expended per cycle of in charging and discharging can never be less than CV^2

Copyright 2001, Regents of University of California