

EECS 42 Intro. electronics for CS Spring 2003 Handout on RC Circuits. A.R. Neureuther  
Version Date 02/09/03

## Charging and Discharging RC Circuits Handout for EECS 42

Developed by Professor W.G. Oldham to provide understanding of transient issues in computer logic.

Extensions by Professor A.R. Neureuther in Spring 2003 to include sequential switching of logic gates as occurs in the EECS 43 logic gate experiment.

Copyright 2001, Regents of University of California

EECS 42 Intro. electronics for CS Spring 2003 Handout on RC Circuits. A.R. Neureuther  
Version Date 02/09/03

### Charging and discharging in RC Circuits (an enlightened approach)

- Before we analyze real electronic circuits - lets study RC circuits
- Rationale: Every node in a circuit has capacitance to ground, like it or not, and it's the charging of these capacitances that limits real circuit performance (speed)

Relevance to digital circuits:  
We communicate with pulses  
We send beautiful pulses out

But we receive lousy-looking pulses and must restore them

RC charging effects are responsible .... So lets review them.

Copyright 2001, Regents of University of California

EECS 42 Intro. electronics for CS Spring 2003 Handout on RC Circuits. A.R. Neureuther  
Version Date 02/09/03

### LOGIC GATE DELAY $\tau_D$

Time delay  $\tau_D$  occurs between input and output: "computation" is not instantaneous  
Value of input at  $t = 0^+$  determines value of output at later time  $t = \tau_D$

Copyright 2001, Regents of University of California

EECS 42 Intro. electronics for CS Spring 2003 Handout on RC Circuits. A.R. Neureuther  
Version Date 02/09/03

### SIGNAL DELAY: TIMING DIAGRAMS

Show transitions of variables vs time

Note B changes one gate delay after A switches

Note that C changes two gate delays after A switches.

Note that D changes two gate delays after A switches.

Copyright 2001, Regents of University of California

EECS 42 Intro. electronics for CS Spring 2003 Handout on RC Circuits. A.R. Neureuther  
Version Date 02/09/03

### Simplification for time behavior of RC Circuits

Before any input change occurs we have a dc circuit problem (that is we can use dc circuit analysis to relate the output to the input).

Long after the input change occurs things "settle down" .... Nothing is changing .... So again we have a dc circuit problem.

We call the time period during which the output changes the *transient*

We can predict a lot about the transient behavior from the pre- and post-transient dc solutions

Copyright 2001, Regents of University of California

EECS 42 Intro. electronics for CS Spring 2003 Handout on RC Circuits. A.R. Neureuther  
Version Date 02/09/03

### What environment do pulses face?

- Every real wire in a circuit has resistance.
- Every junction (*node*) has capacitance to ground and to other nodes.
- The active circuit elements (transistors) add additional resistance in series with the wires, and additional capacitance in parallel with the node capacitance.

Thus the most basic model circuit for studying transients consists of a resistor driving a capacitor.

A pulse originating at node I will arrive delayed and distorted at node O because it takes time to charge C through R

If we focus on the circuit which distorts the pulses produced by  $V_{in}$ , its most simple form consists simply of an R and a C. ( $V_{in}$  represents the time-varying source which produces the input pulse.)

Copyright 2001, Regents of University of California

EECS 42 Intro. electronics for CS Spring 2003 Handout on RC Circuits. A.R. Neureuther  
Version Date 02/09/03

### The RC Circuit to Study

(All single-capacitor circuits reduce to this one)

Input node  $\xrightarrow{R}$  Output node  $\xrightarrow{C}$  ground

- R represents total resistance (wire plus whatever drives the input node)
- C represents the total capacitance from node to the outside world (from devices, nearby wires, ground etc)

Copyright 2001, Regents of University of California

EECS 42 Intro. electronics for CS Spring 2003 Handout on RC Circuits. A.R. Neureuther  
Version Date 02/09/03

### RC RESPONSE

**Case 1 – Rising voltage.** Capacitor uncharged: Apply + voltage step

- $V_{in}$  "jumps" at  $t=0$ , but  $V_{out}$  cannot "jump" like  $V_{in}$ . Why not?
- Because an instantaneous change in a capacitor voltage would require instantaneous increase in energy stored ( $1/2CV^2$ ), that is, infinite power. (Mathematically,  $V$  must be differentiable:  $I=CdV/dt$ )

$V$  does not "jump" at  $t=0$ , i.e.  $V(t=0^+) = V(t=0^-)$

Therefore the dc solution before the transient tells us the capacitor voltage at the beginning of the transient.

Copyright 2001, Regents of University of California

EECS 42 Intro. electronics for CS Spring 2003 Handout on RC Circuits. A.R. Neureuther  
Version Date 02/09/03

### RC RESPONSE

**Case 1 Continued – Capacitor uncharged: Apply voltage step**

- $V_{out}$  approaches its final value asymptotically (It never actually gets exactly to  $V_1$ , but it gets arbitrarily close). Why?

After the transient is over (nothing changing anymore) it means  $d(V)/dt = 0$ ; that is all currents must be zero. From Ohm's law, the voltage across R must be zero, i.e.  $V_{in} = V_{out}$ .

That is,  $V_{out} \rightarrow V_1$  as  $t \rightarrow \infty$ . (Asymptotic behavior)

Again the dc solution (after the transient) tells us (the asymptotic limit of) the capacitor voltage during the transient.

Copyright 2001, Regents of University of California

EECS 42 Intro. electronics for CS Spring 2003 Handout on RC Circuits. A.R. Neureuther  
Version Date 02/09/03

### RC RESPONSE

**Example – Capacitor uncharged: Apply voltage step of 5V**

- Clearly  $V_{out}$  starts out at 0V (at  $t = 0^+$ ) and approaches 5V.
- We know this because of the pre-transient dc solution ( $V=0$ ) and post-transient dc solution ( $V=5V$ ).

So we know a lot about  $V_{out}$  during the transient - namely its initial value, its final value, and we know the general shape.

We even know the initial slope from  $I = C(dV/dt)$  as  $(dV/dt) = (1/C)I = (1/C)(V_{in}-0)/R = (V_{in}-0)/(RC)$

Copyright 2001, Regents of University of California

EECS 42 Intro. electronics for CS Spring 2003 Handout on RC Circuits. A.R. Neureuther  
Version Date 02/09/03

### RC RESPONSE: Case 1 (cont.)

Equation for  $V_{out}$ : Do you remember general form?

$$V_{out} = V_1(1 - e^{-t/\tau})$$

Exact form of  $V_{out}$ ? Exponential!

Copyright 2001, Regents of University of California

EECS 42 Intro. electronics for CS Spring 2003 Handout on RC Circuits. A.R. Neureuther  
Version Date 02/09/03

### Review of simple exponentials.

**Rising Exponential from Zero**

$$V_{out} = V_1(1 - e^{-t/\tau})$$

at  $t = 0$ ,  $V_{out} = 0$ , and  
at  $t \rightarrow \infty$ ,  $V_{out} \rightarrow V_1$ , also  
at  $t = \tau$ ,  $V_{out} = 0.63 V_1$

**Falling Exponential to Zero**

$$V_{out} = V_1 e^{-t/\tau}$$

at  $t = 0$ ,  $V_{out} = V_1$ , and  
at  $t \rightarrow \infty$ ,  $V_{out} \rightarrow 0$ , also  
at  $t = \tau$ ,  $V_{out} = 0.37 V_1$

Copyright 2001, Regents of University of California

EECS 42 Intro. electronics for CS Spring 2003 Handout on RC Circuits. A.R. Neureuther  
Version Date 02/09/03

### Further Review of simple exponentials:

Rising Exponential from Zero  $V_{out} = V_1(1 - e^{-t/\tau})$   
 Falling Exponential to Zero  $V_{out} = V_1 e^{-t/\tau}$

We can add a constant (positive or negative)  
 $V_{out} = V_1(1 - e^{-t/\tau}) + V_2$        $V_{out} = V_1 e^{-t/\tau} + V_2$

Copyright 2001, Regents of University of California

EECS 42 Intro. electronics for CS Spring 2003 Handout on RC Circuits. A.R. Neureuther  
Version Date 02/09/03

### Further Review of simple exponentials:

Rising Exponential  $V_{out} = V_1(1 - e^{-t/\tau}) + V_2$   
 Falling Exponential  $V_{out} = V_1 e^{-t/\tau} + V_2$

Both equations can be written in one simple form:  $V_{out} = A + B e^{-t/\tau}$

Initial value (t=0):  $V_{out} = A + B$ . Final value (t >> τ):  $V_{out} = A$

Thus: if B < 0, rising exponential; if B > 0, falling exponential

Copyright 2001, Regents of University of California

EECS 42 Intro. electronics for CS Spring 2003 Handout on RC Circuits. A.R. Neureuther  
Version Date 02/09/03

### RC RESPONSE: Case 1 (Rising exponential)

$V_{out} = V_1(1 - e^{-t/\tau})$

- How is  $\tau$  related to R and C?
  - If C is bigger, it takes longer ( $\tau \uparrow$ ).
  - If R is bigger, it takes longer ( $\tau \uparrow$ ).
  - Thus,  $\tau$  is proportional to RC.**
- In fact,  $\tau = RC$ !
- Thus,  $V_{out} = V_1(1 - e^{-t/RC})$**

Copyright 2001, Regents of University of California

EECS 42 Intro. electronics for CS Spring 2003 Handout on RC Circuits. A.R. Neureuther  
Version Date 02/09/03

### RC RESPONSE: Case 1 (cont.)

Proof that  $V_{out} = V_1(1 - e^{-t/RC})$

$i_R = \frac{V_{in} - V_{out}}{R}$  (Ohm's law)  
 $i_C = C \frac{dV_{out}}{dt}$  (capacitance law)

But  $i_R = i_C$ !

Thus,  $\frac{V_{in} - V_{out}}{R} = C \frac{dV_{out}}{dt}$   
 or  $\frac{dV_{out}}{dt} = \frac{1}{RC} (V_{in} - V_{out})$

Copyright 2001, Regents of University of California

EECS 42 Intro. electronics for CS Spring 2003 Handout on RC Circuits. A.R. Neureuther  
Version Date 02/09/03

### RC RESPONSE Case 1 (cont.)

Proof that  $V_{out} = V_1(1 - e^{-t/RC})$

We have:  $\frac{dV_{out}}{dt} = \frac{1}{RC} (V_{in} - V_{out})$  Proof by substitution:

But  $V_{in} = V_1 = \text{constant}$   
 and  $V_{out} = 0$  at  $t = 0^+$

I claim that the solution to this first-order linear differential equation is:

$V_{out} = V_1(1 - e^{-t/RC})$        $\frac{dV_{out}}{dt} = \frac{1}{RC} (V_1 - V_1(1 - e^{-t/RC}))$   
 clearly

and

Copyright 2001, Regents of University of California

EECS 42 Intro. electronics for CS Spring 2003 Handout on RC Circuits. A.R. Neureuther  
Version Date 02/09/03

### RC RESPONSE (cont.)

**Generalization**

$V_{in}$  switches at  $t = 0$ ; then for any time interval  $t > 0$ , in which  $V_{in}$  is a constant,  $V_{out}$  is **always** of the form:  $V_{out} = A + B e^{-t/RC}$

We determine A and B from the initial voltage on C, and the value of  $V_{in}$ . Assume  $V_{in}$  "switches" at  $t=0$  from  $V_{co}$  to  $V_1$ :

Thus,  $V_{out}(0) = A + B e^{-0/RC} = A + B = V_{co}$

Thus,  $V_{out}(\infty) = A = V_1$

You may choose to solve RC problems using this "A and B" formulation, but in the next lecture we show you an easier way.

Copyright 2001, Regents of University of California



EECS 42 Intro. electronics for CS Spring 2003 Handout on RC Circuits. A.R. Neureuther  
Version Date 02/09/03

### Re-Cap: Charging and discharging in RC Circuits

**Last Time:**  
We learned that simple the simple RC circuit with a step input has a universal exponential solution of the form:  
 $V_{out} = A + Be^{-t/RC}$

Example 0:  $R = 1K, C = 1pF, V_{in}$  steps from zero to 10V at  $t=0$ :

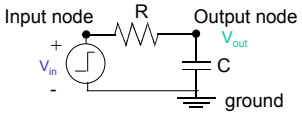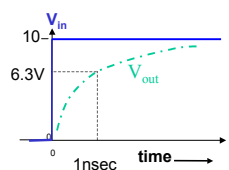- 1) Initial value of  $V_{out}$  is 0
- 2) Final value of  $V_{out}$  is 10V
- 3) Time constant is  $RC = 10^{-9}$  sec
- 4)  $V_{out}$  reaches  $0.63 \times 10$  in  $10^{-9}$  sec





Copyright 2001, Regents of University of California

EECS 42 Intro. electronics for CS Spring 2003 Handout on RC Circuits. A.R. Neureuther  
Date 02/09/03
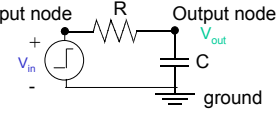
### Charging and discharging in RC Circuits - Example 1 (rising exponential) continued -

For this example:  $R = 1K, C = 1pF, V_{in}$  steps from zero to 10V at  $t=0$ :



$V_{out}$  starts at 0, ends at 10 and has time constant of 1nsec  
 $V_{out} = 10 - 10e^{-t/1nsec}$

Note that we found this graph without even using the equation  $V_{out} = A + Be^{-t/RC}$  (That is we did not try to evaluate A and B). We simply used the dc solution for  $t < 0$  and the dc solution for  $t > 0$  to get the limits and we used the time constant to get the horizontal scale. We only need the equation to remind us the solution is an exponential. So this will be the basis of our **easy method**.


Copyright 2001, Regents of University of California

EECS 42 Intro. electronics for CS Spring 2003 Handout on RC Circuits. A.R. Neureuther  
03

### Charging and discharging in RC Circuits (The official EE42 Easy Method)

**Method of solving for any node voltage in a single capacitor circuit.**

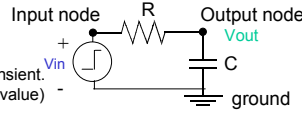- 1) Simplify the circuit so it looks like one resistor, a source, and a capacitor (it will take another two weeks to learn all the tricks to do this.) But then the circuit looks like this:
- 2) The time constant of the transient is  $\tau = RC$ .
- 3) Solve the dc problem for the capacitor voltage before the transient. This is the starting value (initial value) for the transient voltage.
- 4) Solve the dc problem for the capacitor voltage after the transient is over. This is the asymptotic value.
- 5) Sketch the Transient. It is 63% complete after one time constant.
- 6) Write the equation by inspection.





Copyright 2001, Regents of University of California

EECS 42 Intro. electronics for CS Spring 2003 Handout on RC Circuits. A.R. Neureuther  
03

### Charging and discharging in RC Circuits (Example 1 of the EE42 Easy Method)

Find  $V_c(t)$  for the following circuit: (input switches from 2V to -1V at  $t = 0$ )

- 1) Simplify the circuit:

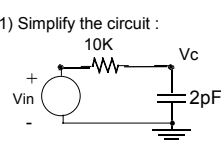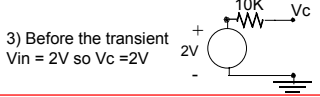- 2) The time constant of the transient is  $\tau = RC = 20nsec$
- 3) Before the transient  $V_{in} = 2V$  so  $V_c = 2V$
- 4) After the transient is over  $V_{in} = -1V$  so  $V_c = -1V$ . This is the asymptotic value.

Copyright 2001, Regents of University of California


EECS 42 Intro. electronics for CS Spring 2003 Handout on RC Circuits. A.R. Neureuther  
03

### Charging and discharging in RC Circuits (Example 1 of the EE42 Easy Method)

Find  $V_c(t)$  for the following circuit: (input switches from 2V to -1V at  $t = 0$ )

We have: Initial value of  $V_c$  is 2V, final value is -1V and  $\tau = 20nsec$

5) Sketch  $V_c(t)$ :

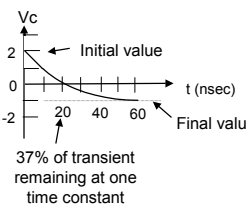

37% of transient remaining at one time constant

What is the equation for an exponential beginning at 2V, decaying to -1V, with  $\tau = 20nsec$ ?





$$V_c(t) = -1 + 3e^{-t/20nsec}$$

Copyright 2001, Regents of University of California

EECS 42 Intro. electronics for CS Spring 2003 Handout on RC Circuits. A.R. Neureuther  
Version Date 02/09/03

### 2 MORE EXAMPLES ---OUR METHOD AVOIDS ALL MATH!

- 1) Sketch waveform (starts at  $V_{co}$ , ends asymptotically at  $V_1$ , initial slope intersects at  $t = RC$  or transient is 63% complete at  $t=RC$ )
- 2) Write equation:
  - 2a. constant term A = limit of V as  $t \rightarrow \infty$
  - 2b. pre-exponent B = initial value - constant term

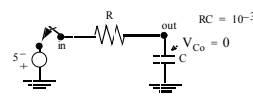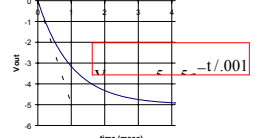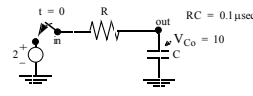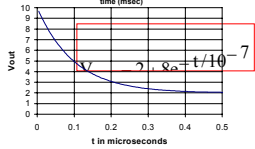Copyright 2001, Regents of University of California

EECS 42 Intro. electronics for CS Spring 2003 Handout on RC Circuits. A.R. Neureuther  
Version Date 02/09/03

### 4 Examples

$V_{out} = A + Be^{-t/RC}$

$t = 0$

$R$   $C$   $RC = 0.01 \text{ sec}$

$V_{C0} = 0$

$V_{C0} = 5 \text{ V}$

$V_1 = 10$

$V_1 = 0$

Copyright 2001, Regents of University of California

EECS 42 Intro. electronics for CS Spring 2003 Handout on RC Circuits. A.R. Neureuther  
Version Date 02/09/03

### COMPLICATION: Event Happens at $t \neq 0$

(Solution: Shift reference time to time of event)

Example: switch closes at  $1 \mu\text{sec}$

$t = 1 \mu\text{sec}$

$R$   $C$   $RC = 2 \mu\text{sec}$   $V_{C0} = 5 \text{ V}$

We shift the time axis here by one microsecond, i.e. imagine a new time coordinate  $t^* = t - 1 \mu\text{sec}$  so that in the new time domain, the event happens at  $t^* = 0$  and our standard solution applies. Of course we replace  $t^*$  by  $t - 1 \mu\text{sec}$  in the equations and plots. Thus instead of  $t^* = 0$  we have  $t = 1 \mu\text{sec}$ , etc.

Copyright 2001, Regents of University of California

EECS 42 Intro. electronics for CS Spring 2003 Handout on RC Circuits. A.R. Neureuther  
Version Date 02/09/03

### EXAMPLE of CHARGING to 95%

Your photo flash charges a  $1000 \mu\text{F}$  capacitor from a  $50 \text{ V}$  source through a  $2 \text{ K}$  resistor. If the capacitor is initially uncharged, how long must you wait for it to reach 95% charged ( $47.5 \text{ V}$ )?

**Solution:**  $RC = 2 \text{ K} \times 10^{-3} = 2 \text{ sec}$

$50 \text{ V}$   $2 \text{ K}$   $10^{-3} \text{ F}$   $V_{out}$   $V_{C0} = 0 \text{ V}$

By inspection:  $V_o = 50 - 50e^{-t/2}$ , so

$47.5 = 50(1 - e^{-t/2}) \Rightarrow e^{-t/2} = (1 - \frac{47.5}{50}) \Rightarrow t = 6 \text{ sec}$

Copyright 2001, Regents of University of California

EECS 42 Intro. electronics for CS Spring 2003 Handout on RC Circuits. A.R. Neureuther  
Version Date 02/09/03

### EXAMPLE of a SWITCHING LOGIC GATE

$R_u = 20 \text{ k}\Omega$   $t = 2 \text{ ns}$   $V_{out} = 5 \text{ V}$   $0.1 \text{ pF}$   $R_p = 10 \text{ k}\Omega$   $t = 4 \text{ ns}$   $V_{out}$   $(3.16 \text{ V}, 4 \text{ ns})$   $(1.16 \text{ V at } 5 \text{ ns})$   $(0.43 \text{ V at } 6 \text{ ns})$

Prior to  $t = 2 \text{ ns}$  Switch has been down a long time.  $V_{out} = 0$

At  $2 \text{ ns}$  Switch goes up: heads for  $5 \text{ V}$  with  $RC = 20 \text{ k}\Omega \cdot 0.1 \text{ pF} = 2 \text{ ns}$

$V_{out} = 5 - 5e^{-(t-2 \text{ ns})/2 \text{ ns}}$

At  $4 \text{ ns}$  Switch goes down: starts from present value of  $3.16 \text{ V}$  and heads down to zero.  $V_{out} = 3.16e^{-(t-4 \text{ ns})/1 \text{ ns}}$

Copyright 2001, Regents of University of California