


Department of EECS
University of California, Berkeley

Logic gates – Lab Report


Bart Muthuswamy and W. G. Oldham

September 1st 2001

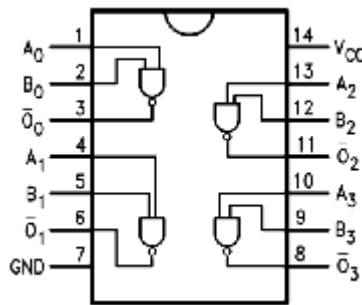1. Construct your LED logic probe. What color LED do you have (red is best)? Describe how is the LED a simple visual indicator of a NOT gate?
2. What R do you use in your LED logic probe and how much current is flowing through the LED? What is its brightness at 2V and 5V? WARNING: THE INPUT LOGIC VOLTAGE CANNOT EXCEED V_{CC} !!!
3. Draw the circuit schematic of how you construct a NOT gate using the MM74HC00 chip. What is the high-to-low and low-to-high delay for $V_{CC} = 5V$ and $V_{CC} = 2V$?



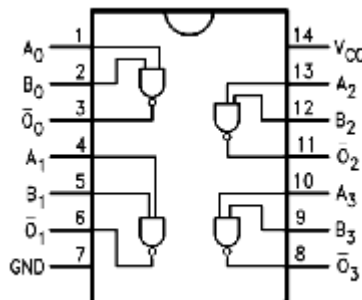4. Draw the circuit schematic of how you construct a chain of 4 inverters using the MM74HC00 chip. What is the high-to-low and low-to-high delay for each inverter?



Vcc = 5V	1 gate	2 gates	3 gates	4 gates
High-to-low				
Low-to-high				
Avg gate delay				

5. Now using the digital probes, what is the high-to-low and low-to-high delay for each inverter for Vcc = 5V and Vcc = 2V?

Vcc = 5V	1 gate	2 gates	3 gates	4 gates
High-to-low				
Low-to-high				
Avg gate delay				

Vcc = 2V	1 gate	2 gates	3 gates	4 gates
High-to-low				
Low-to-high				
Avg gate delay				

6. Based on the gate delay difference between 1 and 3 gates (two gate delays) what is the average gate delay at each of the supply voltages. (Note: we do not want to use the difference between 2 and 4 delays because the last gate is not loaded by the input to any other logic circuit).
Average Gate Delay = _____ at 5V; Average Gate Delay = _____ at 2V.