

EECS151/251A - Homework 3 Solutions

Problem 1

(1.1)

$$\begin{aligned} Out = & \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}C\bar{D} + \bar{A}\bar{B}CD + \bar{A}B\bar{C}\bar{D} + \bar{A}B\bar{C}D \\ & + \bar{A}BC\bar{D} + \bar{A}BCD \\ & + A\bar{B}\bar{C}\bar{D} + A\bar{B}\bar{C}D + A\bar{B}C\bar{D} + A\bar{B}CD \end{aligned}$$

(1.2)

		CD			
		00	01	11	10
AB	00	1	1	0	1
	01	1	1	1	1
	11	0	0	0	1
	10	1	1	0	1

$$Q = \bar{A}B + \bar{B}\bar{C} + C\bar{D}$$

(1.3)

 


Figure 1: *Direct implementation of the simplified SOP representation.*

 


Figure 2: *NAND-only implementation of the simplified SOP representation.*

Problem 2

(2.1)

		<i>EF</i>				<i>EF</i>			
		00	01	11	10	00	01	11	10
<i>CD</i>	00	0	0	0	0	0	0	0	1
	01	1	1	1	1	1	x	0	1
	11	0	0	0	0	1	1	0	0
	10	0	0	0	x	x	x	0	0
		<i>AB= 00</i>				<i>AB= 01</i>			

		<i>AB= 10</i>				<i>AB= 11</i>			
<i>CD</i>	00	1	1	x	1	1	1	0	1
	01	1	1	1	1	1	1	0	1
	11	0	0	0	0	1	1	0	0
	10	1	1	0	0	x	1	0	0

$$Q = \overline{B}\overline{C}D + A\overline{B}\overline{C} + A\overline{D}\overline{E} + B\overline{D}\overline{E} + B\overline{C}E\overline{F}$$

(2.2)

		<i>EF</i>			
		00	01	11	10
<i>CD</i>	00	0	0	0	0
	01	1	1	1	1
	11	0	0	0	0
	10	0	0	0	x

AB = 00

		<i>EF</i>			
		00	01	11	10
<i>CD</i>	00	0	0	0	1
	01	1	x	0	1
	11	1	1	0	0
	10	x	x	0	0

AB = 01

		<i>EF</i>			
		00	01	11	10
<i>CD</i>	00	1	1	x	1
	01	1	1	1	1
	11	0	0	0	0
	10	1	1	0	0

AB = 10

		<i>EF</i>			
		00	01	11	10
<i>CD</i>	00	1	1	0	1
	01	1	1	0	1
	11	1	1	0	0
	10	x	1	0	0

AB = 11


$$Q = \overline{(CE + \overline{A}\overline{B}\overline{D} + \overline{A}\overline{D}\overline{E} + \overline{B}CD + BEF)}$$
$$Q = (\overline{C} + \overline{E})(A + B + D)(A + D + E)(B + \overline{C} + \overline{D})(\overline{B} + \overline{E} + \overline{F})$$

(2.3)

For this choice of x values, the functions are identical - they have the same truth table if evaluated. However, there can be configurations such that the same x is utilized differently for SOP and POS representations, resulting in different functions representing the same specification truth table.

Problem 3

(3.1)

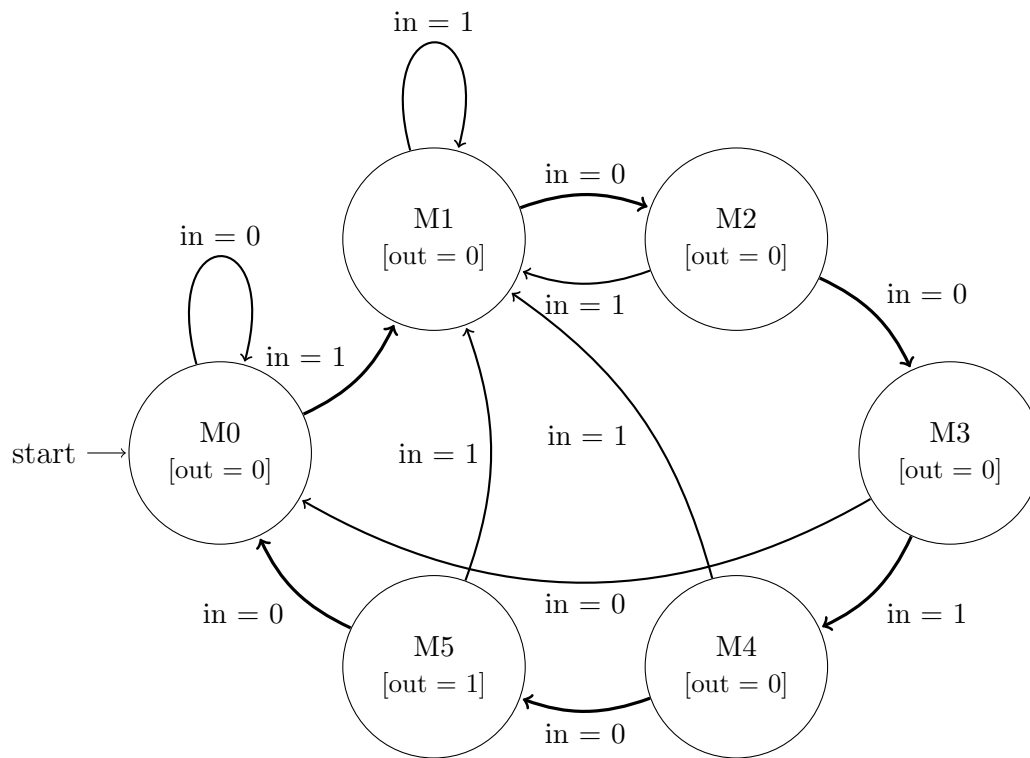

(3.2)


```
1 module pattern_detector (  
2   input wire in,  
3   input wire clk,  
4   output wire out);  
5  
6   reg [2:0] state = 0;  
7   localparam M0 = 0;  
8   localparam M1 = 1;  
9   localparam M2 = 2;  
10  localparam M3 = 3;  
11  localparam M4 = 4;  
12  localparam M5 = 5;  
13
```

```

14  assign out = (state == M5) ? 1'b1 : 1'b0;
15
16  always @ (posedge clk)
17  begin
18
19  case(state)
20  M0:
21  begin
22      if(in == 1) state <= M1;
23      else if(in == 0) state <= M0;
24  end
25
26  M1:
27  begin
28      if(in == 1) state <= M1;
29      else if(in == 0) state <= M2;
30  end
31
32  M2:
33  begin
34      if(in == 1) state <= M1;
35      else if(in == 0) state <= M3;
36  end
37
38  M3:
39  begin
40      if(in == 1) state <= M4;
41      else if(in == 0) state <= M0;
42  end
43
44  M4:
45  begin
46      if(in == 1) state <= M1;
47      else if(in == 0) state <= M5;
48  end
49
50  M5:
51  begin
52      if(in == 1) state <= M1;
53      else if(in == 0) state <= M0;
54  end
55  endcase
56  end
57  endmodule

```

(3.3)

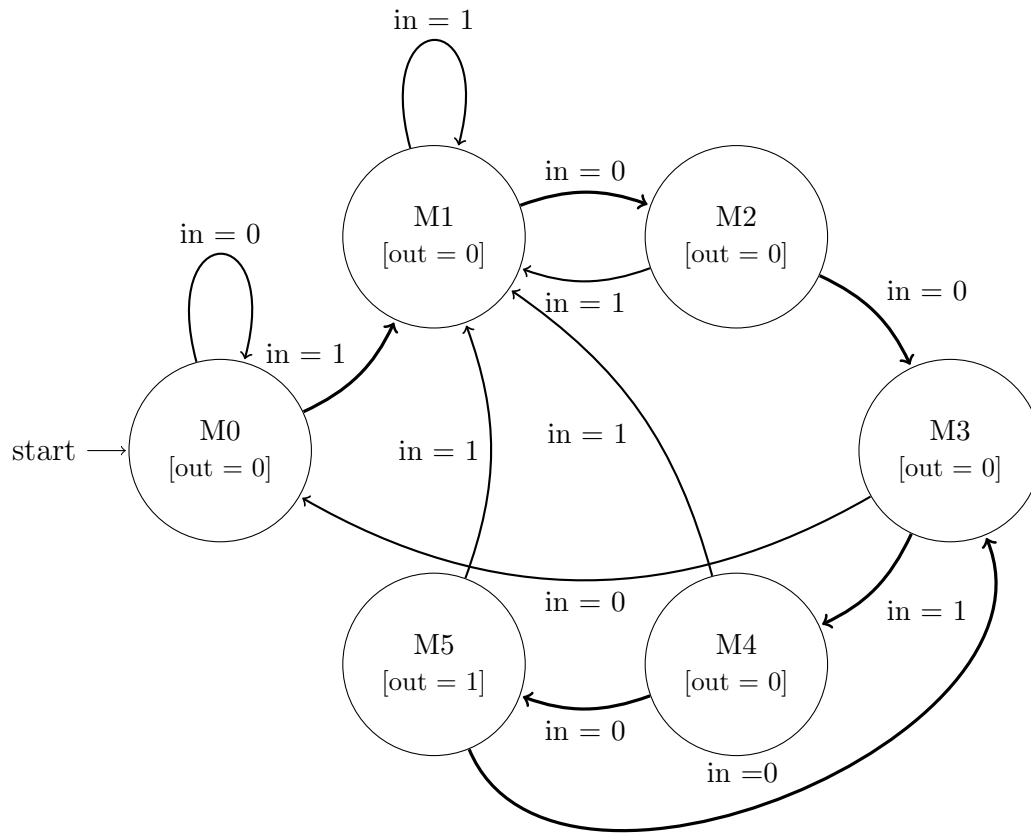

```
1 module pattern_detector (  
2   input wire in,  
3   input wire clk,  
4   output wire out);  
5  
6   reg [2:0] state = 0;  
7   localparam M0 = 0;  
8   localparam M1 = 1;  
9   localparam M2 = 2;  
10  localparam M3 = 3;  
11  localparam M4 = 4;  
12  localparam M5 = 5;  
13
```




```

14  assign out = (state == M5) ? 1'b1 : 1'b0;
15
16  always @ (posedge clk)
17  begin
18
19  case(state)
20  M0:
21  begin
22      if(in == 1) state <= M1;
23      else if(in == 0) state <= M0;
24  end
25
26  M1:
27  begin
28      if(in == 1) state <= M1;
29      else if(in == 0) state <= M2;
30  end
31
32  M2:
33  begin
34      if(in == 1) state <= M1;
35      else if(in == 0) state <= M3;
36  end
37
38  M3:
39  begin
40      if(in == 1) state <= M4;
41      else if(in == 0) state <= M0;
42  end
43
44  M4:
45  begin
46      if(in == 1) state <= M1;
47      else if(in == 0) state <= M5;
48  end
49
50  M5:
51  begin
52      if(in == 1) state <= M1;
53      else if(in == 0) state <= M3;
54  end
55  endcase
56  end
57  endmodule

```

(3.4)

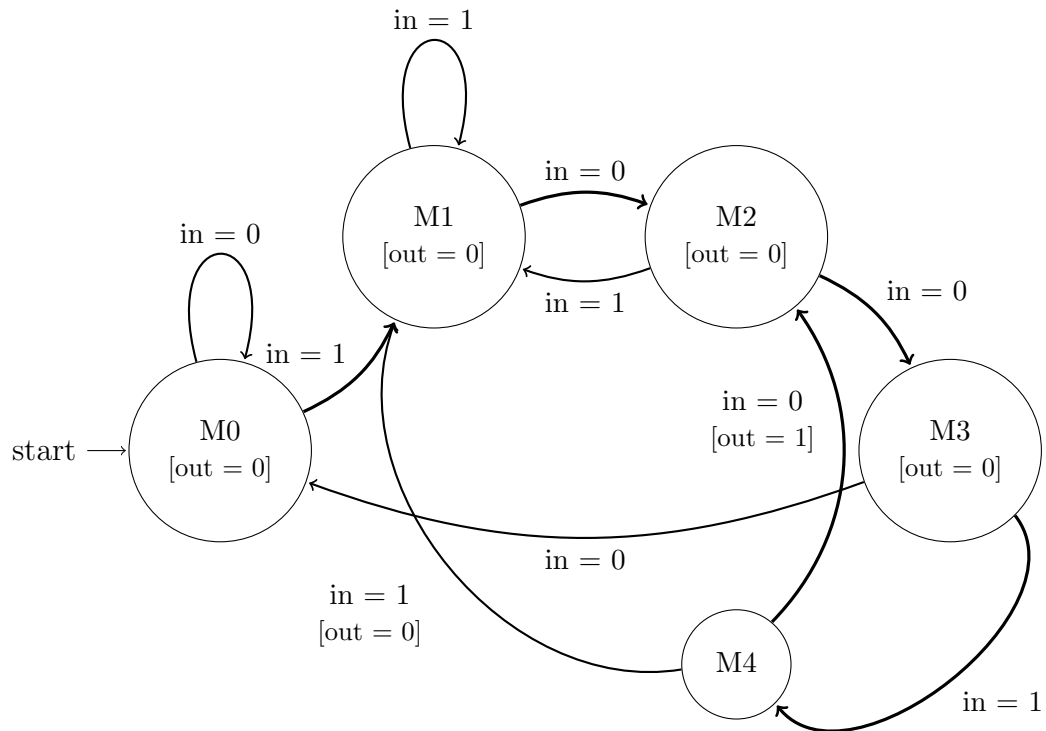

(3.5)

```
1 module pattern_detector (
2   input wire in,
3   input wire clk,
4   output reg out);
5
6   reg [2:0] state = 0;
7   localparam M0 = 0;
8   localparam M1 = 1;
9   localparam M2 = 2;
10  localparam M3 = 3;
11  localparam M4 = 4;
12
13
14  always @ (posedge clk)
```

```

15  begin
16
17  case(state)
18  M0:
19  begin
20      out <= 1'b0;
21      if(in == 1) state <= M1;
22      else if(in == 0) state <= M0;
23  end
24
25  M1:
26  begin
27      out <= 1'b0;
28      if(in == 1) state <= M1;
29      else if(in == 0) state <= M2;
30  end
31
32  M2:
33  begin
34      out <= 1'b0;
35      if(in == 1) state <= M1;
36      else if(in == 0) state <= M3;
37  end
38
39  M3:
40  begin
41      out <= 1'b0;
42      if(in == 1) state <= M4;
43      else if(in == 0) state <= M0;
44  end
45
46  M4:
47  begin
48      if(in == 1) state <= M1;
49      else if(in == 0)
50      begin
51          state <= M2;
52          out <= 1'b1;
53      end
54  end
55  endcase
56  end
57  endmodule

```
