

## EECS 151/251A Homework 3

Due Friday, Sept 25<sup>th</sup>, 2020

2020-10-03

### For this HW Assignment

You will be asked to write several Verilog modules as part of this HW assignment. You will need to test your modules by running them through a simulator. A useful tool is <https://www.edaplayground.com>, a free, online Verilog simulator.

For all problems, include your Verilog code, test bench, and test results (including the simulation output and a waveform). Also explain what aspects of your design are being verified by your testbench.

**Problem 1: Logic Simplification [5 pts]**

Take this truth table consisting of 4 input variables(A, B, C, D) and 1 output(Out):

A	B	C	D	Out
0	0	0	0	0
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

1. Write a sum-of-products directly from the truth table. [1 pt]
2. Use a Karnaugh Map to simplify the logic and write the simplified sum-of-products and product-of-sums representations. [2 pts]
3. Using the simplified sum-of-products representation, draw the circuit that implements this function. Transform this circuit such that it is made up only of inverters and NAND gates. All gates should have 2 inputs and 1 output. [2 pts]

**Solution:**

$$1. \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}C\bar{D} + \bar{A}B\bar{C}\bar{D} + \bar{A}B\bar{C}D + \bar{A}BC\bar{D} + \bar{A}BCD + A\bar{B}\bar{C}\bar{D} + A\bar{B}C\bar{D}$$

2.

		CD			
		00	01	11	10
AB	00	0	0	1	1
	01	1	1	1	1
	11	0	0	0	0
	10	1	0	0	1

SoP:  $\bar{A}B + A\bar{B}\bar{D} + \bar{A}C$

PoS:  $(\bar{A} + \bar{B})(\bar{A} + \bar{D})(A + B + C)$

3.

 


Figure 1: Direct implementation of the simplified SoP representation

 


Figure 2: NAND-only implementation of the simplified SoP representation

## Problem 2: Combinational Logic [4 pts]

Consider the following Boolean function:

$$\bar{a}\bar{b}\bar{c}\bar{d} + \bar{a}\bar{b}c\bar{d} + \bar{a}b\bar{c}d + \bar{a}bd + \overline{(\bar{a} + \bar{b} + c)} + \overline{(\bar{a} + \bar{b} + \bar{c})}$$

1. Use a K-map to simplify. Show your work. [1 pts]
2. Use a Boolean algebra to simplify. Show your work. [1 pts]
3. Using the simplified sum-of-products representation, draw the circuit that implements this function. Then bubble push to transform the circuit into products-of-sum form. All gates should have 2 inputs and 1 output. [2 pts]

Solution:

1.

		cd			
		00	01	11	10
ab	00	1	1	1	0
	01	0	0	0	0
	11	1	1	1	1
	10	0	1	1	0

$$ab + \bar{a}\bar{b}\bar{c} + \bar{b}d$$

$$\begin{aligned}
 2. \quad & \bar{a}\bar{b}\bar{c}\bar{d} + \bar{a}\bar{b}c\bar{d} + \bar{a}b\bar{c}d + \bar{a}bd + \overline{(\bar{a} + \bar{b} + c)} + \overline{(\bar{a} + \bar{b} + \bar{c})} \\
 &= \bar{a}\bar{b}\bar{c}\bar{d} + \bar{a}\bar{b}c\bar{d} + \bar{a}b\bar{c}d + \bar{a}bcd + \bar{a}bd + \overline{(\bar{a} + \bar{b} + c)} + \overline{(\bar{a} + \bar{b} + \bar{c})} \\
 &= \bar{a}\bar{b}\bar{c}(\bar{d} + d) + \bar{a}\bar{b}(\bar{c} + c)d + \bar{a}bd + ab\bar{c} + abc \\
 &= \bar{a}\bar{b}\bar{c} + \bar{a}\bar{b}d + \bar{a}bd + ab(\bar{c} + c) \\
 &= \bar{a}\bar{b}\bar{c} + (\bar{a} + a)\bar{b}d + ab \\
 &= \bar{a}\bar{b}\bar{c} + \bar{b}d + ab
 \end{aligned}$$

3.

 


Figure 3: Direct implementation of the simplified SoP representation

 


Figure 4: PoS representation after bubble pushing

### Problem 3: FSM DNA sequencing[ 6 pts]

Help your TAs design a DNA sequencing machine! We want the machine to be able to detect some DNA sequences of bases(A, C, G, T) that we are interested in. The machine receives a one-hot encoded ACGT input every clock cycle, and outputs whether the sequence has been detected. **OUT** is pulled high for 1 clock cycle to indicate a pattern is detected, and then pulled low to prepare for the next match. The machine also has a **RESET** button that lets the user interrupt and start over at any time.

sequence to detect: **ACCTG**

inputs: **ACGT(4 bits)**, **RESET(1 bit)**

output: **OUT**

1. Draw the state diagram of this circuit, marking the transition conditions and output values. Your implementation should be in the style of a Moore machine. [1 pts]
2. Write the Verilog that corresponds to your circuit in part a). Simulate your circuit using both the given and other sequences. Show the waveform. [2 pts]
3. Draw the state diagram of this circuit as a Mealy state machine. [1 pts]
4. Write the Verilog that corresponds to your circuit in part (c). Simulate your circuit using both the given and other sequences. Show the waveform. [2 pts]

Solution:

1.

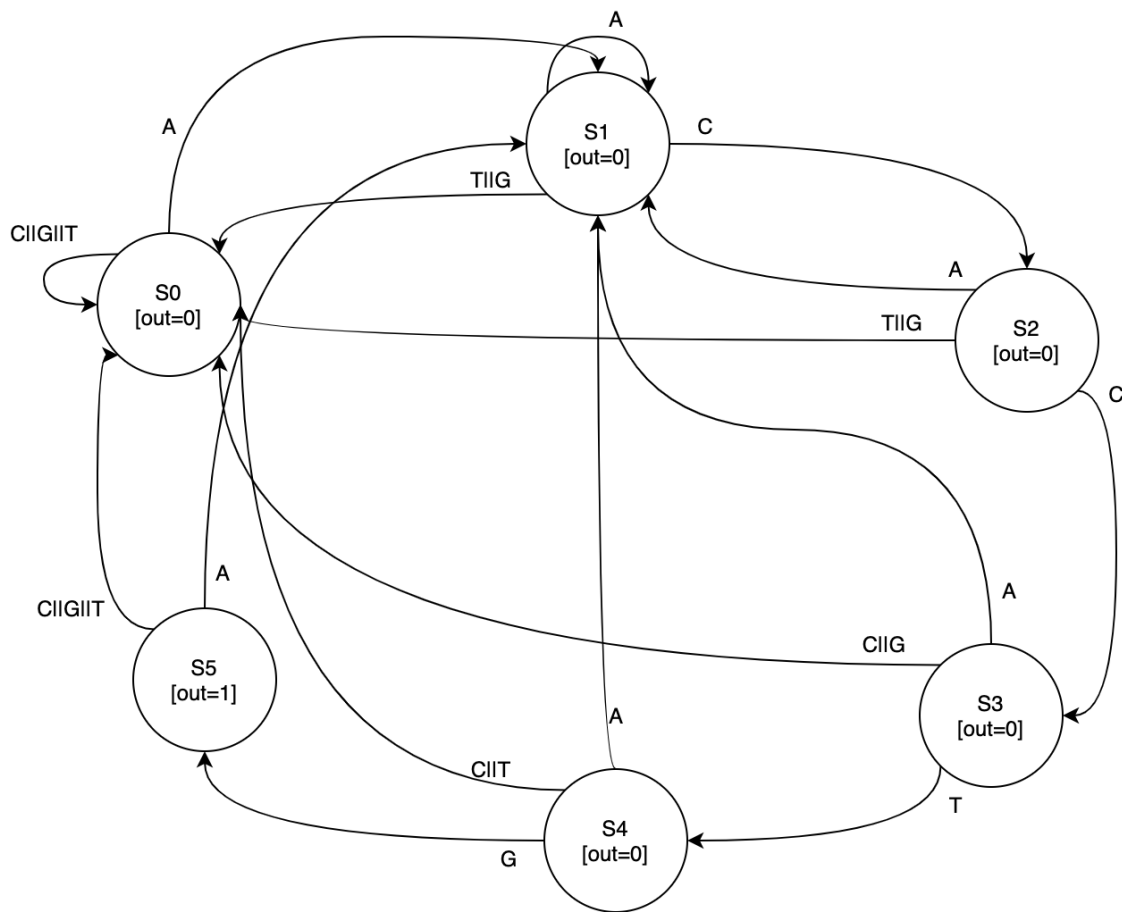


Figure 5: Moore FSM

2. Design:

```

module moore (input clk,
              input rst,
              input [3:0] acgt,
              output out
              );

  localparam S0 = 0;
  localparam S1 = 1;
  localparam S2 = 2;
  localparam S3 = 3;

```



```
localparam S4 = 4;
localparam S5 = 5;

reg [2:0] current_state, next_state;

assign out = (current_state == S5) ? 1'b1 : 1'b0;

always @(posedge clk) begin
    if (rst) current_state <= S0;
    else current_state <= next_state;
end

always @(*) begin
    case (current_state)

        S0:
            begin
                if (acgt == 4'b1000) next_state = S1;
                else next_state = S0;
            end

        S1:
            begin
                if (acgt == 4'b0100) next_state = S2;
                else if (acgt == 4'b1000) next_state = S1;
                else next_state = S0;
            end

        S2:
            begin
                if (acgt == 4'b0100) next_state = S3;
                else if (acgt == 4'b1000) next_state = S1;
                else next_state = S0;
            end

        S3:
            begin
                if (acgt == 4'b0001) next_state = S4;
                else if (acgt == 4'b1000) next_state = S1;
                else next_state = S0;
            end

        S4:
            begin
                if (acgt == 4'b0010) next_state = S5;
                else if (acgt == 4'b1000) next_state = S1;
                else next_state = S0;
            end
    endcase
end
```

```
        end

    S5:
    begin
        if (acgt == 4'b1000) next_state = S1;
            else next_state = S0;
        end

        default:
        begin
            next_state = S0;
        end
    endcase
end
endmodule
```

**Testbench:**

```
`timescale 1ns/1ns

module moore_test;
    reg clk, rst;
    reg [3:0] acgt;
    wire out;

    initial clk = 0;

    moore dut(.clk(clk), .rst(rst), .acgt(acgt), .out(out));

    always #(2) clk <= ~clk;
    initial begin
        $dumpfile("dump.vcd");
        $dumpvars(1, moore_test);

        clk = 0;

        rst = 1;
        #4;
        rst = 0;

        // sequence acgtg
        acgt = 4'b1000;
        #4;
        acgt = 4'b0100;
        #4;
        acgt = 4'b0100;
```

```
#4;
acgt = 4'b0001;
#4;
acgt = 4'b0010;
#4;

// sequence cccat
acgt = 4'b0100;
#4;
acgt = 4'b0100;
#4;
acgt = 4'b0100;
#4;
acgt = 4'b1000;
#4;
acgt = 4'b0001;
#4;
$finish();

end
endmodule
```

Waveform:



Figure 6: Moore FSM testbench waveform

3.

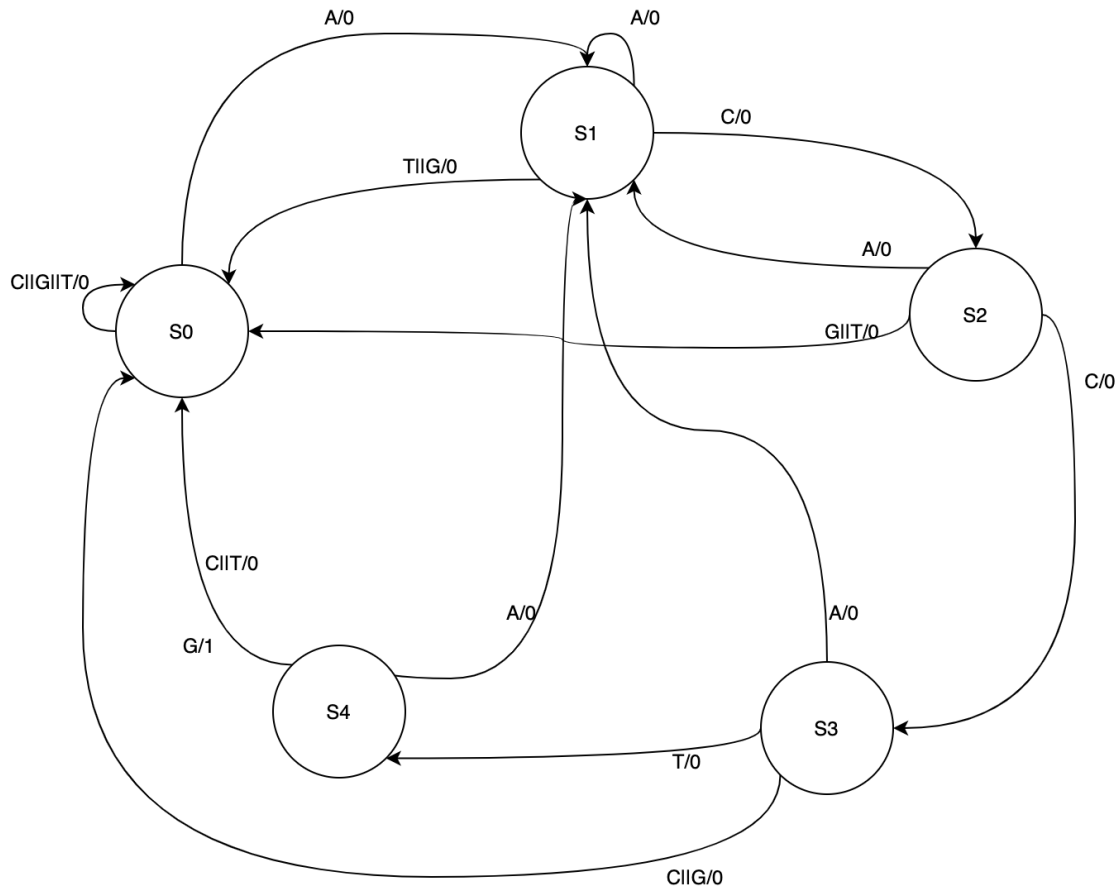


Figure 7: Mealy FSM

## 4. Design:

```

module mealy (input clk,
              input rst,
              input [3:0] acgt,
              output reg out
              );

  localparam S0 = 0;
  localparam S1 = 1;
  localparam S2 = 2;
  localparam S3 = 3;
  localparam S4 = 4;

  reg [2:0] current_state, next_state;
  reg out_sig;

```

```
always @(posedge clk) begin
    if (rst) current_state <= S0;
    else current_state <= next_state;
    out <= out_sig;
end

always @(*) begin
    case (current_state)

        S0:
            begin
                out_sig = 1'b0;
                if (acgt == 4'b1000) next_state = S1;
                else next_state = S0;
            end

        S1:
            begin
                out_sig = 1'b0;
                if (acgt == 4'b0100) next_state = S2;
                else if (acgt == 4'b1000) next_state = S1;
                else next_state = S0;
            end

        S2:
            begin
                out_sig = 1'b0;
                if (acgt == 4'b0100) next_state = S3;
                else if (acgt == 4'b1000) next_state = S1;
                else next_state = S0;
            end

        S3:
            begin
                out_sig = 1'b0;
                if (acgt == 4'b0001) next_state = S4;
                else if (acgt == 4'b1000) next_state = S1;
                else next_state = S0;
            end

        S4:
            begin
                if (acgt == 4'b0010) begin
                    out_sig = 1'b1;
                    next_state = S0;
                end
            end
    endcase
end
```

```
        else if (acgt == 4'b1000) begin
            out_sig = 1'b0;
            next_state = S1;
        end
        else begin
            out_sig = 1'b0;
            next_state = S0;
        end
    end
end

    default:
begin
        next_state = S0;
        out_sig = 1'b0;
    end
endcase
end
endmodule
```

**Testbench:**

```
`timescale 1ns/1ns

module mealy_test;
    reg clk, rst;
    reg [3:0] acgt;
    wire out;

    initial clk = 0;

    mealy dut(.clk(clk), .rst(rst), .acgt(acgt), .out(out));

    always #(2) clk <= ~clk;
    initial begin
        $dumpfile("dump.vcd");
        $dumpvars(1, mealy_test);

        clk = 0;

        rst = 1;
        #4;
        rst = 0;

        // sequence acctg
        acgt = 4'b1000;
        #4;
```

```
acgt = 4'b0100;
#4;
acgt = 4'b0100;
#4;
acgt = 4'b0001;
#4;
acgt = 4'b0010;
#4;

// sequence cccat
acgt = 4'b0100;
#4;
acgt = 4'b0100;
#4;
acgt = 4'b0100;
#4;
acgt = 4'b1000;
#4;
acgt = 4'b0001;
#4;
$finish();

end
endmodule
```

Waveform:

 


Figure 8: Mealy FSM testbench waveform