

EECS 151/251A Homework 7

Due Friday, Oct 30th, 2020

Problem 1: RC Delay and Logical Effort Basics

Take a CMOS inverter in a process where $\gamma = \frac{C_d}{C_g}$ ($\gamma = 1$ in lecture), and the PMOS effective on-resistance is equal to K times that of the NMOS (i.e. $R_p = K \cdot R_n$, $K = 1$ in lecture) for minimally sized transistors.


- (a) Draw the inverter at the transistor-level and size each FET for equal pull-up and pull-down strength. Assume the NMOS is of size '1', normalized to the minimum width of the process.
- (b) Write down the delay of this unloaded inverter using RC time constants in terms of γ , R_n , and C_g . Call this delay $t_{parasitic}$. Assume input step transitions.
- (c) Now let the inverter have a load of C_L attached to its output. Call the quantity $f = C_L/C_{in}$. Write the delay of the inverter in terms of γ , $t_{parasitic}$, and f .
- (d) Recall that the gate delay for any CMOS gate can be expressed as:

$$t_{p,gate} = \tau_{inv}(p + f \cdot LE)$$

where τ_{inv} is a process constant, p is the intrinsic delay of the gate, and LE is the logical effort of the gate.

What are these values for an inverter?

 - (e) Take the following sizing of a NAND2 gate. What is W_p for inverter equivalent delay? Prove that $W_{n,a} = W_{n,b} = 2$ so the gate has equivalent self-loaded delay to an inverter and consumes minimal area.



-
- (f) Find the logical effort of this NAND2 gate for both inputs. What happens to the LE as K increases, and why does it make intuitive sense?
- (g) What is the intrinsic delay of a NAND2 gate (i.e. find p_{NAND2})? Make the assumption that $K = 2$.

Problem 2: Complementary CMOS


- (a) Design a complex CMOS logic gate that implements the function below:

$$Y = \overline{(A + B)} \cdot \overline{CD} \quad (1)$$

- (b) You are using a modern technology in which a minimum sized inverter has PMOS with width 1 and NMOS with width 1 ($R_{ON,PMOS} = R_{ON,NMOS}$). Size your design in (a) and try to minimize the overall area. Assume the total area is proportional to the sum of transistors' width.
- (c) Calculate the logic effort for input A and C with the assumptions in (b).

 Problem 3: Path delay with logical effort

For this problem, assume you have a reference inverter with $W_P = W_N = 1$. This technology has $\gamma = 1.2$



- Determine the path effort from input to output, and optimal stage effort for the circuit shown above. Note that a and b are the input capacitance of each input.
- Find the optimum a and b in terms of C_{in} for minimum delay in the critical path (input to output).