

# EECS 151/251A Homework 9

Due Friday, Nov 20<sup>th</sup>, 2020

## Problem 1: Adders

a) Draw the block diagram of an 8-bit ripple carry adder and an 8-bit carry-lookahead adder. For each, derive the critical path in terms of the following constants. Use only 2-input gates. Include the final carry-out bit.

$$t_{MUX} = 6ps$$

$$t_{OR} = 5ps$$

$$t_{AND} = 4ps$$

$$t_{XOR} = 6ps$$

b) Now derive, generally, the critical path and area for an N-bit ripple-carry adder and an N-bit carry-lookahead adder. It is okay to make approximations for cases where  $\sqrt{N}$  or  $\log_2(N)$  are not integers. Use only 2-input gates and include the final carry-out bit.

## Problem 2: Tree Adders

The goal of this problem is to design a 10-bit Kogge-Stone adder optimized for delay:

a) Design the following logic blocks at a gate level. You may draw the gates or write the Boolean functions. Use the given inputs and outputs as hints.

 


Figure 1: Building Blocks for Kogge-Stone Adder

b) Using the logic blocks you designed in part (a), design a 10-bit logarithmic adder with a carry

input and a carry output. Use a radix-2 Kogge-Stone implementation. Highlight the critical path of your design? Give a block-level estimate, assuming that more complex blocks have more delay.

### Problem 3: Multipliers

- Draw a 5 x 5 Carry-Save multiplier and compute the critical path using  $t_{carry}$ ,  $t_{sum}$  and  $t_{and}$ .
- Draw a wallace tree for a 5 x 5 multiplier using Full Adder and Half Adder cells. What is the critical path?

### Problem 4: Latches & Flip-flops

Consider the latch design shown below. You may assume that the inverters are symmetrical with input capacitance  $C$ , self-loading capacitance also  $C$  and equivalent driving resistance  $R$ . The transmission gate is sized to have an equivalent resistance  $R$  and parasitic capacitance  $C$  on each side.

 


Figure 2: Dynamic Latch

- Calculate the Clk-Q and D-Q delays as a function of  $R$  and  $C$  of this latch. In each case, show the equivalent RC circuit and explain.
- What is the approximate setup time for this latch? Explain your answer.

 


Figure 3: flip-flop

c) We build a flip-flop (figure 3) with two dynamic latches. Is the flip-flop positive-edge triggered or negative-edge triggered?