

**EECS 151/251A**

**Fall 2018**

**Digital Design and Integrated Circuits**

Instructor:

John Wawrzynek & Nicholas Weaver

**Lecture 7**

# *Announcements...*

- Midterm, in the class slot, February 15th... ;(

# *Procedural Assignments*

The sequential semantics of the blocking assignment allows variables to be multiply assigned within a single always block. Unexpected behavior can result from mixing these assignments in a single block. Standard rules:

- i. Use blocking assignments to model combinational logic within an always block (“=”).
- ii. Use non-blocking assignments to implement sequential logic (“<=”).
- iii. Do not mix blocking and non-blocking assignments in the same always block.
- iv. Do not make assignments to the same variable from more than one always block.

# Combinational logic always blocks

Make sure all signals assigned in a combinational always block are explicitly assigned values every time that the always block executes. Otherwise latches will be generated to hold the last value for the signals not assigned values.

*Sel case value 2'd2 omitted.*

*Out is not updated when select line has 2'd2.*

*Latch is added by tool to hold the last value of out under this condition.*

*Similar problem with if-else statements.*

```
module mux4to1 (out, a, b, c, d, sel);
output out;
input a, b, c, d;
input [1:0] sel;
reg out;
always @(sel or a or b or c or d)
begin
    case (sel)
        2'd0: out = a;
        2'd1: out = b;
        2'd3: out = d;
    endcase
end
endmodule
```

# Combinational logic always blocks (cont.)

To avoid synthesizing a latch in this case, add the missing select line:

```
2'd2: out = c;
```

Or, in general, use the “default” case:

```
default: out = foo;
```

If you don't care about the assignment in a case (for instance you know that it will never come up) then you can assign the value “x” to the variable. Example:

```
default: out = 1'bx;
```

The x is treated as a “don't care” for synthesis and will simplify the logic.

Be careful when assigning x (don't care). If this case were to come up, then the synthesized circuit and simulation may differ.

# Special Values: x and z...


- ❑ 1'bx == single bit of "don't care" for synthesis
  - ❑ Result can actually become anything... 0... 1... bouncing up and down, etc etc etc...
    - ❑ It gives freedom to the compiler/simulator to do whatever it wants
    - ❑ Simulator: Usually process it as an explicit X output
    - ❑ Compiler: Optimizes it to produce either a 0, 1, or Z depending on everything else in the circuit
- ❑ 1'bz == "High impedance"
  - ❑ Result is "disconnect": **nothing** is driving this output
  - ❑ Needed to implement connections that can be both input & output

# FSM Comparison

## Solution A
 
### Moore Machine

- output function only of PS
- maybe more states (why?)
- synchronous outputs
  - Input glitches not send at output
  - one cycle “delay”
  - full cycle of stable output



## Solution B

### Mealy Machine

- output function of both PS & input
- maybe fewer states
- asynchronous outputs
  - if input glitches, so does output
  - output immediately available
  - output may not be stable long enough to be useful (below):

*If output of Mealy FSM goes through combinational logic before being registered, the CL might delay the signal and it could be missed by the clock edge.*

# General FSM Design Process with Verilog Implementation



## Design Steps:

1. Specify **circuit function** (English)
  2. Draw **state transition diagram**
  3. Write down **symbolic state transition table**
  4. Assign encodings (bit patterns) to symbolic states
  5. Code as Verilog behavioral description.. (Or just skip from 1 to 4+5...)
- ✓ Use parameters to represent encoded states.
  - ✓ Use separate always blocks for register assignment and CL logic block.
  - ✓ Use case for CL block. Within each case section (state) assign all outputs and next state value based on inputs. Note: For Moore style machine make outputs dependent only on state not dependent on inputs.

# Finite State Machine in Verilog

## Implementation Circuit Diagram

### State Transition Diagram

  

**CL functions to determine output**  
**Holds a symbol to keep value and next state based on input**  
**track of which bubble**  
**the FSM is in.**

**$out = f(in, \text{current state})$**   
 **$next\ state = f(in, \text{current state})$**

# Finite State Machines

```
module FSM1 (clk, rst, in, out);  
input clk, rst;  
input in;  
output out;
```

**Must use reset to force to initial state.**

**reset not always shown in STD**

```
// Defined state encoding:
```

```
parameter IDLE = 2'b00;
```

```
parameter S0 = 2'b01;
```

```
parameter S1 = 2'b10;
```

**Constants local to this module.**

```
reg out;
```

**out not a register, but assigned in always block**

```
reg [1:0] present_state, next_state;
```

**Combinational logic signals for transition.**


**THE register to hold the "state" of the FSM.**

```
// always block for state register
```

```
always @(posedge clk)
```

```
if (rst) present_state <= IDLE;
```

 
```
else present_state <= next_state;
```



**A separate always block should be used for combination logic part of FSM. Next state and output generation. (Always blocks in a design work in parallel.)**
 
# FSMs (cont.)

```
// always block for combinational logic portion
always @(present_state or in)
case (present_state)
// For each state def output and next
  IDLE : begin
    out = 1'b0;
    if (in == 1'b1) next_state = S0;
    else next_state = IDLE;
  end
  S0 : begin
    out = 1'b0;
    if (in == 1'b1) next_state = S1;
    else next_state = IDLE;
  end
  S1 : begin
    out = 1'b1;
    if (in == 1'b1) next_state = S1;
    else next_state = IDLE;
  end
  default: begin
    next_state = IDLE;
    out = 1'b0;
  end
endcase
endmodule
```



Each state becomes a case clause.


For each state define:  
Output value(s)  
State transition

Use "default" to cover unassigned state. Usually unconditionally transition to reset state.

Mealy or Moore?

# Edge Detector Example


## Mealy Machine

 

```

always @(posedge clk)
    if (rst) ps <= ZERO;
    else ps <= ns;
always @(ps in)
    case (ps)
        ZERO: if (in) begin
                out = 1'b1;
                ns = ONE;
            end
            else begin
                out = 1'b0;
                ns = ZERO;
            end
        ONE: if (in) begin
                out = 1'b0;
                ns = ONE;
            end
            else begin
                out = 1'b0;
                ns = ZERO;
            end
        default: begin
                out = 1'bx;
                ns = default;
            end
    endcase
    
```

## Moore Machine

 


```


always @(posedge clk)
    if (rst) ps <= ZERO;
    else ps <= ns;
always @(ps in)
    case (ps)
        ZERO: begin
                out = 1'b0;
                if (in) ns = CHANGE;
                else ns = ZERO;
            end
        CHANGE: begin
                out = 1'b1;
                if (in) ns = ONE;
                else ns = ZERO;
            end
        ONE: begin
                out = 1'b0;
                if (in) ns = ONE;
                else ns = ZERO;
            end
        default: begin
                out = 1'bx;
                ns = default;
            end
    endcase
    
```
 
# FSM CL block (original)

```
always @(present_state or in)
case (present_state)
  IDLE : begin
    out = 1'b0;
    if (in == 1'b1) next_state = S0;
    else next_state = IDLE;
  end
  S0 : begin
    out = 1'b0;
    if (in == 1'b1) next_state = S1;
    else next_state = IDLE;
  end
  S1 : begin
    out = 1'b1;
    if (in == 1'b1) next_state = S1;
    else next_state = IDLE;
  end
default: begin
  next_state = IDLE;
  out = 1'b0;
end
endcase
endmodule
```



# FSM CL block rewritten

 

```
always @*
```

*\* for sensitivity list*

```
begin
```

```
next_state = IDLE;
```

```
out = 1'b0;
```

*Normal values: used unless specified below.*

```
case (state)
```

```
  IDLE : if (in == 1'b1) next_state = S0;
```

```
  S0   : if (in == 1'b1) next_state = S1;
```

```
  S1   : begin
```

```
    out = 1'b1;
```

```
    if (in == 1'b1) next_state = S1;
```

```
  end
```

```
  default: ;
```

```
endcase
```

```
end
```

```
Endmodule
```

*Within case only need to specify exceptions to the normal values.*

*Note: The use of “blocking assignments” allow signal values to be “rewritten”, simplifying the specification.*

# Incomplete Triggers


Leaving out an input trigger usually results in latch generation for the missing trigger.

```
module and_gate (out, in1, in2);  
  input    in1, in2;  
  output   out;  
  reg      out;  
  
  always @(in1) begin  
    out = in1 & in2;  
  end  
  
endmodule
```

in2 not in always sensitivity list.

A latched version of in2 is synthesized and used as input to the and-gate, so that the and-gate output is not always sensitive to in2.

 
Easy way to avoid incomplete triggers for combinational logic is with: *always @\**



# Intro to Logic Synthesis
 
# EECS151/251A Design Methodology

Hierarchically define structure and/or behavior of circuit.



Functional verification.

Maps specification to resources of implementation platform (FPGA or ASIC).

Note: This is not the entire story. Other tools are often used to analyze HDL specifications and synthesis results. More on this later.

# Logic Synthesis

- ❑ Verilog and VHDL started out as simulation languages, but quickly people wrote programs to automatically convert Verilog code into low-level circuit descriptions (netlists).



- ❑ Synthesis converts Verilog (or other HDL) descriptions to implementation technology specific primitives:
  - For FPGAs: LUTs, flip-flops, and RAM blocks
  - For ASICs: standard cell gate and flip-flop libraries, and memory blocks.

# *Why Logic Synthesis?*

1. Automatically manages many details of the design process:
  - ⇒ Fewer bugs
  - ⇒ Improved productivity
2. Abstracts the design data (HDL description) from any particular implementation technology.
  - Designs can be re-synthesized targeting different chip technologies. Ex: first implement in FPGA then later in ASIC.
3. In some cases, leads to a more optimal design than could be achieved by manual means (ex: logic optimization)

## *Why Not Logic Synthesis?*

1. *May lead to non-optimal designs in some cases.*
2. *Often less transparent than desired: Good performance requires basically modeling the compiler in your head...*

*foo.v*



## **Main Logic Synthesis Steps**

**Parsing and  
Syntax Check**

Load in HDL file, run macro preprocessor for `define, `include, etc..

**Design  
Elaboration**

Compute parameter expressions, process generates, create instances, connect ports.

**Inference  
and Library  
Substitution**

Recognize and insert special blocks (memory, flip-flops, arithmetic structures, ...)

**Logic  
Expansion**

Expand combinational logic to primitive Boolean representation.

**Logic  
Optimization**

Apply Boolean algebra and heuristics to simplify and optimize under constraints.

**Map, Place &  
Route**

CL and state elements to LUTs (FPGA) or Technology Library (ASCI) , assign physical locations, route connections.




*foo.ncd, foo.gates*

# Operators and Synthesis


- ❑ Logical operators map into primitive logic gates
- ❑ Arithmetic operators map into adders, subtractors, ...
  - Unsigned 2s complement
  - Model carry: target is one-bit wider than source
  - Watch out for \*, %, and /
- ❑ Relational operators generate comparators
- ❑ Shifts by constant amount are just wire connections
  - No logic involved
- ❑ Variable shift amounts, a whole different story --- shifters are **expensive!**
- ❑ Conditional expression generates logic or MUX

$$Y = \sim X \ll 2$$

 

# Simple Synthesis Example

```
module foo (A, B, s0, s1, F);  
  input [3:0] A;  
  input [3:0] B;  
  input s0,s1;  
  output [3:0] F;  
  reg F;  
  always @ (*)  
    if (!s0 && s1 || s0) F=A; else F=B;  
endmodule
```

 

Should expand if-else into 4-bit wide multiplexor and optimize the control logic and ultimately to 4 4-LUT on an FPGA:


# Encoder Example

Nested IF-ELSE might lead to “priority logic”

 Example: 4-to-2 encoder

```
always @(x)
begin : encode
if (x == 4'b0001) y = 2'b00;
else if (x == 4'b0010) y = 2'b01;
else if (x == 4'b0100) y = 2'b10;
else if (x == 4'b1000) y = 2'b11;
else y = 2'bxx;
end
```


This style of cascaded logic may adversely affect the performance of the circuit.


 
# Encoder Example (cont.)

To avoid “priority logic” use the case construct:


```
always @(x)
begin : encode
case (x)
4'b0001: y = 2'b00;
4'b0010: y = 2'b01;
4'b0100: y = 2'b10;
4'b1000: y = 2'b11;
default: y = 2'bxx;
endcase
end
```



*All cases are matched in parallel.*
 
## Encoder Example (cont.)

This circuit would be simplified during synthesis to take advantage of constant values as follows and other Boolean equalities:



*A similar simplification would be applied to the if-else version also.*

# *More On Karnaugh Maps*

- ❑ Realize I should have covered this in more detail...
  - ❑ So lets snag some older slides...

# Algorithmic Two-level Logic Simplification

Key tool: The Uniting Theorem:

$$xy' + xy = x(y' + y) = x(1) = x$$

<i>ab</i>	<i>f</i>
00	0
01	0
10	1
11	1

$$f = ab' + ab = a(b' + b) = a$$

b values change within the on-set rows

a values don't change

b is eliminated, a remains

<i>ab</i>	<i>g</i>
00	1
01	0
10	1
11	0

$$g = a'b' + ab' = (a' + a)b' = b'$$



b values stay the same

a values changes


b' remains, a is eliminated
  
# Karnaugh Map Method

- K-map is an alternative method of representing the TT and to help visual the adjacencies.



Note: "gray code" labeling.

 

5 & 6 variable k-maps possible

# Karnaugh Map Method

- Adjacent groups of 1's represent product terms

		a	
		0	1
b	0	0	1
	1	0	1

$f = a$

		a	
		0	1
b	0	1	1
	1	0	0

$g = b'$

		ab			
		00	01	11	10
c	0	0	0	1	0
	1	0	1	1	1

$cout = ab + bc + ac$

		ab			
		00	01	11	10
c	0	0	0	1	1
	1	0	0	1	1

$f = a$

## *K-map Simplification*

1. Draw K-map of the appropriate number of variables (between 2 and 6)
2. Fill in map with function values from truth table.
3. Form groups of 1's.
  - ✓ Dimensions of groups must be even powers of two (1x1, 1x2, 1x4, ..., 2x2, 2x4, ...)
  - ✓ Form as large as possible groups and as few groups as possible.
  - ✓ Groups can overlap (this helps make larger groups)
  - ✓ Remember K-map is periodical in all dimensions (groups can cross over edges of map and continue on other side)
4. For each group write a product term.
  - the term includes the “constant” variables (use the uncomplemented variable for a constant 1 and complemented variable for constant 0)
5. Form Boolean expression as sum-of-products.

## K-maps (cont.)

	ab			
c	00	01	11	10
0	1	0	0	1
1	0	0	1	1

$$f = b'c' + ac$$

	ab			
cd	00	01	11	10
00	1	0	0	1
01	0	1	0	0
11	1	1	1	1
10	1	1	1	1

$$f = c + a'bd + b'd'$$

(bigger groups are better)

## Product-of-Sums Version

1. Form groups of 0's instead of 1's.
2. For each group write a sum term.
  - the term includes the “constant” variables (use the uncomplemented variable for a constant 0 and complemented variable for constant 1)
3. Form Boolean expression as product-of-sums.

		ab			
		00	01	11	10
cd	00	1	0	0	1
	01	0	1	0	0
	11	1	1	1	1
	10	1	1	1	1

$$f = (b' + c + d)(a' + c + d')(b + c + d')$$

# BCD incrementer example

## Binary Coded Decimal

	<i>a</i>	<i>b</i>	<i>c</i>	<i>d</i>	<i>w</i>	<i>x</i>	<i>y</i>	<i>z</i>
0	0	0	0	0	0	0	0	1
1	0	0	0	1	0	0	1	0
2	0	0	1	0	0	0	1	1
3	0	0	1	1	0	1	0	0
4	0	1	0	0	0	1	0	1
5	0	1	0	1	0	1	1	0
6	0	1	1	0	0	1	1	1
7	0	1	1	1	1	0	0	0
8	1	0	0	0	1	0	0	1
9	1	0	0	1	0	0	0	0
	1	0	1	0	-	-	-	-
	1	0	1	1	-	-	-	-
	1	1	0	0	-	-	-	-
	1	1	0	1	-	-	-	-
	1	1	1	0	-	-	-	-
	1	1	1	1	-	-	-	-

{*a*,*b*,*c*,*d*}

4 ↓



4 ↓

{*w*,*x*,*y*,*z*}

## *BCD Incrementer Example*

- Note one map for each output variable.
- Function includes “don’t cares” (shown as “-” in the table).
  - These correspond to places in the function where we don’t care about its value, because we don’t expect some particular input patterns.
  - We are free to assign either 0 or 1 to each don’t care in the function, as a means to increase group sizes.
- In general, you might choose to write product-of-sums or sum-of-products according to which one leads to a simpler expression.

# BCD incrementer example

**W**

		ab			
cd	\	00	01	11	10
00		0	0	-	1
01		0	0	-	0
11		0	1	-	-
10		0	0	-	-

**X**

		ab			
cd	\	00	01	11	10
00		0	1	-	0
01		0	1	-	0
11		1	0	-	-
10		0	1	-	-

w =

x =

**y**

		ab			
cd	\	00	01	11	10
00		0	0	-	0
01		1	1	-	0
11		0	0	-	-
10		1	1	-	-



**Z**

		ab			
cd	\	00	01	11	10
00		1	1	-	1
01		0	0	-	0
11		0	0	-	-
10		1	1	-	-

y =

z =

# Higher Dimensional K-maps

  



**Digital abstraction**

# *Bridging the digital and the analog worlds*



- How to represent 0's and 1's in a world that is analog?

# Noise and Digital Systems

- Circuit needs to work despite “analog” noise
  - Digital gates can and must reject noise
  - This is actually how digital systems are defined
  
- Digital system is one where:
  - Discrete values mapped to analog levels and back
  - All the elements (gates) can reject noise
    - For “small” amounts of noise, output noise is less than input noise
  - Thus, for sufficiently “small” noise, the system acts as if it was noiseless
  - This is called **regeneration**

***Noise?***

  
# Noise Rejection and the Voltage Transfer Characteristic



 
# Noise Rejection

- ❑ To see if a gate rejects noise
  - Look at its DC voltage transfer characteristic (VTC)
  - See what happens when input is not exactly 1 or 0

- ❑ Ideal digital gate:
  - Noise needs to be larger than  $V_{DD}/2$  to have any effect on gate output




 
## Realistic Voltage Transfer Characteristic Definitions




$$\begin{aligned}V_{OH} &= f(V_{OL}) \\V_{OL} &= f(V_{OH}) \\V_M &= f(V_M)\end{aligned}$$

Nominal Voltage Levels

# Voltage Mapping

  

# Definition of Noise Margins

 

Noise margin high:

$$NM_H = V_{OH} - V_{IH}$$

Noise margin low:

$$NM_L = V_{IL} - V_{OL}$$