


DOGGO 151/251A SP2022 Discussion 8

GSI: DIMA NIKIFOROV, YIKUAN CHEN



Agenda



- Power/Energy
- Adders

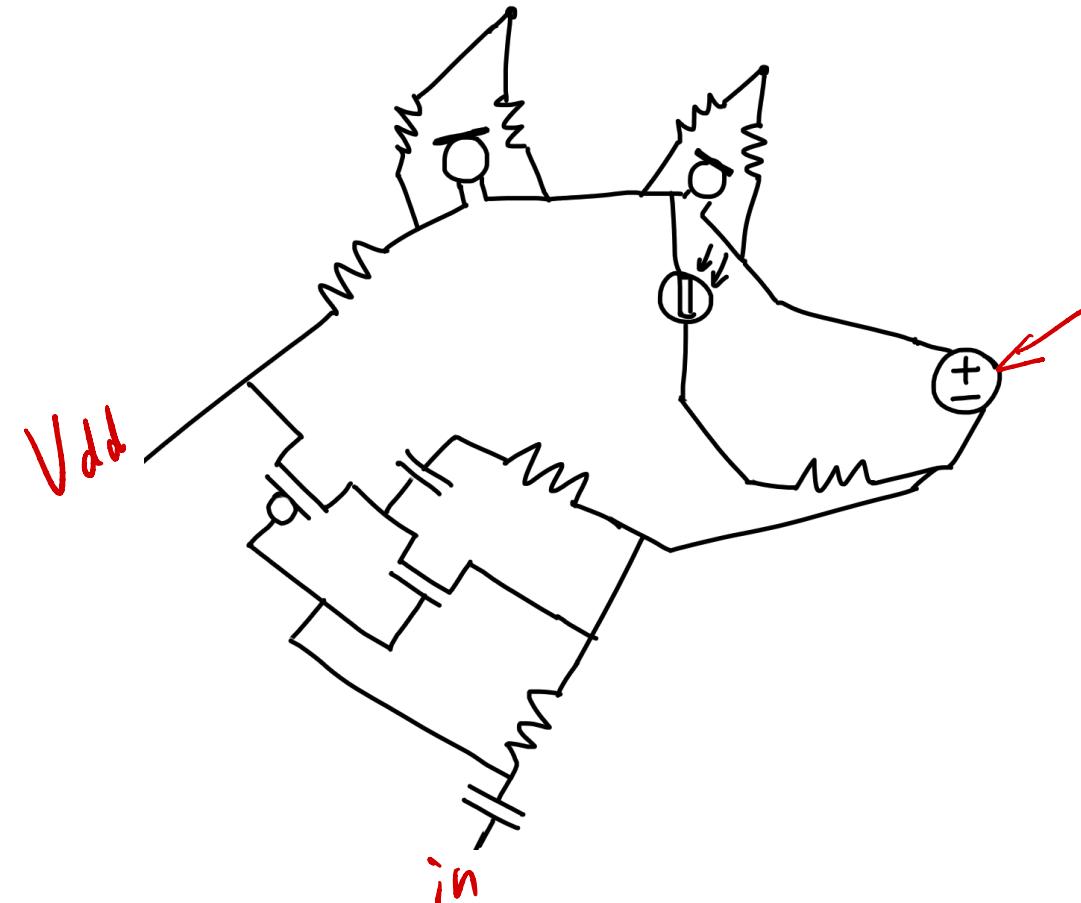

Energy


Power/Energy in Digital Circuits

- Fundamentally, charging/discharging capacitors (gate, parasitic, load) through resistances (PMOS, NMOS, wires)
 - Capacitors draw CV^2 joules from supply over 1 charge/discharge cycle
 - $\frac{1}{2}CV^2$ dissipated in PMOS as heat when charging
 - $\frac{1}{2}CV^2$ stored on capacitor, then dissipated in NMOS when discharging
- Dynamic power = $P_{\text{switching}} = \alpha CV^2 f$
 - How to minimize each term? $\uparrow \text{freq} \rightarrow V \downarrow$ $\xrightarrow{\in [0, 1]}$
 - Minimizing which terms reduces total energy consumed?
- Static power = leakage \rightarrow wasted energy!

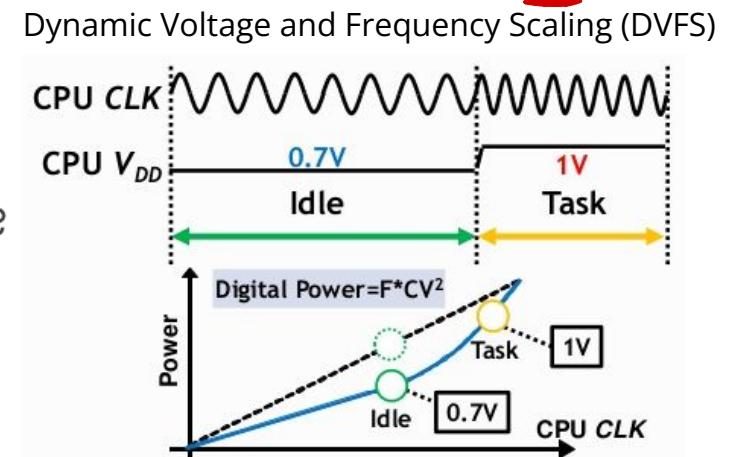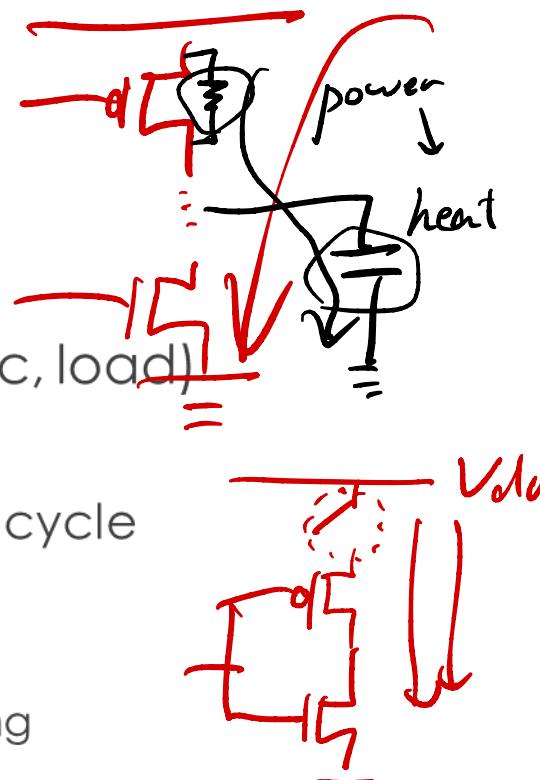


Power/Energy in Digital Circuits Causes

Dynamic Power

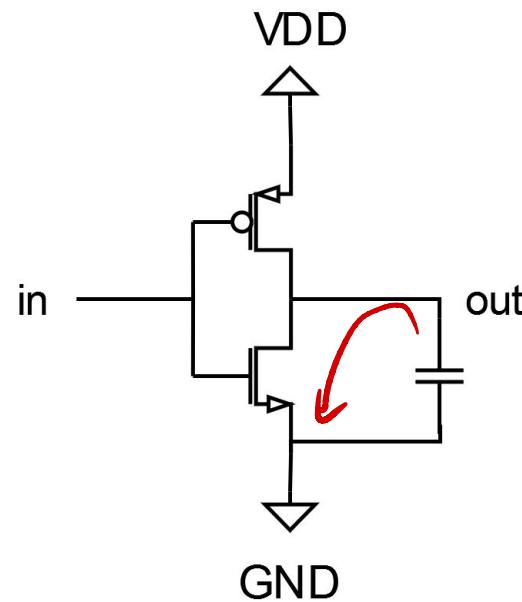

$$\frac{1}{2} C V^2$$


Switching Power

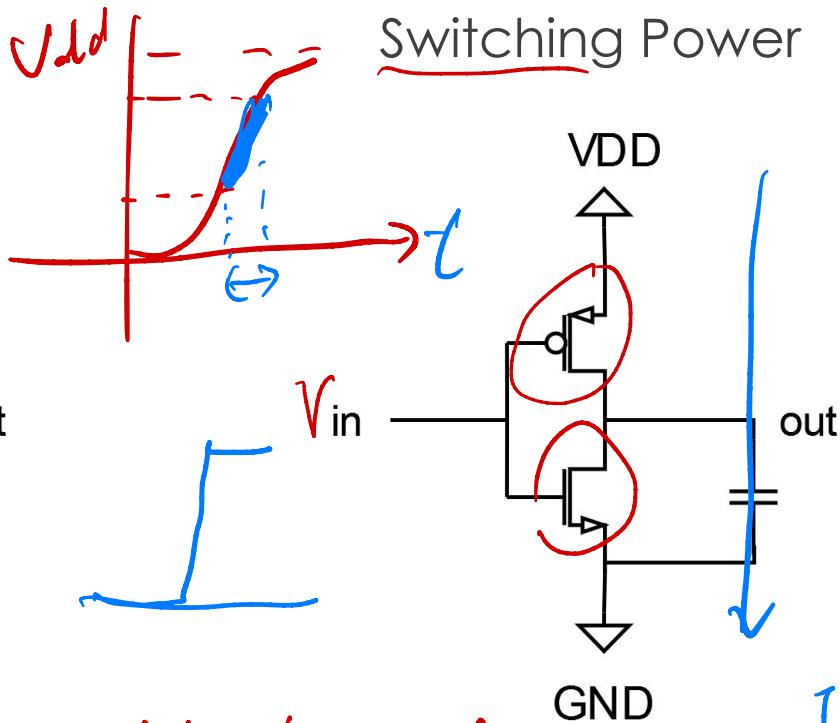

$$V_{dd} - V_{thp} > V > V_{th}$$


$$= \frac{IV}{R} = \frac{V^2}{R}$$

Leakage Power

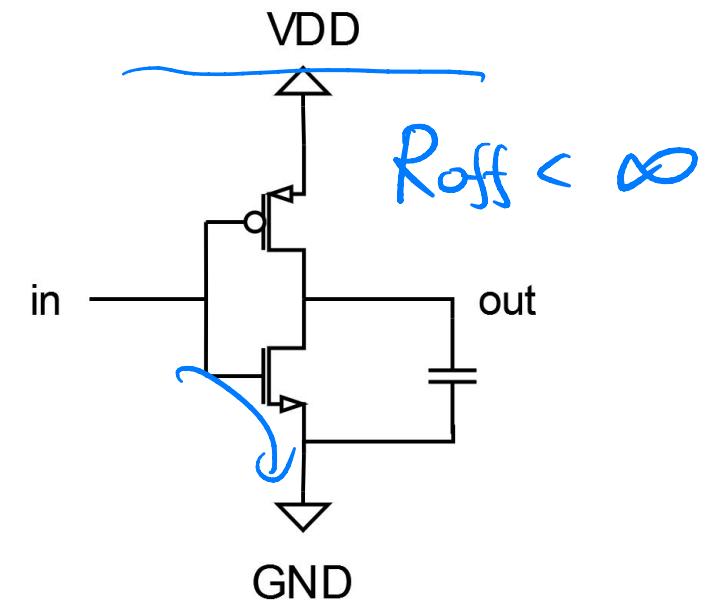

Energy Example

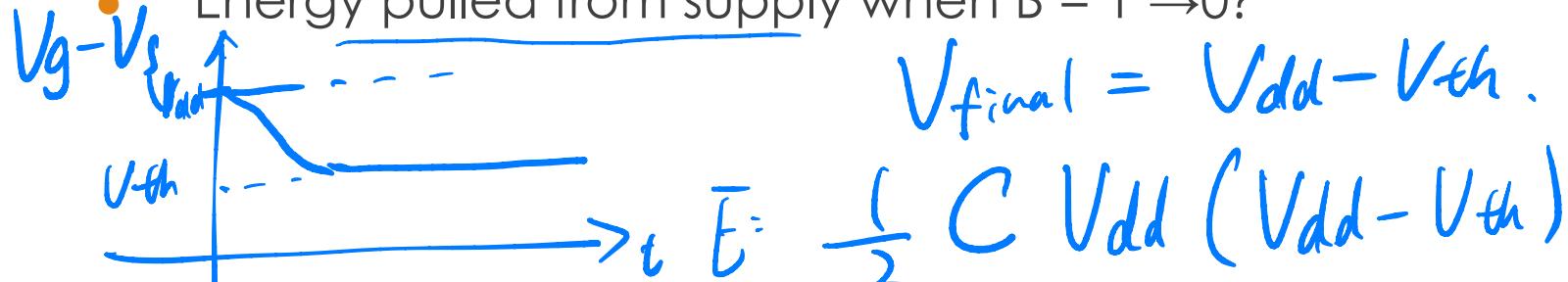
- Initially: $A = 1, C = 1, \text{Out} = 0$
- Energy pulled from supply when $B = 1 \rightarrow 0$?



- Then, how much energy dissipated when $C = 1 \rightarrow 0$?

$$V_{cap} : V_{dd} - V_{th,n} \rightarrow \underline{\underline{V_{th,p}}}$$
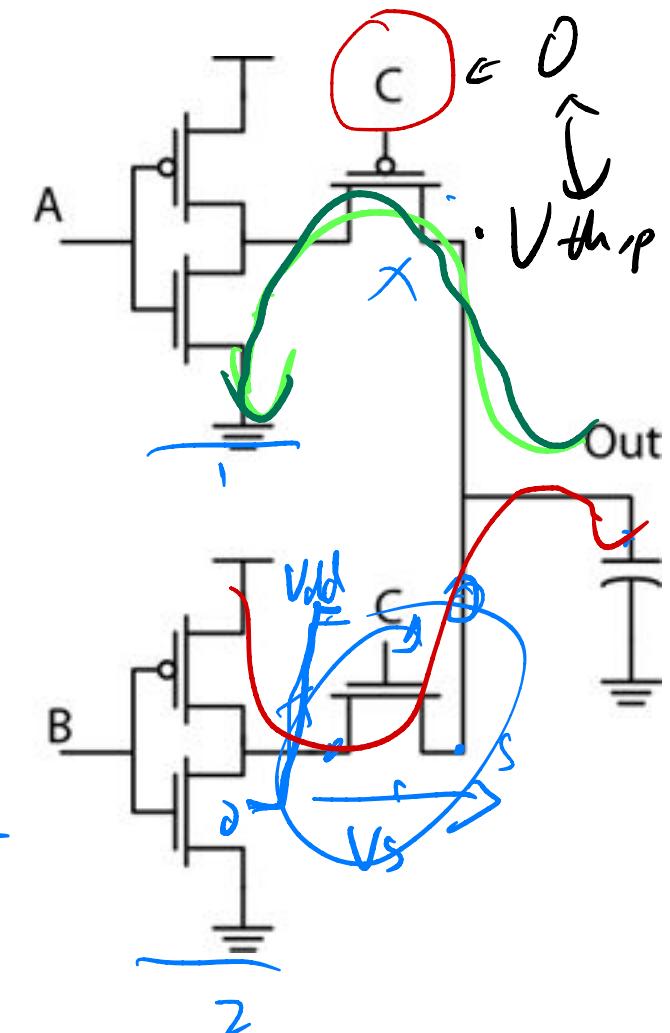
$$\bar{E} : \frac{1}{2} C (V_{dd} - V_{th,n})^2 - \frac{1}{2} C V_{th,p}^2$$




Adders

$$2 \overline{\downarrow} + 3 \overline{\uparrow} = \overline{\uparrow} 5$$


Adder Components

$$2 + 3 = 5$$

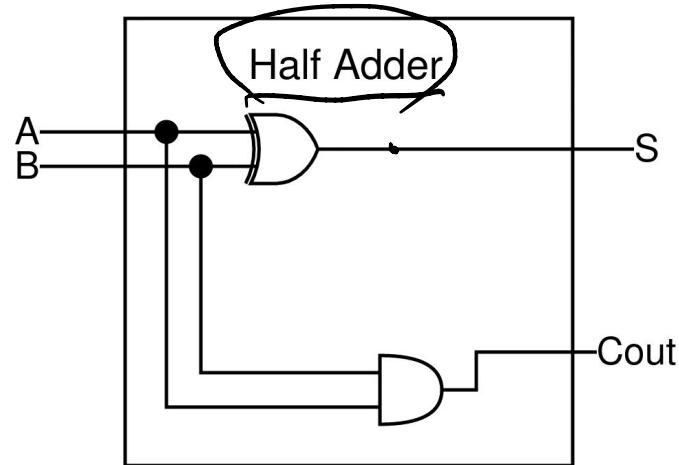


$$S = A \oplus B$$

$$C_o = AB$$

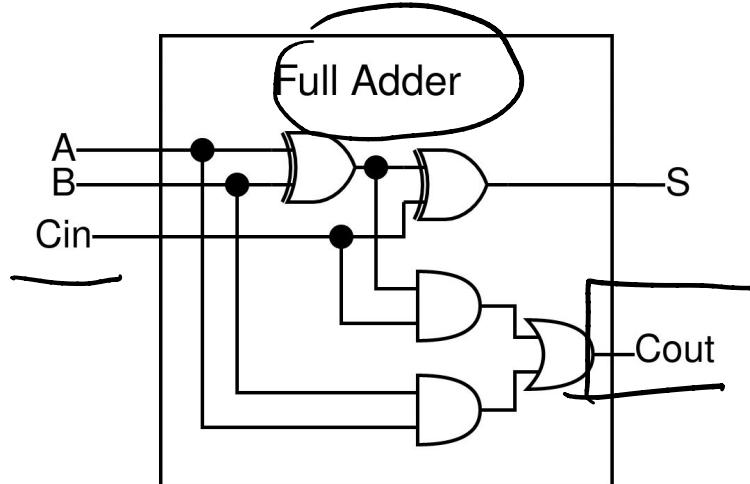


$$\underline{S = A \oplus B \oplus Ci}$$

$$C_o = AB + BCi + ACi$$

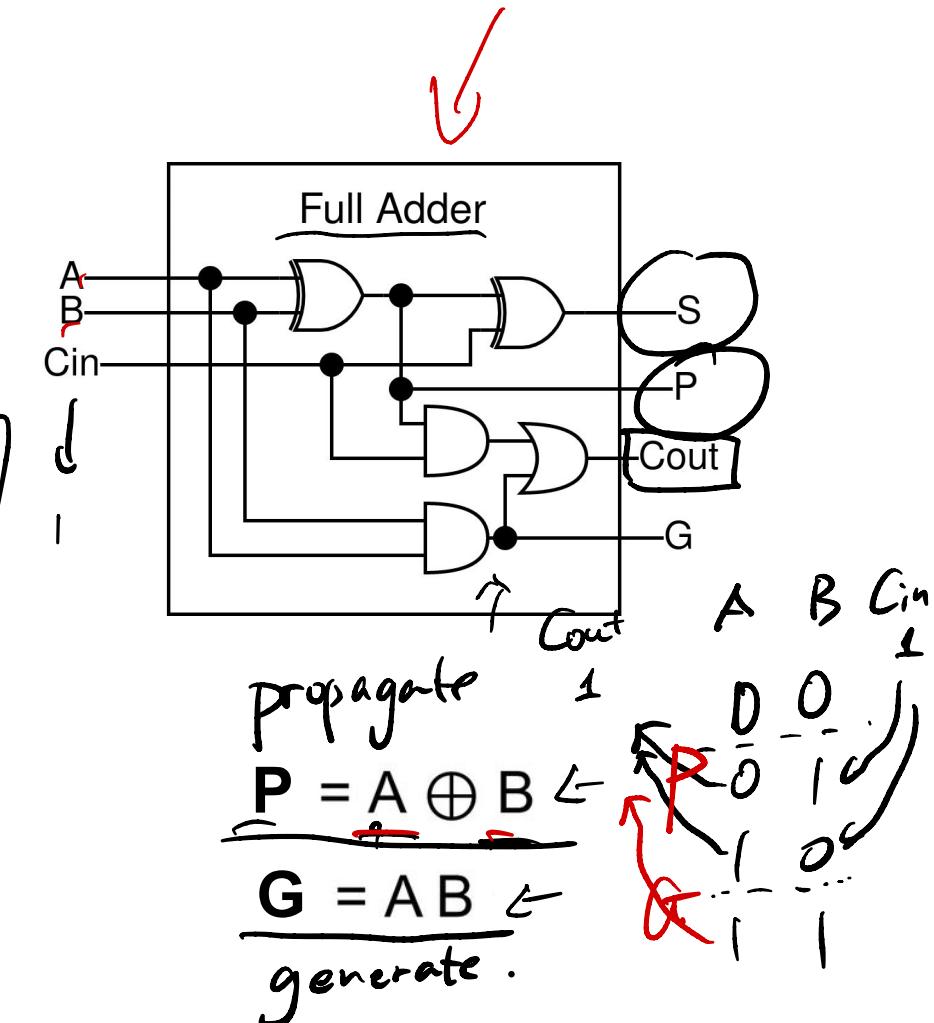


Ripple-Carry Adder

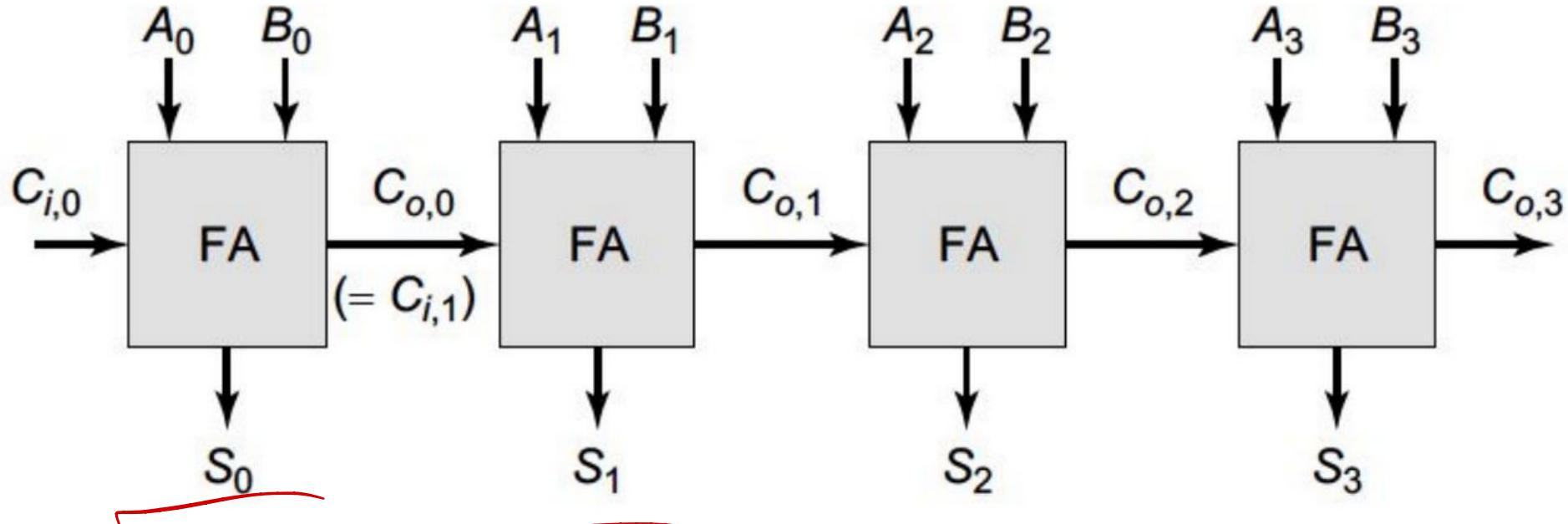


- Time Complexity? $O(N)$
- Area Complexity? $O(N)$

Carry-Lookahead Adder

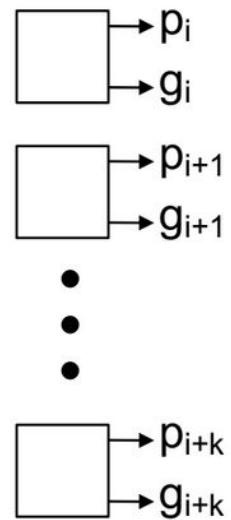

$$P = p_i p_{i+1} \dots p_{i+k}$$
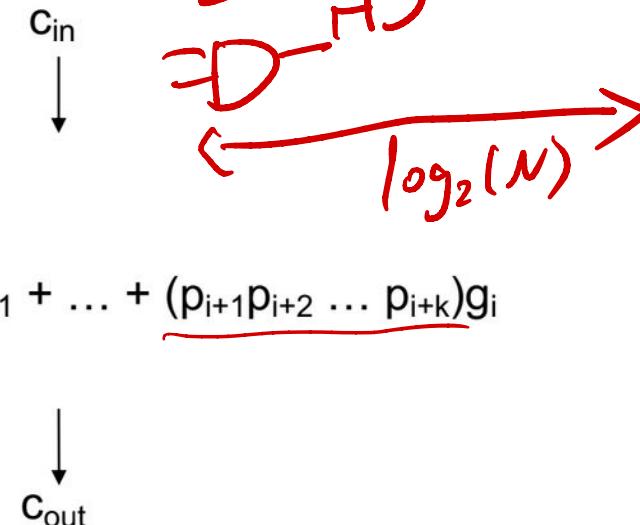
$$G = g_{i+k} + p_{i+k}g_{i+k-1} + \dots + \underline{(p_{i+1}p_{i+2} \dots p_{i+k})g_i}$$




- Time Complexity?

$O(1)$ $\leftarrow N \text{ is big, } O(0)$
 $O(N^2)$ $\leftarrow \text{not possible, } O(\log N)$ $\leftarrow O(0)$
 $\leftarrow O(0)$ $\leftarrow O(0)$ $\leftarrow O(0)$ $\leftarrow O(0)$ $\propto N^2$

10 bit adder
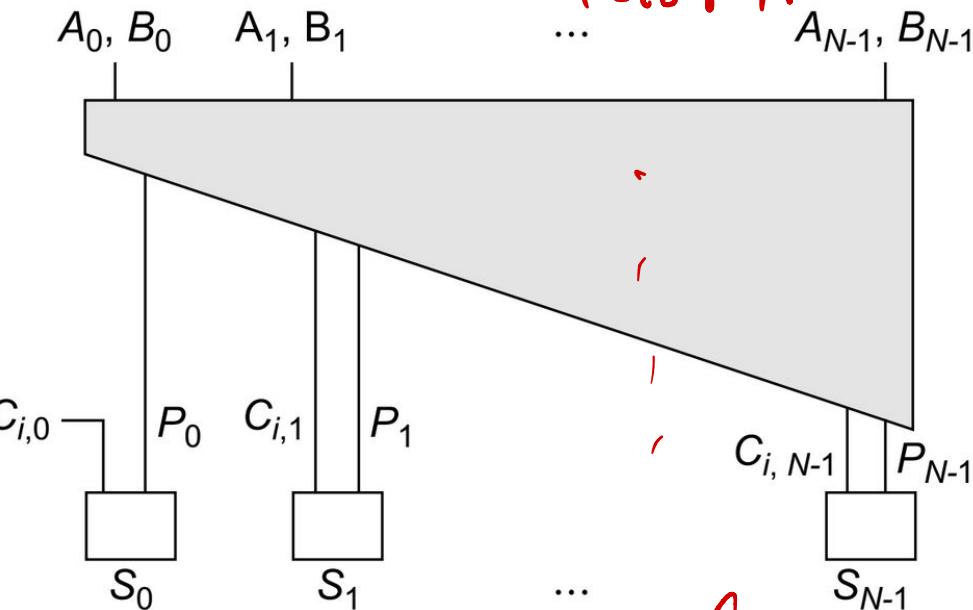
$$\begin{aligned} C_{10} &= \underline{G_{10}} + \cancel{\overline{G_8} P_9 P_{10}} \\ &+ \cancel{\overline{G_8} P_9 P_{10}} \end{aligned}$$



$$C_{o,k} = f(A_k, B_k, C_{o,k-1}) = G_k + P_k C_{o,k-1}$$

$+ \cancel{C_{in} P_0 P_1 P_2 \dots P_{10}}$

Carry-Lookahead Tree Adder

$P_{1:0} = \overline{P_1 \cdot P_0}$; Group Gen; Group Prop.

$$C_{out6} = G_{6:0} + P_{6:0} \cdot C_{0,in}$$

$$P_{1:0} = P_1 \cdot P_0, G_{1:0} = G_1 + P_1 \cdot G_0, \rightarrow C_{out1} = G_{1:0} + P_{1:0} \cdot C_{0,in}$$

- Time Complexity?


$$\mathcal{O}(\log_2 N)$$

- Area Complexity?








$$4 + 2 + 1$$

$$= 2^3 - 1$$

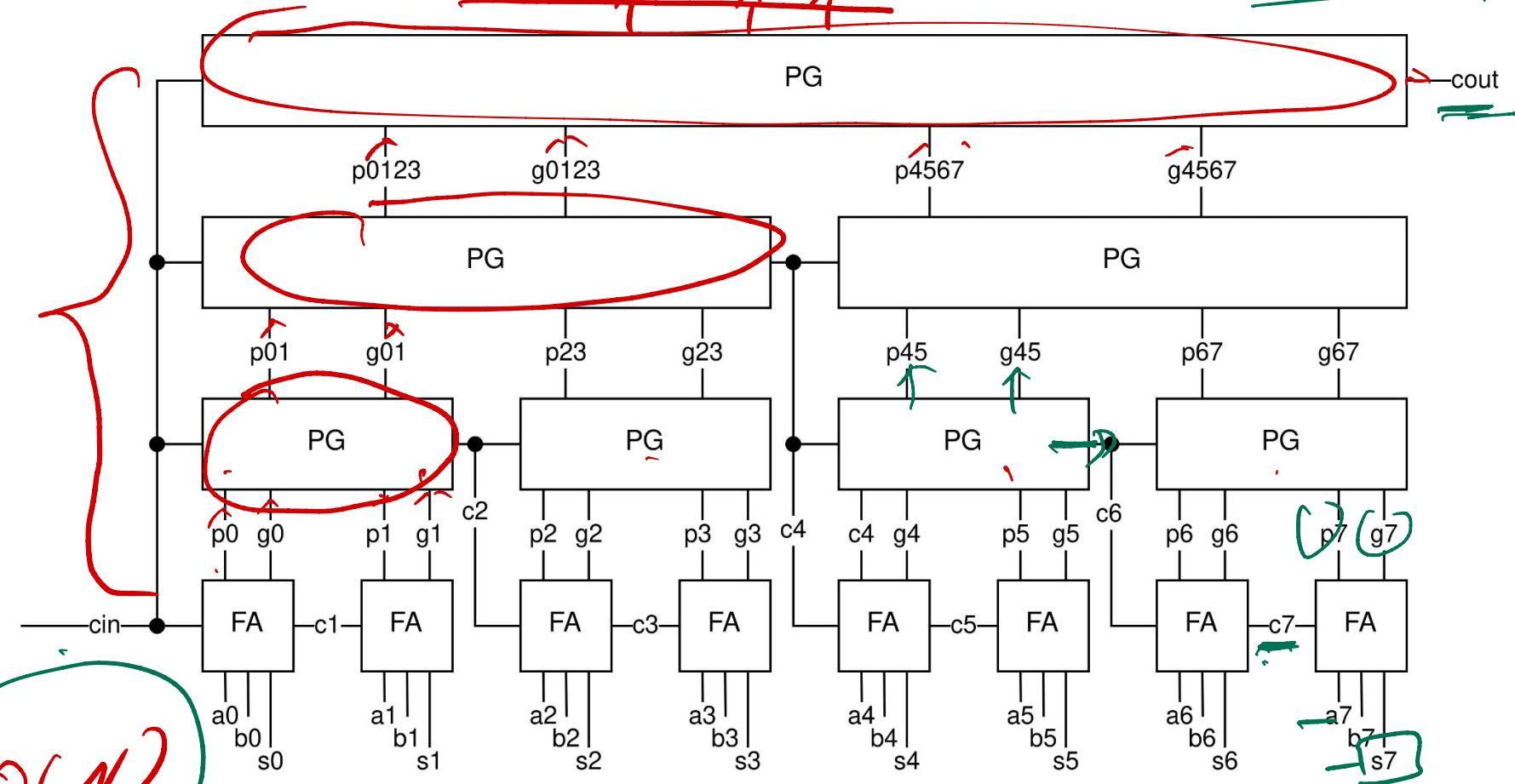
$$= \frac{2^{\log_2 8}}{8} - 1 \Rightarrow \mathcal{O}(N)$$



Kogge-Stone Tree Adder (Components)

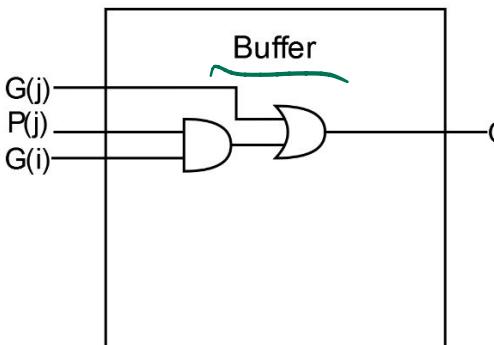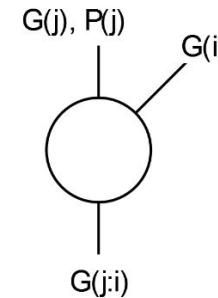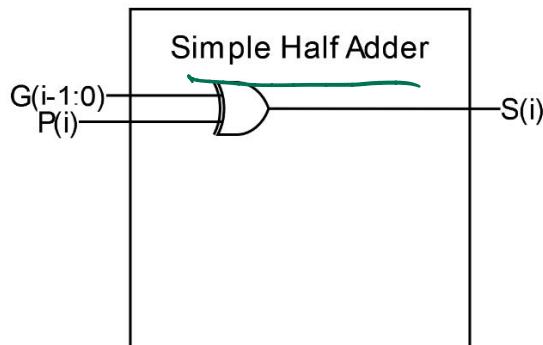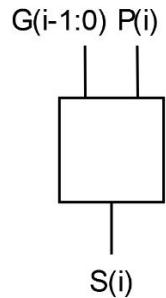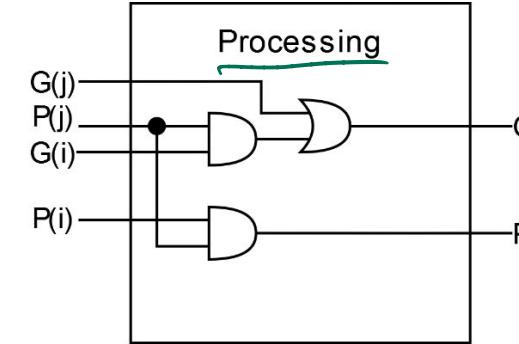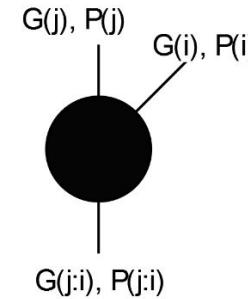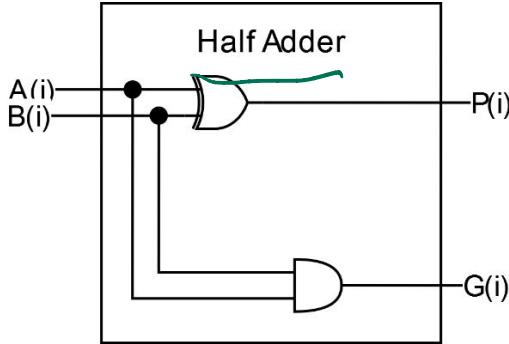

Kogge-Stone Tree Adder

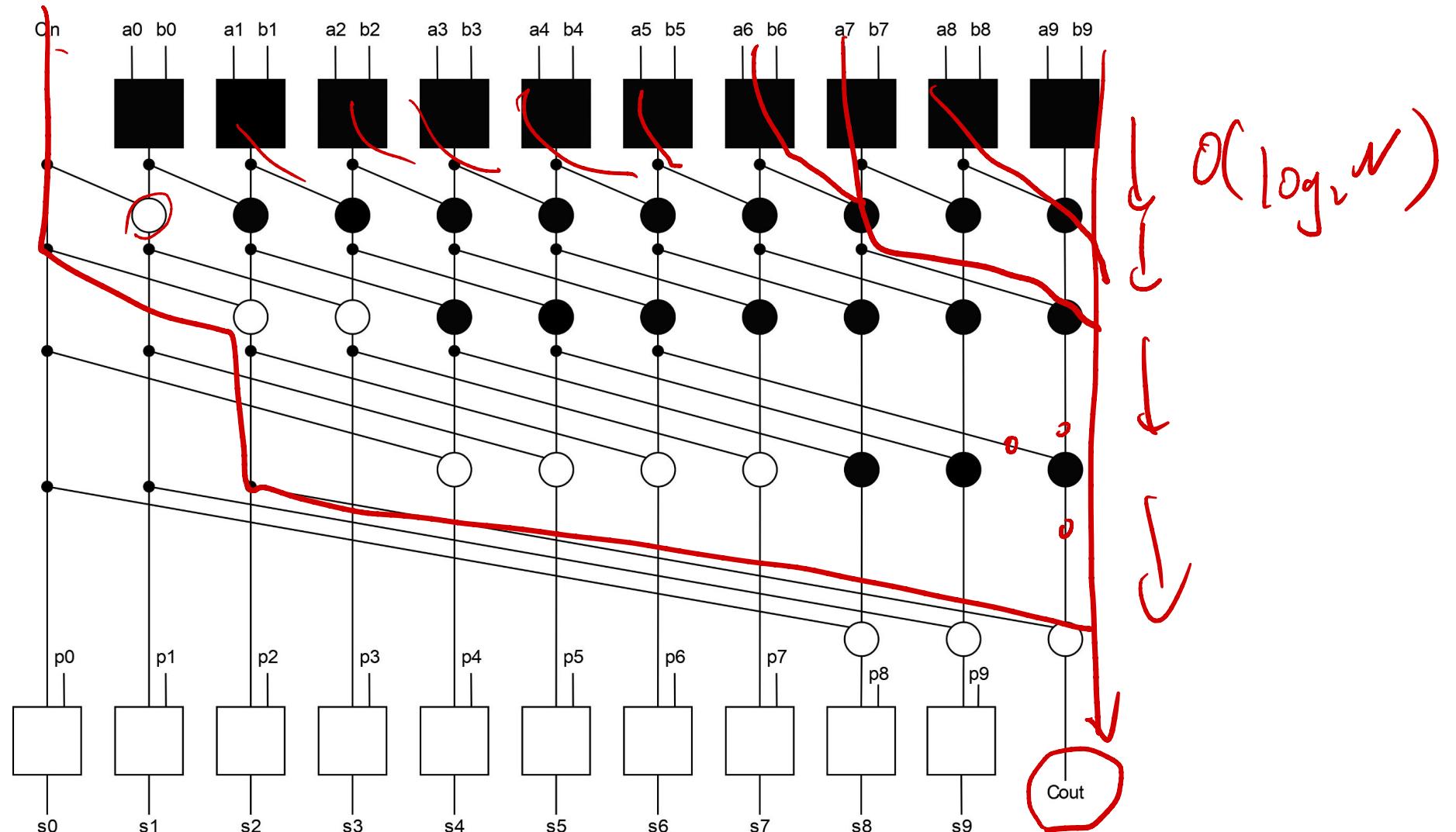

Doggo Adder



+



=



Questions?