

# EECS 151/251A

## SP2022 Discussion 9


GSI: Yikuan Chen, Dima Nikiforov

---

# Agenda

- Multiplier
- Latch

# Multiplier

 

# Unsigned Multiplication Example

$$\begin{array}{r}
 4'b0011 \quad (3) \\
 \times 4'b0110 \quad (6) \\
 \hline
 \end{array}$$


- Partial Products can be generated in parallel
- Challenge: improve the **addition** of partial products

$$\begin{array}{r}
 4'b0011 \quad (3) \\
 \times 4'b0110 \quad (6) \\
 \hline
 \phantom{00}0000 \\
 \phantom{00}0011 \\
 \phantom{00}0011 \\
 + 0000 \\
 \hline
 00010010 \quad (18) \\
 \phantom{00}16 + 2
 \end{array}$$


} Partial Products
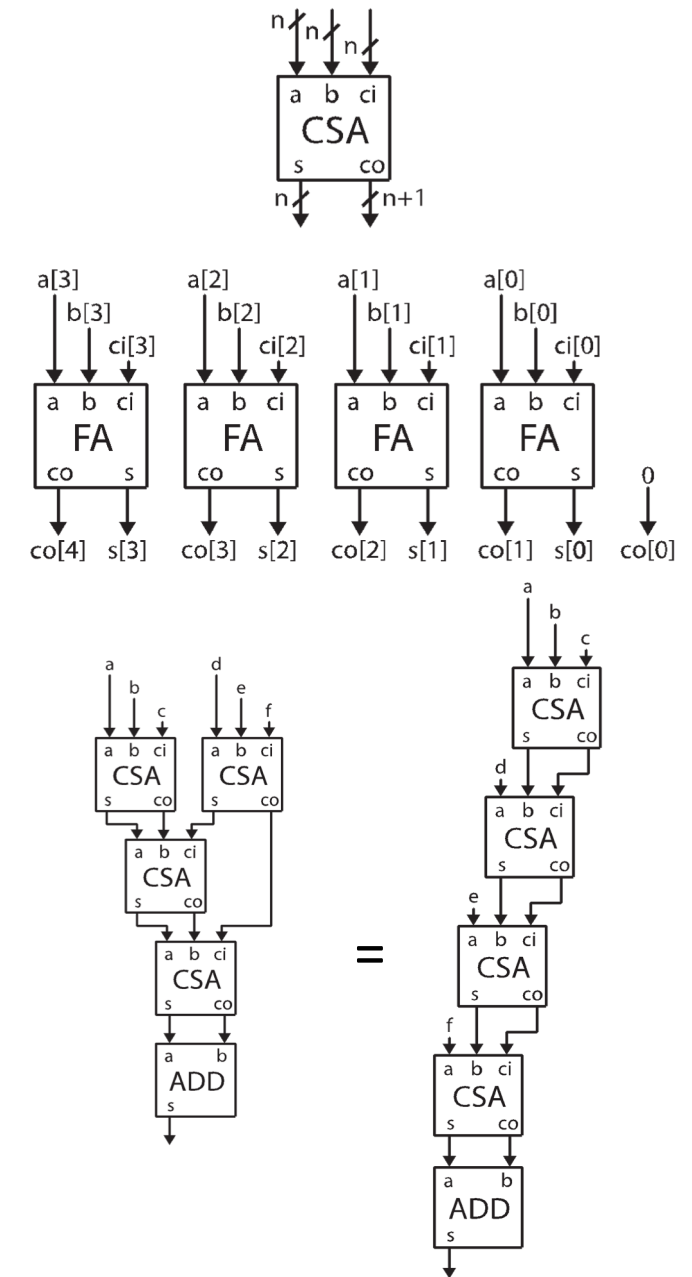
# Carry-Save Addition

- When you want to add **more than 2 numbers**
- When we generate a carry in a given column, add it to the 2 values in the next column.
  - In turn, may generate its own new carry
- Delay adding carry bits until the end
- Basis of Unit Carry-Save Adder:
  - Takes in  $a$ ,  $b$ ,  $c_{in}$  (all are multi-bit)
  - Produces a sum and  $c_{out}$  (all are multi-bit)
- Benefits:
  - CSAs have no carry ripple => small & fast!
  - Only 1 standard CLA/Parallel Prefix Adder at end
  - Addition is associative => trees!



# Array Multiplier w/ CSA

 


# Wallace Tree Multiplier – Reduce the rows!

Method to construct Wallace Tree:


1. Draw a dot diagram where each column has as many dots as number of partial products
2. Group dots in the same column by 2 (half adder) or 3 (full adder)
3. Propagate carries and sum by adding one dot in the grouped column and one dot in the next column

Partial products

 


(a)

First stage

 


(b)

Second stage

 

(c)

Final adder

 

(d)

# Radix-4 Multiplication

- Binary multiplication  $\rightarrow$   $N$  partial products! Can we reduce this?
  - Yes! Let's use a larger radix (think: base)
- E.g. 2 bits at a time (radix 4)  $\rightarrow$  halve number of partial products

b Digit	Partial Product	Partial Product (Rewritten)
00	$0*A$	0
01	$1*A$	A
10	$2*A$	$4*A - 2*A$
11	$3*A$	$4*A - A$

$$1101 * 0110 \rightarrow 1101 * [01][10]$$



# Booth Recoding –

- $4*A = A \ll 2$
- $2*A = A \ll 1$
- Recall: radix 4 multiplication => shift left by 2 positions for next partial product
- Therefore, any  $4*A$  term can be handled in the next partial product!
  - Multiplier looks a 3 (rather than just 2) bits
  - Extra bit is MSB of the previous

B Digit	Partial Product	Partial Product (Rewritten)
00	$0*A$	0
01	$1*A$	A
10	$2*A$	$4*A - 2*A$
11	$3*A$	$4*A - A$

# Booth Recoding


$B_{i+1}$	$B_i$	$B_{i-1}$	Action	Comment
0	0	0	Add 0	
0	0	1	Add A	Includes $+4*A$ from previous radix 4 digit = $+A$ in this position due to left shift by 2
0	1	0	Add A	
0	1	1	Add $2*A$	Includes $+4*A$ from previous round ( $+A$ in this position). $*2$ is implemented as a left shift by 1
1	0	0	Sub $2*A$	$4*A$ will be added in when handling next radix 4 digit. $*2$ is implemented as a left shift by 1
1	0	1	Sub A	$4*A$ will be added in when handling next radix 4 digit. Includes $+4*A$ from previous radix 4 digit ( $+A$ in this position)
1	1	0	Sub A	$4*A$ will be added in when handling next radix 4 digit.
1	1	1	Add 0	$4*A$ will be added in when handling next radix 4 digit. Includes $+4*A$ from previous radix 4 digit ( $+A$ in this position)

# Booth Recoding Example (Unsigned)

- $6 * 7$
- $B_{-1} = 0$

$$\begin{array}{r}
 4'b0110 \quad (6) \\
 * 4'b0111 \quad (7) \\
 \hline
 - \quad 0110 \quad (\text{Sub } A) \\
 + \quad 01100 \quad (\text{Add } 2A) \\
 + \quad 0000 \quad (\text{Add } 0) \\
 \hline
 + \quad 1111010 \quad (\text{Sub } A) \\
 + \quad 01100 \quad (\text{Add } 2A) \\
 + \quad 0000 \quad (\text{Add } 0) \\
 \hline
 \text{(1)00101010} \quad (42)
 \end{array}$$

$B_{i+1}$	$B_i$	$B_{i-1}$	Action
0	0	0	Add 0
0	0	1	Add A
0	1	0	Add A
0	1	1	Add 2*A
1	0	0	Sub 2*A
1	0	1	Sub A
1	1	0	Sub A
1	1	1	Add 0

 

# Signed Multiplication: Baugh-Wooley

- Recall: 2's complement MSB has negative weight, meaning:  
If  $a[N-1:0]$  has its MSB=1, then rather than meaning  $2^{(N-1)}$ , it means  $-2^{(N-1)}$
- Nominally:
  - Subtract last partial product
  - Sign-extend the rest of the partial products
- Recall 2's complement negation: subtract  $A = \text{add } (\sim(A) + 1)$ 
  - Result: basically same hardware as unsigned mult.
  - Implementation: invert some bits, insert a 1 left of the first & last partial products


$$\begin{array}{rcccccccc} & & & & 1 & p0[3] & p0[2] & p0[1] & p0[0] \\ + & & & & \sim p1[3] & p1[2] & p1[1] & p1[0] & 0 \\ + & & & \sim p2[3] & p2[2] & p2[1] & p2[0] & 0 & 0 \\ + & 1 & \sim p3[3] & \sim p3[2] & \sim p3[1] & \sim p3[0] & 0 & 0 & 0 \\ \hline P[7] & P[6] & P[5] & P[4] & P[3] & P[2] & P[1] & P[0] \end{array}$$

# Latch



 
# Latch Timing


- A positive latch is **transparent** ( $q = d$ ) when the **clock is high** and **opaque** ( $q = d$ , sampled at negedge clock) when the **clock is low**
- $t_{d \rightarrow q}$  : delay from  $d$  to  $q$  when the latch is transparent
- $t_{clk \rightarrow q}$  : delay from the rising clock edge to  $d$  propagating to  $q$




# Latch Circuits

 

 'Feedback-breaking' latch  
Transparent high



'State-forcing' latch  
Transparent low

 


SR latch  
Common interview question

S	R	Q	$\bar{Q}$
0	0	latch	latch
0	1	0	1
1	0	1	0
1	1	0	0

 
# Building a Flip-Flop from Latches

- Clock pulsed latch
  - Latch becomes transparent for the pulse duration only, then holds data
  - Not common anymore, sometimes used in high performance circuits
  - Positive hold time


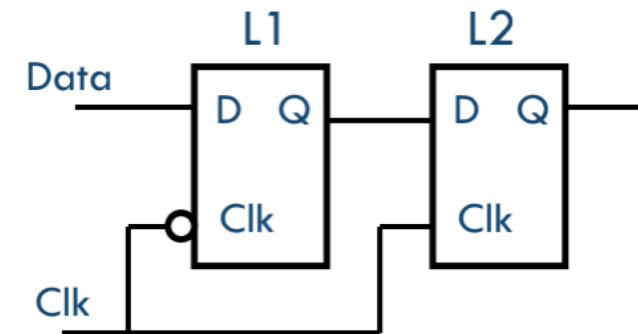
## Pair of latches – edge triggered (posedge clk!!!)

- Commonly used technique
- L2 holds output data stable when clock is high.
- Negative hold time





Questions?