

(21)

EE16A

Lecture 2 - Module 2

Touchscreen intro - modeling with circuit elements

Today: - Review ckt analysis (voltage divider example)


Note 12
(reading)

- Touchscreen construction


- Modeling

- Analysis + Modeling to design a touchscreen


Q2

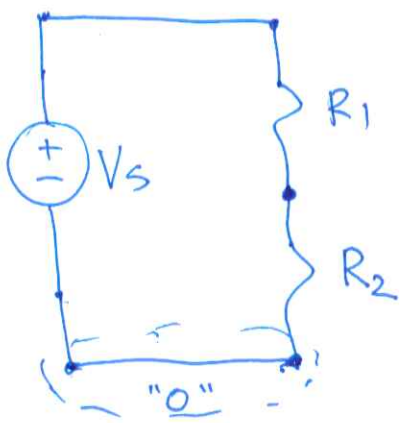


step 1
label a "ref node"

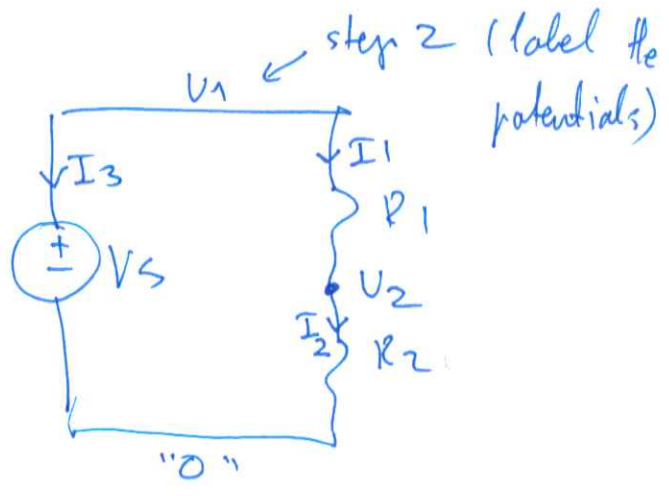

step 3

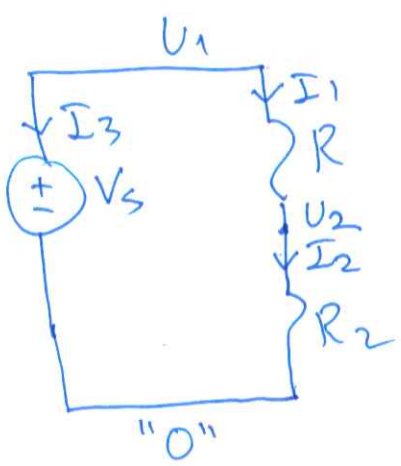

"tricky" step 4

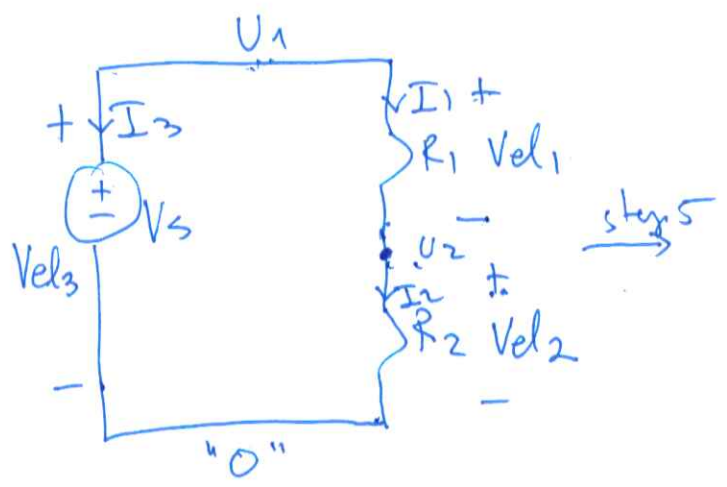

step 5
identify the unknowns

$$\vec{x} = \begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ U_1 \\ U_2 \end{bmatrix}$$

step 6
KCL

$$I_1 + I_3 = 0 \quad (1)$$

$$I_1 = I_2 \Rightarrow -I_1 + I_2 = 0 \quad (2)$$


step 7
element voltages

Voltage-potential def

$$\begin{aligned} Vel_1 &= U_1 - U_2 \\ Vel_2 &= U_2 - 0 = U_2 \\ Vel_3 &= U_1 - 0 = U_1 \end{aligned}$$

element I-V
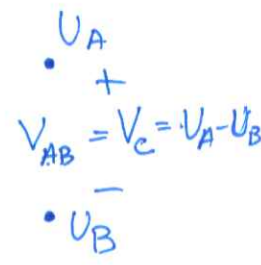
$$\begin{aligned} Vel_1 &= R_1 \cdot I_1 \\ Vel_2 &= R_2 I_2 \\ Vel_3 &= V_s \end{aligned}$$



$$\begin{aligned} R_1 I_1 &= U_1 - U_2 \Rightarrow \\ U_2 &= R_2 I_2 \Rightarrow \\ U_1 &= V_s \quad (5) \end{aligned}$$

$$R_1 I_1 - U_1 + U_2 = 0 \quad (3)$$

$$R_2 I_2 - U_2 = 0 \quad (4)$$

l3

$$\begin{bmatrix} 1 & 0 & 1 & 0 & 0 \\ -1 & 1 & 0 & 0 & 0 \\ R_1 & 0 & 0 & -1 & 1 \\ 0 & R_2 & 0 & 0 & -1 \\ 0 & 0 & 0 & 1 & 0 \end{bmatrix} \cdot \begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ U_1 \\ U_2 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \\ V_s \end{bmatrix}$$



$$I_1 = \frac{V_s}{R_1 + R_2} \quad , \quad I_2 = \frac{V_s}{R_1 + R_2} \quad , \quad I_3 = -\frac{V_s}{R_1 + R_2}$$

$$U_1 = V_s \quad , \quad \boxed{U_2 = \frac{R_2}{R_1 + R_2} \cdot V_s = R_2 \cdot \frac{V_s}{R_1 + R_2}}$$

$\underbrace{\frac{R_2}{R_1 + R_2}}_{\alpha < 1} \quad \underbrace{\frac{V_s}{R_1 + R_2}}_{I_2}$

voltage divider

Resistive touchscreen

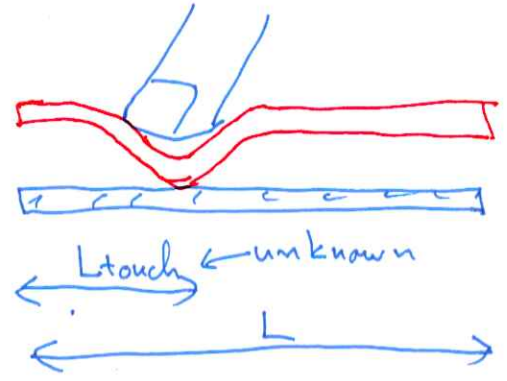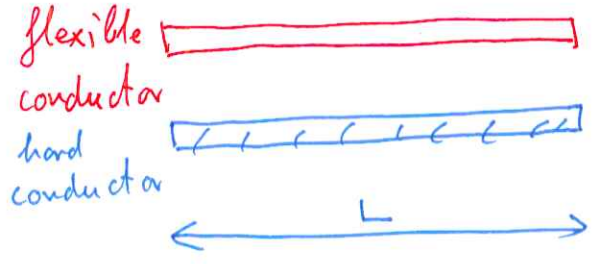

Want to measure $\frac{L_{touch}}{L}$

Need to convert to electrical quantity.

16A Physics

* Charge - can be either positive or negative
basic element of electrical flow (e.g. electron)

Unit: Coulomb [C]

* current - Net amount of charge that passes through some cross-section area over some period of time

$$[A] \rightarrow I = \frac{dQ \leftarrow [C]}{dt \leftarrow [s]}$$

Always do unit checks

* Voltage - Represents the energy to move a positive unit of charge from one point to the other



$$[V] = \frac{[J] \leftarrow \text{energy}}{[C]}$$

25

* Resistance - real pieces of metal always require a certain amount of energy to allow charge to flow through


$$V = I \cdot (R)$$

$$[V] = [A] \cdot [\Omega]$$



$$R = \rho \cdot \frac{L}{A}$$

Physical:

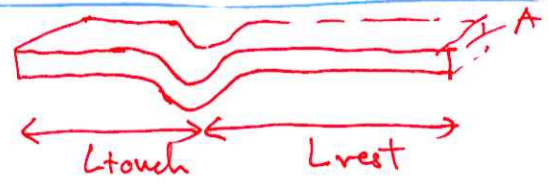

$$R_1 = \rho \cdot \frac{L_{rest}}{A} \quad (1)$$


Model:



$$R_2 = \rho \cdot \frac{L_{touch}}{A} \quad (2)$$

Build a circuit using this model to

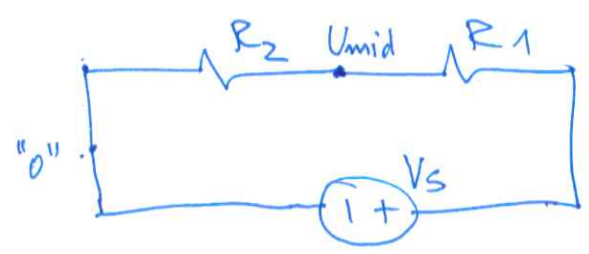measure $\frac{L_{touch}}{L}$ as an electrical quantity.



$$V_{mid} = \frac{R_2}{R_2 + R_1} \cdot V_s \quad (\text{voltage divider})$$

$$= \frac{\rho \cdot \frac{L_{touch}}{A}}{\rho \cdot \frac{L_{touch}}{A} + \rho \cdot \frac{L_{rest}}{A}} \cdot V_s$$


$$= \frac{L_{touch}}{L_{touch} + L_{rest}} \cdot V_s = \frac{L_{touch}}{L} \cdot V_s$$

$$V_{mid} = \frac{L_{touch}}{L} \cdot V_s$$




can always measure $\frac{L_{touch}}{L}$ regardless of the material type

l6

A more realistic model :

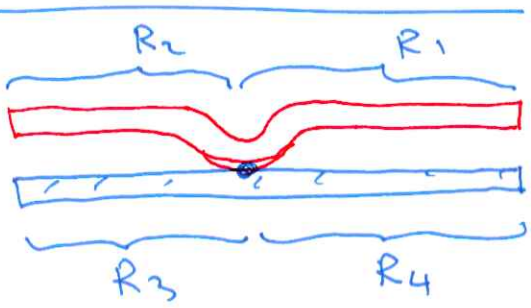

R_1, R_2, R_3 & R_4 are unknown

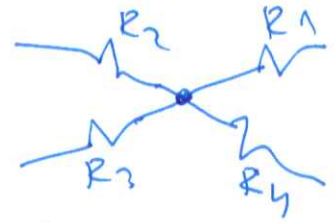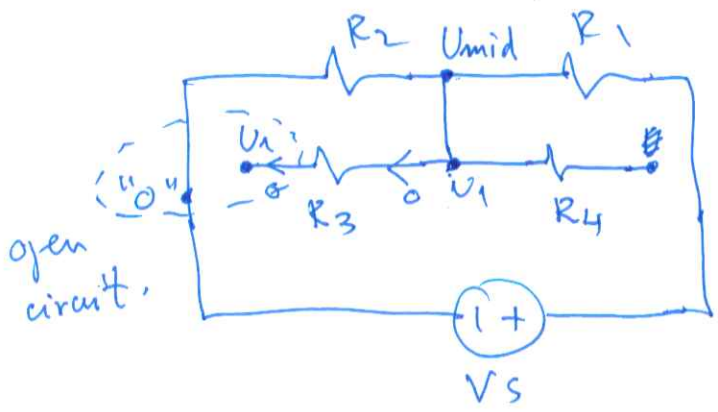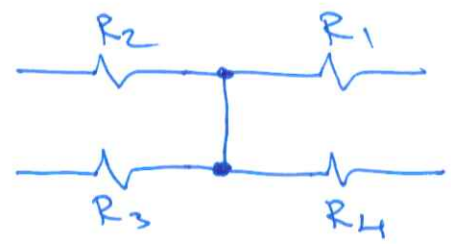

$U_1 = U_{mid}$