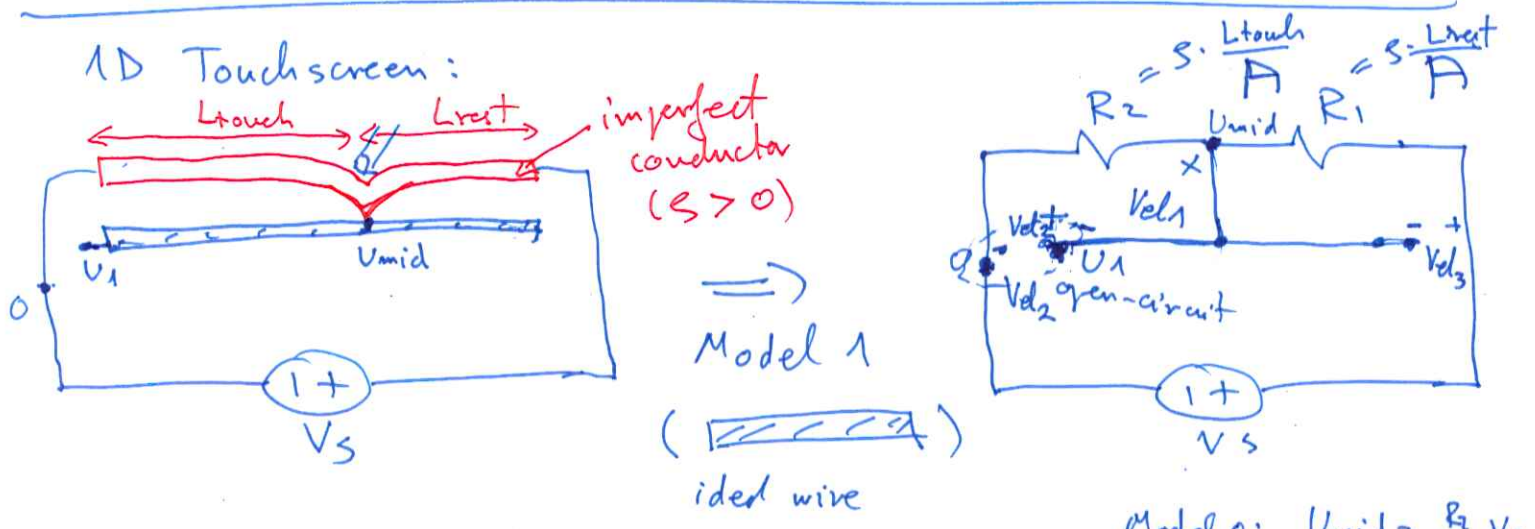


Lecture 3 - Module 2

Today:

- * Revisit 1D Touchscreen
- * Measuring voltage & current
- * Power
- * An interesting circuit

Note 13
and part
of
Note 14




Model 1: added (with respect to Model 0)

el 1: wire

el 2: open-circuit (V_{el2})



el 3: open-circuit (V_{el3})

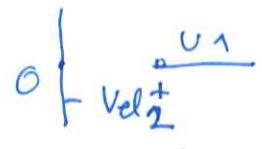

el 2: $V_1 - 0 = V_{el2}$ (definition of elem. voltage)

el 1: $U_{mid} - V_1 = V_{el1}$ (definition of elem. voltage)

KVL: $U_{mid} - 0 = V_{el2} + V_{el1}$

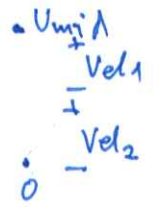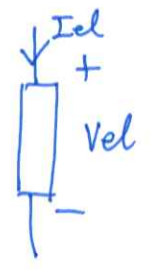

(2)

$V_1 = V_{el2}$

$V_{mid} - V_1 + V_1 - 0 = V_{el1} + V_{el2}$

$V_{mid} - V_1 = V_{el1}$

$V_{mid} = V_{el1} + V_{el2}$

def of the element voltage : $V_{el1} = 0$

$V_{mid} = V_{el2} + 0 = V_{el2} = V_1$


what I wanted : by measuring V_{el2} we get V_{mid} for any L_{touch} .

Model 2:

imperfect



conductor (resistor)

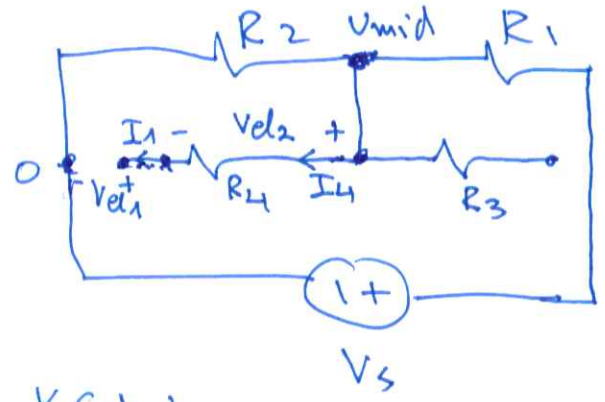

el1: open-circuit

el2: resistor

$V_{el2} = R_4 \cdot I_4$
(Ohm's Law)

KCL: $I_1 = I_4$

d1 def: $I_1 = 0$

\Downarrow
 $I_4 = 0$


KVL: $V_{mid} - 0 = V_{el1} + V_{el2}$

$V_{mid} = V_{el1} + R_4 \cdot I_4 \overset{0}{\rightarrow}$

$V_{mid} = V_{el1}$

Measure V_{mid} at V_{el1} regardless of the backplane conductor material and value of L_{touch} .

23

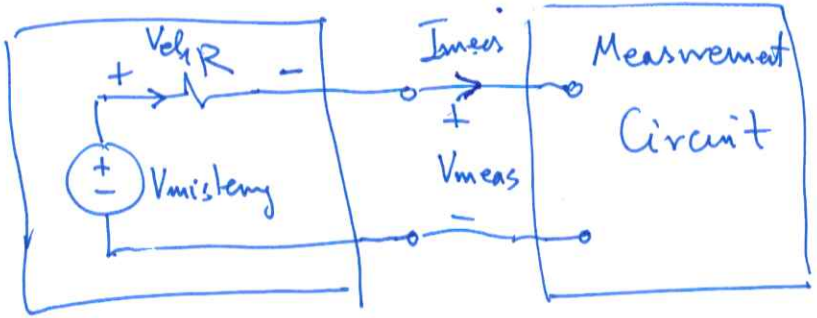

Goal : $V_{meas} = V_{mystery}$

$$V_R = I_{meas} \cdot R$$

KVL:
$$V_{mystery} = V_{meas} + V_R = V_{meas} + I_{meas} \cdot R$$

$$V_{mystery} = V_{meas} \quad |$$

$$I_{meas} = 0$$

Measurement should not change the energy of the circuit (cause energy dissipation)

Defined a voltage between points A and B


as :
$$V_{AB} = \frac{dE}{dq}$$
 dE energy required to to move dq from B to A.

Power (rate of energy change) :

$$P = \frac{dE}{dt} = \underbrace{\frac{dE}{dq}}_V \cdot \underbrace{\frac{dq}{dt}}_I = V \cdot I$$

(24)

passive - sign convention :

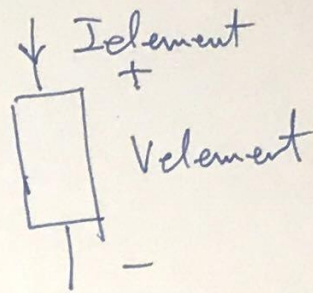


$$P_{element} = V_{element} \cdot I_{element}$$

$$= \left(\underbrace{R \cdot I_{element}}_{\substack{\text{if element } V \\ \text{is } R}} \right) \cdot I_{element} = R \cdot I_{element}^2 \geq 0$$

$$(V_{element} = R \cdot I_{element})$$

$$\frac{V_{element}}{R} = I_{element}$$
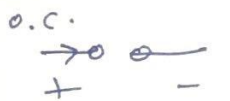
$$= V_{element} \cdot \frac{V_{element}}{R} = \frac{V_{element}^2}{R} \geq 0$$



$$P_{element} = V_{element} \cdot I_{element}^{\circ} = 0$$




$$P_{element} = V_{element}^{\circ} \cdot I_{element} = 0$$

Units: Power [W] [W] = [V] · [A]

(15)

Example:

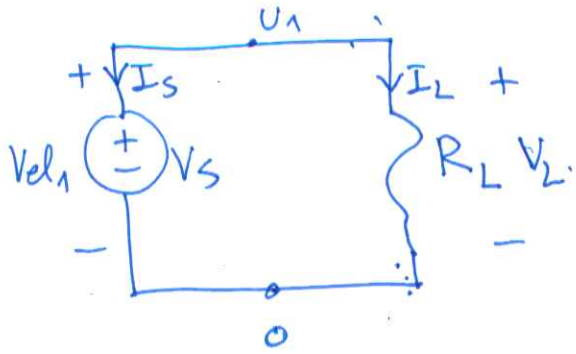

$$I_L = -I_S \Leftrightarrow I_L + I_S = 0 \quad (\text{KCL})$$

$$V_1 - 0 = V_L = V_{sl1} \quad (\text{KVL})$$

$$V_{sl1} = V_S \quad (\text{elem. def})$$

$$P_L = I_L \cdot V_L \quad (\text{def})$$

$$P_L = (-I_S) \cdot V_L$$

$$= (-I_S) \cdot V_{sl1}$$

$$= (-I_S) \cdot V_S$$


$$P_S = I_S \cdot V_{sl1} \quad (\text{def})$$

$$= I_S \cdot V_S \leq 0$$

$$P_L + P_S = 0$$

$$P_L = -P_S$$

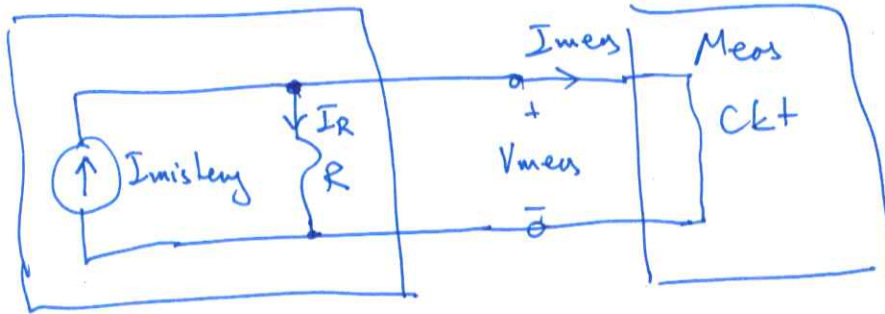Conservation of energy (power) $P_L \geq 0$ (since R_L is a resistor)



Task:
Measure I_{mistry}

$$(\text{KCL}) \quad I_{mistry} = I_R + I_{meas}$$

$$V_{meas} = I_R \cdot R$$

$$P_{meas} = V_{meas} \cdot I_{meas}$$

$$= 0$$

$$= I_{meas} \cdot \underbrace{I_R}_{= 0}$$

$$I_R = \frac{V_{meas}}{R}$$


$$V_{meas} = 0$$

(by def)

looks like if Meas ckt
looks like a wire.

Q6


An interesting circuit:

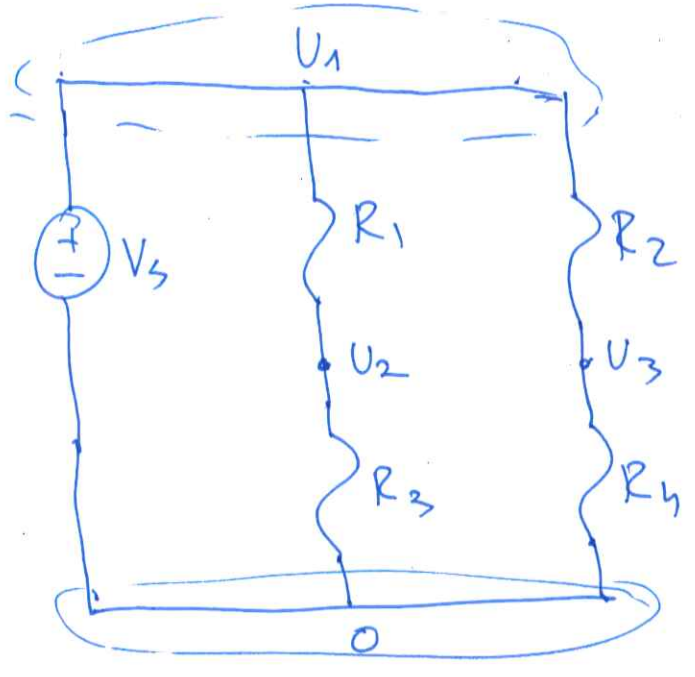

$$V_s = U_1 - 0$$

$$U_2 - 0 = \frac{R_3}{R_1 + R_3} \cdot (U_1 - 0) \quad V_s$$
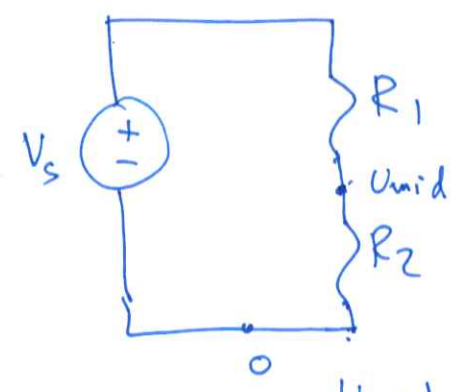
$$U_3 - 0 = \frac{R_4}{R_2 + R_4} \cdot (U_1 - 0) \quad V_s$$



voltage divider
$$U_{mid} = \frac{R_2}{R_1 + R_2} V_s$$

What are U_2 & U_3 ?

$$U_2 = \frac{R_3}{R_1 + R_3} V_s \quad U_3 = \frac{R_4}{R_2 + R_4} V_s$$