

(Q1)

Today: * Superposition } Circuit Jedi techniques
 Note 15 * Equivalence }

Goal: Want to design interesting systems
 - Need the tools that provide insight

Reminder: Circuit analysis objective:

Find $\vec{x} = \begin{bmatrix} I_1 \\ \vdots \\ I_m \\ V_1 \\ \vdots \\ V_k \end{bmatrix}$ for some ckt matrix A and some stimulus vector $\vec{b} = \begin{bmatrix} I_{s1} \\ \vdots \\ I_{sl} \\ V_{s1} \\ \vdots \\ V_{s_{m+k-l}} \end{bmatrix}$ independent sources

$A\vec{x} = \vec{b} \Rightarrow \underbrace{\vec{x} = A^{-1} \cdot \vec{b}}_{\text{solution}}$





$\Rightarrow \begin{cases} I_i = \alpha_1 I_{s1} + \dots + \alpha_l I_{sl} + \dots + \alpha_{m+k} V_{s_{m+k-l}} \\ \text{and } V_j = \beta_1 I_{s1} + \dots + \beta_{m+k} V_{s_{m+k-l}} \end{cases}$

lin. combinations of sources

$I_i = \underbrace{I_{i,1}}_{\alpha_1 I_{s1}} + \dots + \underbrace{I_{i,l}}_{\alpha_l I_{sl}} + \dots + \underbrace{I_{i,m+k}}_{\alpha_{m+k} V_{s_{m+k-l}}}$

\Rightarrow can calculate I_i by calculating $I_{i,1} \dots I_{i,m+k}$ separately (i.e. by nulling the other sources).

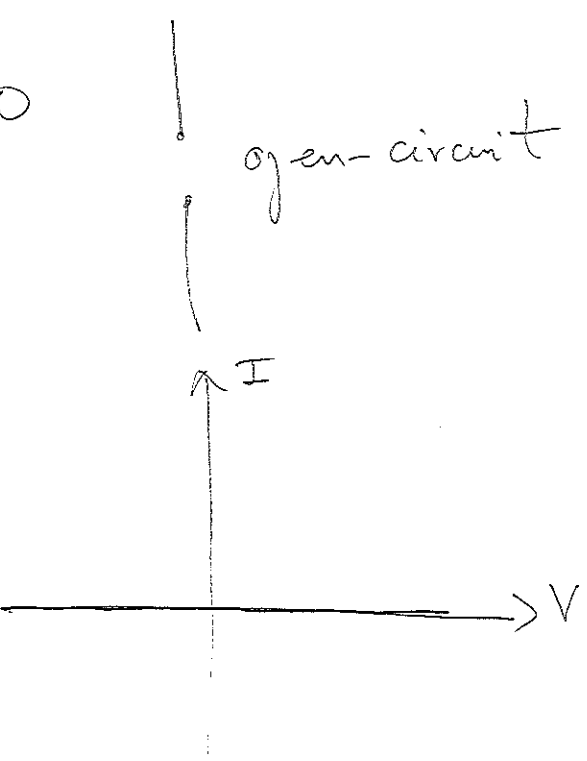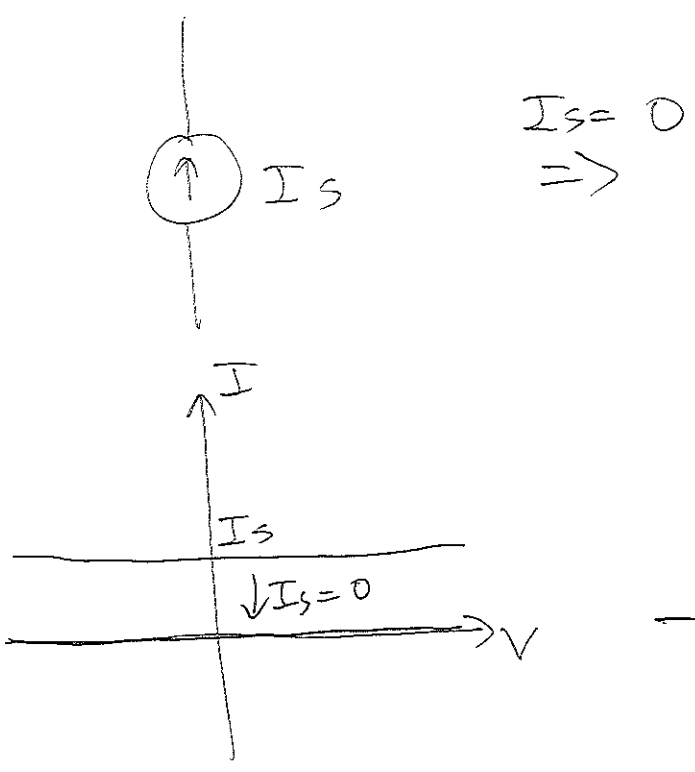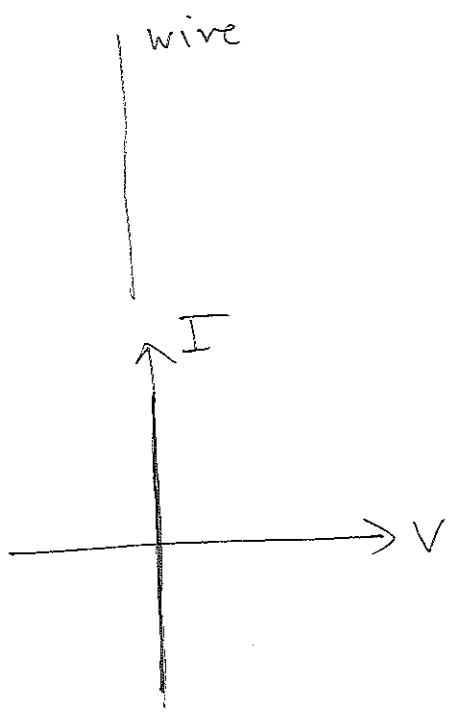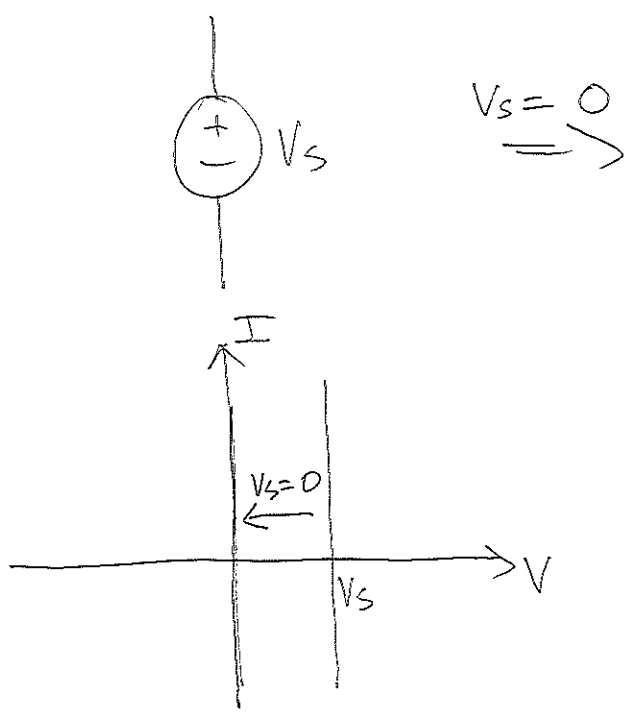
(b2) What does it really mean to "null" a source?



(3) Superposition: Find I's and V's by turning independent sources on one at a time and solving the circuit.

Example:


voltage summer

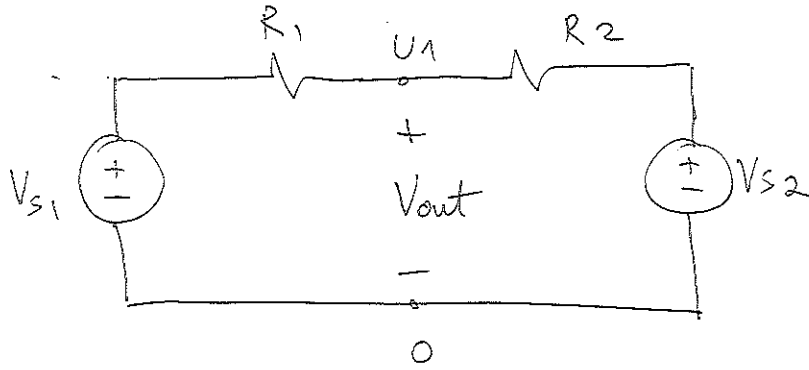

$$U_1 - 0 = V_{out}$$

$$U_1 = V_{out}$$

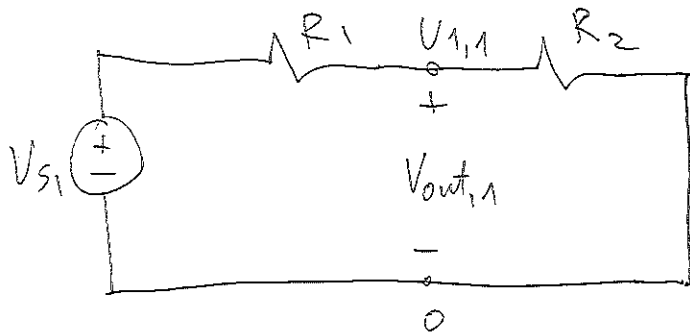
step 1: Compute a response to V_{s1} (set $V_{s2} = 0$)



voltage divider 😊

$$V_{out,1} = \frac{R_2}{R_1 + R_2} \cdot V_{s1}$$

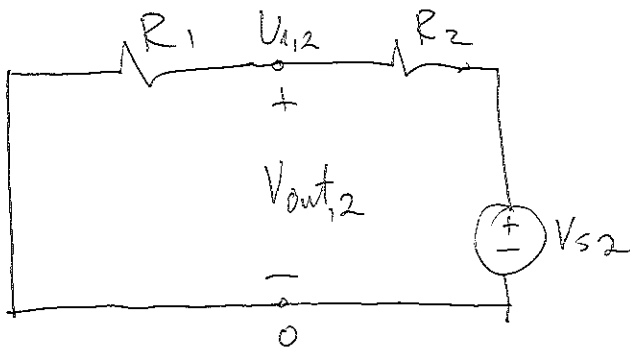step 2: Compute a response to V_{s2} (set $V_{s1} = 0$)



voltage divider 😊

$$V_{out,2} = \frac{R_1}{R_1 + R_2} \cdot V_{s2}$$


$$V_{out} = V_{out,1} + V_{out,2} = \frac{R_2}{R_1 + R_2} V_{s1} + \frac{R_1}{R_1 + R_2} V_{s2}$$

$\underbrace{\frac{R_2}{R_1 + R_2}}_{\alpha < 1} \quad \underbrace{\frac{R_1}{R_1 + R_2}}_{\beta < 1}$



$U_1 \quad U_{1,1} \quad U_{1,2}$

Q4

Equivalence:


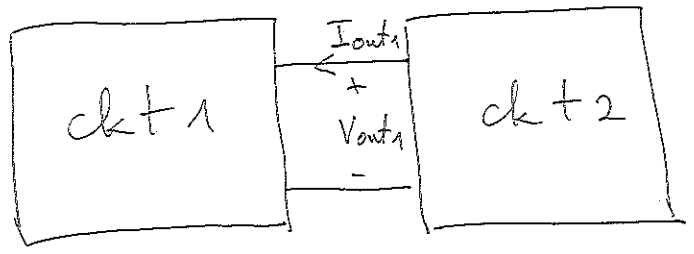


(1)

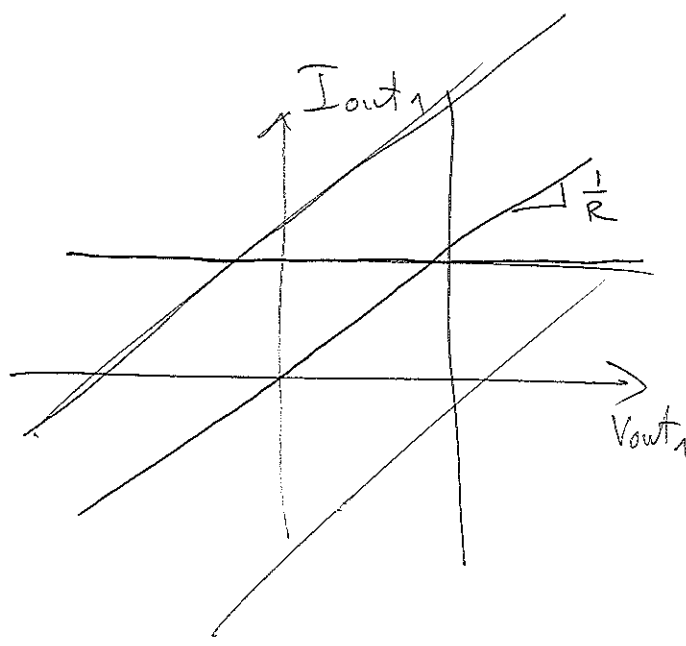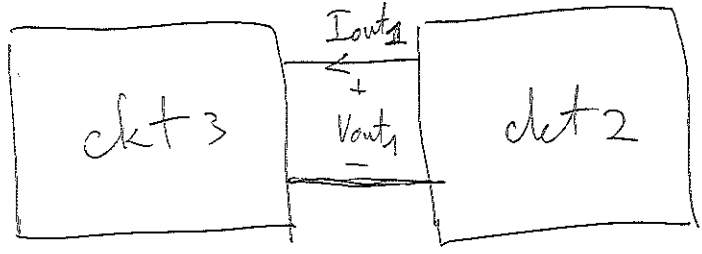

In circuits, two elements are equivalent if they have the same I-V characteristics.

Example:

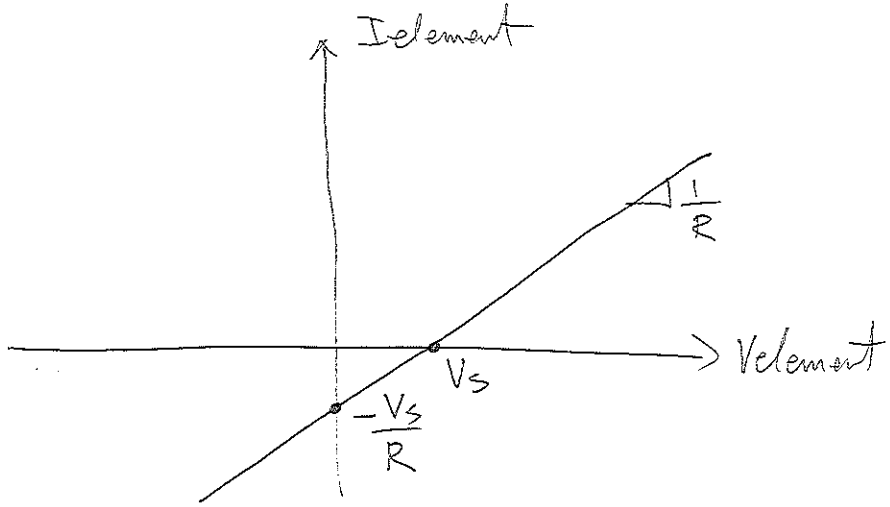
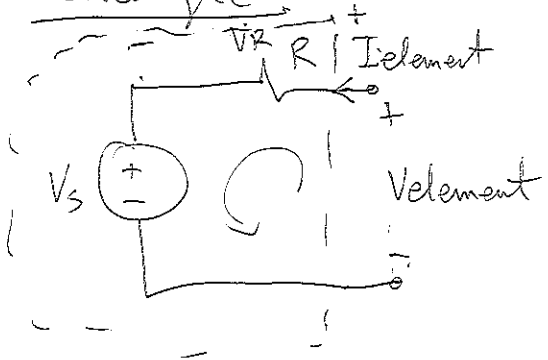


$$V_{element} = V_s + V_R$$



$$V_{element} = V_s + I_{element} \cdot R$$

$$I_{element} = \frac{1}{R} \cdot V_{element} - \frac{V_s}{R}$$

(25)

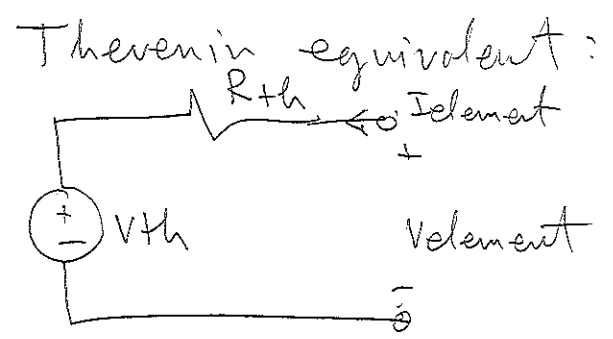
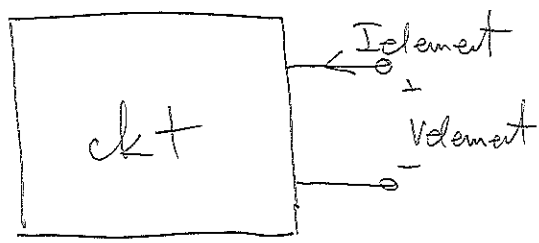


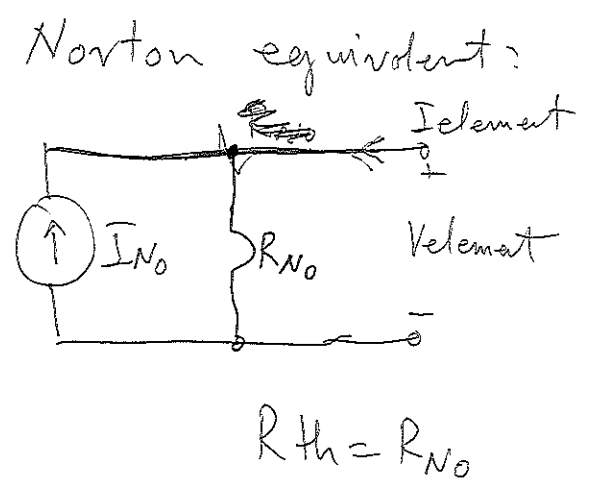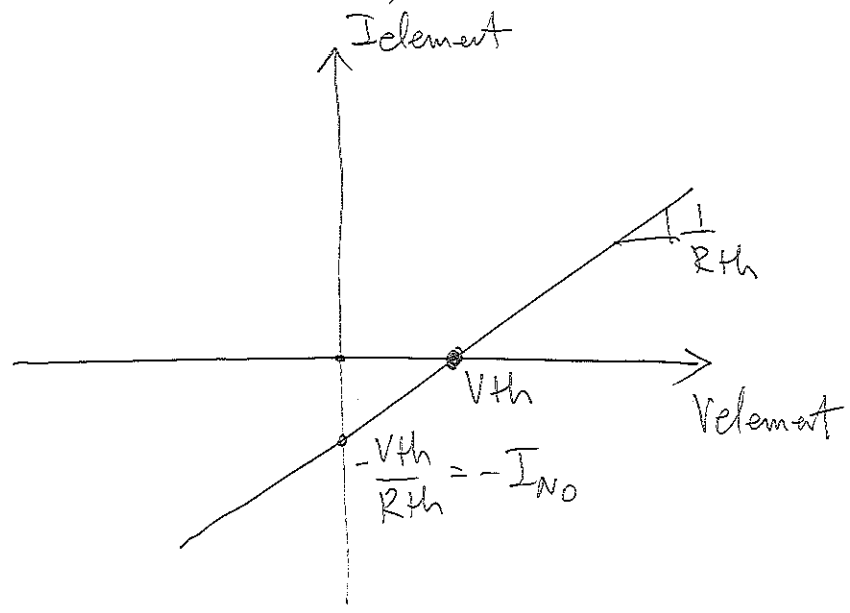Need a min. of two elements (a resistor and a source) to create any I-V line.





To find V_{th} : "Connect" an "open-circuit", across two terminals and measure $V_{open-circuit} = V_{th}$

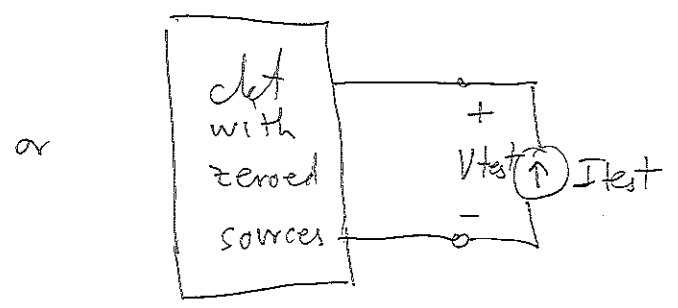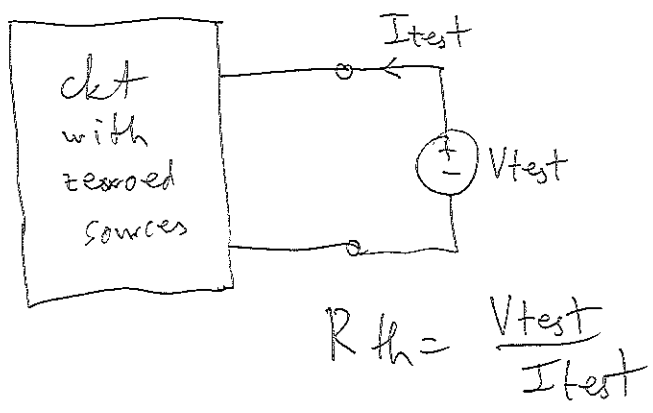To find R_{th} : zero-out independent sources (to find a slope)





(k6)



Dependent sources:

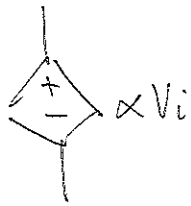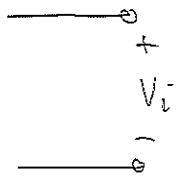



Voltage-controlled voltage source
(VCVS)

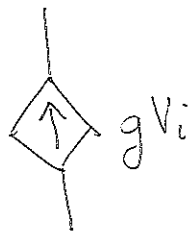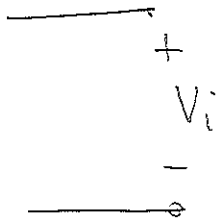

Voltage-controlled current source
(VCCS)

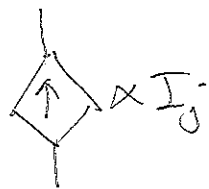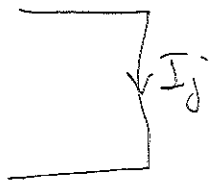



Current-controlled current source
(CCCS)

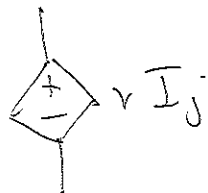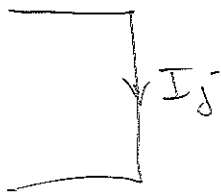


Current-controlled voltage source
(CCVS)

(27)

Example 1:

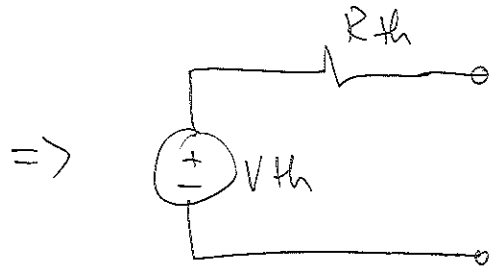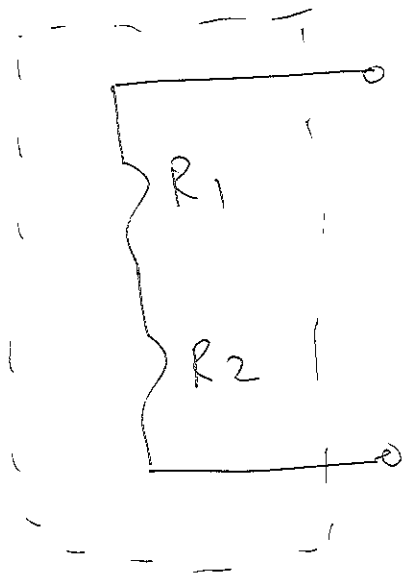


step 1:

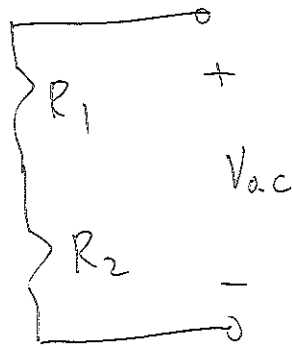

$$V_{ac} = 0 \Rightarrow V_{th} = 0$$

step 2: No sources & apply test current

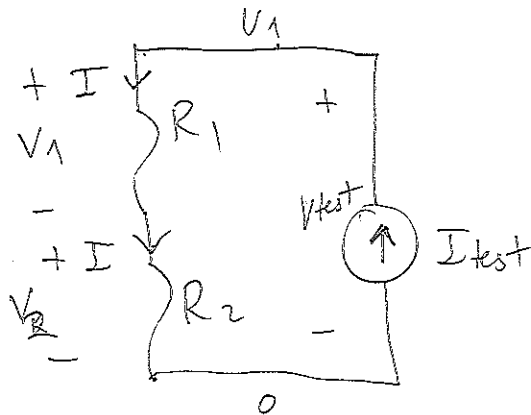

$$V_{test} = (R_1 + R_2) \cdot I_{test}$$

$$= I \cdot R_1 + I \cdot R_2$$


$$= I_{test} R_1 + I_{test} R_2$$

$$I = I_{test}$$

$$R_{th} = \frac{V_{test}}{I_{test}} = \boxed{R_1 + R_2}$$


"In series" means that the same current flows through the elements.

(8)

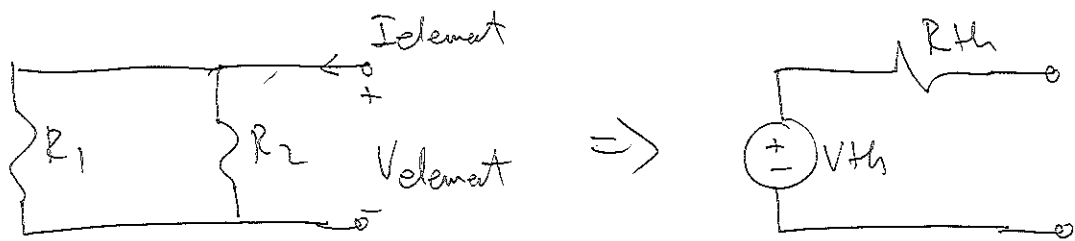

step 1: $V_{th} = 0$

step 2:

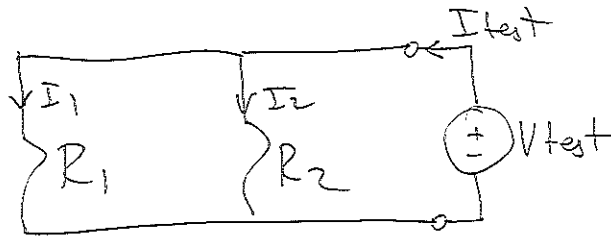


$$I_1 = \frac{V_{test}}{R_1}$$

$$I_2 = \frac{V_{test}}{R_2}$$

$$I_{test} = I_1 + I_2 = V_{test} \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$
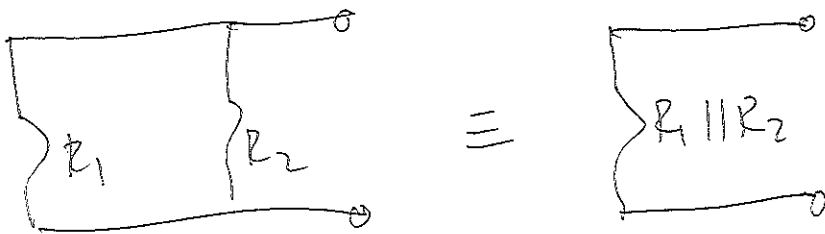
$$R_{th} = \frac{V_{test}}{I_{test}} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} = \frac{R_1 R_2}{R_1 + R_2} = R_1 \parallel R_2$$



parallel operator

"in parallel" means voltage across them is the same.