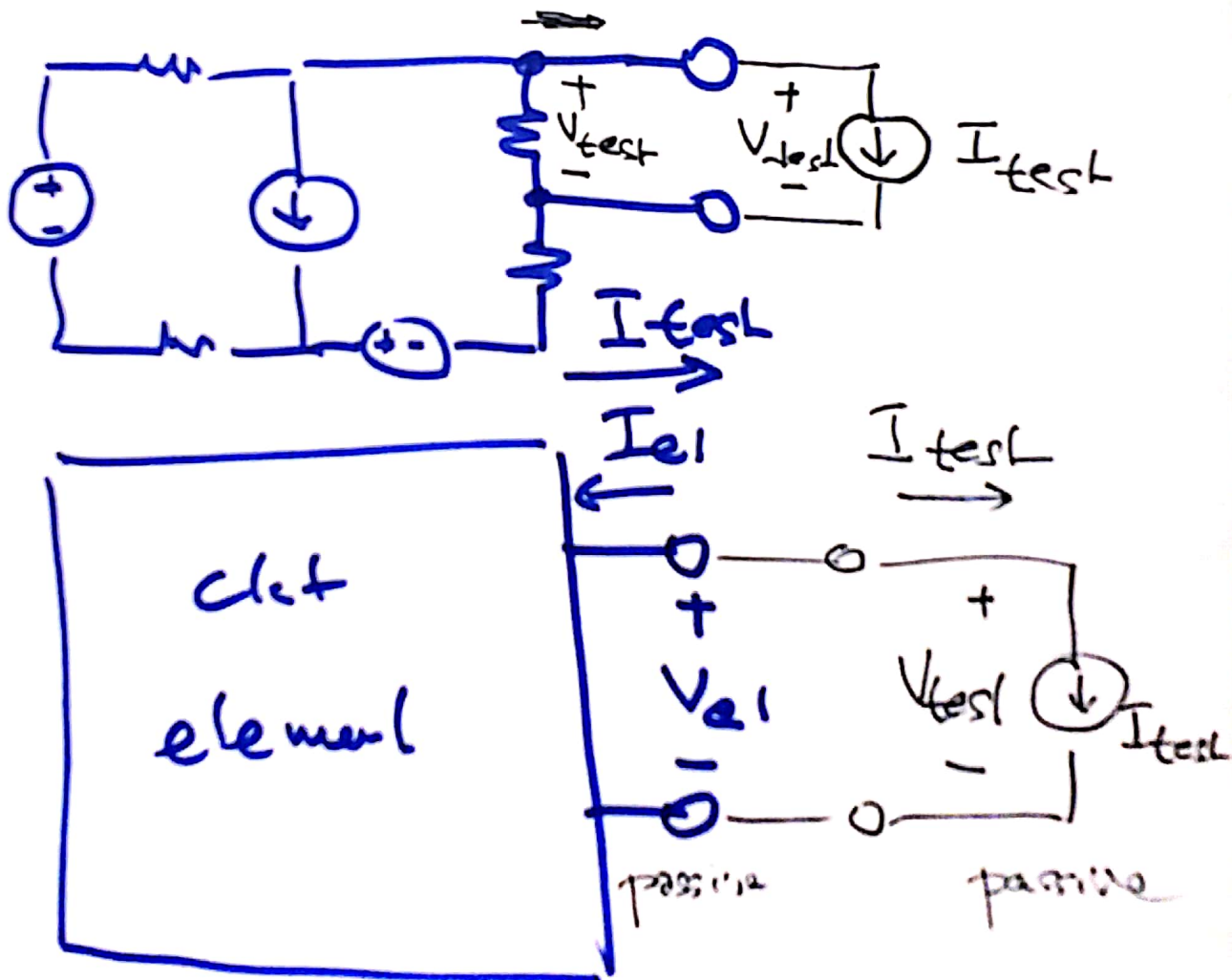



Lecture 5, Module 2

1)

- Thévenin & Norton Equivalents
- Capacitors






$$I_{el} = -I_{test}$$

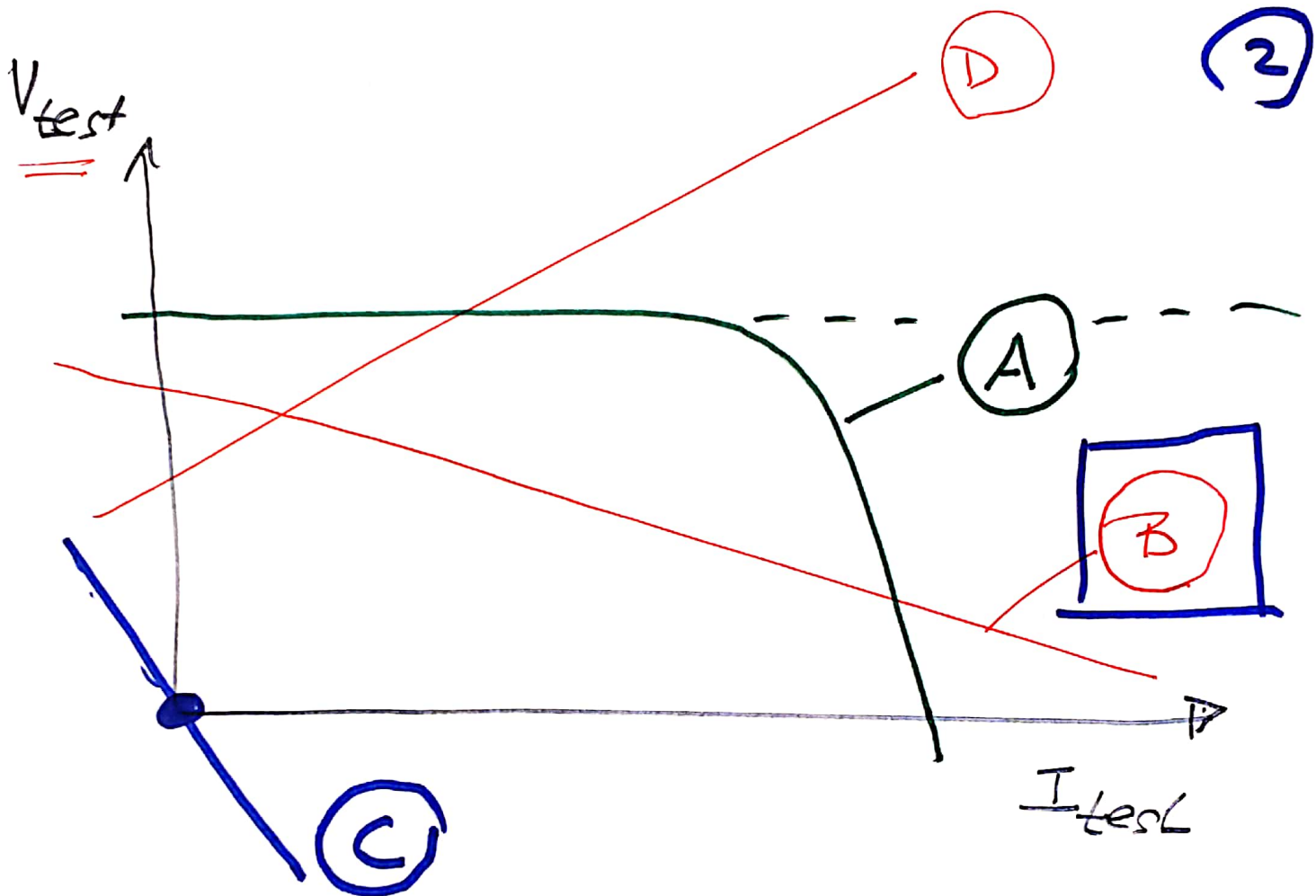


$$A^{-1} \mid A \cdot \vec{v}_n = \vec{b}$$


$$\vec{v}_n = A^{-1} \cdot \vec{b}$$

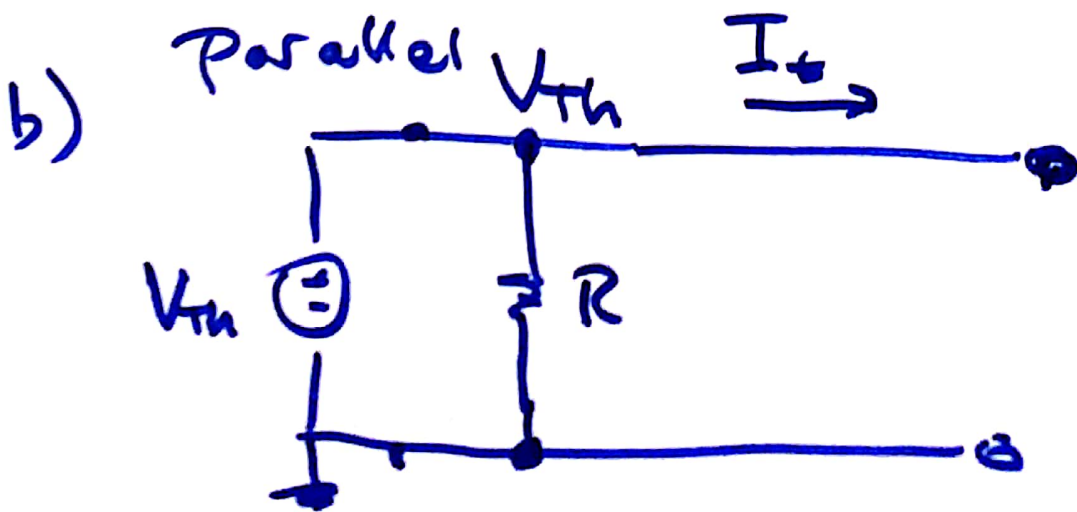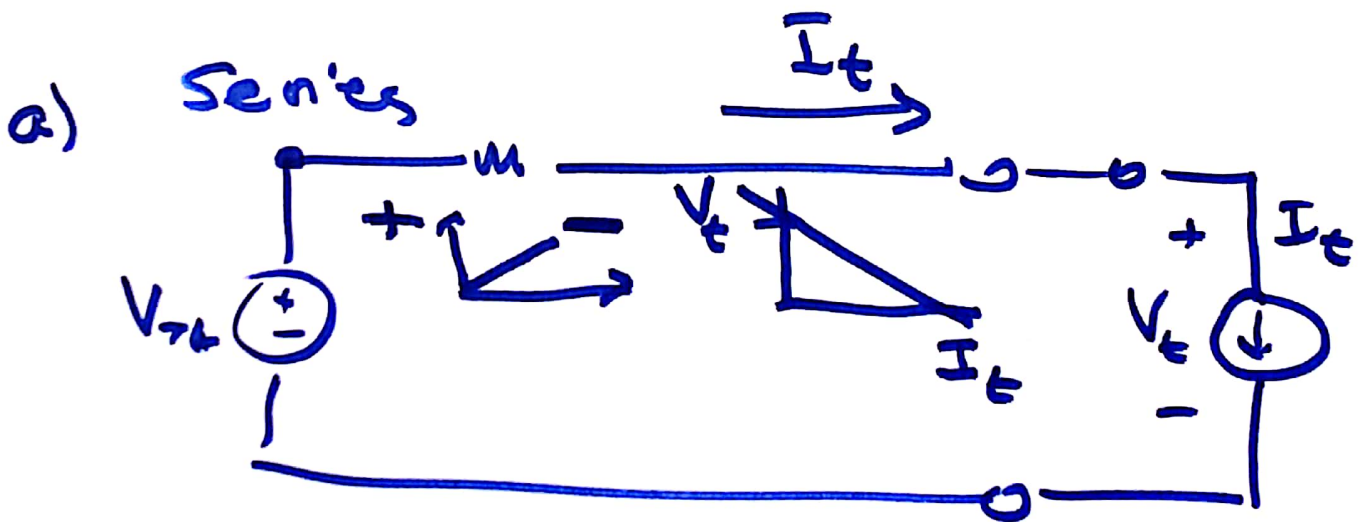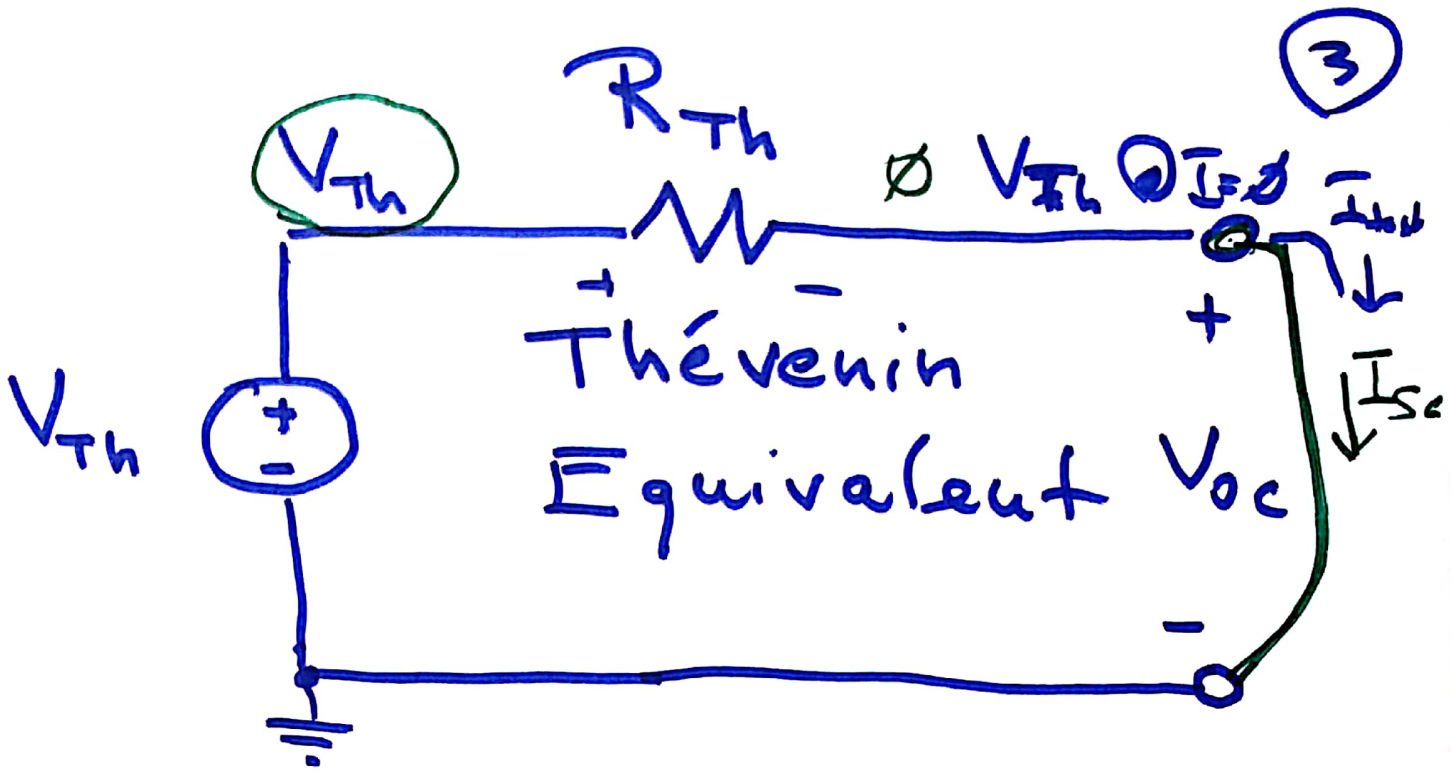

(4)

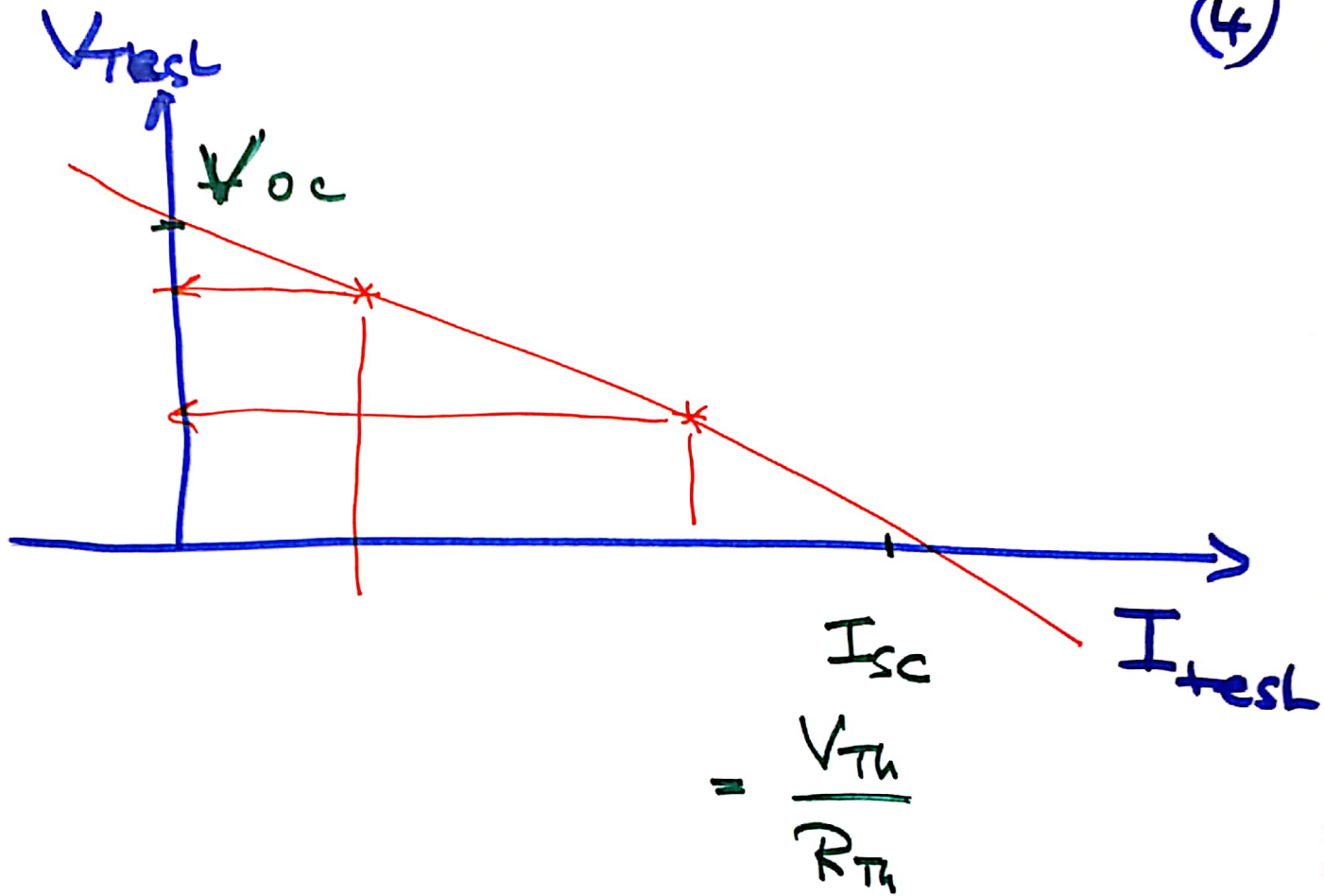



Example :

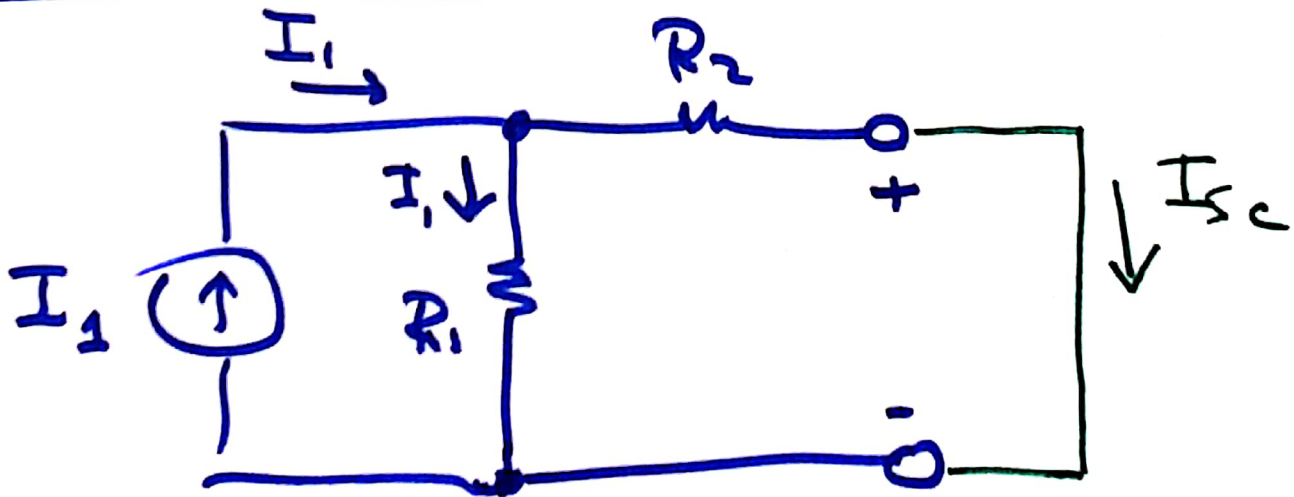

5


(a) $V_{oc} = R_1 \cdot I_1$

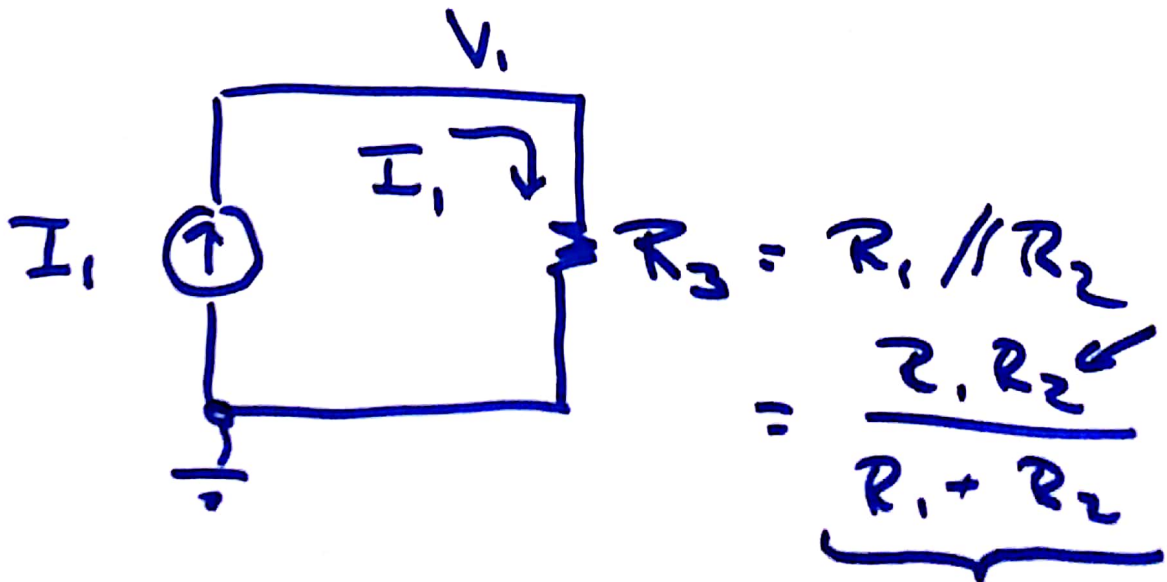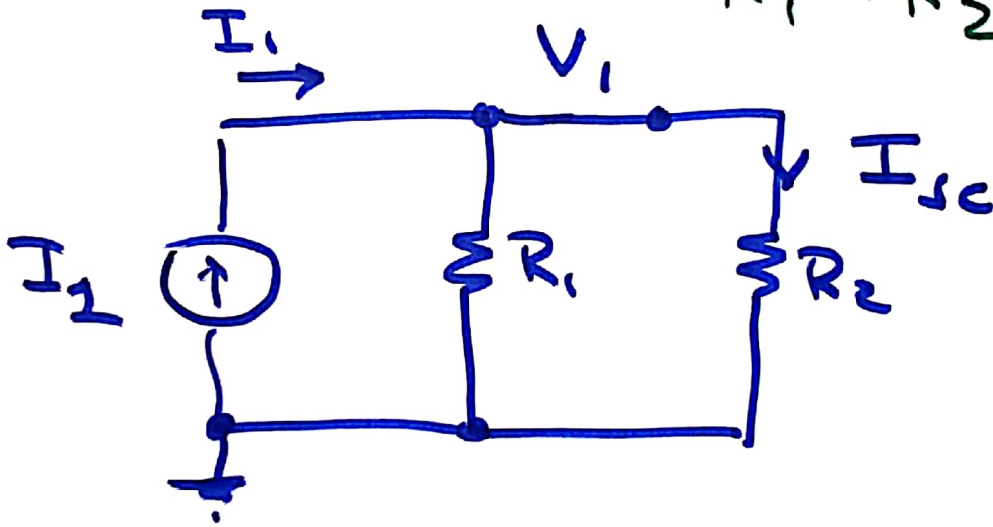(b) $I_{sc} = I_1 \cdot \frac{R_1}{R_1 + R_2}$




$V_1 = I_1 \cdot R_3$
 $I_{sc} = \frac{V_1}{R_2} = I_1 \cdot \frac{R_1}{R_1 + R_2}$

6

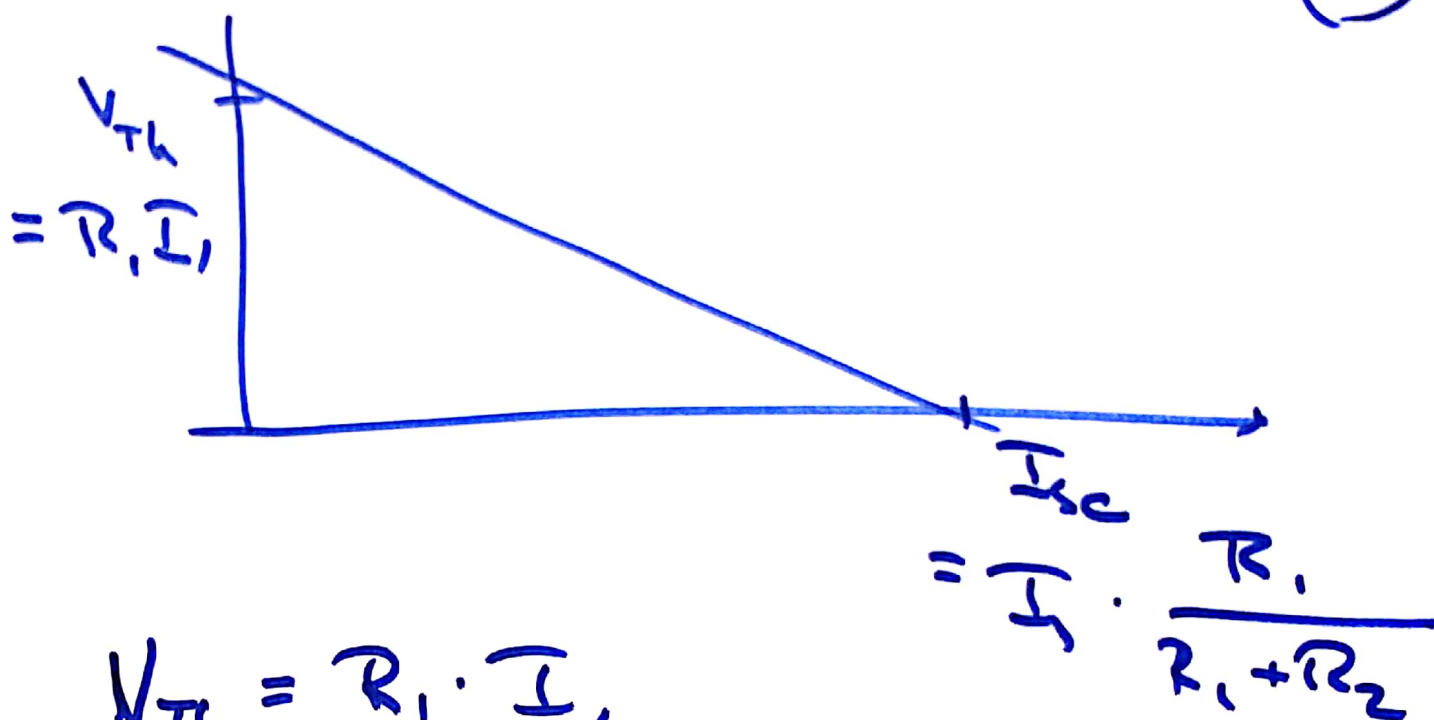


$$V_{TH} = R_1 \cdot I_1$$

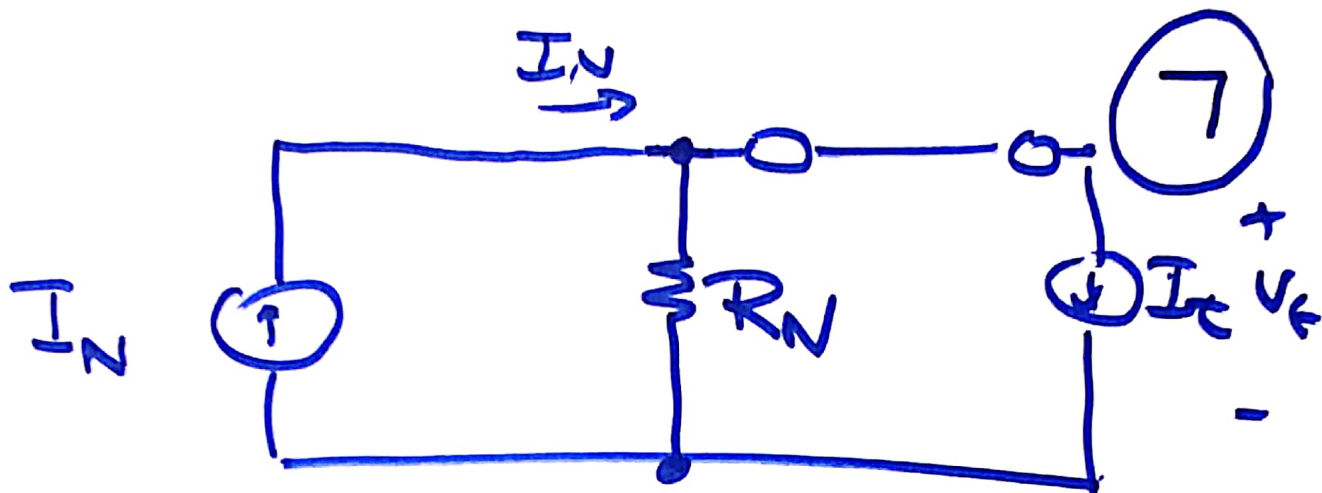
$$R_{TH} = \frac{V_{TH}}{I_{sc}} = \frac{R_1 \cdot I_1}{I_1 \cdot \frac{R_1}{R_1 + R_2}} = R_1 + R_2$$




Norton Equivalent

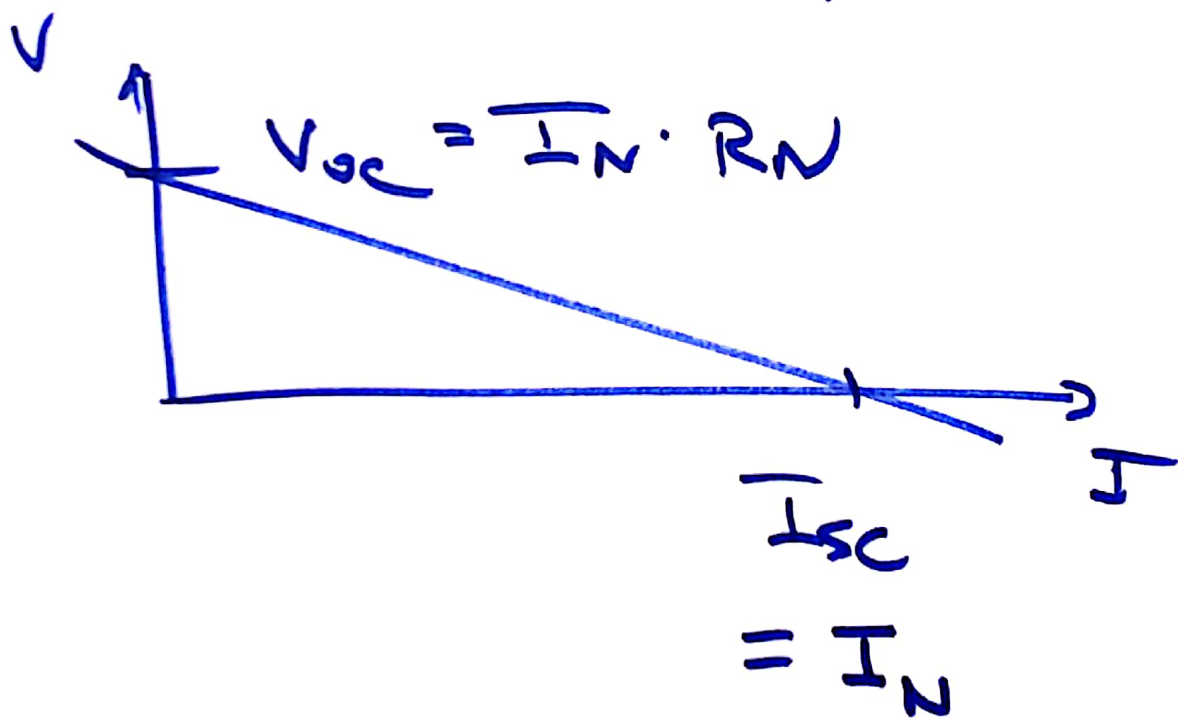

Thévenin

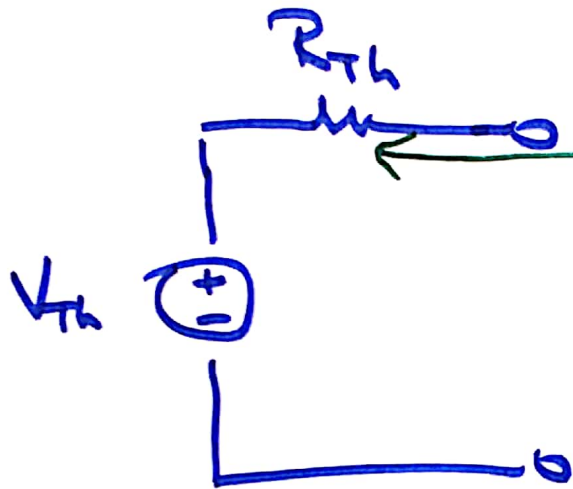

Norton

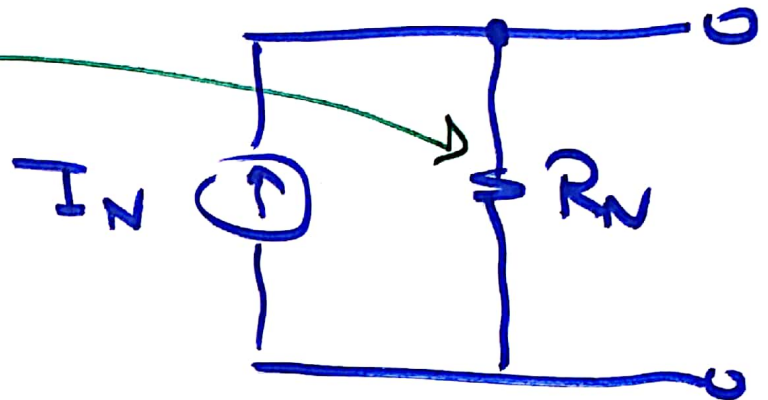

$$V_{oc} = V_{th}$$

=

$$V_{oc} = I_N \cdot R_N$$

$$I_{sc} = \frac{V_{th}}{R_{th}}$$

=

$$I_{sc} = I_N$$

$$V_{th} = I_N \cdot R_N$$

$$R_N = \frac{V_{th}}{I_N} = R_{th}$$

$$\frac{V_{th}}{R_{th}} = I_N \quad \rightarrow \quad V_{th} = I_N \cdot R_{th}$$
$$V_{th} = I_N \cdot R_N$$

9

Ckt Analysis Techniques

- KVL, KCL
 - Ohm's Law
- } Basics

• NVA

~~NOE~~

} Procedure universes

- Equivalence
 - Resistors : series, //
 - Thévenin, Norton Equivalents
- Superposition
 - Analysis
 - Linear superposition