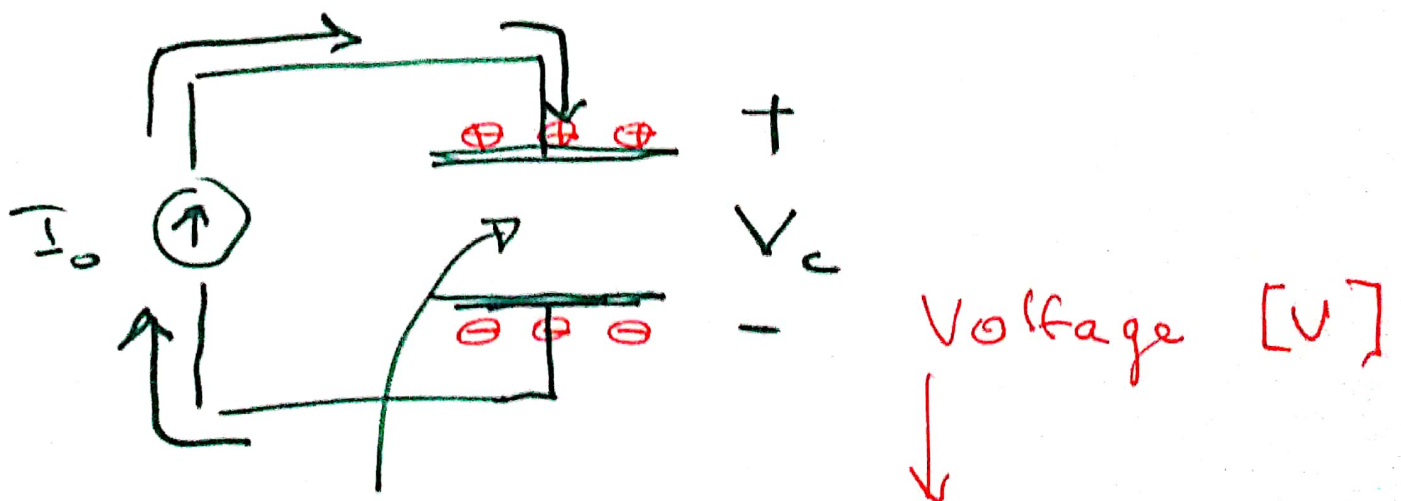


# EE 16 A, Lect 6, Mod 2 (1)

- Capacitance
  - Physics
  - Models (equations)
  - Circuits

## Virtual Experiment




$$Q_c = C \cdot V_c$$

Charge  
Coulomb [C]

Capacitance  
Farad [F]

②

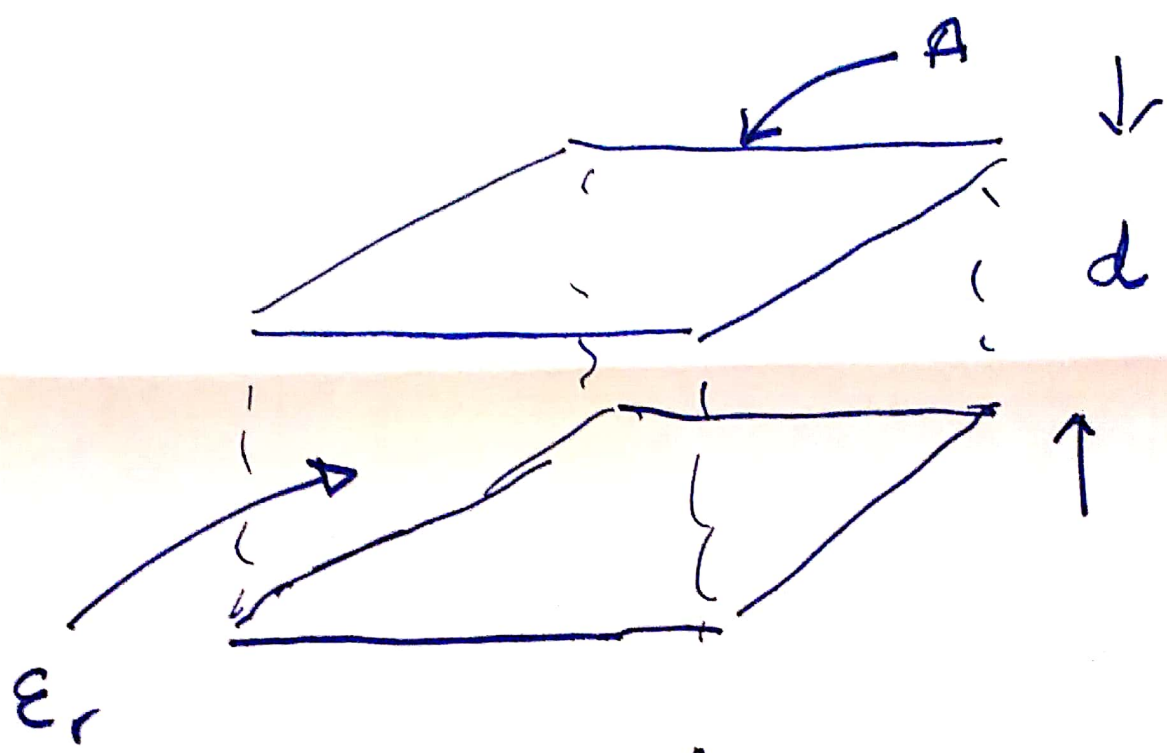

$$C = \epsilon \cdot \frac{A}{d}$$

↑  
permittivity

Material  
 ↓ (1) Vacuum, Air  
 $\epsilon_r = 1$   
 ↓ (2) Water  
 $\epsilon_r \approx 80$

$$\epsilon = \epsilon_0$$

↑↑

$$8.85 \cdot 10^{-12} \text{ F/m}$$

$$8.85 \text{ pF/m}$$

$$p = 10^{-12}$$

3


# I/V characteristics?

$$Q = C \cdot V$$

$$I = \frac{dQ}{dt} = C \cdot \frac{dV}{dt}$$

$$I(t) = C \cdot \frac{dV(t)}{dt}$$

Example 1:  $\vec{I}_C$

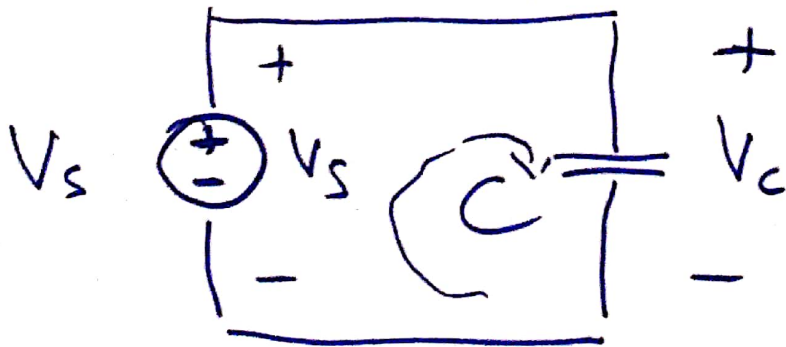

steady state  
 $\frac{dV}{dt} = \frac{dI}{dt} = \cancel{\emptyset}$


KVL :  $-(V_s) + V_c = \cancel{\emptyset}$

$$V_c = V_s = \text{const}$$

$$I_c = C \cdot \frac{dV_c}{dt} = \cancel{\emptyset}$$

(6)

Ex 2:

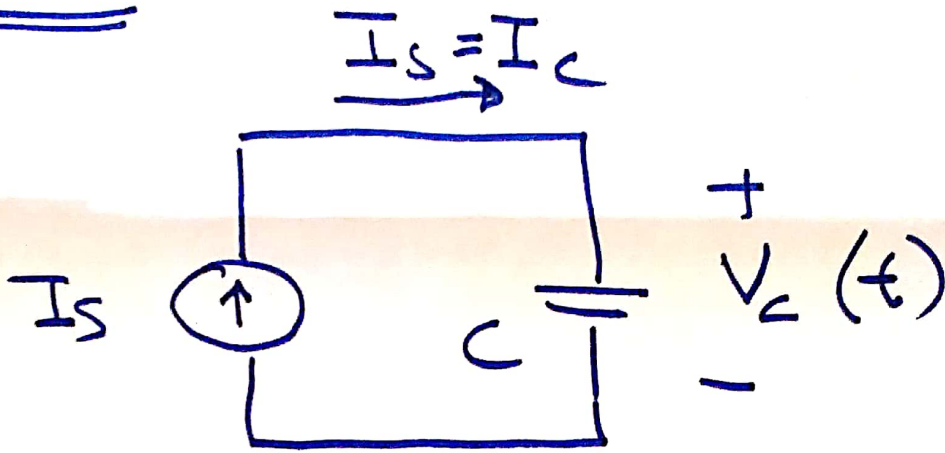


$$I_c = I_s = C \cdot \frac{dV_c(t)}{dt}$$

$$\therefore \frac{dV_c(t)}{dt} = \frac{I_c}{C}$$

$$\int_0^T dV_c(t) = \int_0^T \frac{I_c}{C} \cdot dt$$


$$V_c(t) = \frac{I_c}{C} \int_0^t dt$$

$$= \frac{I_c}{C} \cdot T + V_c(t=0)$$

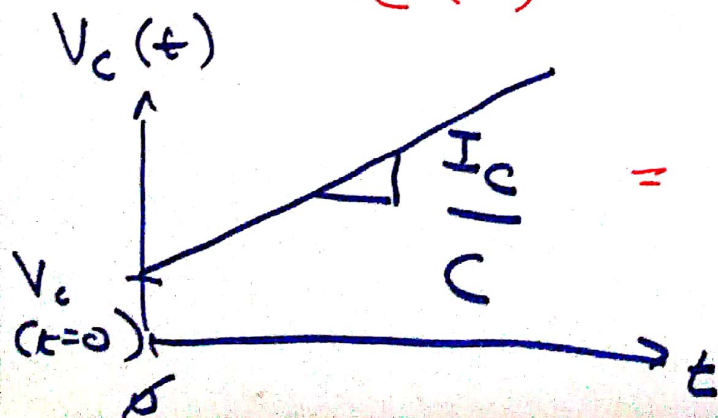


(5)

App: Memory

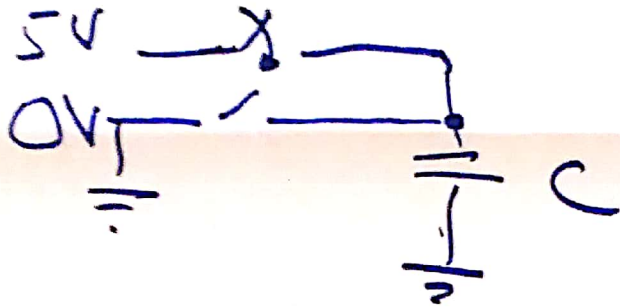


## Equivalent Capacitance

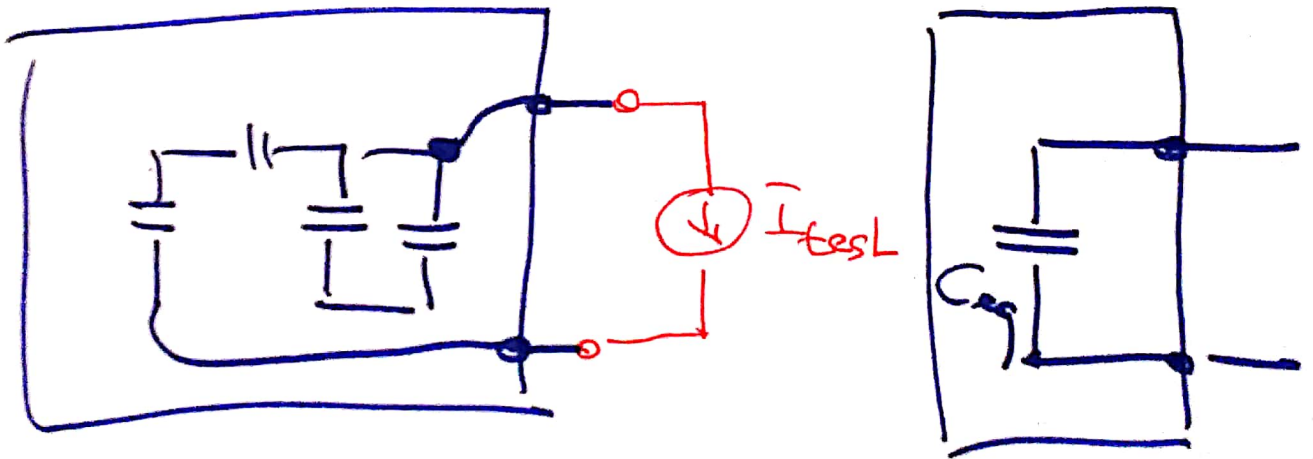

$$\frac{dV_{test}}{dt} = 0 \Rightarrow I = 0$$

Ex:

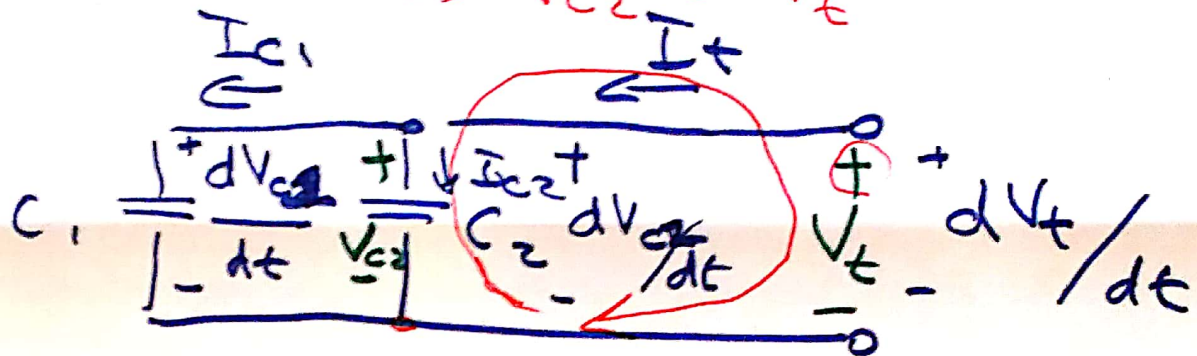KVL  $-V_{C2} + V_t = 0$  (6)  
 $\Rightarrow V_{C2} = V_t$





$$I_{C1} = C_1 \cdot \frac{dV_{C1}}{dt} = C_1 \cdot \frac{dV_t}{dt}$$

$$I_{C2} = C_2 \cdot \frac{dV_t}{dt}$$


$$I_{C1} + I_{C2} = (C_1 + C_2) \cdot \frac{dV_t}{dt}$$
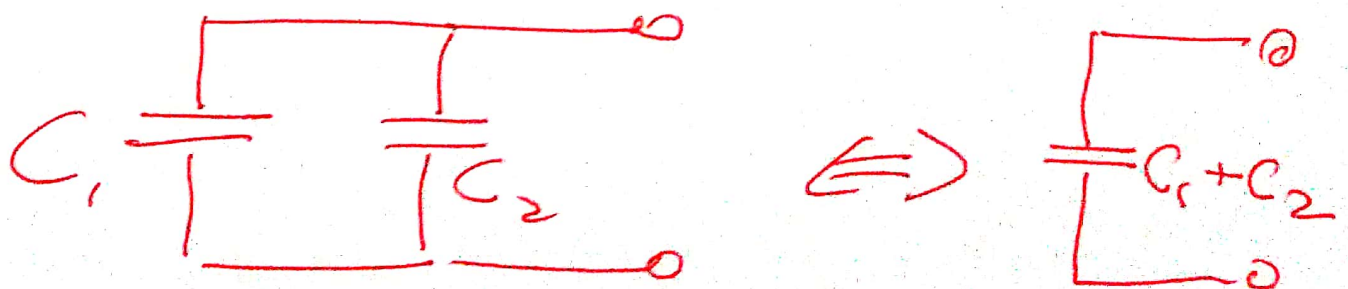
$$\boxed{C_{eq}} = \frac{I_{C1} + I_{C2}}{\frac{dV_t}{dt}} = \boxed{C_1 + C_2}$$




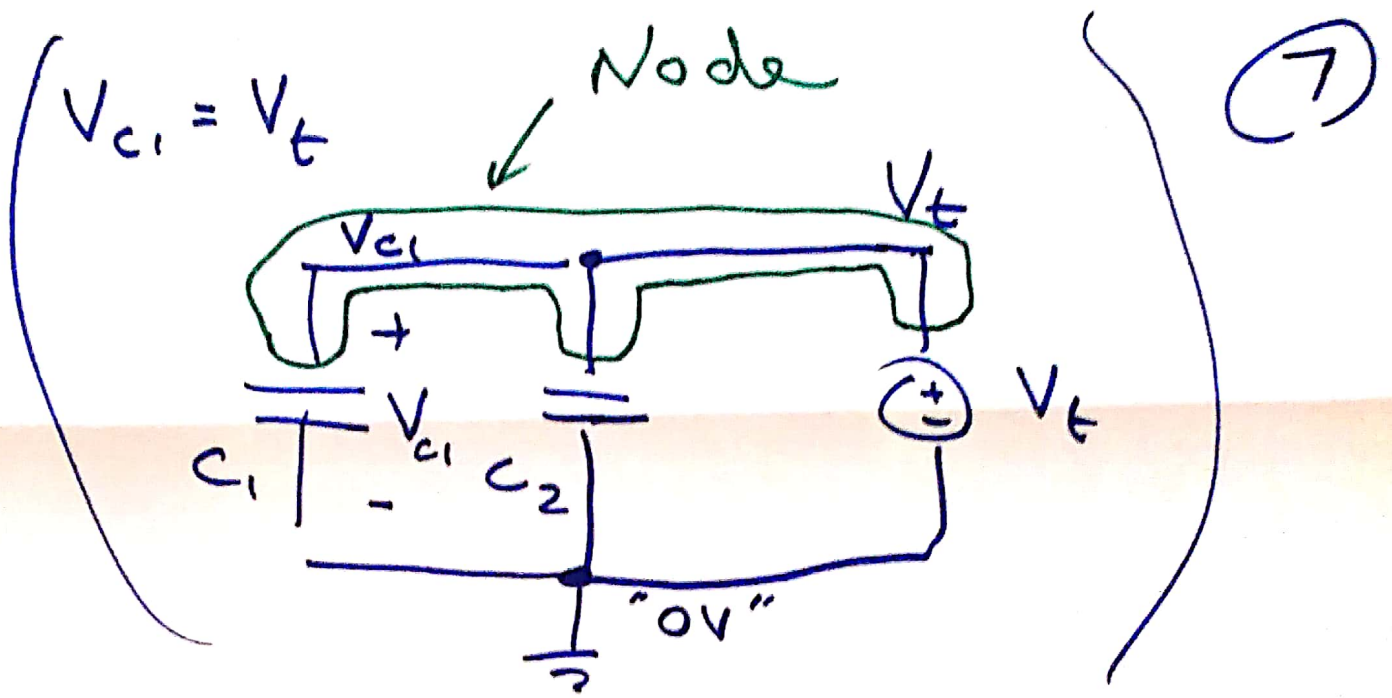

Series:

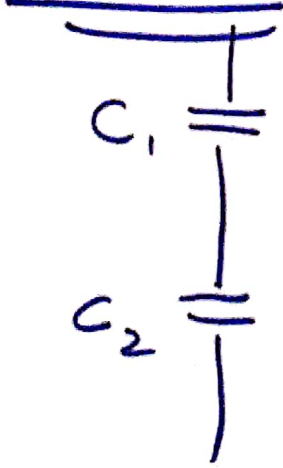

$\Leftrightarrow$

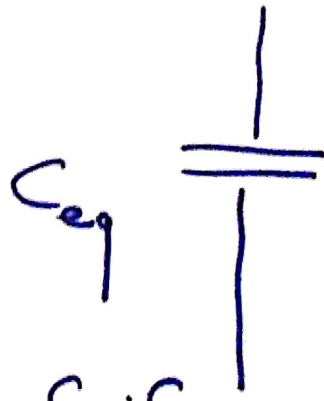


$$C_{eq} = \frac{C_1 \cdot C_2}{C_1 + C_2}$$


$$= C_1 // C_2$$

⑧


Ex:

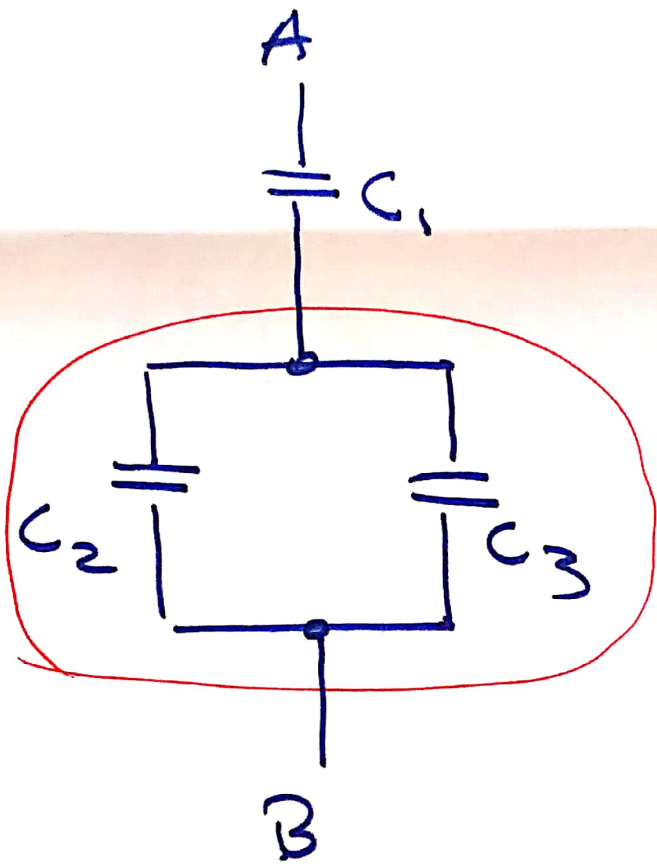

$\Leftrightarrow$

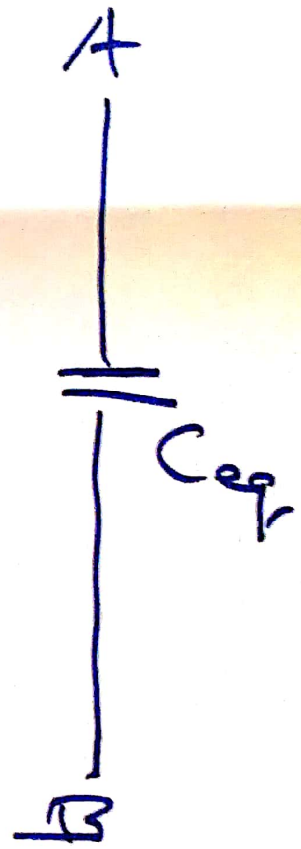


$$C_2 + C_3 = C_{23}$$

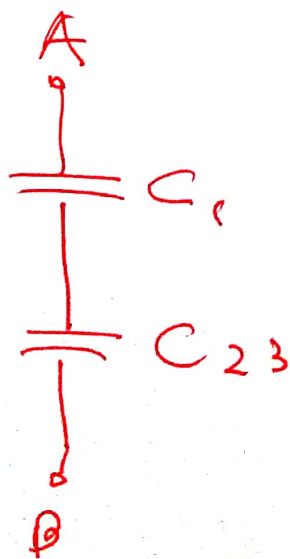

$$C_{eq} = C_1 \parallel (C_2 + C_3) \\ = \frac{C_1 (C_2 + C_3)}{C_1 + C_2 + C_3}$$



9

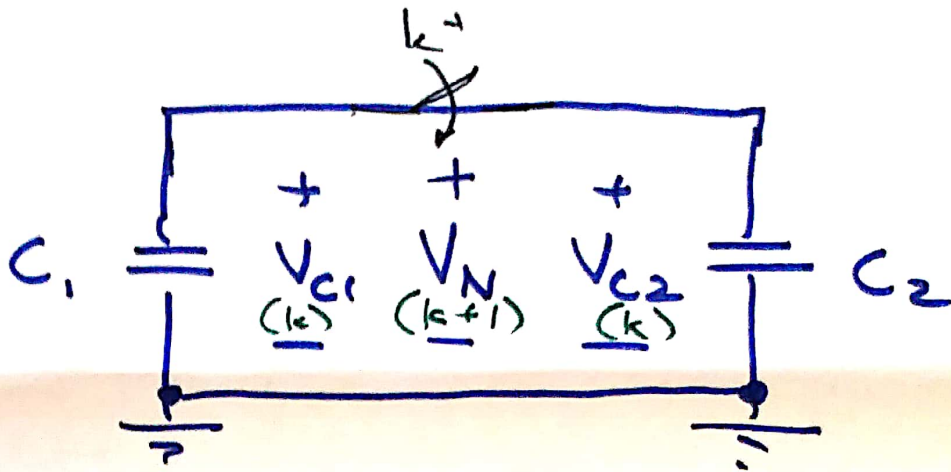

$$Q_1(k) = C_1 \cdot V_{C_1}(k)$$

$$Q_2(k) = C_2 \cdot V_{C_2}(k)$$

$$Q_+(k+1) = Q_1(k) + Q_2(k)$$

$$= C_1 \cdot V_{C_1}(k) + C_2 \cdot V_{C_2}(k)$$


$$= V_N(k+1) \cdot (C_1 + C_2)$$

$$\begin{aligned} & \parallel \\ & V_{C_1}(k+1) = V_{C_2}(k+1) \end{aligned}$$


$$\parallel \therefore V_N(k+1) = \frac{C_1 \cdot V_{C_1}(k) + C_2 \cdot V_{C_2}(k)}{C_1 + C_2} \parallel$$

10


phase 1

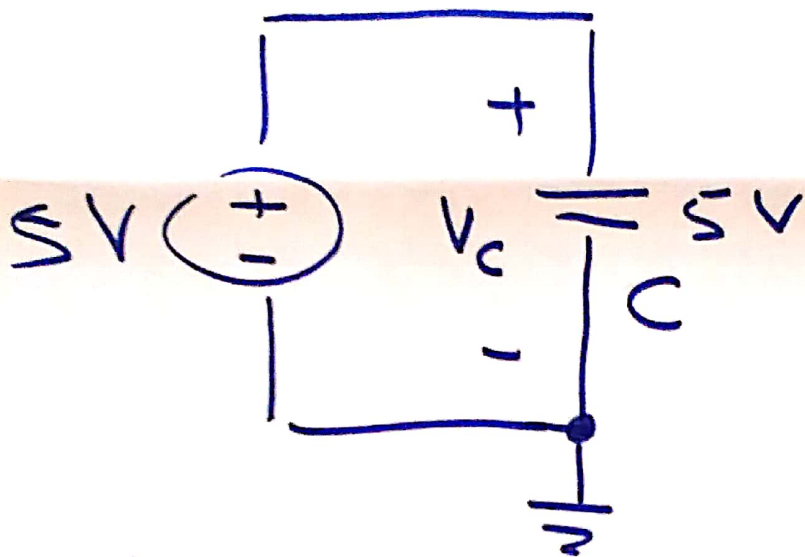

phase 2

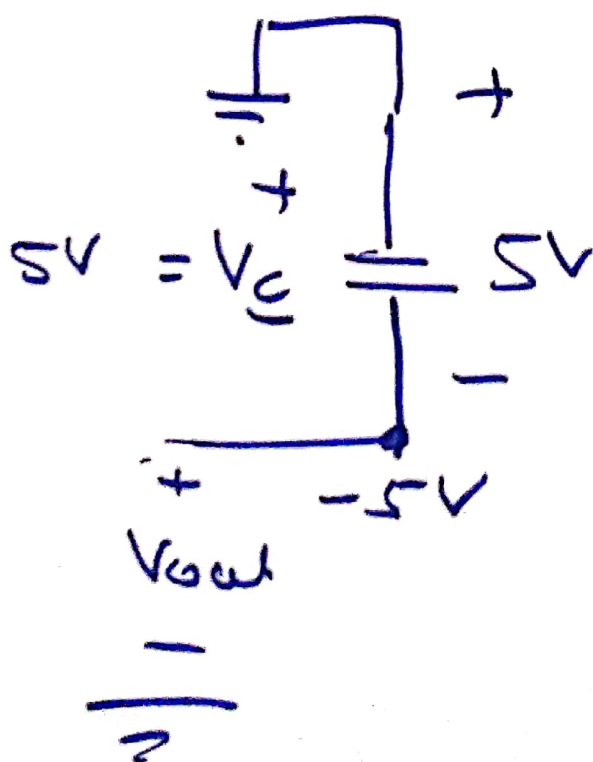

(11)

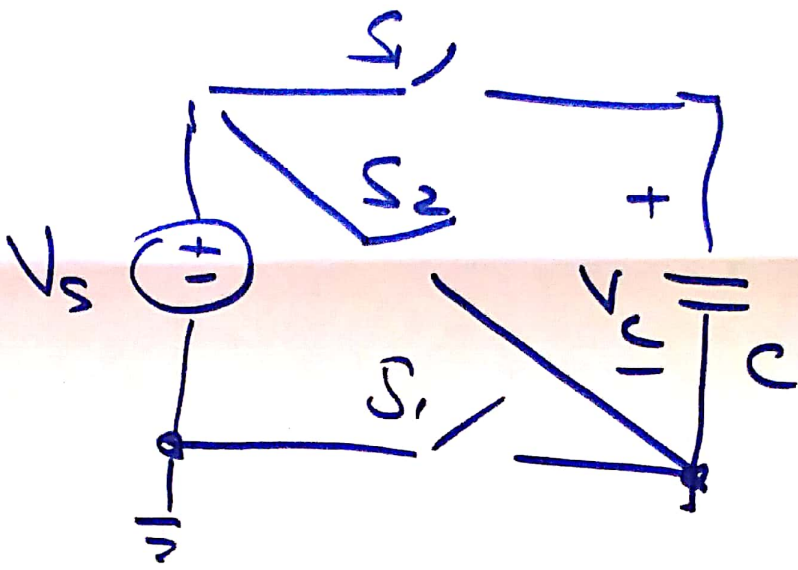

$$\begin{aligned} &+ \\ &V_{out}(k+1) \\ &= V_s + V_C \\ &= 2 \cdot V_s \end{aligned}$$

when