

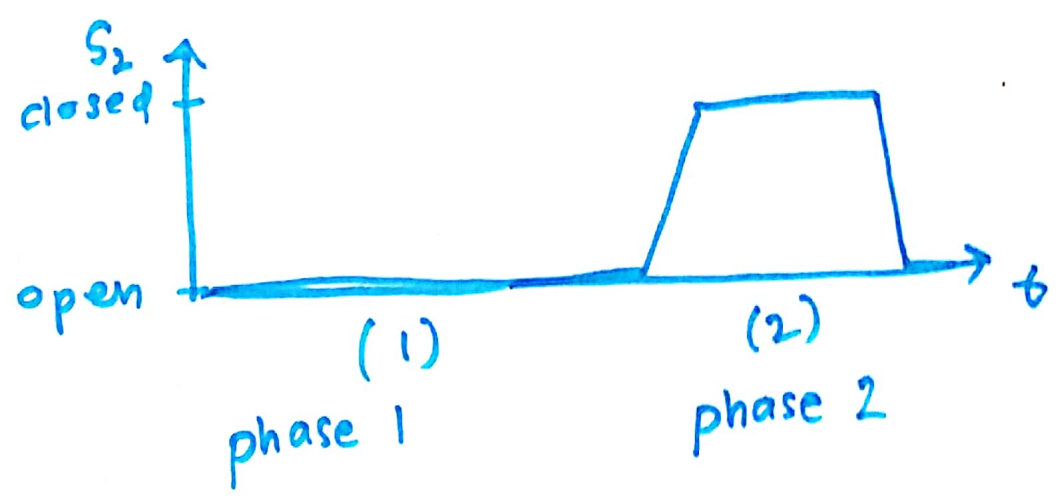


(10)

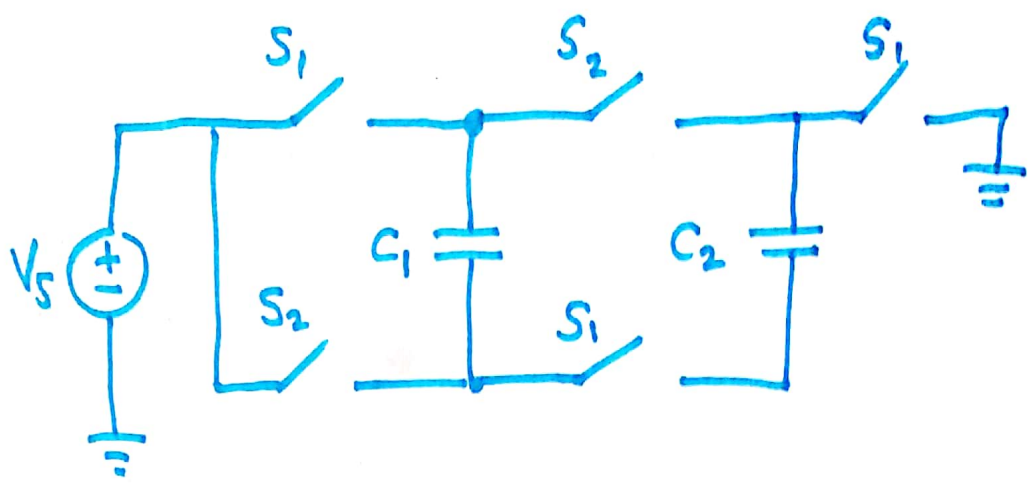


Phase 1



①

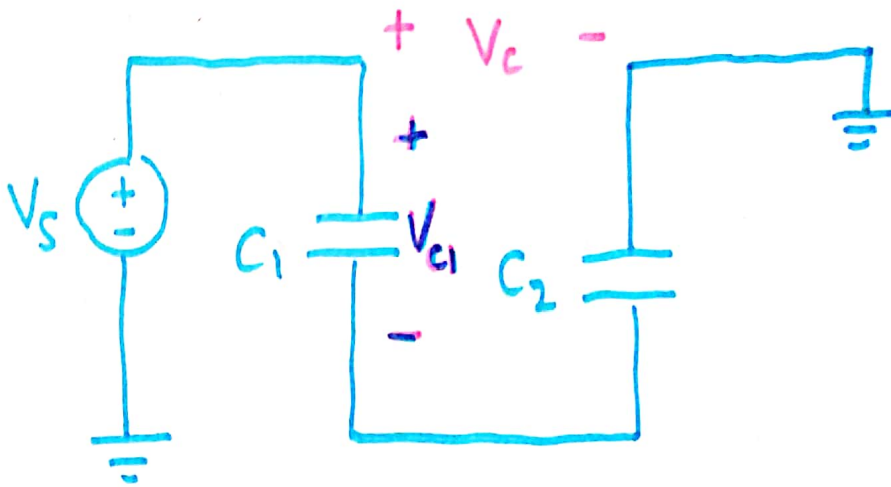

Phase 2

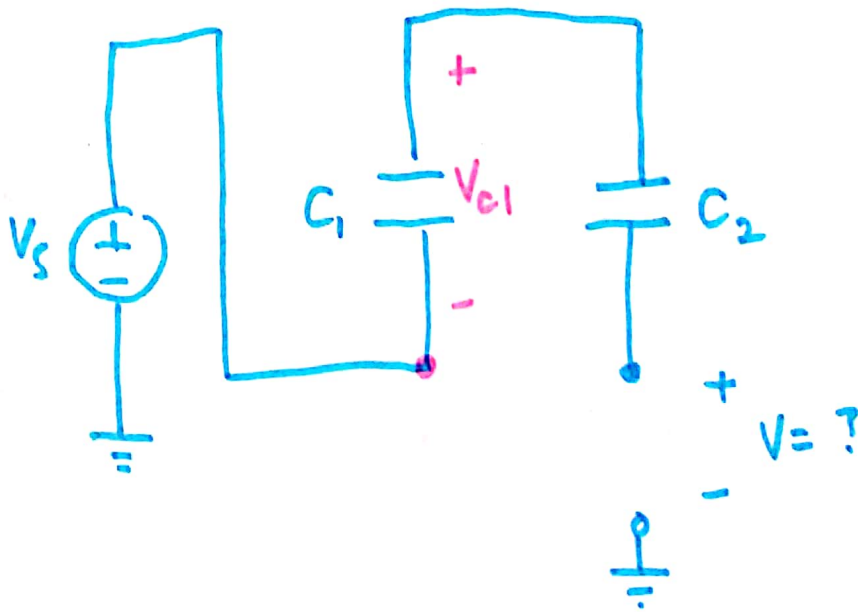


During Phase 1

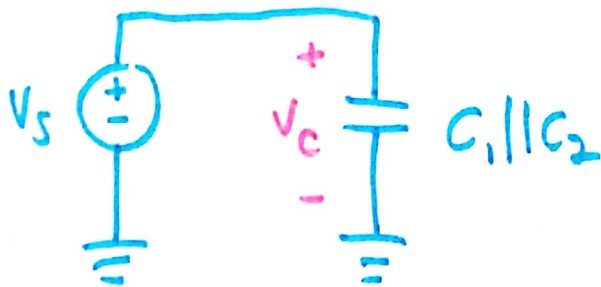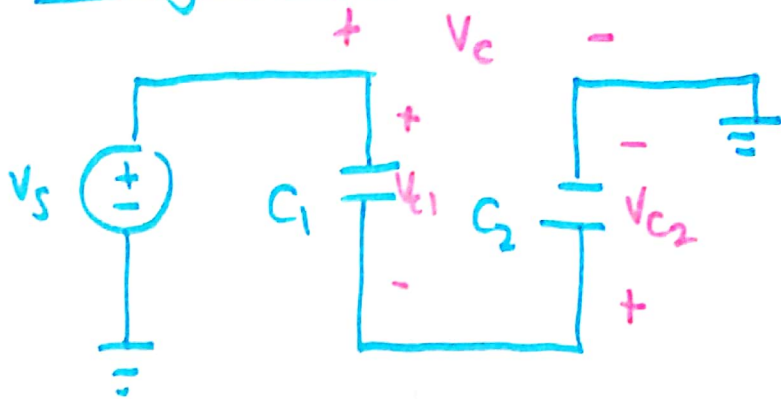

$$V_c = V_s$$



$$V_c = V_{c1} + V_{c2}$$

During phase 2

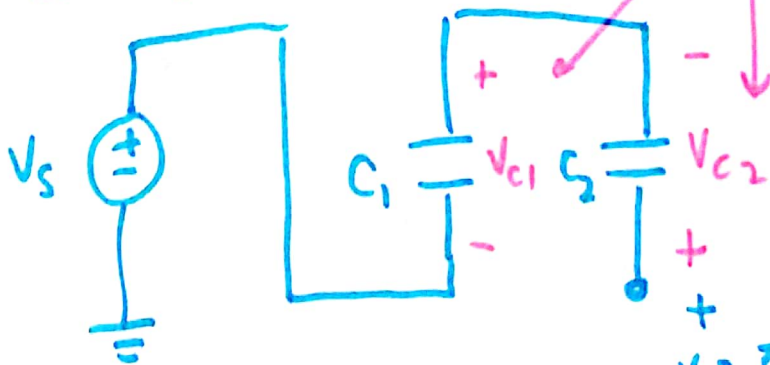

While S_1 switches open and S_2 switches close, there are no currents so these voltages stay the same in value and polarity

Another equivalent model

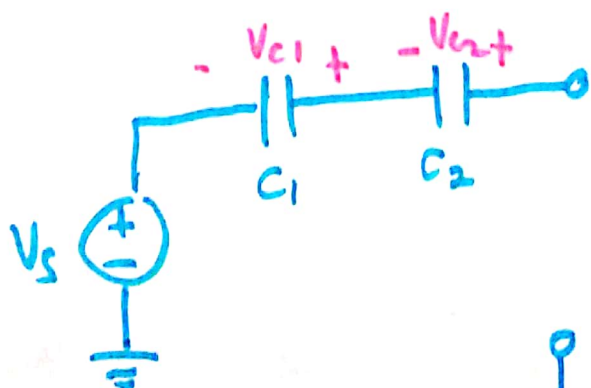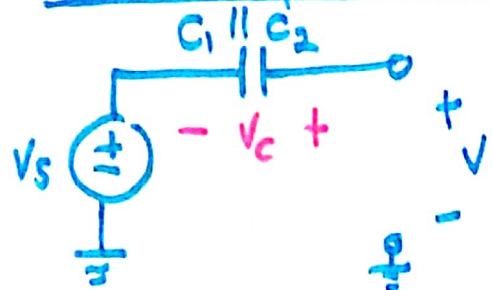


$$V = V_s + V_{c1} + V_{c2}$$


$$= V_s + V_c$$

$$= 2V_s \quad \text{Doubled voltage!}$$

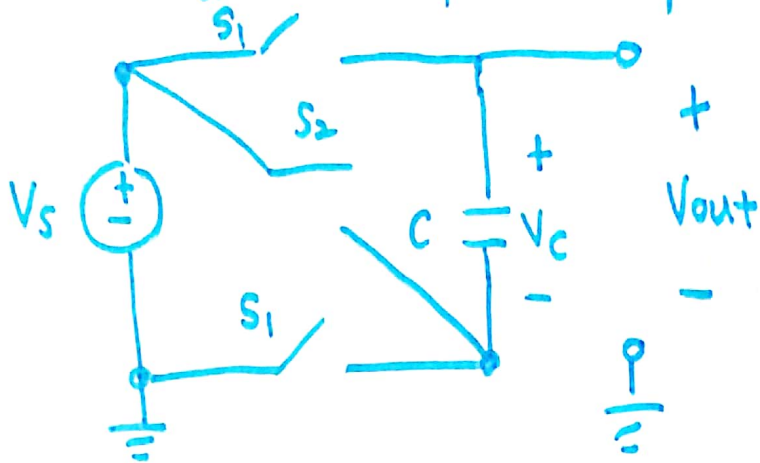
A much simpler implementation shown in lecture (and updated docuam notes) uses only one capacitor



Initially, $V_c = 0V$

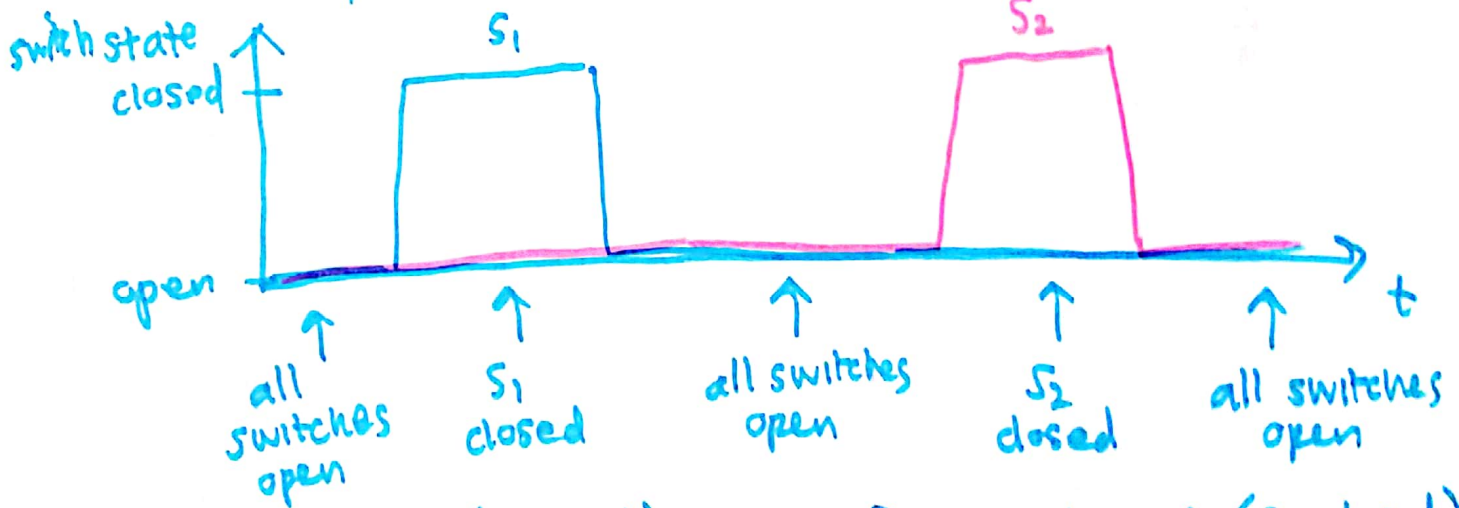

During phase 1 (S_1 closed)

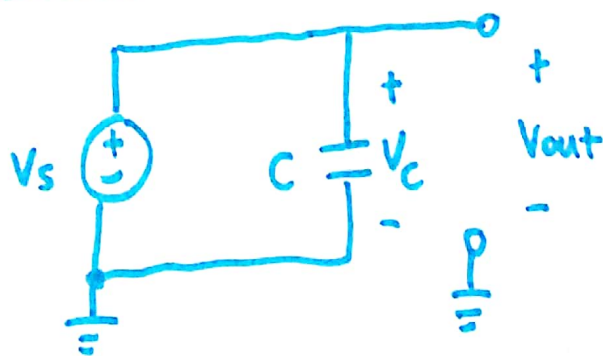


$$V_c = V_s \text{ (capacitor charged)}$$

$$V_{out} = V_c = V_s$$

(Output measured over same nodes)

During phase 2 (S_2 closed)

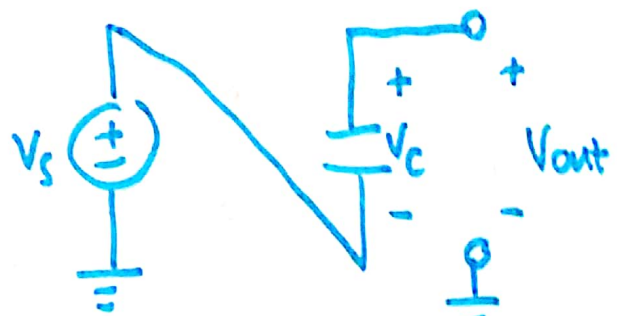

$$V_{out} = V_s + V_c \text{ (KVL)}$$

In phase 1, $V_c = V_s$. This doesn't change when S_1 opens and S_2 closes.

$$\Rightarrow V_{out} = V_s + V_s = 2V_s$$