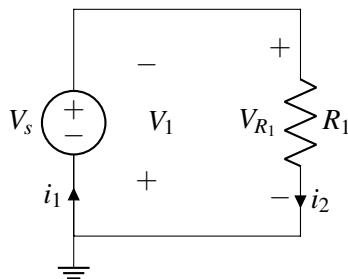


- (c) Suppose we choose a second labeling of the circuit as shown below. Calculate the power dissipated or supplied by every element in the circuit. Let $V_s = 5\text{ V}$ and let $R_1 = 5\ \Omega$.



- (d) Did the values of the element voltages and element currents change with the different labeling? Did the power for each circuit element change? Did the node voltages change? If a quantity didn't change with a difference in labeling, discuss what would have to change for quantity to change.

3. Circuit Analysis

- (a) Use nodal analysis to solve for all node voltages.
 (b) Practice writing out your expressions in matrix vector form. (Recall the form $\mathbf{A}\vec{x} = \vec{b}$, where \vec{x} is your vector of unknown voltages or/and currents).
 (c) Find current I_{R_3} flowing through resistor R_3 .

