


---

EECS 16A    Designing Information Devices and Systems I    Discussion 9A  
 Fall 2021


---

### 1. Capacitors and Charge Sharing Revisited

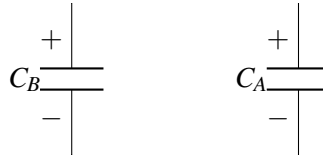- (a) Consider two capacitors,  $C_A$  and  $C_B$  that have been charged to  $Q_{A_1}$  and  $Q_{B_1}$  respectively. Compute the voltages across each one,  $V_{A_1}$  and  $V_{B_1}$ .



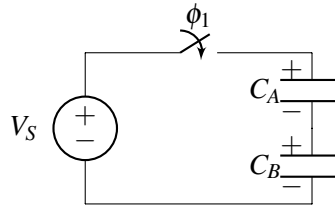
- (b) Consider the following circuit set up with an open switch. Given that these were the same charged capacitors as in the previous part, in phase 1, what is the charge and voltage across both capacitors, **before** the switch is closed?



- (c) Now the switch is closed, and the circuit is allowed to settle. Compute  $V_{B_2}$ , the final voltage drop across  $C_B$ , in terms of the given capacitances, the voltages computed in part (a), and  $V_S$ .
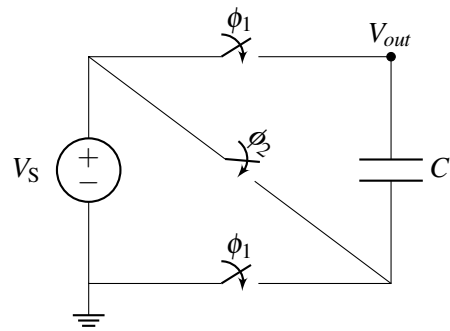
## 2. Voltage Booster

We have made extensive use of resistive voltage dividers to reduce voltage. What about a circuit that boosts voltage to a value greater than the supply  $V_S = 5V$ ? We can do this with capacitors!



- In the circuit above switches  $\phi_1$  are initially closed and switch  $\phi_2$  is initially open. Calculate the value of the output voltage,  $V_{out}$  with respect to ground, and the amount of charge stored on capacitor,  $C$ , at that state (phase 1).
- Now, after the capacitors are charged, switches  $\phi_1$  are opened and switch  $\phi_2$  is closed. Calculate the new voltage output voltage,  $V_{out}$ , at steady state.