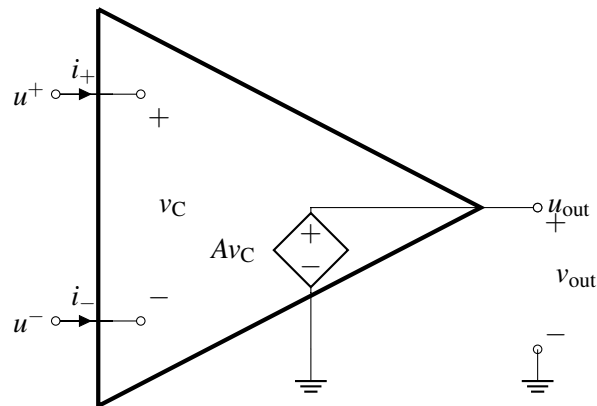


# EECS 16A Designing Information Devices and Systems I

## Fall 2021 Discussion 10A


### 1. Op-Amp Rules

Here is an equivalent circuit of an op-amp (where we are assuming that  $V_{SS} = -V_{DD}$ ) for reference:



- What are the currents flowing into the positive and negative terminals of the op-amp (i.e., what are  $I^+$  and  $I^-$ )? Based on this answer, what are some of the advantages of using an op-amp in your circuit designs?
- Suppose we add a resistor of value  $R_L$  between  $u_{out}$  and ground. What is the value of  $v_{out}$ ? Does your answer depend on  $R_L$ ? In other words, how does  $R_L$  affect  $Av_C$ ? What are the implications of this with respect to using op-amps in circuit design?

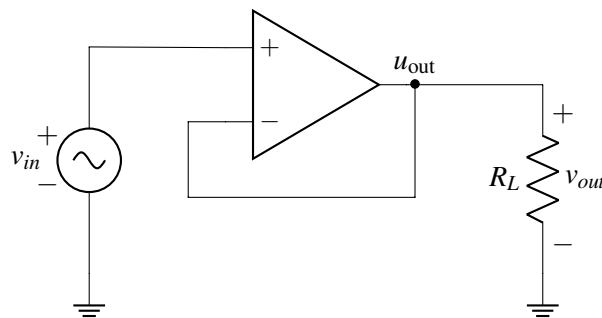
**For the rest of the problem, consider the following op-amp circuit in negative feedback:**



- Assuming that this is an ideal op-amp, what is  $v_{out}$ ?
- Draw the equivalent circuit for this op-amp and calculate  $v_{out}$  in terms of  $A$ ,  $v_{in}$ , and  $R_L$  for the circuit in negative feedback. Does  $v_{out}$  depend on  $R_L$ ? What is  $v_{out}$  in the limit as  $A \rightarrow \infty$ ?
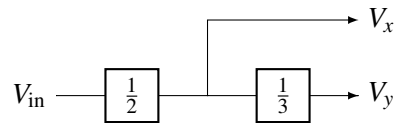
## 2. Modular Circuit Buffer


Let's try designing circuits that perform a set of mathematical operations using op-amps. While voltage dividers on their own cannot be combined without altering their behavior, op-amps can preserve their behavior when combined and thus are a perfect tool for modular circuit design. We would like to implement the block diagram shown below:



In other words, create a circuit with two outputs  $V_x$  and  $V_y$ , where  $V_x = \frac{1}{2}V_{in}$  and  $V_y = \frac{1}{3}V_x = \frac{1}{6}V_{in}$ .

- Draw two voltage dividers, one for each operation (the  $1/2$  and  $1/3$  scalings). What relationships hold for the resistor values for the  $1/2$  divider, and for the resistor values for the  $1/3$  divider?
- If you combine the voltage dividers, made in part (a), as shown by the block diagram (output of the  $1/2$  voltage divider becomes the source for the  $1/3$  voltage divider circuit), do they behave as we hope (meaning  $6V_{in} = 3V_x = V_y$ )?

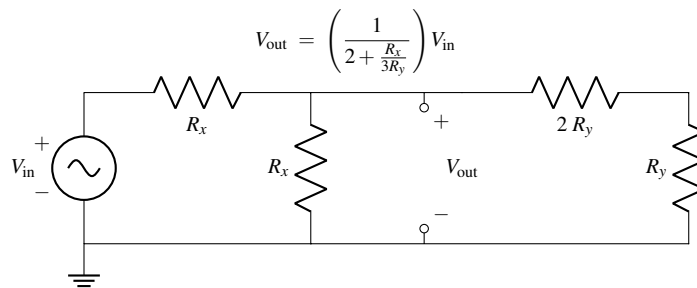HINT: The following circuit and formula may be handy:



- Perhaps we could use an op-amp (in negative-feedback) to achieve our desired behavior. Modify the implementation you tried in part (b) using a negative feedback op-amp in order to achieve the desired  $V_x, V_y$  relations  $V_x = (1/2)V_{in}$  and  $V_y = (1/3)V_x = (1/6)V_{in}$ .

HINT: Place the op-amp in between the dividers such that the  $V_x$  node is an input into the op-amp, while the source of the 2nd divider is the output of the op-amp!