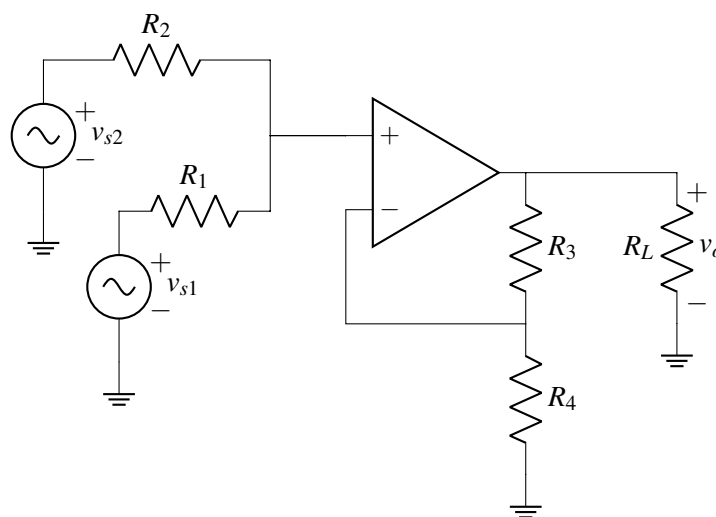

EECS 16A Designing Information Devices and Systems I
Fall 2021 Discussion 11A


1. Multiple Inputs To One Op-Amp



- (a) For the circuit above, find an expression for v_o . (*Hint: Use superposition.*)
- (b) How could you use this circuit to find the sum of different signals, i.e. $V_{s1} + V_{s2}$? What about taking the sum and adding multiplying by 2, i.e. $2(V_{s1} + V_{s2})$?

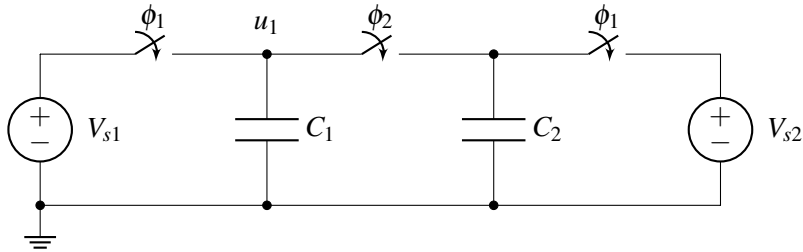2. Capacitive Charge Sharing (from Spring 2020 Midterm 2)

Consider the circuit below with $C_1 = C_2 = 1 \mu\text{F}$ and three switches ϕ_1, ϕ_2 . Suppose that initially the switches ϕ_1 is closed and ϕ_2 is open such that C_1 and C_2 are charged through the corresponding voltage sources $V_{s1} = 1 \text{ V}$ and $V_{s2} = 2 \text{ V}$.



- How much charge is on C_1 and C_2 ? How much energy is stored in each of the capacitors? What is the total stored energy?
- Now suppose that some time later, switch ϕ_1 opens and switch ϕ_2 closes. What is the value of voltage u_1 at steady state?