


---

EECS 16A    Designing Information Devices and Systems I    Discussion 12A  
 Fall 2021

---

### 1. Superposition


Consider the following circuit:

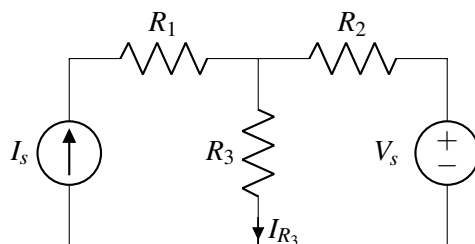


- With the current source turned on and the voltage source off, find the current  $I_{R_3}$ .
- With the voltage source turned on and the current source turned off, find the voltage drop across  $R_3$ ,  $V_{R_3}$ .
- Find the power dissipated by  $R_3$ .
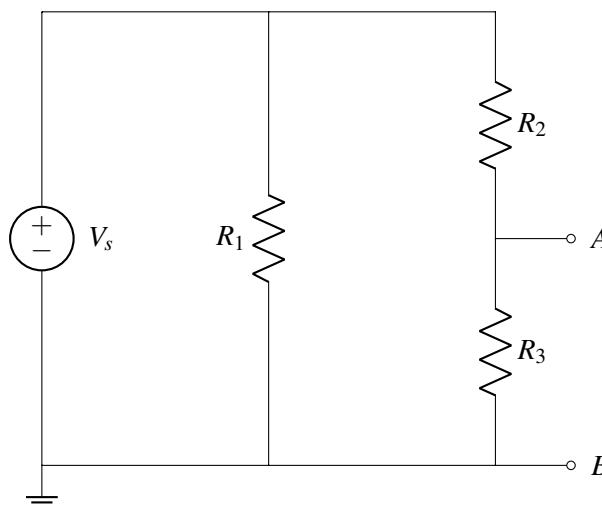
### 2. Thévenin/Norton Equivalence


- Find the Thévenin resistance  $R_{th}$  of the circuit shown below, with respect to its terminals  $A$  and  $B$ .



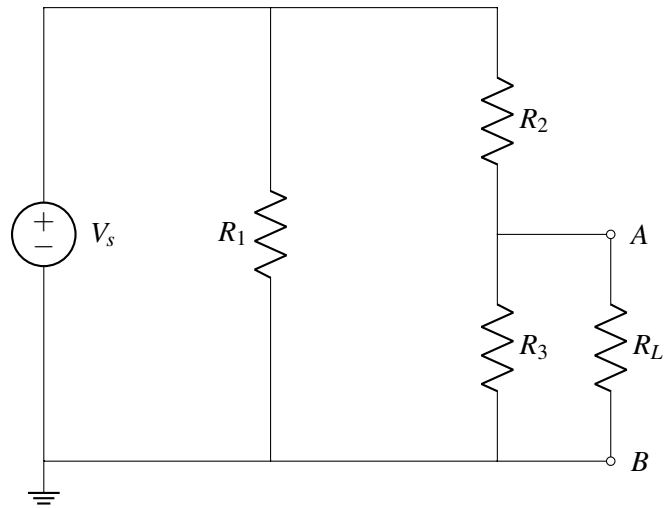- Now a load resistor,  $R_L = R$ , is connected across terminals  $A$  and  $B$  as shown in the circuit below. Find the power dissipated in the load resistor in terms of given variables.



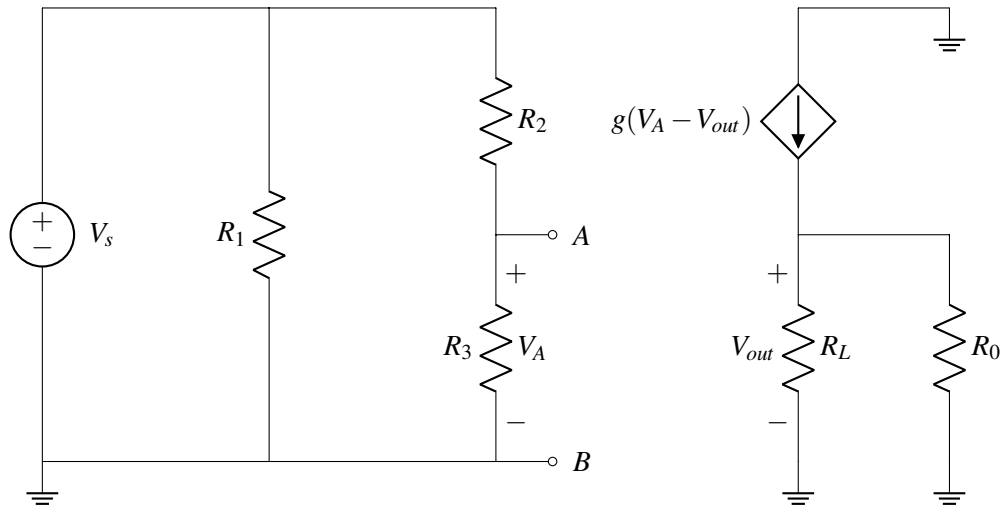(c) We modify the circuit as shown below, where  $g$  is a known constant:




Find a symbolic expression for  $V_{out}$  as a function of  $V_s$ .  
 Hint: Redraw the left part of the circuit using with its Thévenin equivalent.


### 3. A Versatile Opamp Circuit

For each subpart, determine the voltage at  $O$ .

(a) Configuration 1:

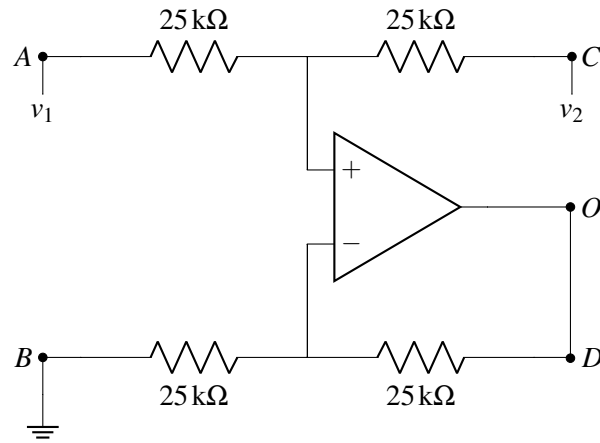

(b) Configuration 2:

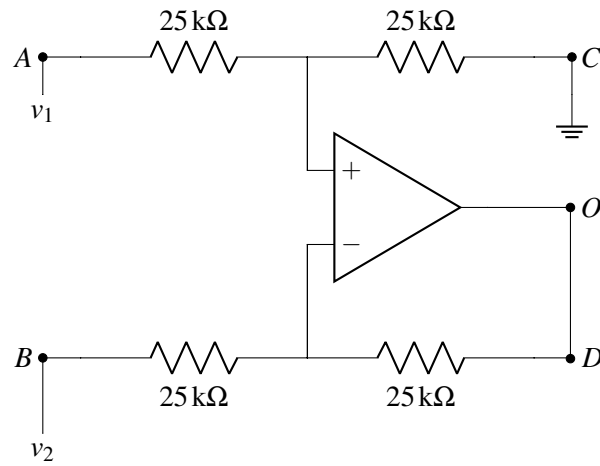

(c) Configuration 3:

