

Feedback form: [tinyurl.com/anushal6a.feedback](http://tinyurl.com/anushal6a.feedback)

**Op-amp Golden Rules:**  
 1.  $I^+ = I^- = 0$   
 2. If neg. feedback,  $V^+ = V^-$

**Voltage divider**  
 (a) For the circuit above, an expression for  $V_o$  in terms of  $V_{s1}$  and  $V_{s2}$  is  
**Superposition:**  
 $V_{s2}$  off:  $V^+ = \left(\frac{R_2}{R_1+R_2}\right) V_{s2}$   
 $V^- = \left(\frac{R_4}{R_3+R_4}\right) V_o$   
 $V_o = \left(\frac{R_3+R_4}{R_4}\right) \left(\frac{R_2}{R_1+R_2}\right) V_{s2}$

$V_{s2}$  off:  $V^+ = \left(\frac{R_1}{R_1+R_2}\right) V_{s2}$   
 $V^- = \left(\frac{R_4}{R_3+R_4}\right) V_o$   
 $V_o = \left(\frac{R_3+R_4}{R_4}\right) \left(\frac{R_1}{R_1+R_2}\right) V_{s2}$

**Final Output:**  
 $V_o = \left(\frac{R_3+R_4}{R_4}\right) \left[ \frac{R_2}{R_1+R_2} V_{s1} + \frac{R_1}{R_1+R_2} V_{s2} \right]$

**Capacitive Charge Sharing (from Lecture 20) Mikrotik 2:**  
 Change sharing! Close switches for each phase. Use floating nodes to die for charge on caps.

**Phase 1:**  
 $Q = CV$   
 $Q_{c1} = C_1 V_{s1}$   
 $Q_{c2} = C_2 V_{s2}$   
 $Q_{c1} + Q_{c2} = Q_{c1} + Q_{c2}$   
 $C_1 V_{s1} + C_2 V_{s2} = C_1 V_1 + C_2 V_1$   
 $V_1 = \frac{C_1 V_{s1} + C_2 V_{s2}}{C_1 + C_2} = 1.5V$

**Questions:**

1. How to solve for  $V_{out}$  in problem 1 without using superposition?

**NVA+KCL**

**Solve for  $V^+$ :**  
 $I_{R2} + I_{R1} = I^+ = 0$   
 $\frac{V_{s2} - V^+}{R_2} + \frac{V_{s1} - V^+}{R_1} = 0$   
 $\frac{V_{s2}}{R_2} - \frac{V^+}{R_2} + \frac{V_{s1}}{R_1} - \frac{V^+}{R_1} = 0$   
 $\frac{V_{s2}}{R_2} + \frac{V_{s1}}{R_1} = V^+ \left( \frac{1}{R_2} + \frac{1}{R_1} \right)$   
 $V^+ = \left( \frac{R_1 R_2}{R_1 + R_2} \right) \left( \frac{R_1 V_{s2} + R_2 V_{s1}}{R_1 R_2} \right)$   
 $V^+ = \left( \frac{R_1 V_{s2} + R_2 V_{s1}}{R_1 + R_2} \right)$

**Solve for  $V^-$ :**  
 $V^- = \left( \frac{R_4}{R_3 + R_4} \right) V_o$

**Equate  $V^+$  and  $V^-$ :**  
 $V^+ = V^-$   
 $\frac{R_1 V_{s2} + R_2 V_{s1}}{R_1 + R_2} = \frac{R_4}{R_3 + R_4} V_o$   
 $V_o = \left( \frac{R_3 + R_4}{R_4} \right) \left[ \frac{R_1 V_{s2}}{R_1 + R_2} + \frac{R_2 V_{s1}}{R_1 + R_2} \right]$

2. How to solve for  $v_1$  in problem 2 w/ different polarities?

**Phase 1:**  
 $Q_{c1} = C_1 V_{s1}$   
 $Q_{c2} = C_2 V_{s2}$   
 $Q_{c2} = -C_2 V_{s2}$

**Phase 2:**  
 $Q_{c1} - Q_{c2} = Q_{c1} - Q_{c2}$   
 $C_1 v_1 - C_2 (0 - v_1) = C_1 V_{s1} - (-C_2 V_{s2})$   
 $C_1 v_1 + C_2 v_1 = C_1 V_{s1} + C_2 V_{s2}$   
 $v_1 = \frac{C_1 V_{s1} + C_2 V_{s2}}{C_1 + C_2}$