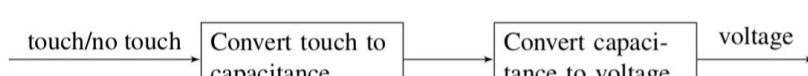


Feedback form: tinyurl.com/anushal6afeedback

When faced with a design problem, a good place to start is to follow the **design procedure** outlined here (from Note 20):

- Step 1 (Specification):** Concretely restate the goals for the design. Frequently, a design prompt will include a lot of text, so we'd like to restate all of the most important features of our design. We'll refer to these specifications later to determine if our design is complete.
- Step 2 (Strategy):** Describe your strategy (often in the form of a block diagram) to achieve your goal. To do this, start by thinking about what you can measure vs. what you want to know. For example in our capacitive touchscreen, we want to know if there is a touch and we can measure voltage. Since we know that a touch can change the capacitance, we break this down into the following block diagram:




Step 3 (Implementation): Implement the components described in your strategy. This is where pattern matching is useful: remind yourself of blocks you know (ex. voltage divider, inverting amplifier) and check if any of these can be used to implement steps of your strategy. If you don't know of a block that does what you want, think about how to modify or extend the blocks you know.

Step 4 (Verification): Check that your design from Step 3 does what you specified in Step 1. It's tempting to think that you're done after implementation, but verification is critical! In particular, check block-to-block connections, as these are the most common point for problems. Does one block load another block causing it to behave differently than expected? Are there any contradictions (ex. a voltage source with both ends connected by a wire, or a current source directed into an open circuit)? Repeat previous steps if necessary to make sure that your final circuit meets the specifications.

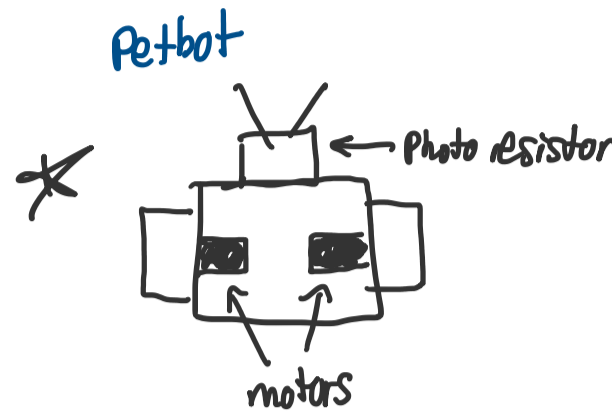1. PetBot Design (from Fall 2016 Final Exam)

In this problem you will design circuits to control PetBot, a simple robot designed to follow light. PetBot measures light using a photoresistor, which is a light-sensitive resistor. As it is exposed to more light, its resistance decreases. The diagram below shows the circuit symbol for a photoresistor.



The basic layout of PetBot can be seen below. It is driven by one motor that will be modeled as a resistor. PetBot drives forward (towards the light source) when a positive voltage is applied across the motor, and conversely a negative applied voltage drives PetBot backward (away from the light source). In this system the light sensor is mounted to the front of the robot, and the speed of PetBot is proportional to the applied voltage to the motor.



$V_m \uparrow$: Forwards
 $V_m \downarrow$: Backwards

Motor circuit


(a) Speed control
In our first circuit design, we will begin by making PetBot decrease speed as it drives towards light. Design a motor-driving circuit that outputs a decreasing positive motor voltage as PetBot drives toward the light source. The motor voltage should be at least 5V when far away from the light. At this far away from the light source, the photoresistor value will be 10kΩ, and then drop towards 100Ω as it approaches the light.

In your design, you may use any number of resistors and op-amps. You also have access to voltage sources of 10V and -10V. Based on your circuit, derive an expression for the motor voltage as a function of the circuit components that you used.

NOTE! Since the motor is a resistor, the circuit design MUST have a buffer so that the applied voltage to the motor does not depend on its resistance.

Far from light: $V_m \geq 5V$
Close to light: $V_m < 5V$
 $R_p = 10k\Omega$
 $R_p \approx 100\Omega$

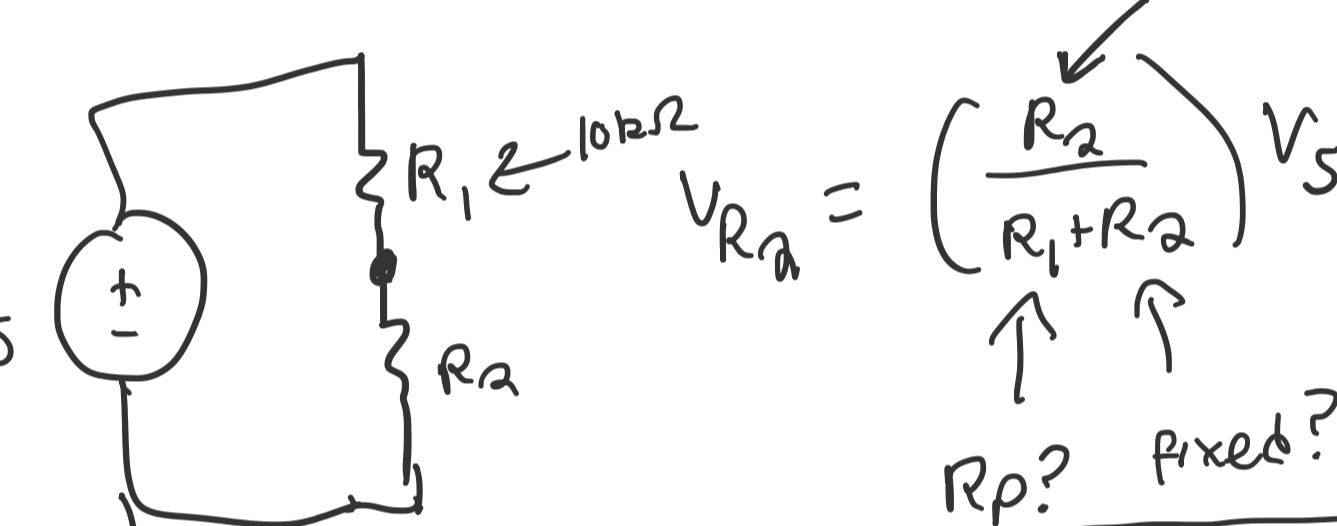$V_m \propto R_p$
 $V_m \uparrow \Rightarrow R_p \uparrow$



$$V_{Ra} = \left(\frac{R_2}{R_1 + R_2} \right) V_S$$

$R_2 = R_p$

$$V_m = \left(\frac{R_p}{R_1 + R_p} \right) \cdot V_S$$

Far from light: $5V = \left(\frac{10k\Omega}{R_1 + 10k\Omega} \right) \cdot 10V$
 $R_1 = 10k\Omega$


(b) Distance control
When the PetBot stops at a distance of 1m away from the light, the photo-resistor has a value 1kΩ. We would like to have the PetBot drive away when closer than 1m from the light (so for lower R_p), and drive towards the light when exceeding 1m (so for greater R_p).

Design a **comparator circuit** that outputs a positive motor voltage when the PetBot exceeds 1m in distance from the flashlight (making the PetBot move toward it), and a negative voltage when PetBot is within 1m of flashlight (making the PetBot back away from the flashlight).

In your design, you may use any number of resistors along with the comparator. You also have access to voltage sources of 10V and -10V.


$d = 1m$ (flipping point)
 $R_p = 1k\Omega$

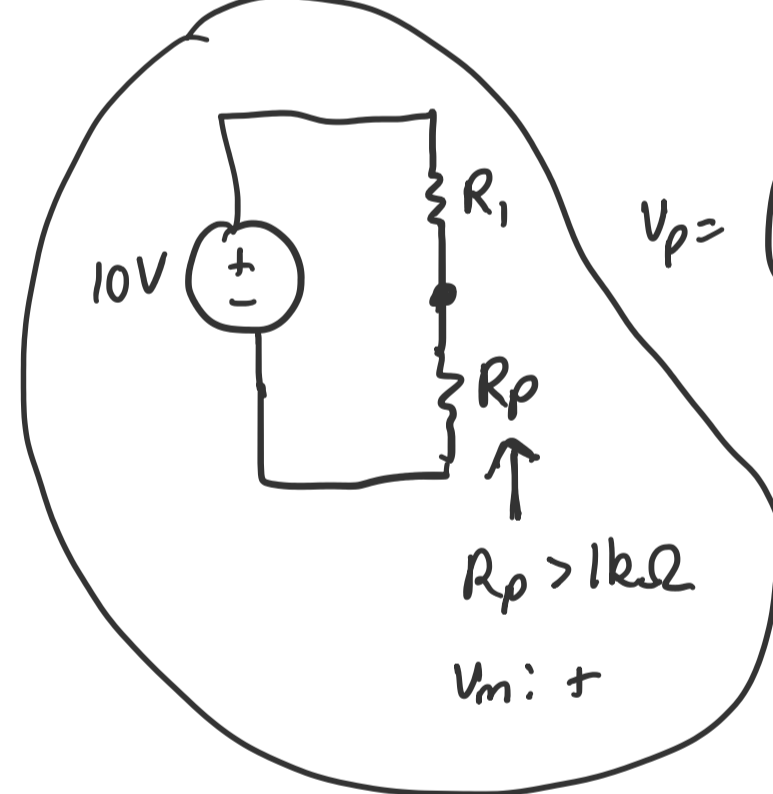$d > 1m$: $R_p > 1k\Omega$, $V_m > 0$
 $d < 1m$: $R_p < 1k\Omega$, $V_m < 0$



$$V_p = \left(\frac{R_p}{R_1 + R_p} \right) \cdot 10V$$

$R_1 = 1k\Omega$
 $R_p = 1k\Omega$

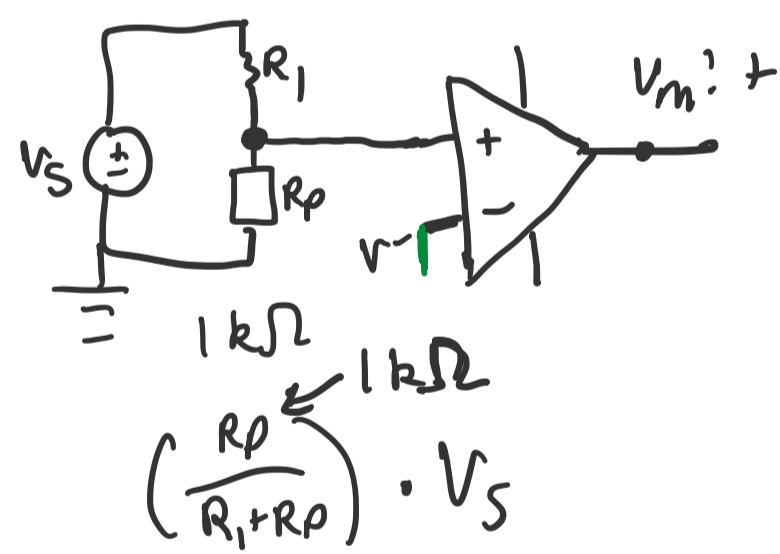

$$V^+ = \left(\frac{1k\Omega}{R_1 + 1k\Omega} \right) \cdot V_S \Rightarrow V^- = +V_m$$


$V^+ = \frac{1k\Omega}{1k\Omega + 1k\Omega} \cdot 10V = 5V \Rightarrow 1m$ away from light source
 $V^- = 5V$

Given 10V and -10V, how can we create 5V voltage source?

$V_S \left(\frac{R_1}{R_1 + R_2} \right)$, $R_1 = R_2$, $V_{Ra} = \frac{1}{2} \cdot V_S$
 $V_{Ra} = 5V$

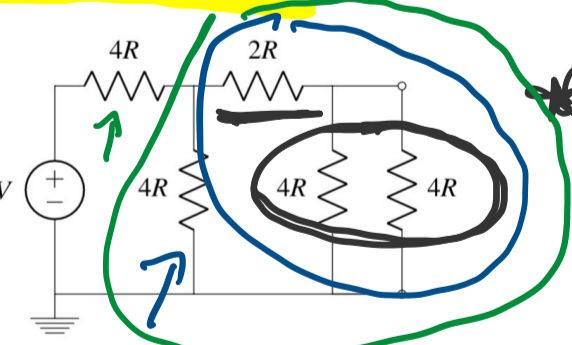2. OPTIONAL: Power to Resist (from Spring 2018 midterm 2)

Find the power dissipated by the voltage source in the circuit below. Be sure to use passive sign convention.



$P = IV$ (using PSC)
power being dissipated

1. Combine resistors to Req

$$4R \parallel 4R = \frac{4R \cdot 4R}{4R + 4R} = 2R$$

series: $2R + 2R = 4R$

$$4R \parallel 4R = 2R$$

series: $4R + 2R = 6R = R_{eq}$



$$P = IV = \frac{V^2}{R} = I^2 R$$

$P_V = \frac{V^2}{6R}$, $P_R = \frac{V^2}{6R}$

(For Reference: Example Circuits) Ckt: cgo1a0002

