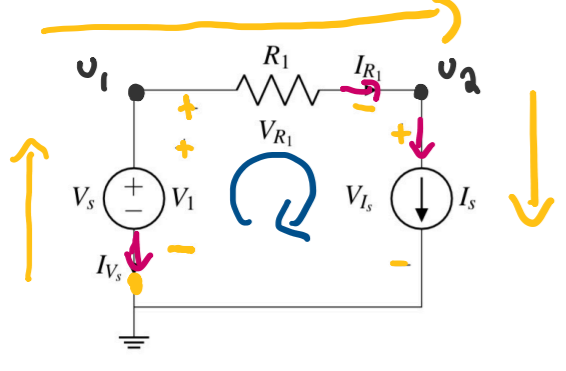


Feedback form: tinyurl.com/anusha6afeedback

I. Passive Sign Convention and Power v 2.0

Suppose we have the following circuit and label the currents as shown below. Calculate the power dissipated or supplied by every element in the circuit. Let $V_s = 5V$, $I_s = 0.5A$ and $R_1 = 5\Omega$.



KVL: $\sum \text{voltages} = 0$

$V_s - V_{R_1} - V_{I_s} = 0$

$V_s = V_{I_s}$

$V_s - V_{R_1} - V_{I_s} = 0$

KCL: @ v_1 : $I_{I_s} + I_{R_1} = 0$ (1)

@ v_2 : $I_{R_1} = I_{I_s}$ (2)

$V_s = 5V$ $I_s = 0.5A$ $R_1 = 5\Omega$

$I_{I_s} = 0.5A = I_{R_1}$

$I_{V_s} = -0.5A$

KVL: $V_s - V_{R_1} - V_{I_s} = 0$ $5V - I_{R_1} \cdot 5\Omega - V_{I_s} = 0$ $5V - 0.5A \cdot 5\Omega - V_{I_s} = 0$

$5V - 2.5V - V_{I_s} = 0$ $V_{I_s} = 2.5V$

Power = $P = IV$

$V = IR$ $P = I^2R$
 $= \frac{V^2}{R}$ } only for resistors

Voltage Source: $P = IV$

$P = I_{V_s} \cdot V_s = -0.5A \cdot 5V = -2.5W$ (supplied)

Resistor: $P_R = I_{R_1} \cdot V_{R_1} = 0.5A \cdot 2.5V = 1.25W$ (dissipating)

Current Source: $P_{I_s} = I_{I_s} \cdot V_{I_s} = 0.5A \cdot 2.5V = 1.25W$ (dissipating)

Powers should sum up to 0 ✓

2. Resist the Touch

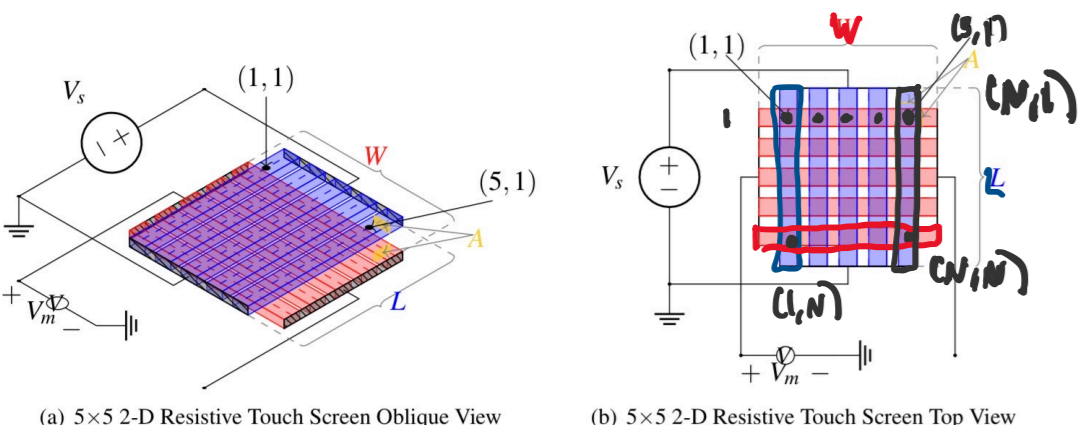


Figure 1: $N \times N$ Resistive Touch Screen, $N = 5$

In this question we will be re-examining the 2-dimensional resistive touchscreen. This touchscreen, is slightly different to the one shown in lecture and more like the one we will be examining in lab.

The touchscreen has length L and width W and is composed of a rigid bottom-layer and a flexible top-layer. Instead of having two continuous resistive sheets on the top and bottom layers, this is a simpler implementation with N vertical strips of conductive material in the top layer and N horizontal strips of conductive material in the bottom layer. The strips of a single layer are all connected by an ideal conducting plate on each side. All strips have resistivity ρ and cross-sectional area A . Assume that all top layer resistive strips and bottom layer resistive strips are spaced apart equally, and that the upper left touch point in Figure 1(b) is position $(1, 1)$, and the upper right touch point is $(N, 1)$. The spacing between the strips in the top layer is $\frac{W}{N+1}$, and the spacing between the strips in the bottom layer is $\frac{L}{N+1}$.

(a) Find the resistance R_x for a single vertical blue strip and R_y for a single horizontal red strip, as a function of the screen dimensions W and L , the strip resistivity ρ , and the cross-sectional area A .

$R = \frac{\rho \cdot L}{A}$
 $R_y = \frac{\rho \cdot L}{A}$ $R_x = \frac{\rho \cdot W}{A}$

(b) Consider a 2×2 example for the touchscreen circuit, shown in Figure 2. Assume that we connect a voltage source V_s between the top and bottom terminals of the blue strips, and a voltmeter V_m to one of the left or right terminals as depicted in the diagram.


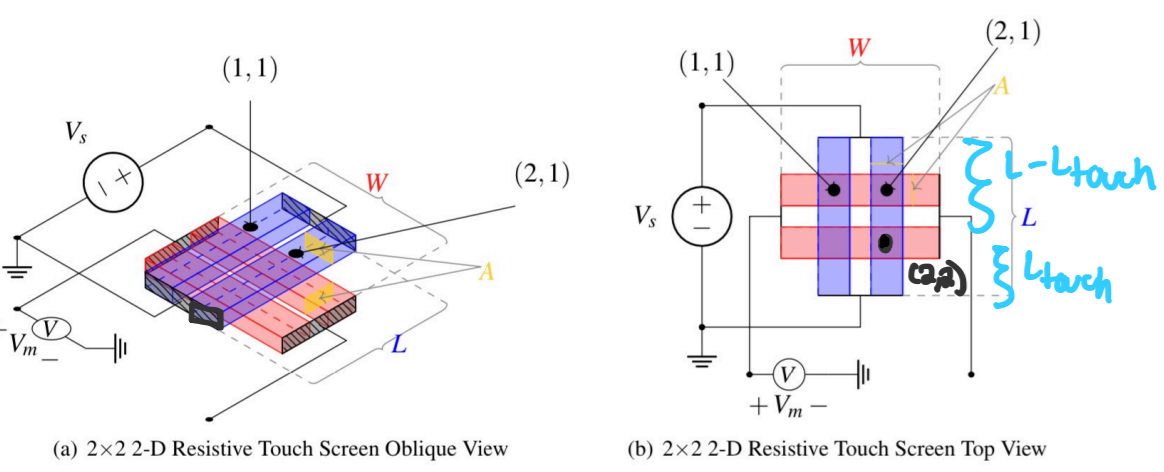


Figure 2: 2×2 Resistive Touch Screen

If $V_s = 3V$, $R_x = 2000\Omega$, and $R_y = 2000\Omega$, draw the equivalent circuit for when the point $(2, 2)$ is pressed and solve for the measured voltage V_m with respect to ground.


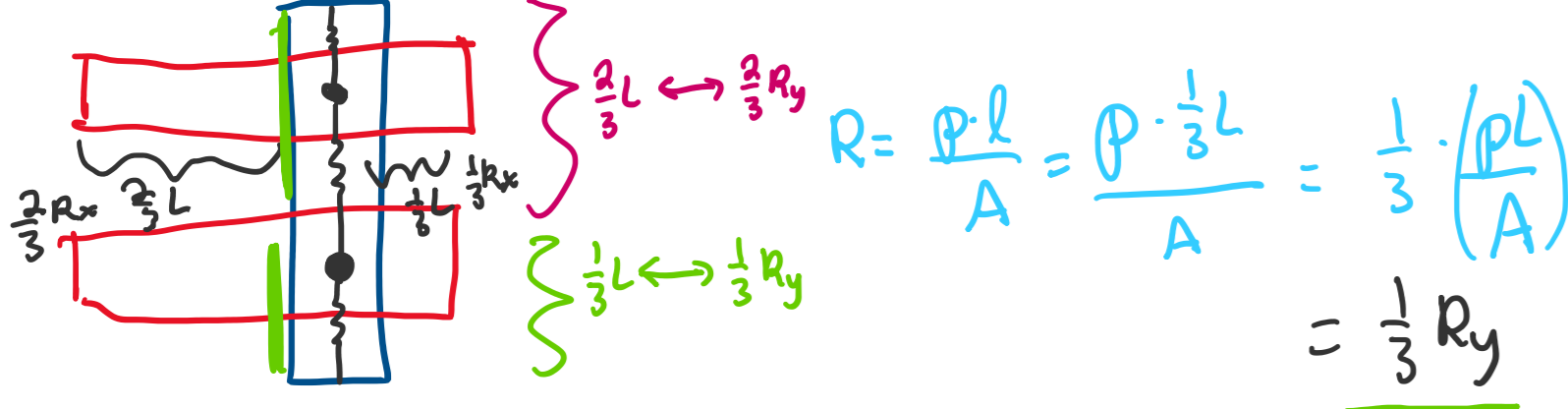
Reminder: all top layer resistive strips and bottom layer resistive strips are spaced apart equally, and that the upper left touch point is position $(1, 1)$. The spacing between the strips in the top layer is $\frac{W}{N+1}$, and the spacing between the strips in the bottom layer is $\frac{L}{N+1}$.



$R = \frac{\rho L}{A} = \frac{\rho \cdot \frac{1}{3}L}{A} = \frac{1}{3} \left(\frac{\rho L}{A} \right) = \frac{1}{3} R_y$


$V_m = \frac{\frac{1}{3} R_y}{\frac{1}{3} R_y + \frac{2}{3} R_y} \cdot V_s = \frac{1}{3} V_s$

2D Touchscreen

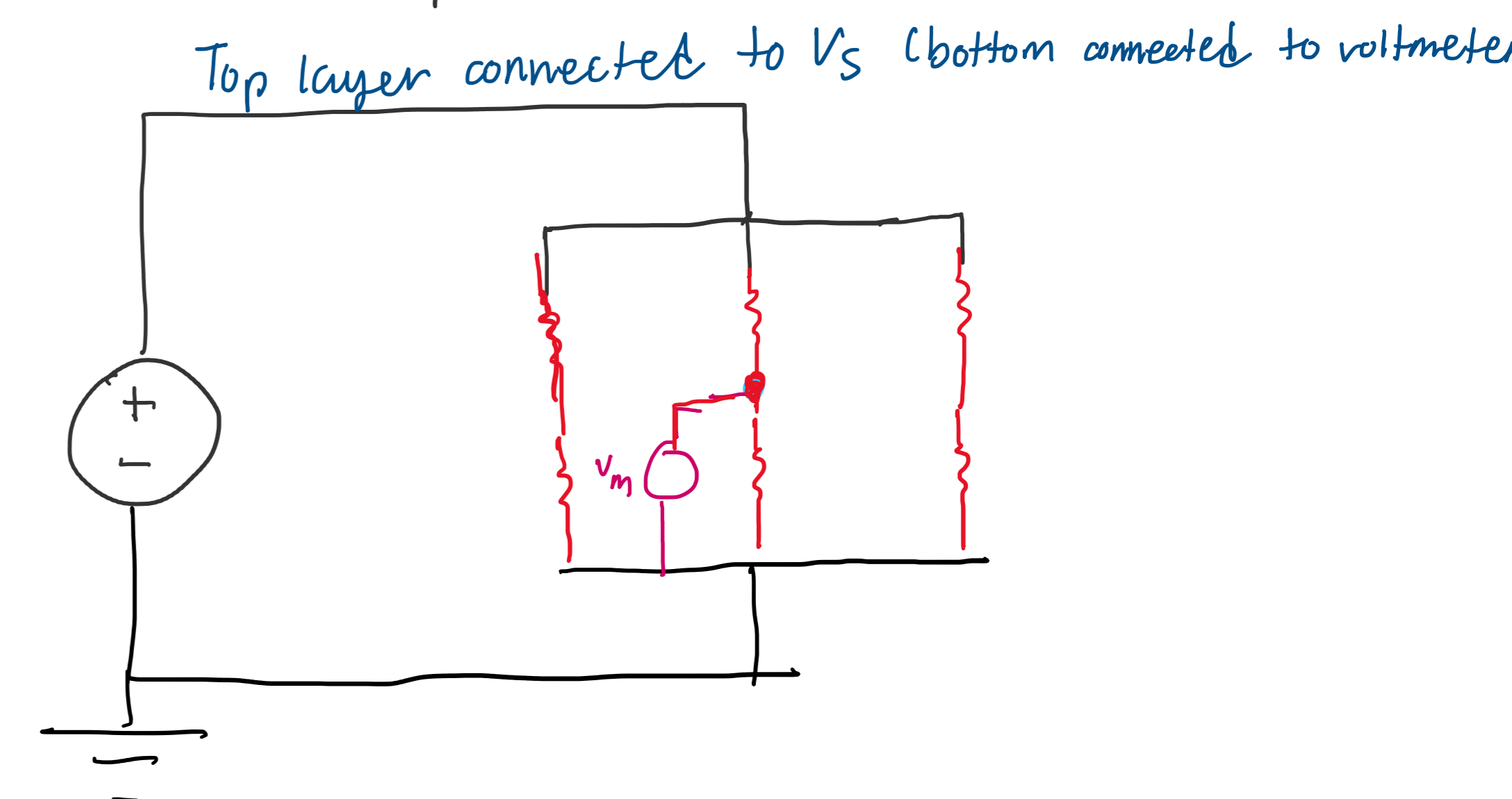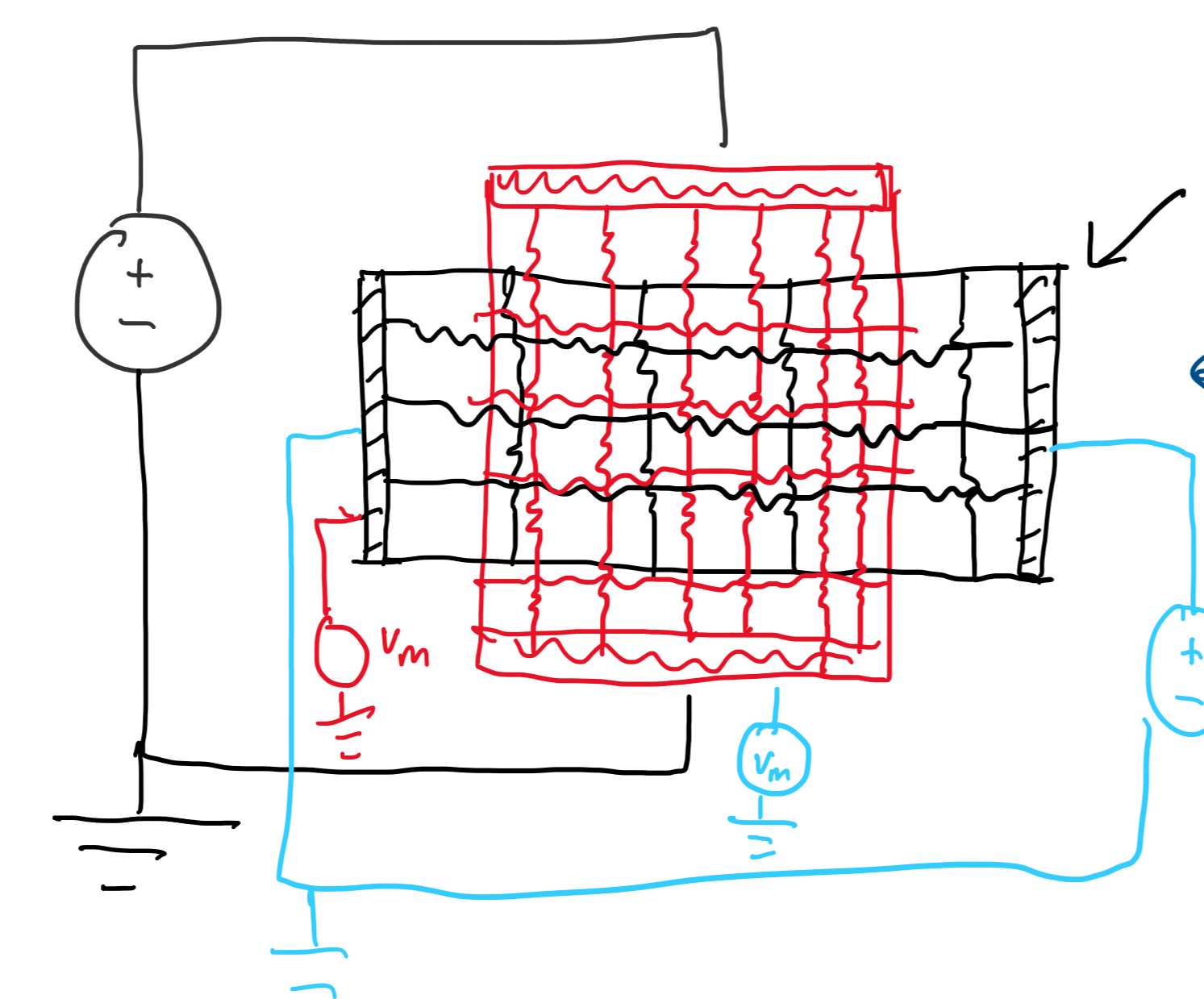

Top layer connected to V_s (bottom connected to voltmeter)

Bottom layer connected to V_s

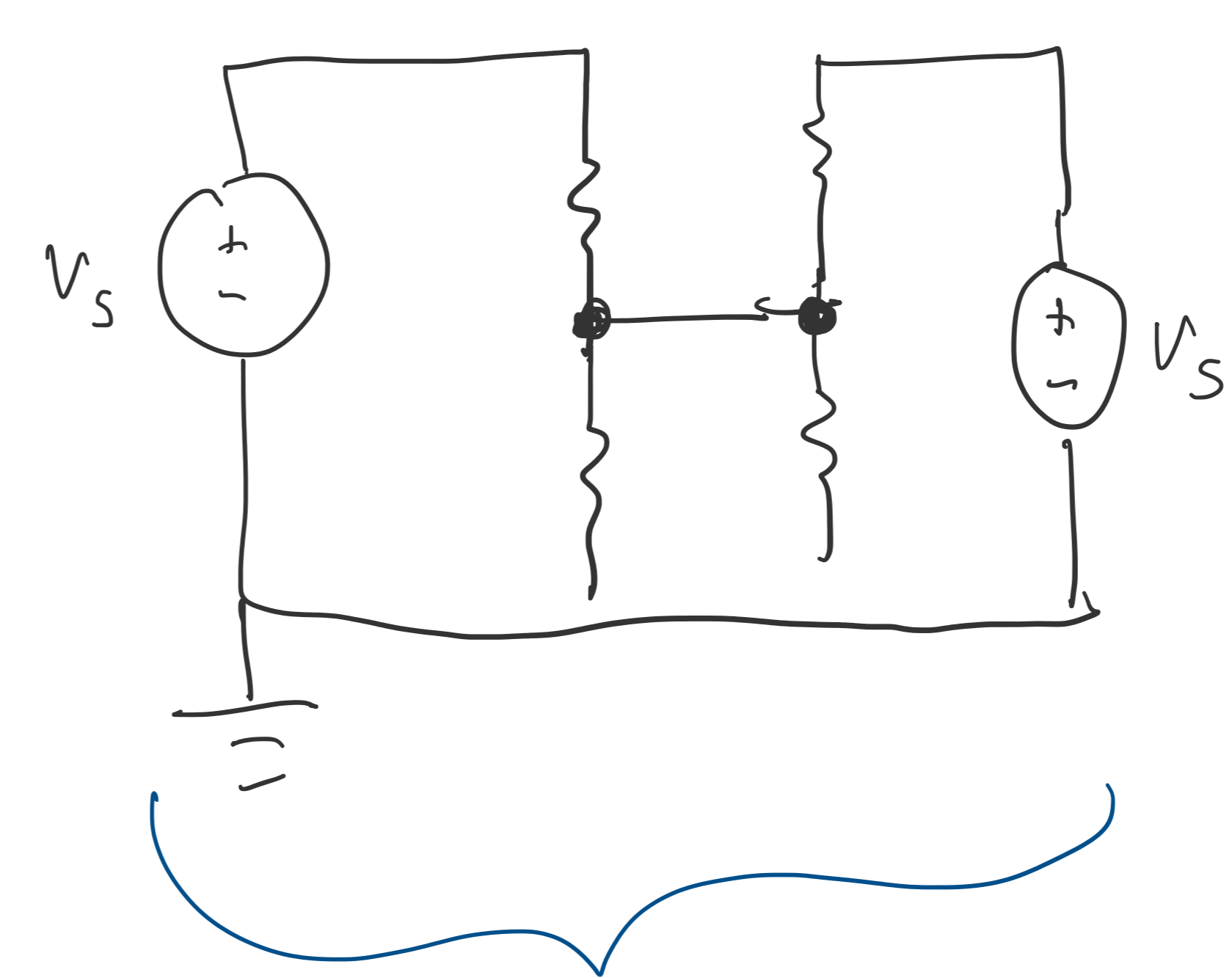


Both top and bottom layers connected to V_s → not possible to measure vertical & horizontal position at the same time

When top layer is connected to V_s & bottom layer is connected to a voltmeter → measures vertical position

When bottom layer is connected to V_s & top layer is connected to a voltmeter → measures horizontal position

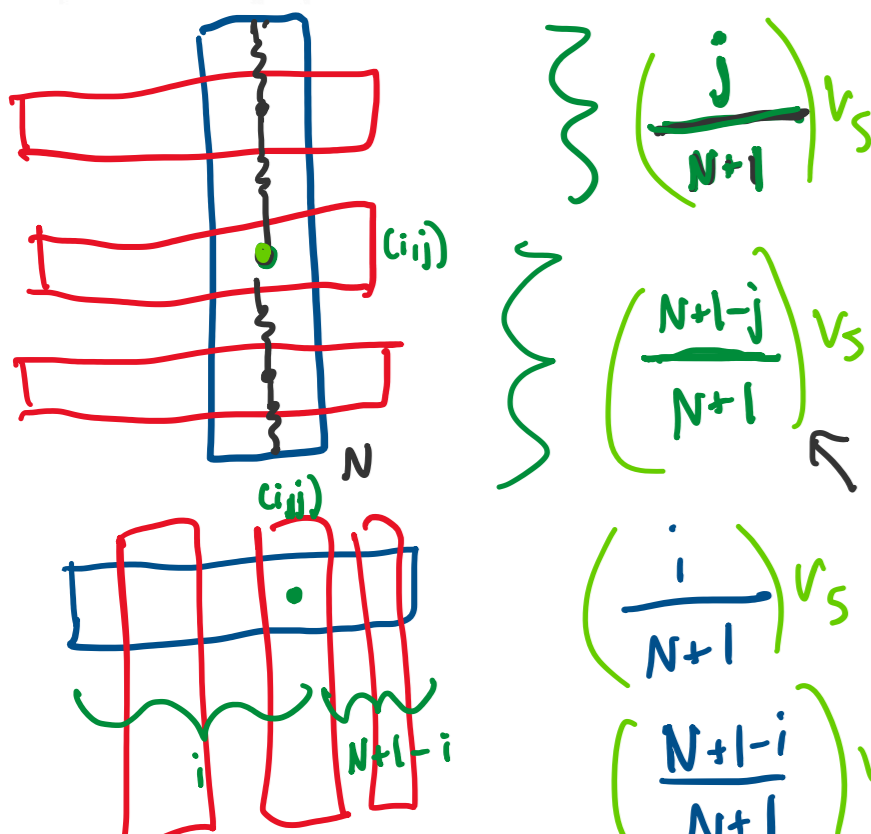(c) Suppose a touch occurs at coordinates (i, j) for an arbitrary $N \times N$ touchscreen, and the voltage source and meter are connected as in the figures. A 5×5 example is shown in Figure 1(b). Find an expression for V_m as a function of V_s , N , i , and j . Again, the upper left corner is the coordinate $(1, 1)$ and the upper right coordinate is $(N, 1)$.



Where does $N+1$ come from?
There are $N+1$ resistors for a strip of length N

$V_m = \left(\frac{N+1-j}{N+1} \right) V_s$
When top layer is connected to V_s & bottom layer is connected to voltmeter

(d) Optional / Fun: Experiment with the TinkerCad models below to validate the theoretical results you just derived.
TinkerCad model of 2×2 equivalent circuit: <https://www.tinkercad.com/things/0w1Xz3MRd7B>
TinkerCad model of 3×2 equivalent circuit: <https://www.tinkercad.com/things/k5ooj2UEN>