
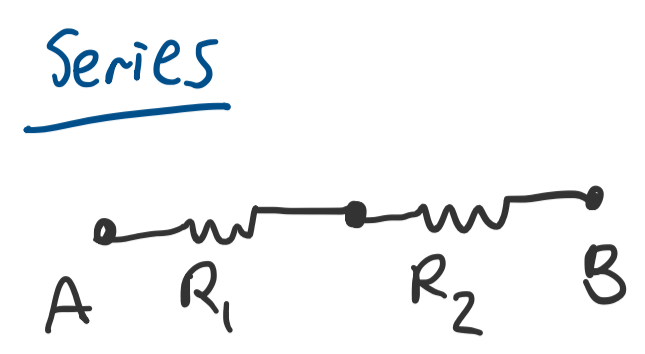
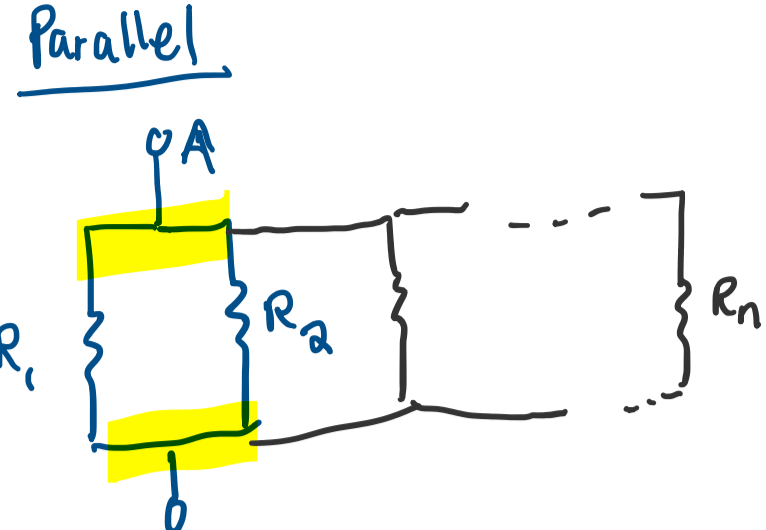


Feedback form: tinyurl.com/anusha16afeedback

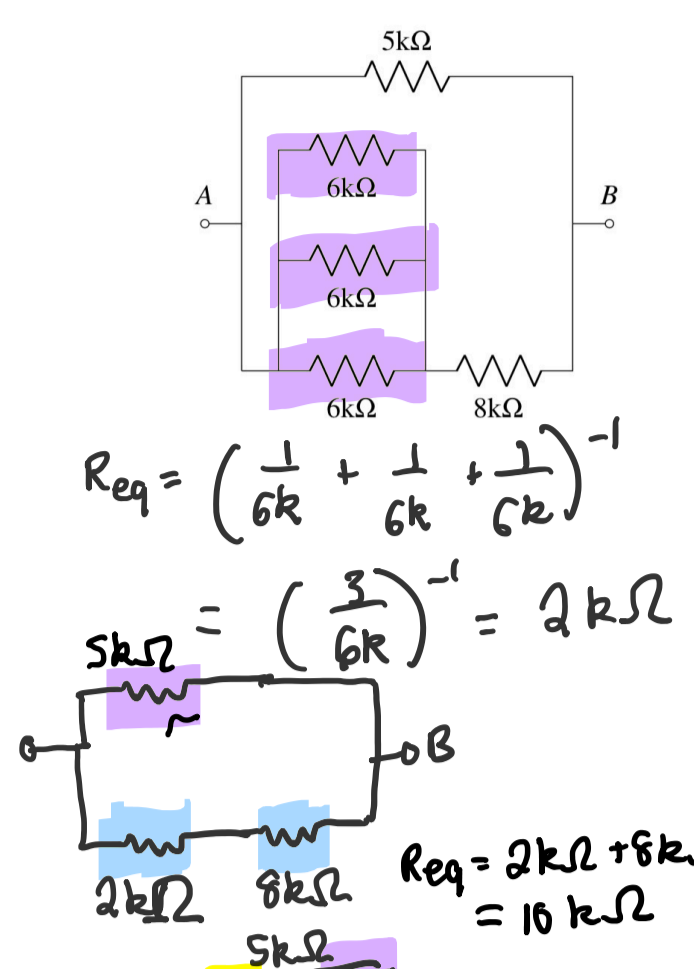1. Series and Parallel Combinations

For the resistor network shown below, find an equivalent resistance between the terminals A and B using the resistor combination rules for series and parallel resistors.




$$R_{eq} = \left(\frac{1}{6k} + \frac{1}{6k} + \frac{1}{6k} \right)^{-1}$$

$$= \left(\frac{3}{6k} \right)^{-1} = 2k\Omega$$

$$R_{eq} = \left(\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N} \right)^{-1}$$

$$R_{eq} = R_1 + R_2$$

$$R_{eq} = R_1 + R_2 + \dots + R_N$$

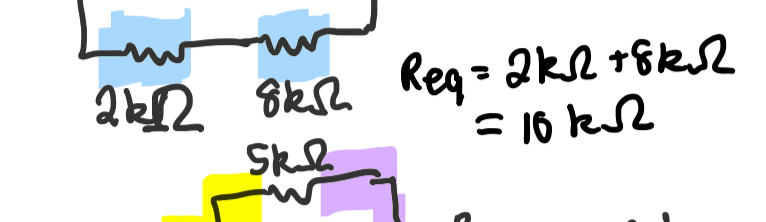


$$R_{eq} = 2k\Omega + 6k\Omega = 10k\Omega$$

$$R_{eq} = \left(\frac{1}{5k} + \frac{1}{10k} \right)^{-1} = \left(\frac{2}{10} + \frac{1}{10k} \right)^{-1} = 3.33k\Omega$$

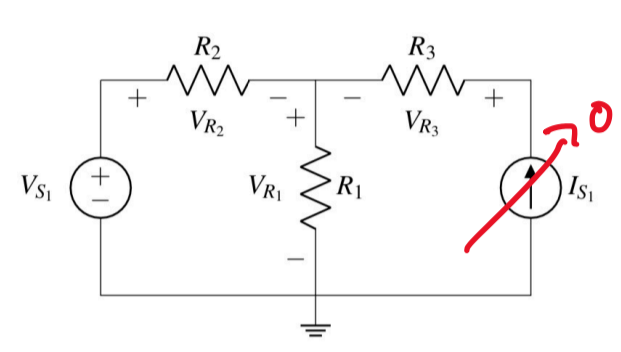
2. Superposition

For the following circuits:
i. Use the superposition theorem to solve for the voltages across the resistors. First, redraw the circuits with just one source (while zero-ing the other source). Then, for each circuit solve for each element voltage. Finally, sum the voltages at each node.





Superposition:

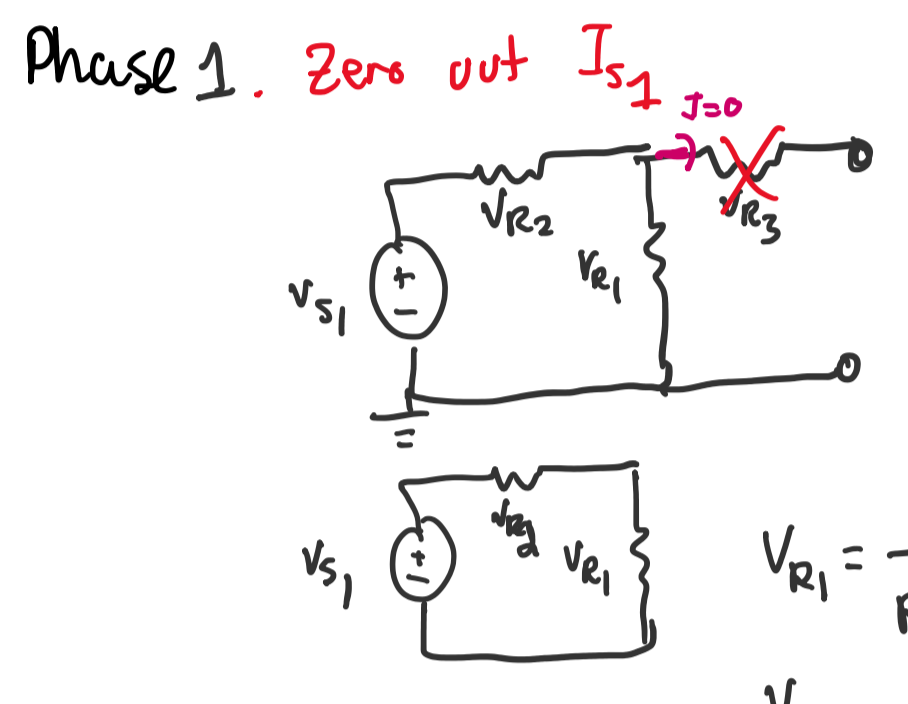1. Leave one independent source on at a time
2. Measure resulting voltages & currents
3. Sum up voltages & currents for final solution.




$$V_{R1} = \frac{R_1}{R_1 + R_2} \cdot V_{S1}$$
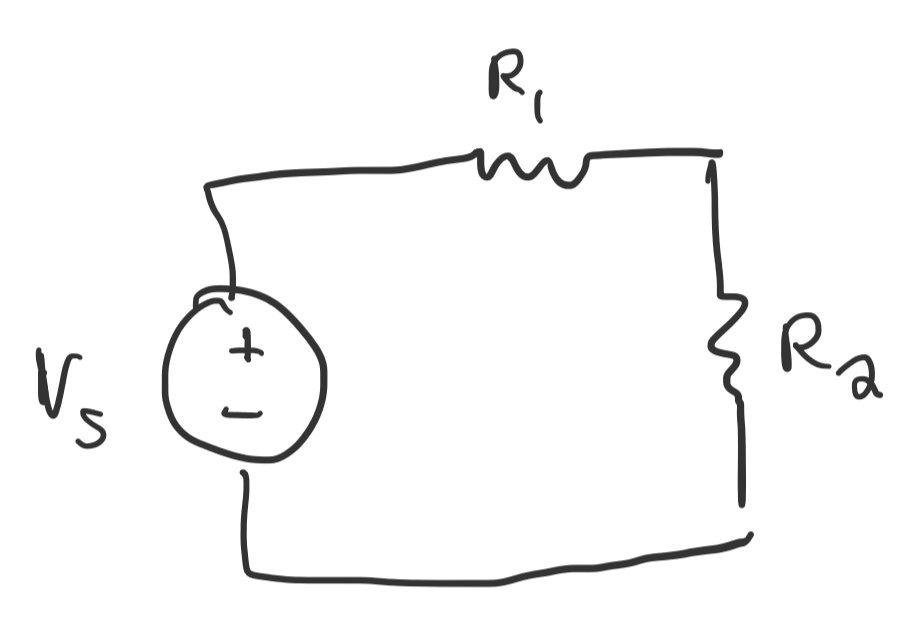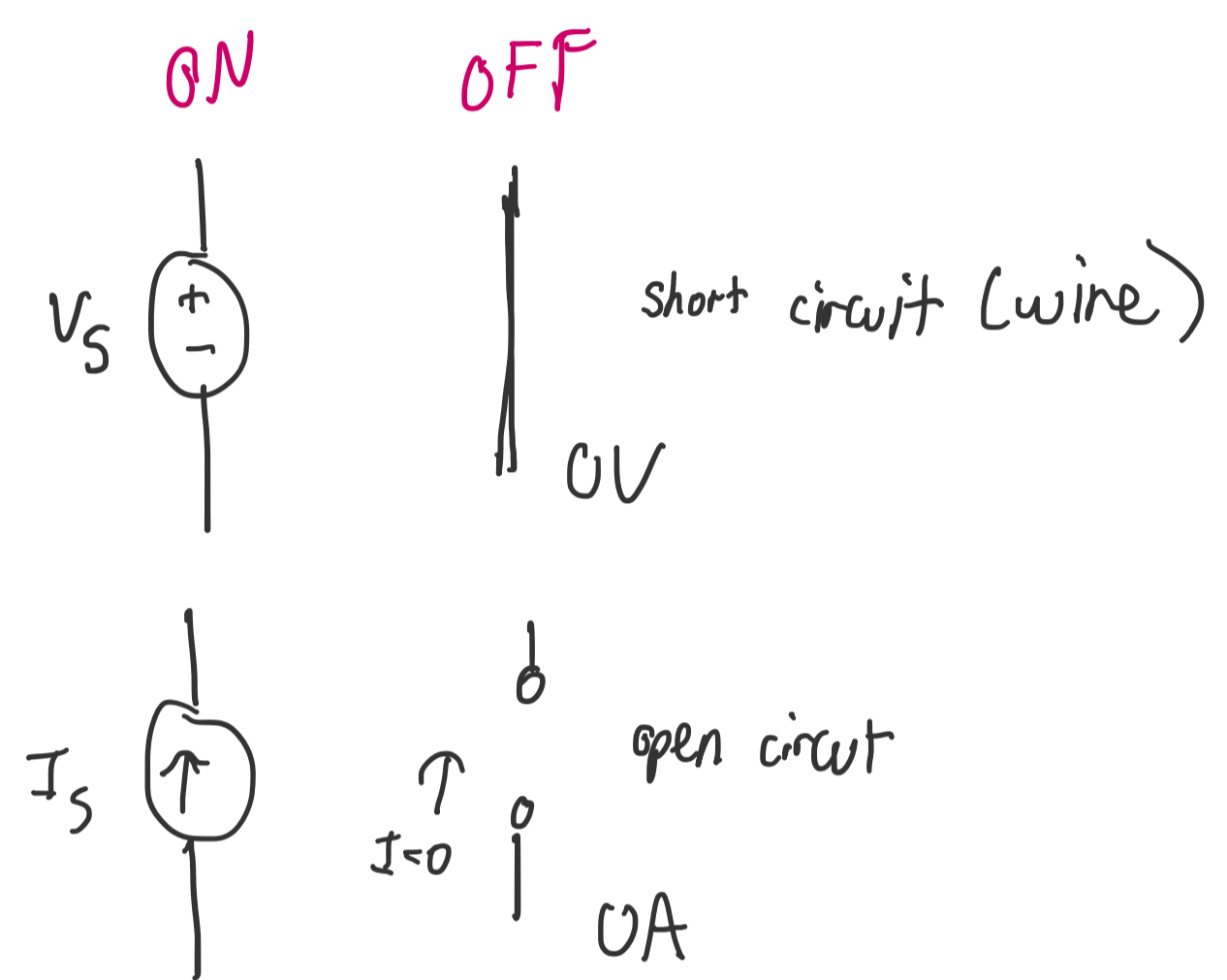
$$V_{R2} = V_{S1} - V_{R1} = \frac{R_2}{R_1 + R_2} \cdot V_{S1}$$


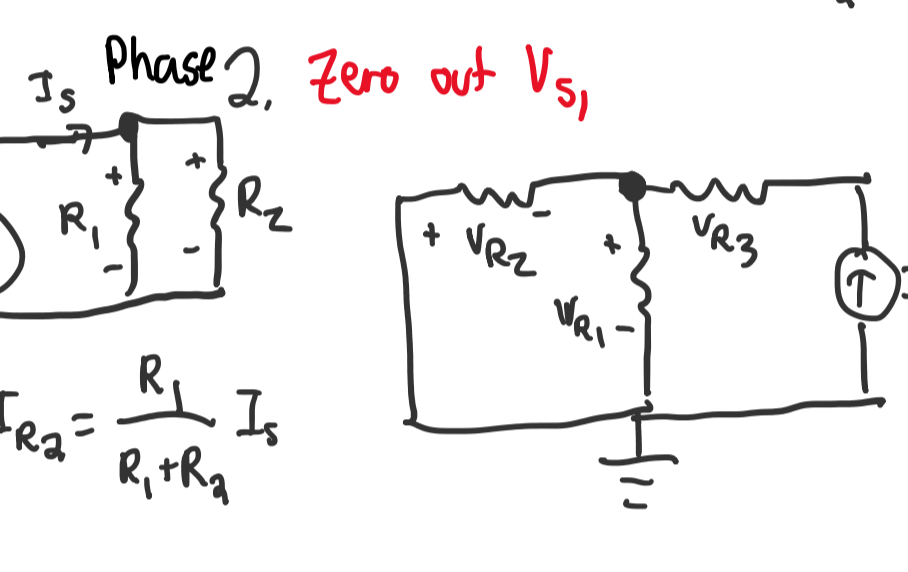
$$V_{R2} = \frac{R_2}{R_1 + R_2} \cdot V_S$$



$$I_{R2} = \frac{-R_1}{R_1 + R_2} I_{S1}$$

$$I_{R1} = \frac{R_2}{R_1 + R_2} I_{S1}$$

$$V = IR$$

$$V_{R2} = \frac{-R_1}{R_1 + R_2} I_{S1} \cdot R_2$$

$$V_{R1} = \frac{R_2}{R_1 + R_2} I_{S1} \cdot R_1$$

$$I_{R3} = I_{S1}$$

$$V_{R3} = I_{S1} \cdot R_3$$


$$V_{R1} = \frac{R_2}{R_1 + R_2} I_{S1} \cdot R_1 + \frac{R_1}{R_1 + R_2} V_{S1}$$

$$V_{R2} = \frac{-R_1}{R_1 + R_2} I_{S1} \cdot R_2 + \frac{R_2}{R_1 + R_2} V_{S1}$$

$$V_{R3} = I_{S1} \cdot R_3$$

Added voltages from phases 1 and 2

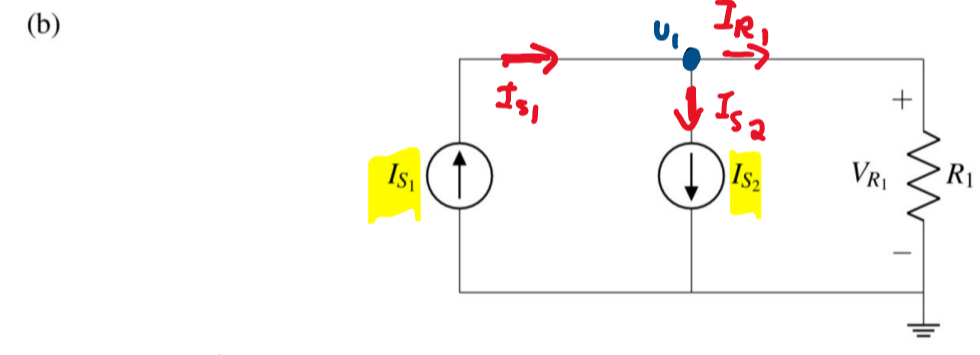Note: Polarities in phases 1 & 2 must remain the same when using superposition



KCL @ u_1 : $I_{S1} = I_{S2} + I_{R1}$


$$I_{S1} - I_{S2} = I_{R1}$$

$$V_{R1} = I_{R1} \cdot R_1$$


$$V_{R1} = (I_{S1} - I_{S2}) \cdot R_1$$

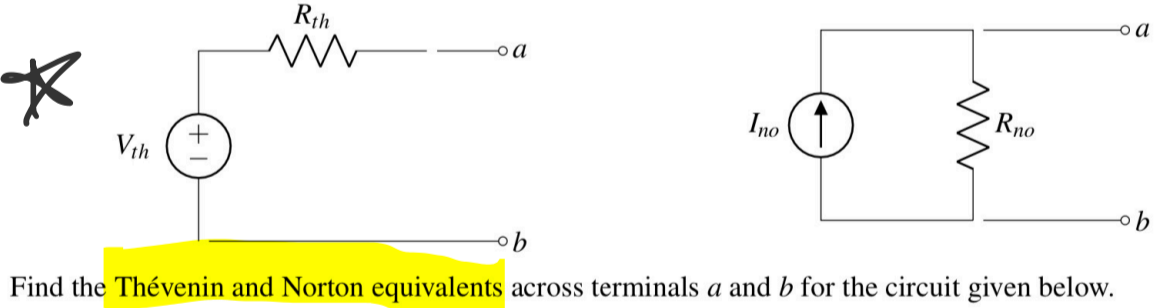3. Thevenin and Norton Equivalence

The general Thevenin and Norton equivalents are shown below:



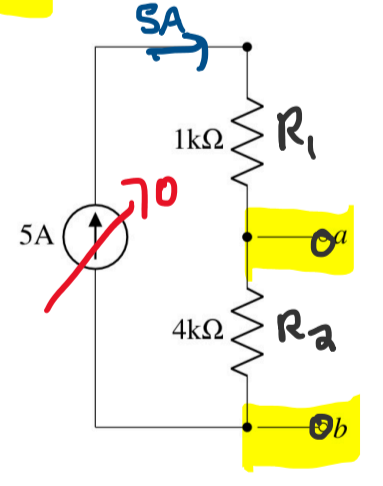Find the Thevenin and Norton equivalents across terminals a and b for the circuit given below.



Thevenin!

1. Connect open circuit across terminals to measure V_{th} .
2. Zero out independent sources and apply a test current/voltage to find R_{th} .

Norton!

1. Connect short circuit across terminals to measure I_{No} .
2. Zero out independent sources and apply a test current/voltage to find R_{th} .



1. Connect open ckt across terminals a & b

$$V_{Ra} = I_{R2} \cdot R_2$$

$$= 5A \cdot 4k\Omega$$

$$= 20kV$$


$$V_{th} = 20kV$$

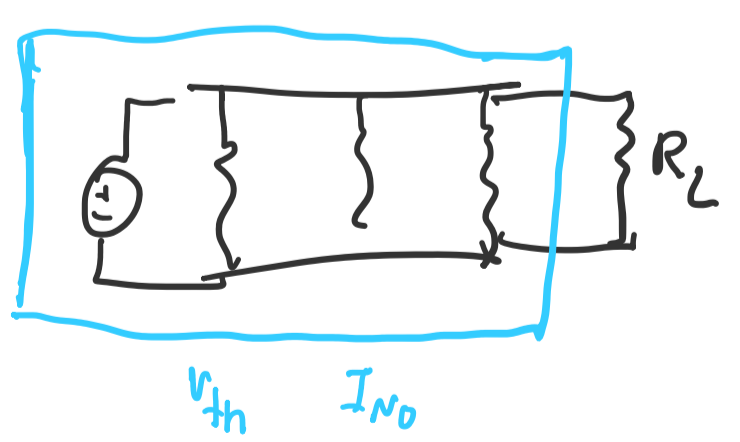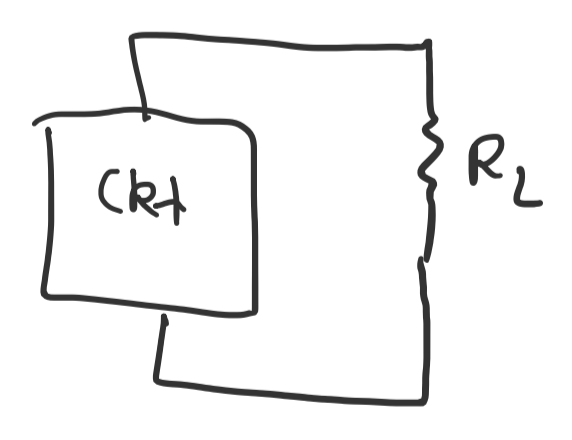

$$R_{th} = R_{No}$$

$$I_{No} = \frac{V_{th}}{R_{th}}$$

$$V_{th} = I_{No} R_{No}$$

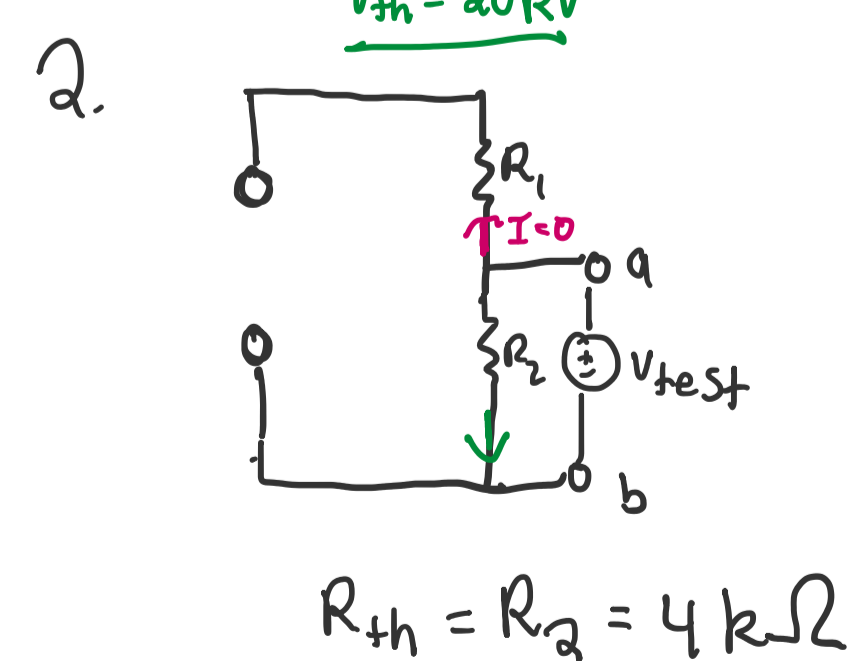

$$V_{R2} = V_{test}$$

$$I_{Ra} = I_{test}$$

$$R_{th} = \frac{V_{test}}{I_{test}} = \frac{V_{R2}}{I_{Ra}} = R_2$$

$$R_{th} = R_2 = 4k\Omega$$

$$\frac{V_{test}}{I_{test}} = R_2$$

$$R_{th} = 4k\Omega$$

$$I_{No} = \frac{V_{th}}{R_{th}} = 5A$$

