

Feedback form: [tinyurl.com/anushal6a-feedback](https://tinyurl.com/anushal6a-feedback)

1. Capacitors and Charge Sharing Revisited


(a) Consider two capacitors,  $C_A$  and  $C_B$  that have been charged to  $Q_{A1}$  and  $Q_{B1}$ , respectively. Compute the voltages across each one,  $V_{A1}$  and  $V_{B1}$ .

$Q = CV$


$Q_{A1} = C_A \cdot V_{A1}$

$\frac{Q_{B1}}{C_B} = V_{B1} \quad \frac{Q_{A1}}{C_A} = V_{A1}$

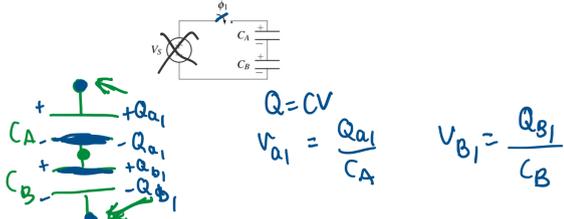(b) Consider the following circuit set up with an open switch. Given that these were the same charged capacitors as in the previous part, in phase 1, what is the charge and voltage across both capacitors before the switch is closed?



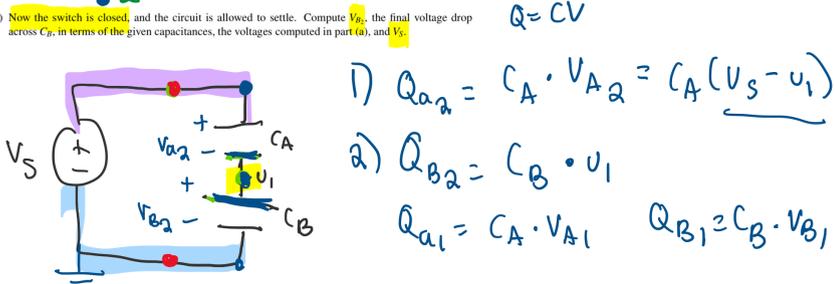(c) Now the switch is closed, and the circuit is allowed to settle. Compute  $V_{B2}$ , the final voltage drop across  $C_B$ , in terms of the given capacitances, the voltages computed in part (b), and  $V_S$ .



@  $V_1$ :  $-Q_{A2} + Q_{B2} = -Q_{A1} + Q_{B1}$

$Q = CV$

$-[C_A(V_S - V_1)] + C_B \cdot V_1 = -C_A V_{A1} + C_B V_{B1}$



$V_{B2} = V_1 - 0 = V_1$

$-C_A V_S + C_A V_1 + C_B V_1 = -C_A V_{A1} + C_B V_{B1}$


$V_1 = \frac{-C_A V_{A1} + C_B V_{B1} + C_A V_S}{C_A + C_B} = V_{B2}$

Charge Sharing Algorithm:

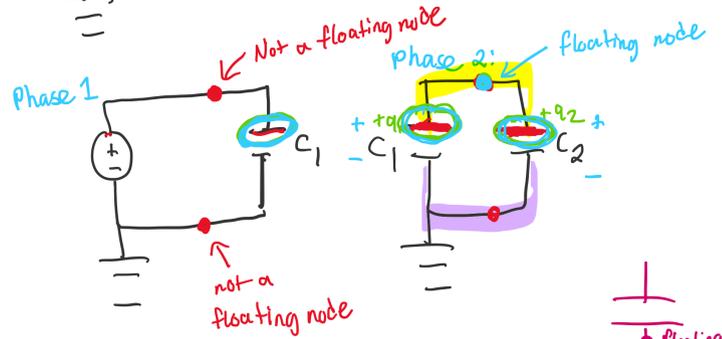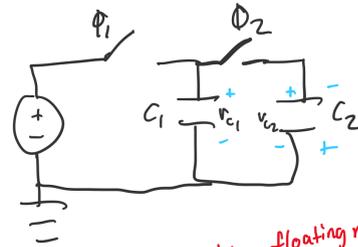1. Label capacitor voltages and choose polarities to be used for rest of the algorithm
2. Draw circuit for each phase
3. In phase 2, label floating nodes
4. For each floating node, solve for  $Q^{\phi_2}$
5. Solve for  $Q^{\phi_2}$
6. Equate  $Q^{\phi_1} = Q^{\phi_2}$  due to charge conservation
7. Repeat steps 4-6 for each floating node



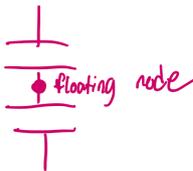Floating node: charge doesn't flow in/out of the node




$Q_2: Q_{C1}^{\phi_2} + Q_{C2}^{\phi_2} = Q_{C1}^{\phi_1}$

Equate charges on plates in phase 2 from charges on plates during phase 1


$Q_2 = \text{phase 2}$

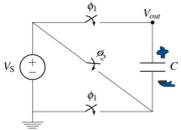2. Voltage Booster


We have made extensive use of resistive voltage dividers to reduce voltage. What about a circuit that boosts voltage to a value greater than the supply  $V_S = 5V$ ? We can do this with capacitors!



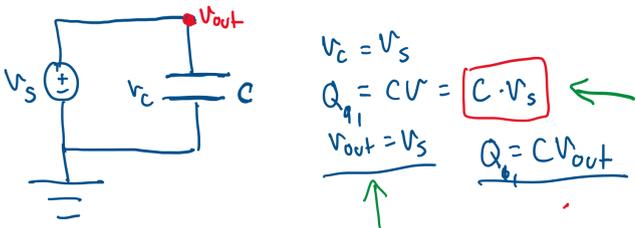(a) In the circuit above switches  $\phi_1$  are initially closed and switch  $\phi_2$  is initially open. Calculate the value of the output voltage,  $V_{out}$  with respect to ground, and the amount of charge stored on capacitor,  $C$ , at that state (phase 1).



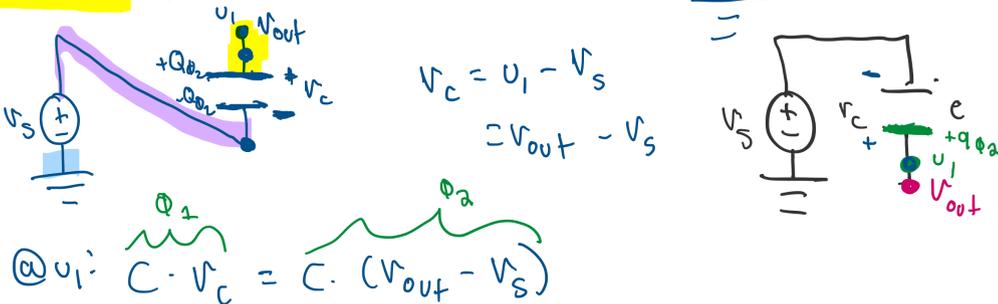(b) Now, after the capacitors are charged, switches  $\phi_1$  are opened and switch  $\phi_2$  is closed. Calculate the new voltage output voltage,  $V_{out}$  at steady state.



$C \cdot (V_{out} - V_S) = C \cdot V_S$

$+Q_{\phi_2} \quad +Q_{\phi_1}$

$C \cdot V_{out} - C V_S = C V_S$

$2 \cdot V_{out} = 2 V_S$

$V_{out} = 2 \cdot V_S$