

# Welcome to EECS 16A!

## Designing Information Devices and Systems I


Ana Claudia Arias and Miki Lustig  
Fall 2021

Module 2  
Lecture 1

Introduction to Circuit Analysis  
(Note 11)


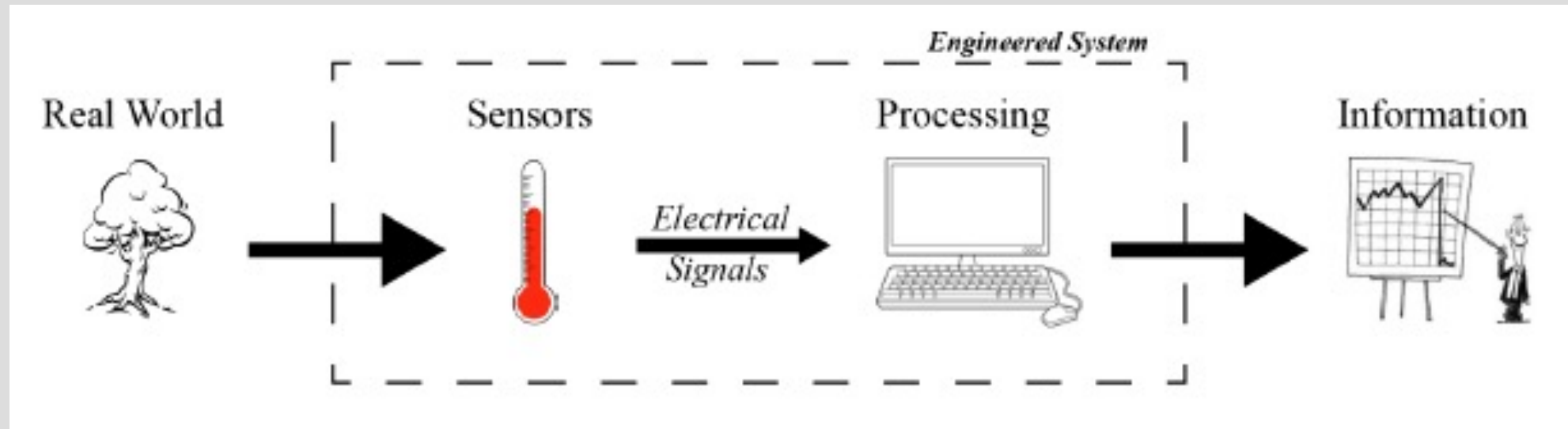
# Designing Information Devices and Systems



# Module 2 – More tools to build systems

Analog World

Sensor

Processing

Actuation

# Module 2 – More tools to build systems

Analog World

Sensor

Processing

Actuation




# Module 2 – More tools to build systems

Analog World

Sensor

Processing

Actuation

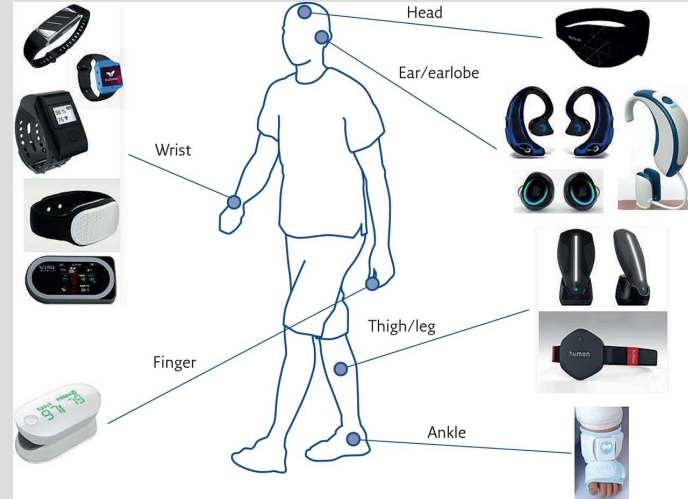

# Module 2 – More tools to build systems



16B

Analog World

Sensor


Processing

Actuation

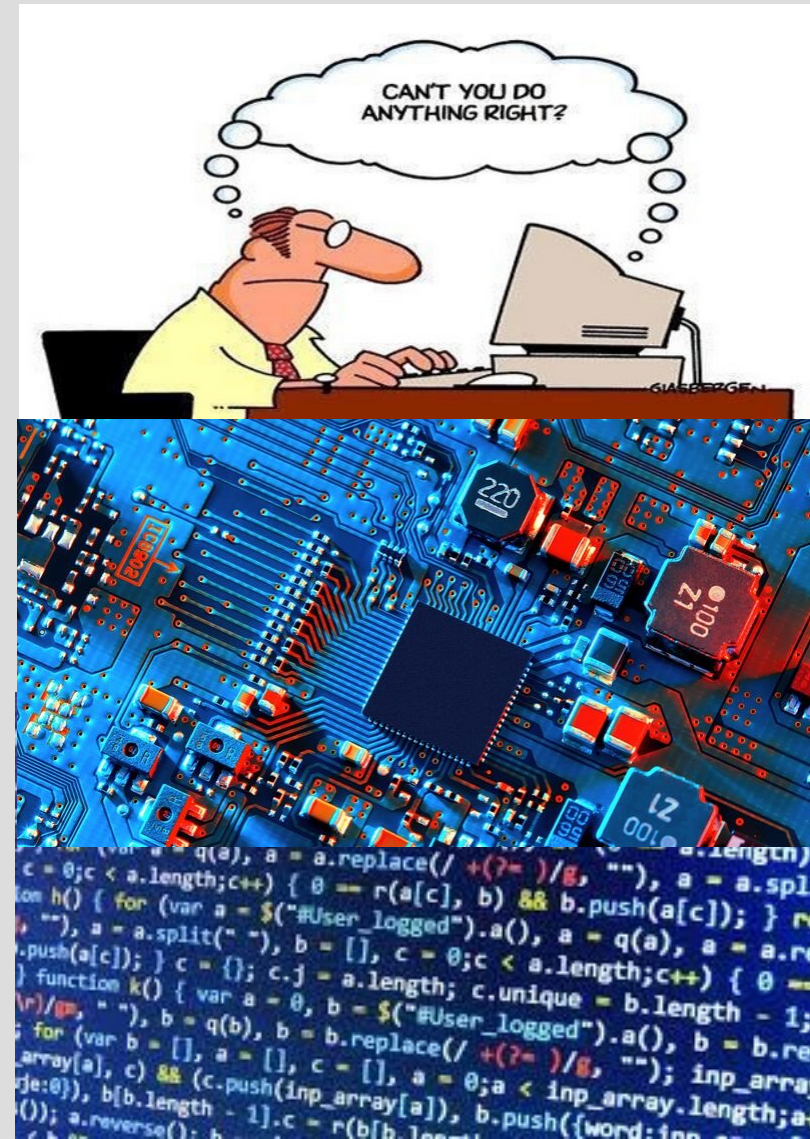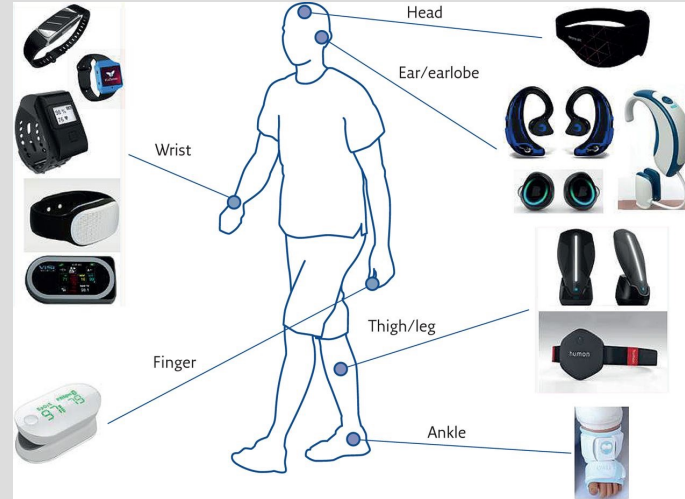
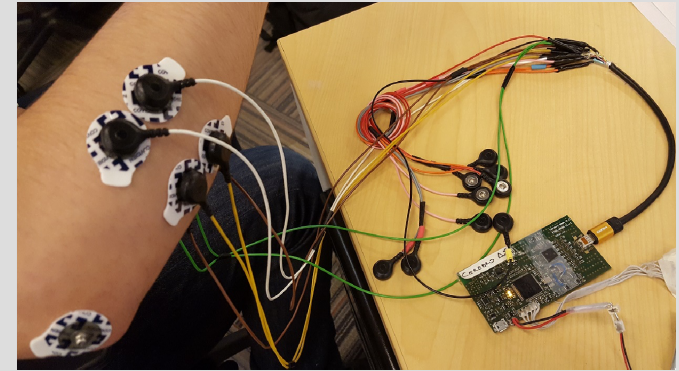
# System Example - Electromyography

- ✓ Monitors muscle activity
- ✓ Used in gesture recognition
- ✓ Impact in rehabilitation
- ✗ Bulky electrodes
- ✗ Poor accuracy – low resolution
- ✗ Computation performed on external devices




# System Example - Electromyography





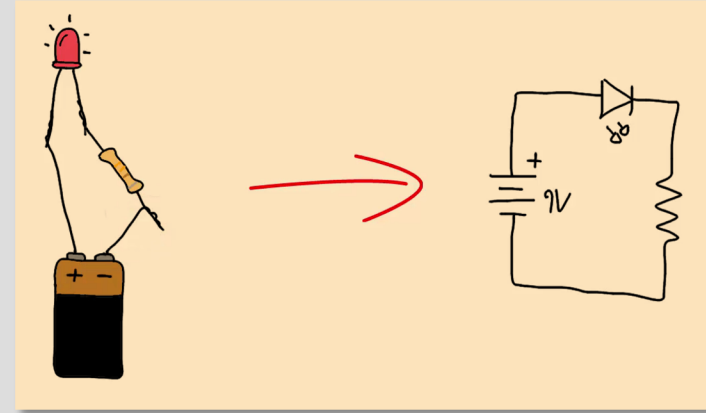
# In Module 2 we will learn how to analyze circuits

We need to be able to go from a real-world circuit, to a circuit model, and vice versa.


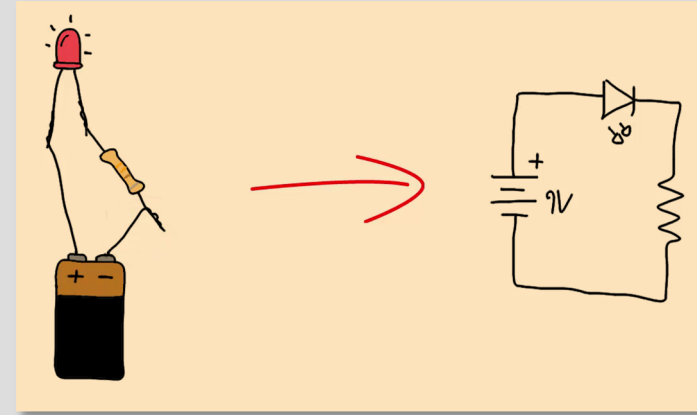
# In Module 2 we will learn how to analyze circuits

We need to be able to go from a real-world circuit, to a circuit model, and vice versa.




## CLASS

Introduction to  
Electrical  
Engineering

## HOPES



## REALITY

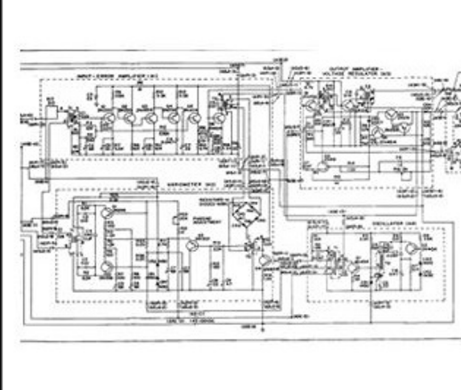

Then we need to know how to solve the model...

**Note:** the tool used by computers to analyze circuits is linear algebra!

# Electrical Circuit Analysis Algorithm (tool)


SPICE (Simulation Program with Integrated Circuit Emphasis): started as a student project at Berkeley!

Now the basis for open-source electronic circuit simulation, to design and model device characteristics and check circuit boards


**cadence**<sup>®</sup>  
**SYNOPSYS**<sup>®</sup>



Prof. Alberto L. Sangiovanni-Vincentelli

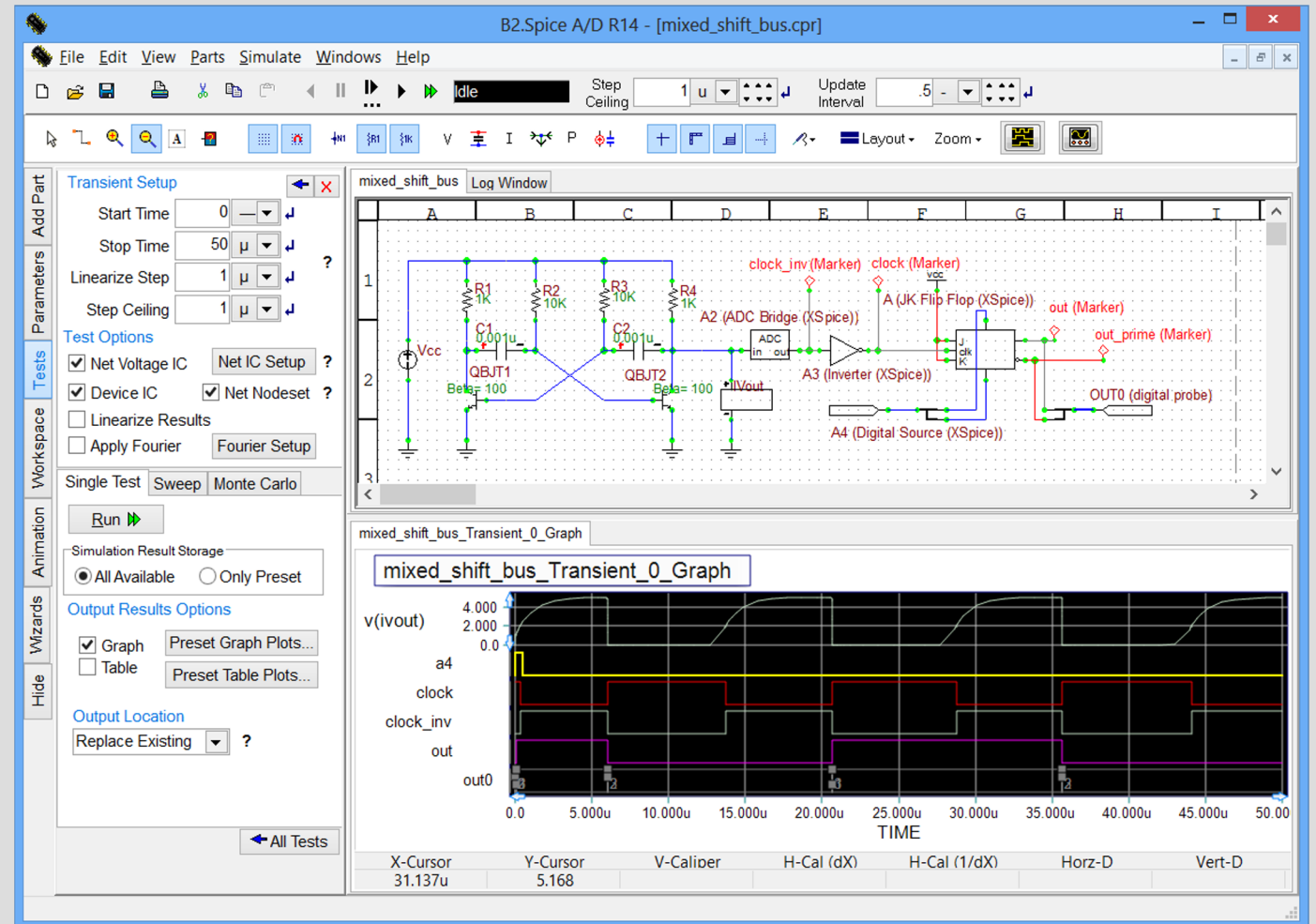
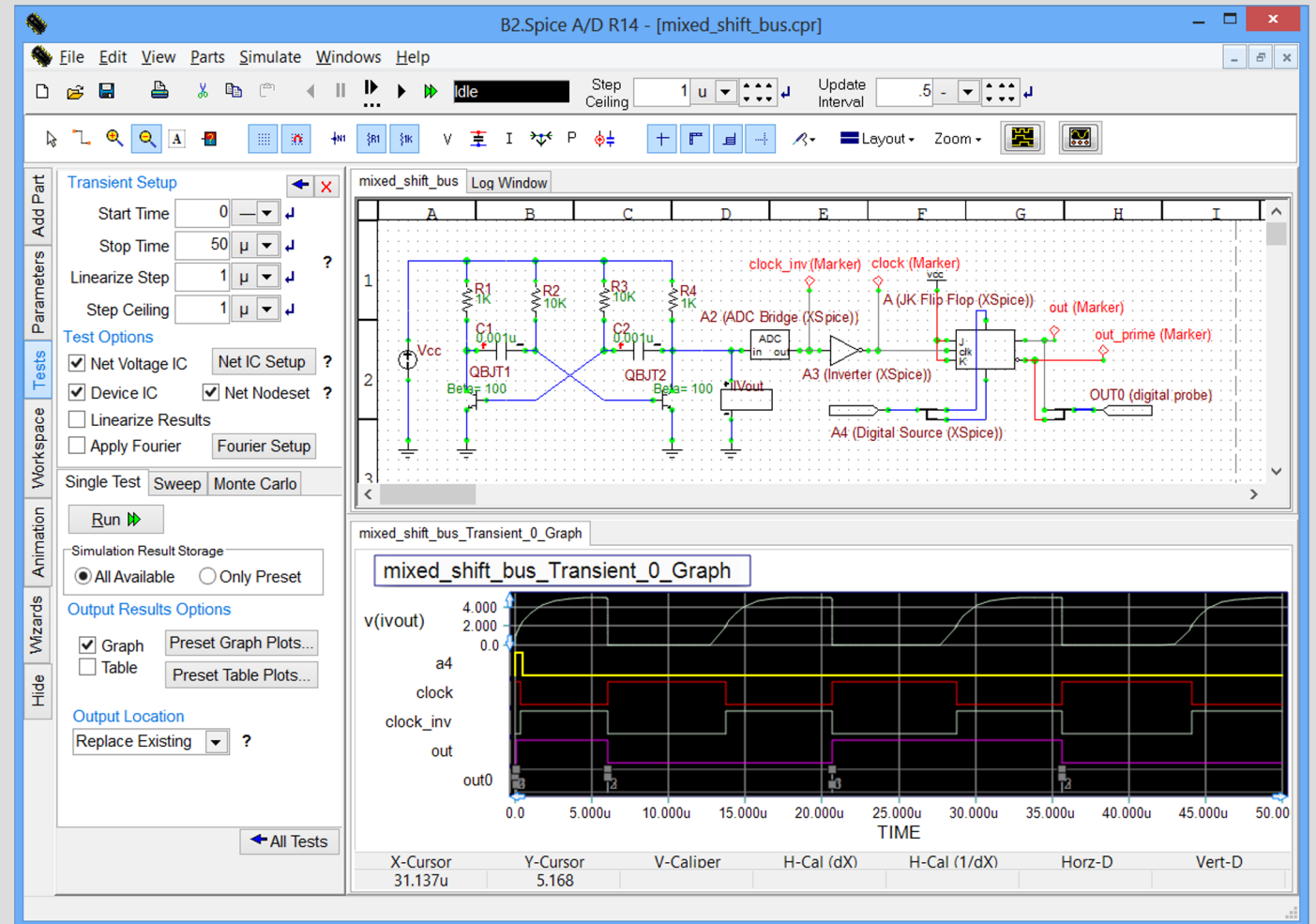
# Electrical Circuit Analysis Algorithm (tool)




# Definitions needed to analyze a circuit :quantities

Quantities	Analytical Symbol	Units
Current	$I$	Amperes [A]
Voltage	$V$	Volts [V]
Resistance	$R$	Ohms [ $\Omega$ ]

$I \Rightarrow$  flows through an element


$V \Rightarrow$  applied across an element

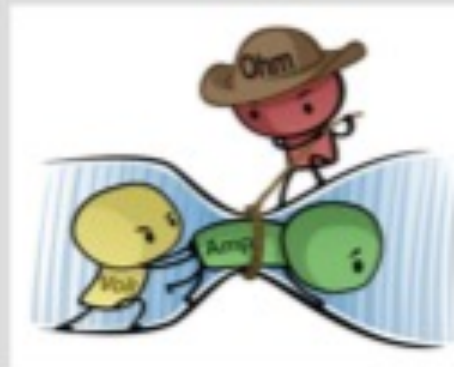$R \Rightarrow$  opposition to current flow




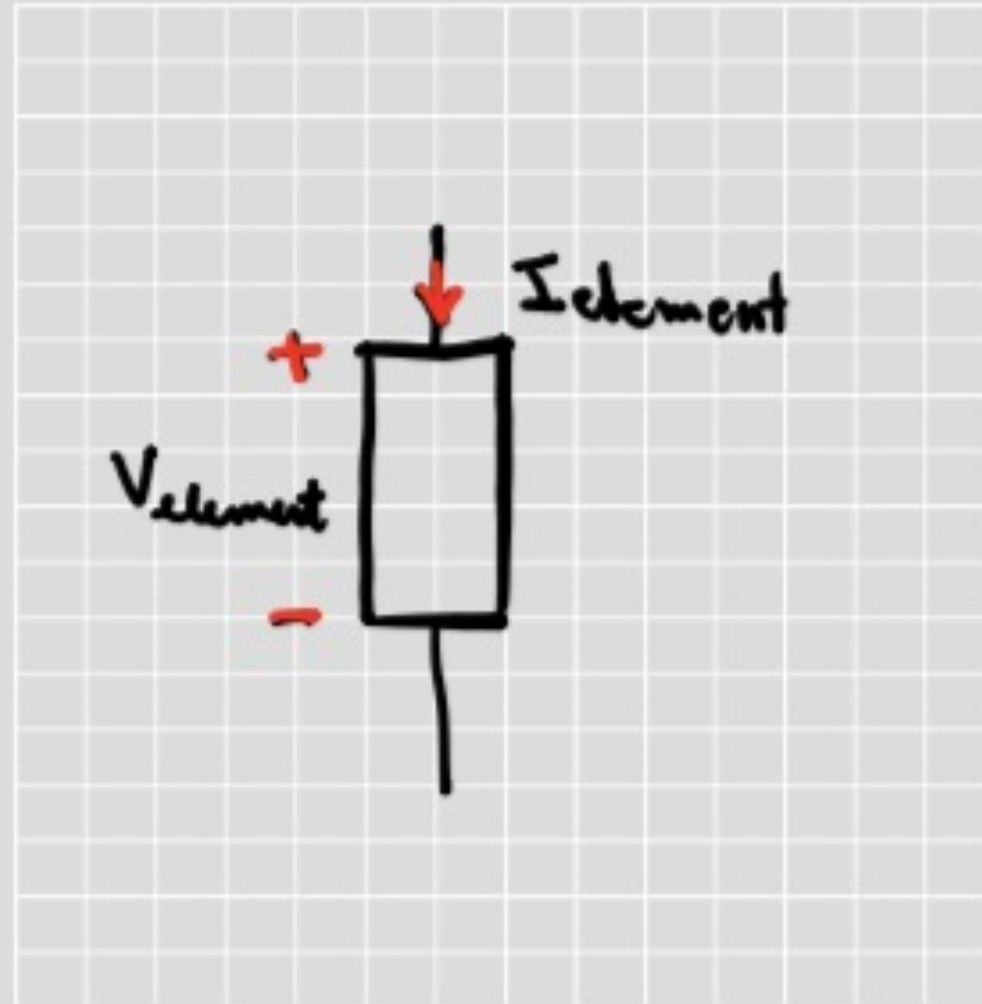
# Definitions needed to analyze a circuit : Circuit Diagram


Collection of elements, where each element has some voltage across it and some current through it



# Key circuit elements: Wire

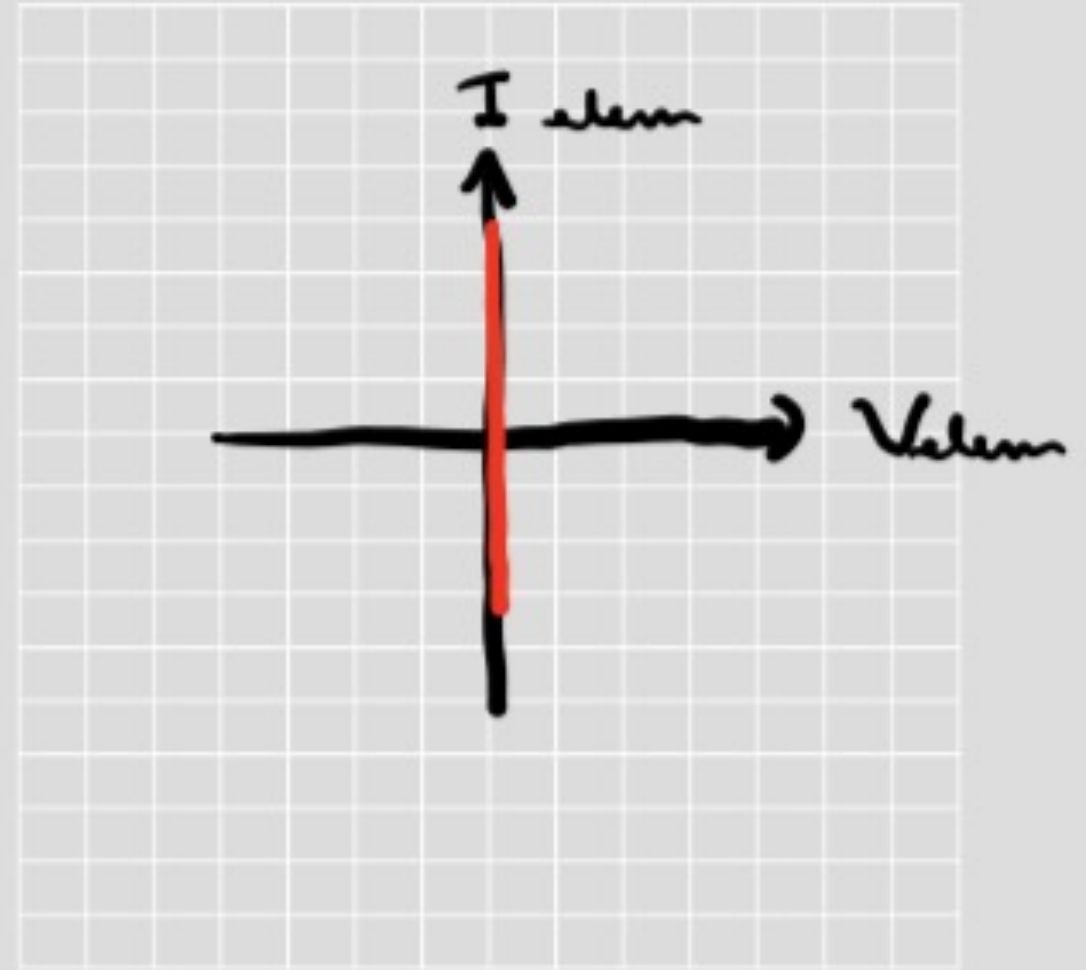
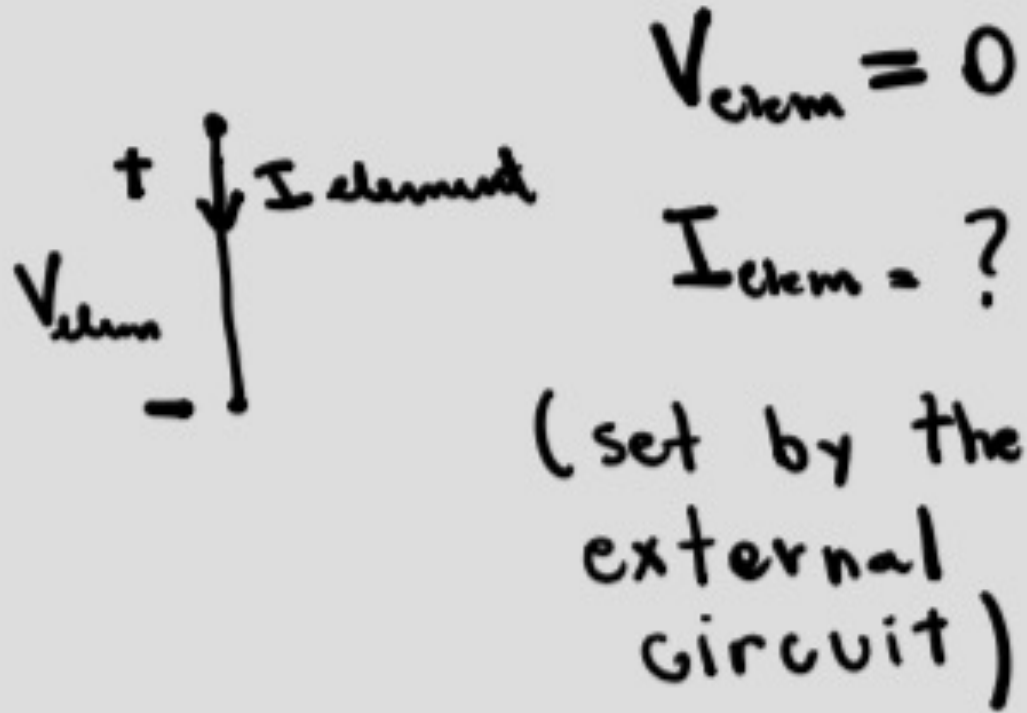


# Key circuit elements: Resistor

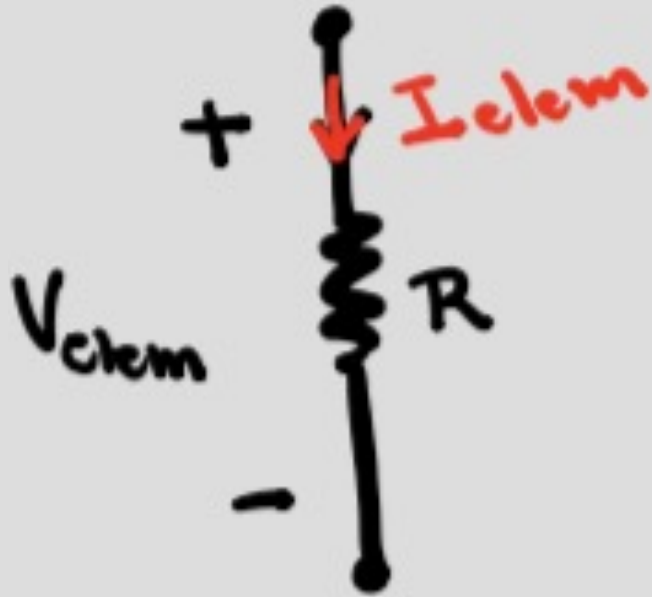



$$V_{elem} = R \cdot I_{elem}$$

(Ohm's law)

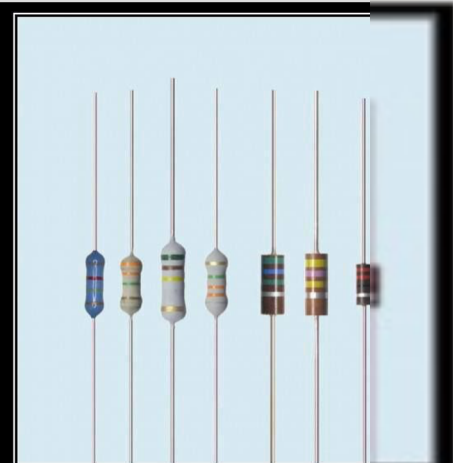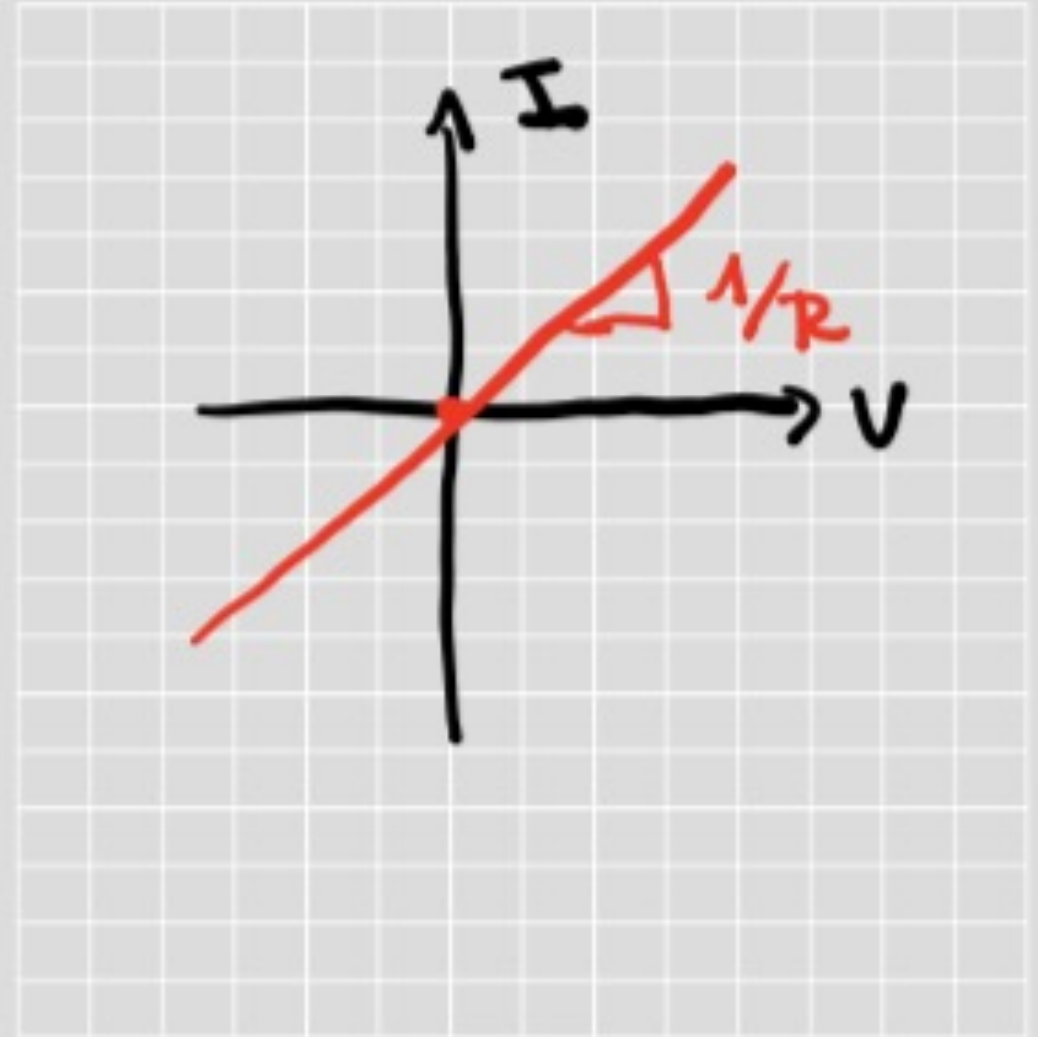




# Key circuit elements: Open circuit

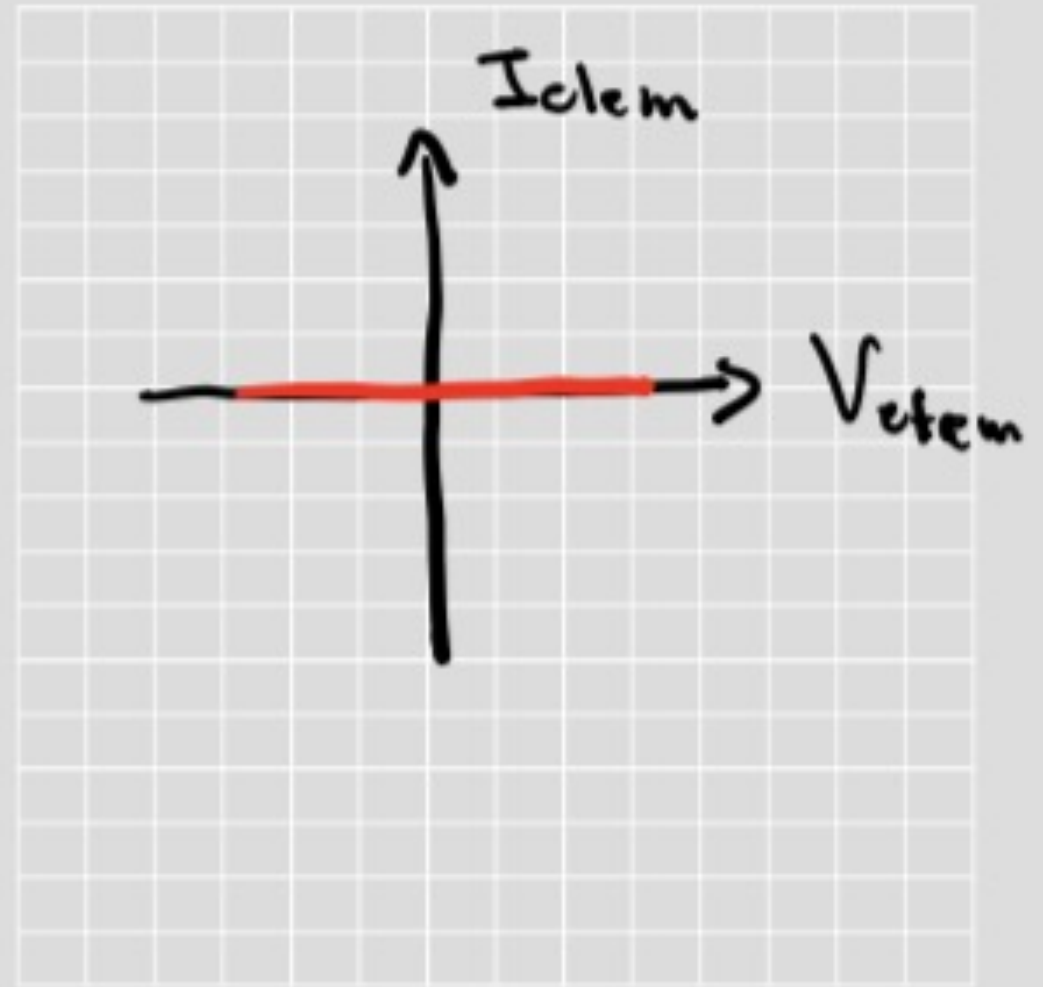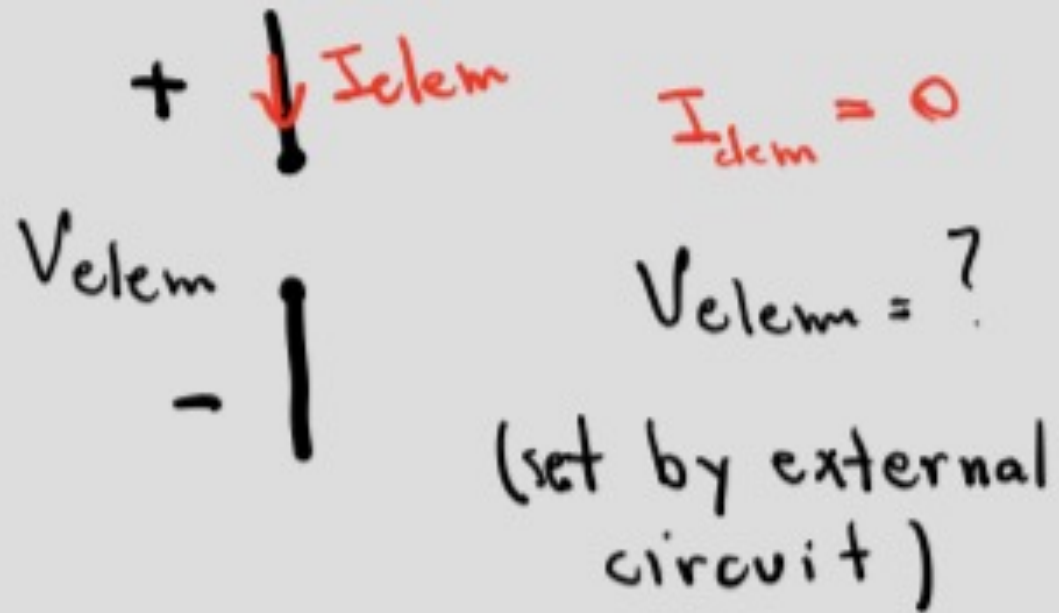



# Key circuit elements: Voltage Source

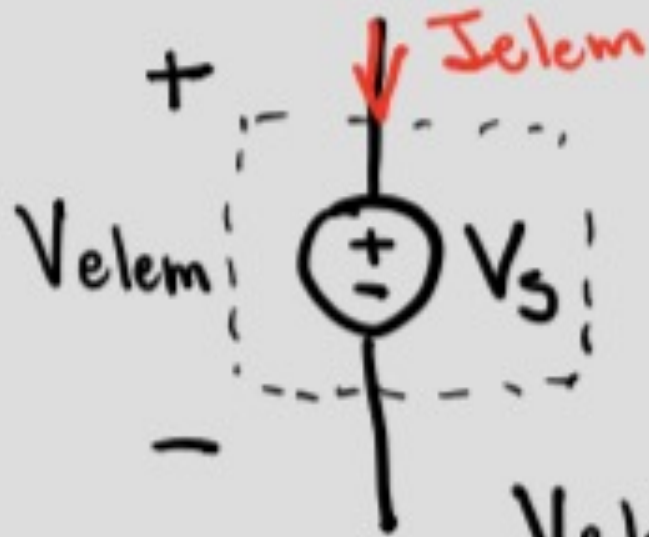


$$V_{elem} = V_s$$

$$I_{elem} = ?$$

(set by external circuit)

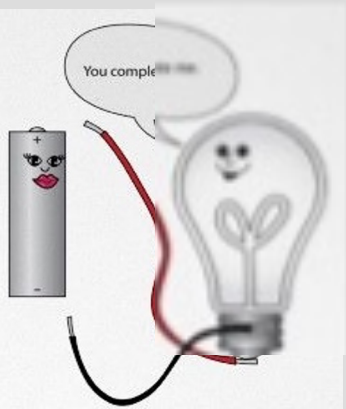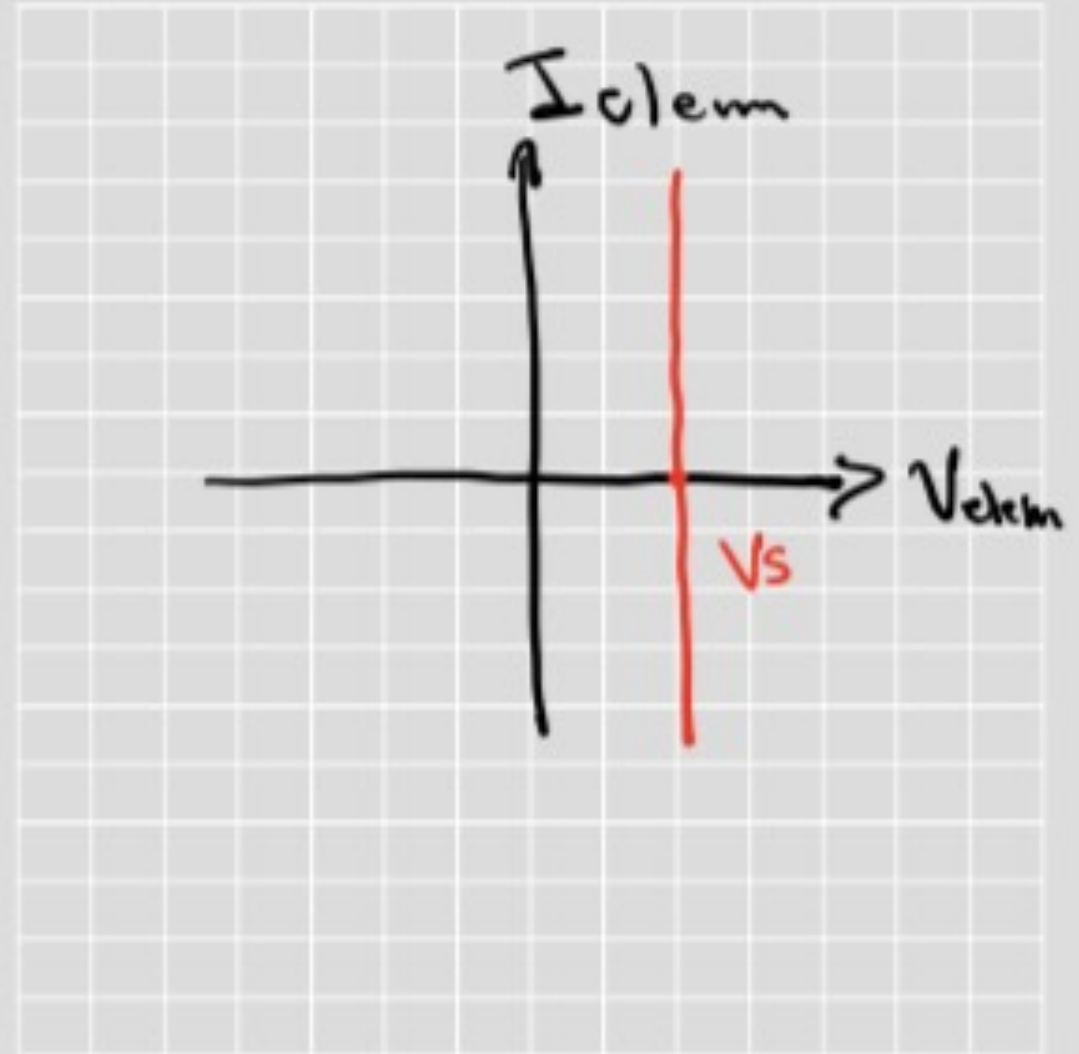


# Key circuit elements: Current Source

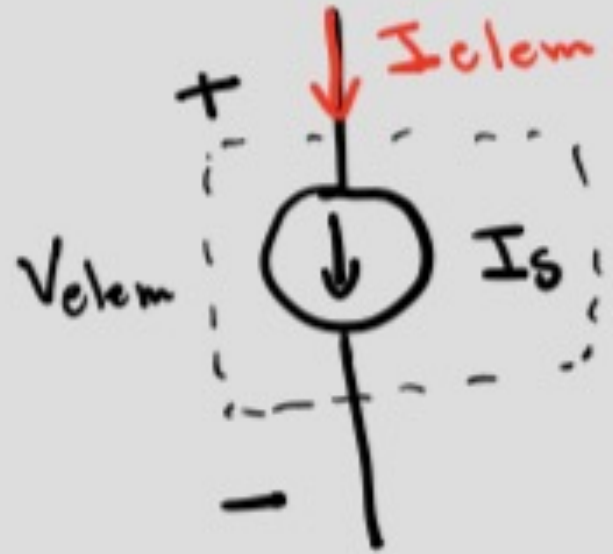

$$I_{elem} = I_s$$
$$V_{elem} = ?$$


(set by ext. circuit)

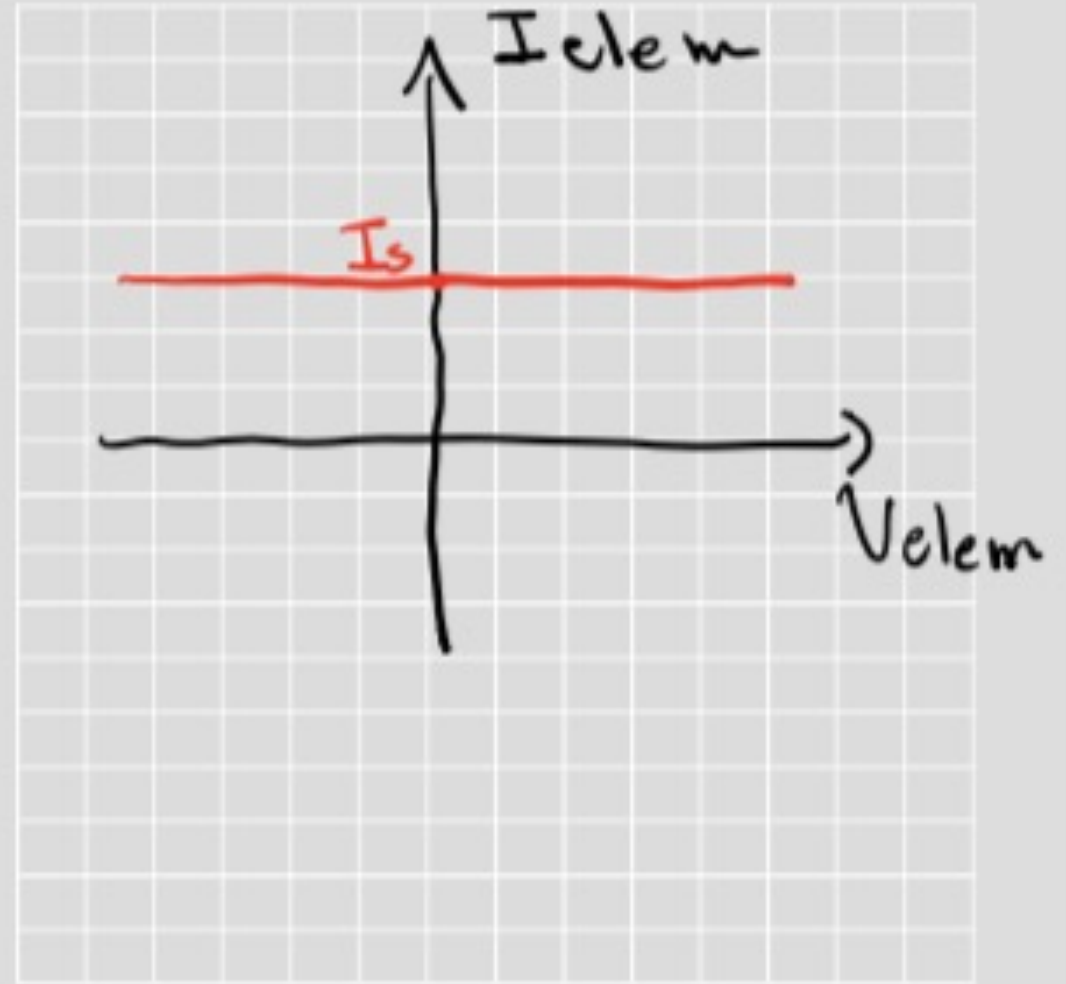


$V_{element}$  and  $I_{element}$  can be positive or negative
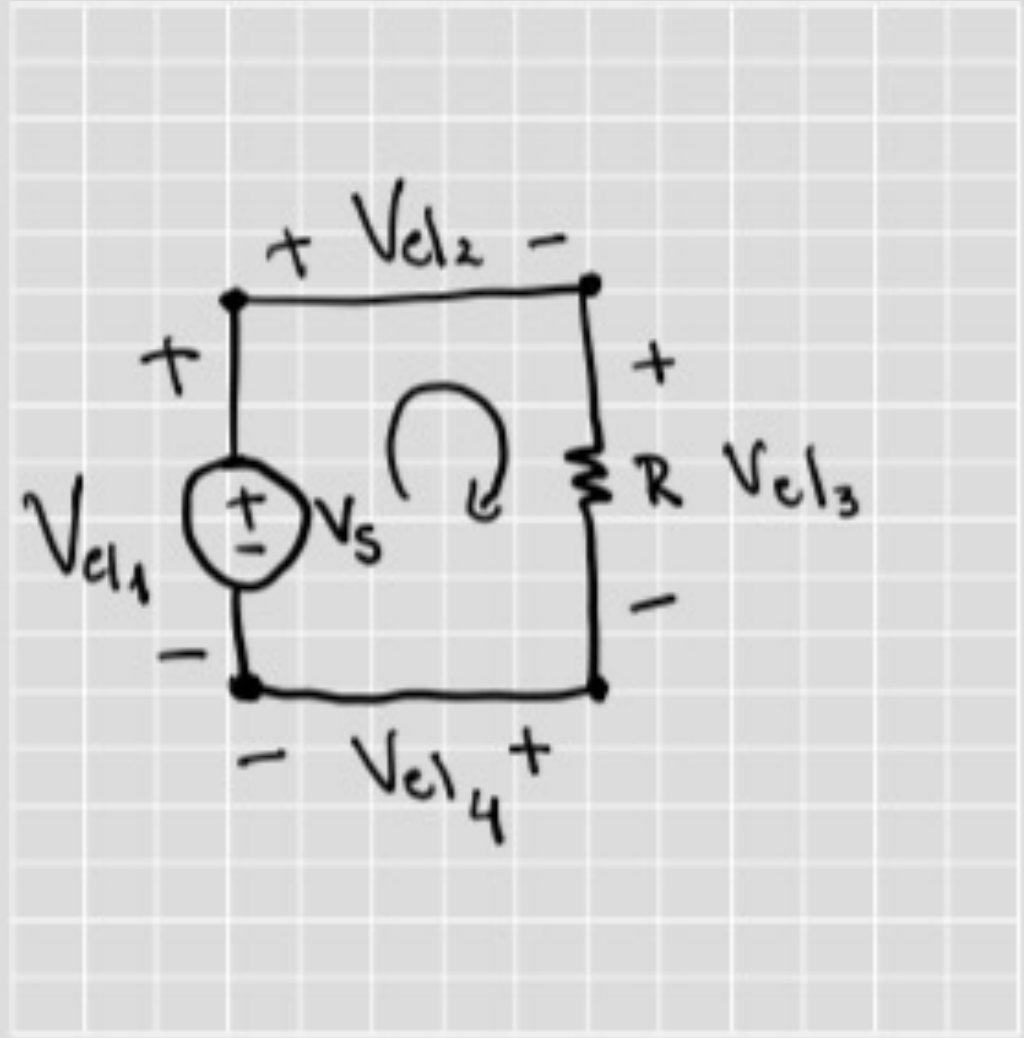
# Rules for circuit analysis: Kirchoff's Voltage Law (KVL)

Sum of Voltages across the elements in a loop equal zero



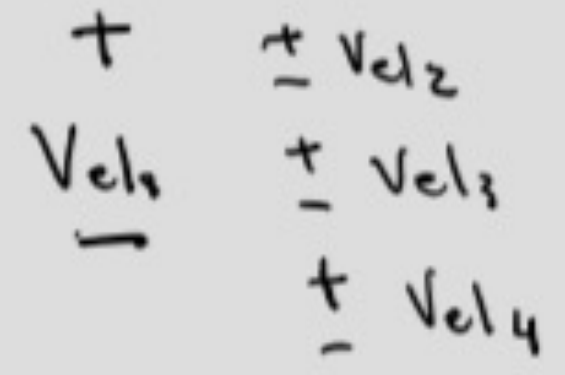
$$V_{e1} - V_{e2} - V_{e3} - V_{e4} = 0$$


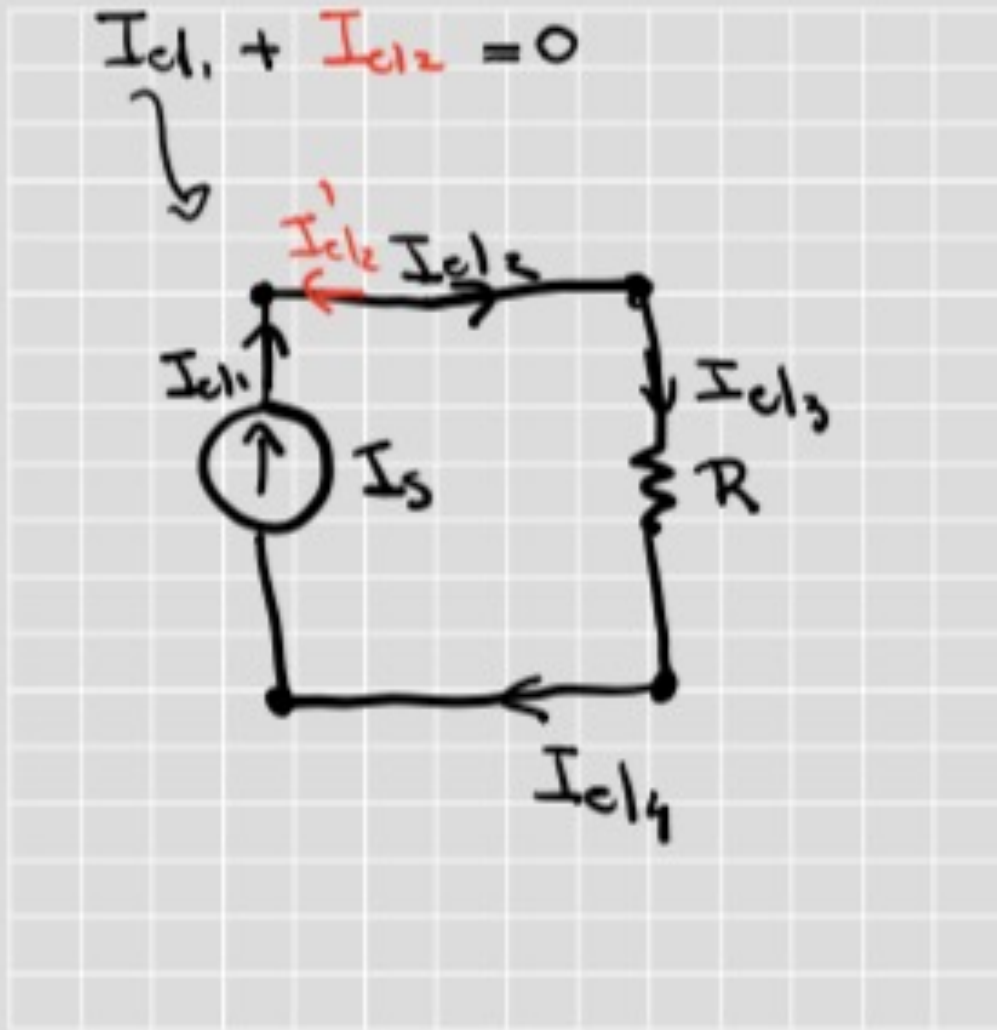
# Rules for circuit analysis: Kirchoff's Current Law (KCL)


The current flowing into any junction must equal the current flowing out



$$\begin{aligned} I_{c11} &= I_{c12} \\ I_{c12} &= I_{c13} \\ I_{c13} &= I_{c14} \\ \cancel{I_{c14}} &= \cancel{I_{c11}} \end{aligned}$$

$$I_{c12} - I_{c11} = 0$$


Example 2:

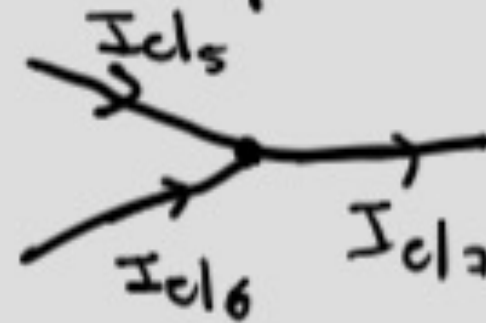

$$I_{c15} + I_{c16} = I_{c17}$$
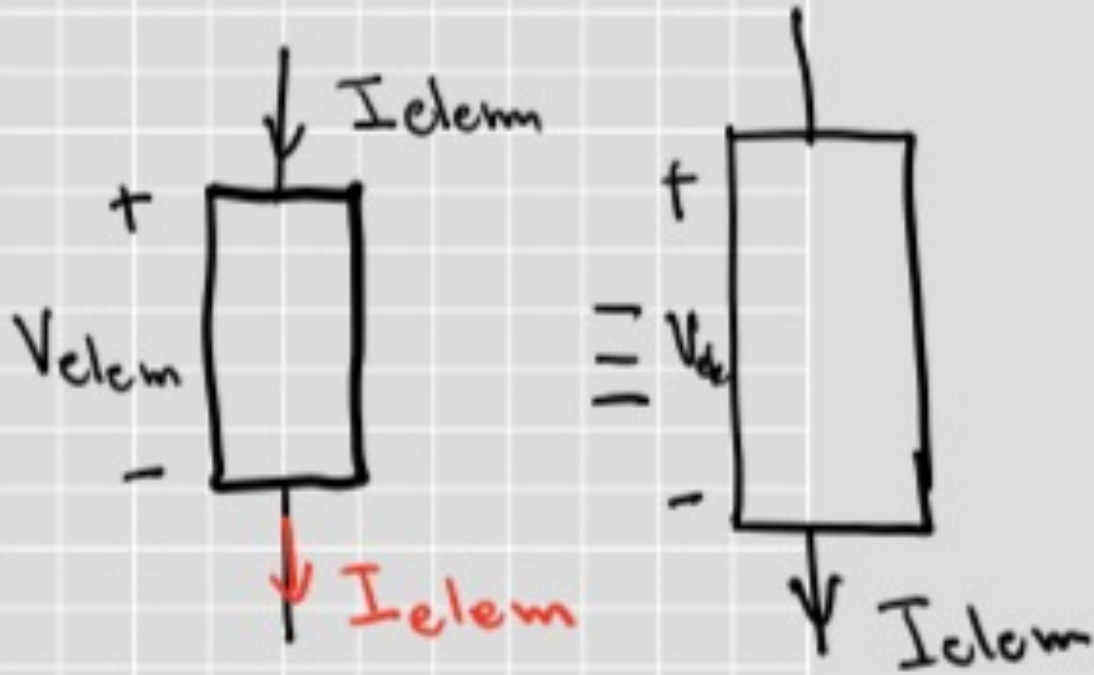
# Rules for circuit analysis: KCL within the element


The current flowing into any junction must equal the current flowing out



Same current!
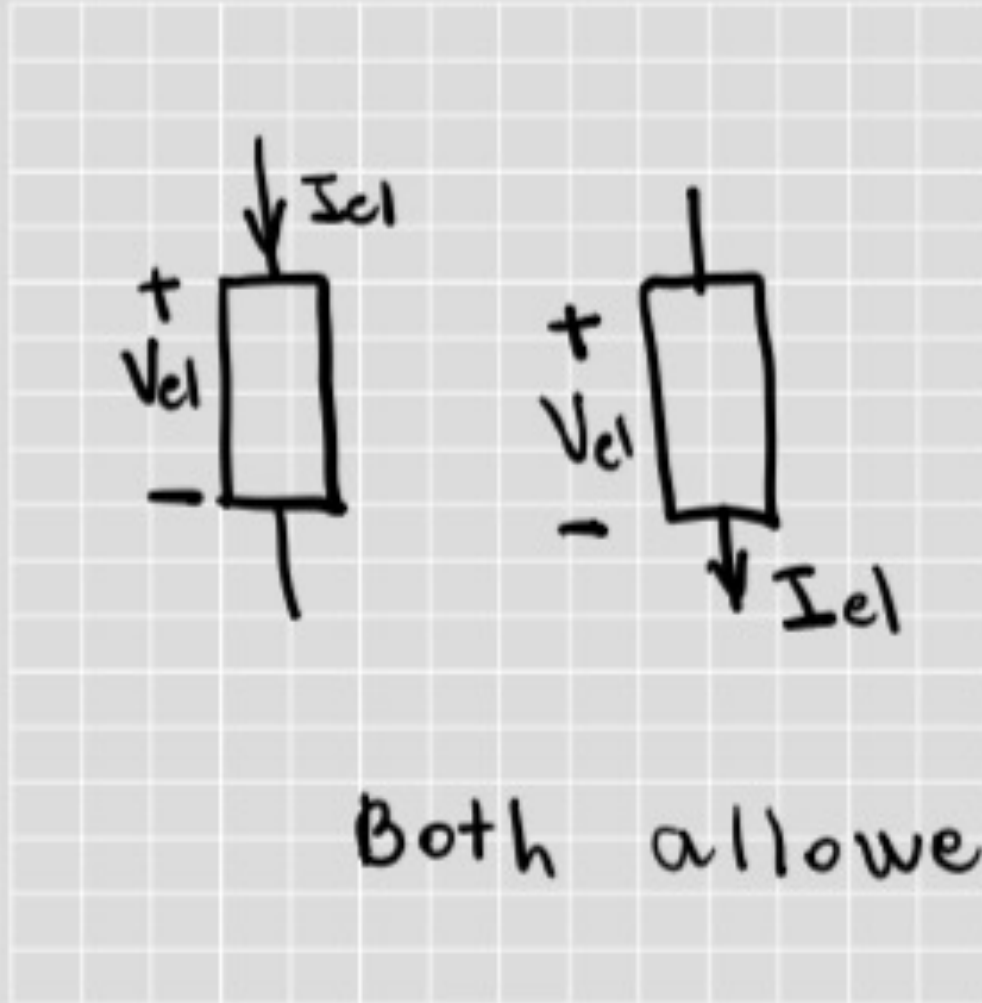
# Rules for circuit analysis: KCL within the element

The current flowing into any junction must equal the current flowing out




$I_{elem}$  goes into a  $\oplus$   
or out of a  $\ominus$  terminal

Passive sign convention
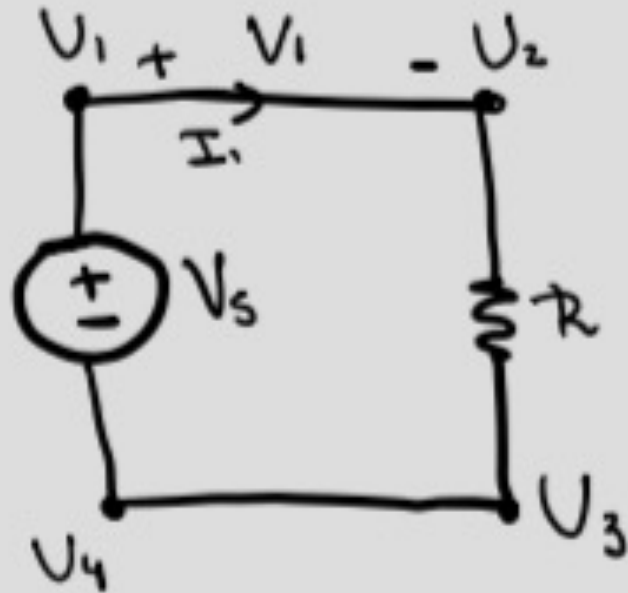
# Circuit Analysis Algorithm

Voltage = difference of two potential

**Find:** currents through elements and potentials of inputs/outputs of each element (junctions)



2 nodes

$U_1, U_2 \dots U_4 \rightarrow$  potentials

$$V_1 = U_1 - U_2 \text{ (Voltage)}$$

$I_1$  - current

Elem 1  $\rightarrow$  WIRE  $\mid \Rightarrow V_1 = 0$   
 $U_1 = U_2$




Collapse junctions with same potential into a node.


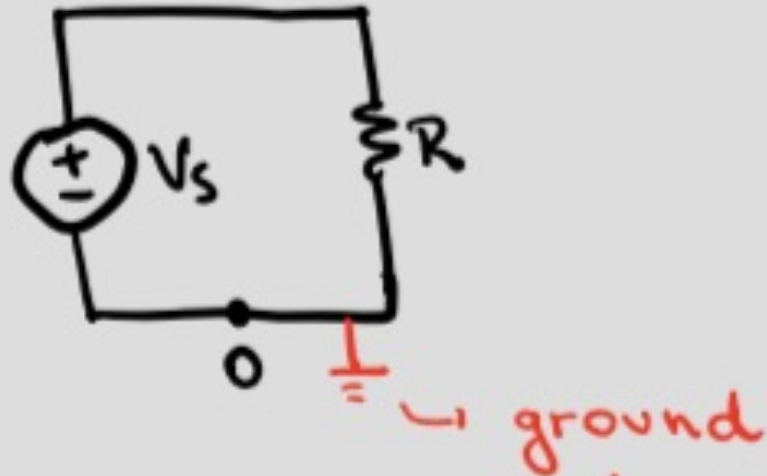
# Circuit Analysis Algorithm : step 1


Pick a reference node and label it as 0 potential. All voltages measured relative to this node.



↓  
Tells you where the reference is.
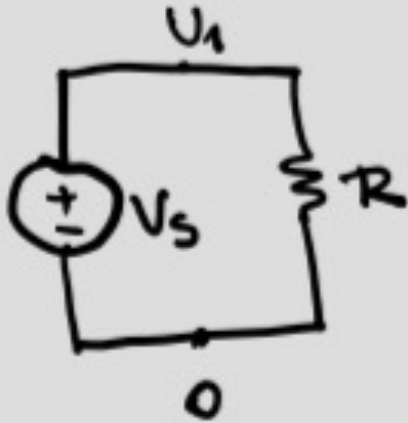
# Circuit Analysis Algorithm : step 2

Label all remaining nodes as potentials  $U_i$   
[ $U_1 \dots U_{N-1}$ ]



$$U_1 - 0 = U_1 = V$$


Voltage between  
node 1 and node "0"

# Circuit Analysis Algorithm : step 3

Label all branch currents with  $I_m$


Arbitrarily pick directions of  $I_m$

$[I_1 \dots I_k]$

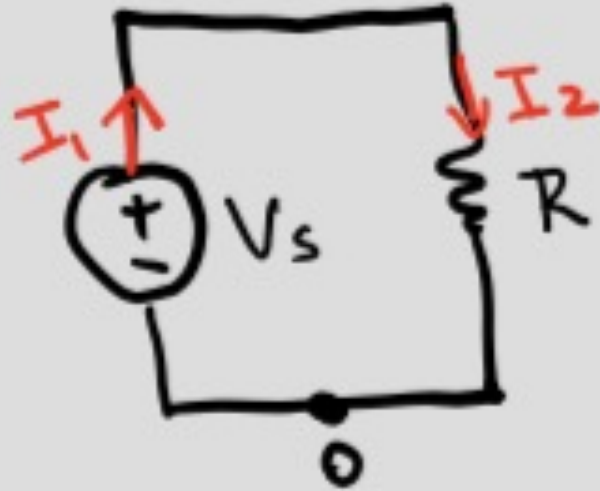
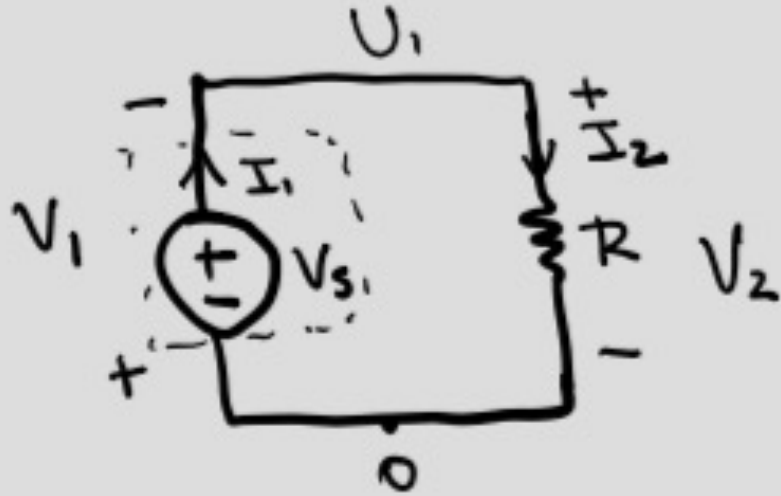
# Circuit Analysis Algorithm : step 4

Add signs + and - element voltages to each element following the passive sign convention



# Circuit Analysis Algorithm : step 5


Formulate  $A \vec{x} = \vec{b}$

$$\vec{x} = \begin{bmatrix} I_1 \\ \vdots \\ I_k \\ \vdots \\ I_{N-1} \end{bmatrix}$$

vector of unknowns
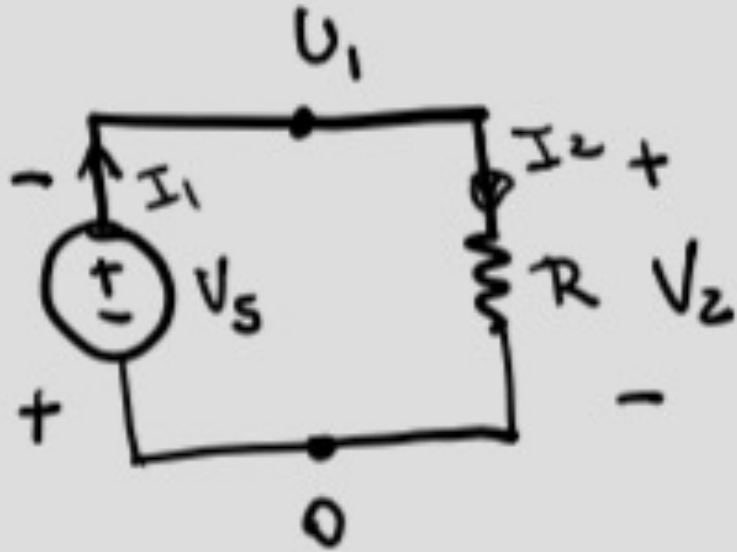
# Circuit Analysis Algorithm : step 6

Use KCL to fill as many rows of A as possible (linear independence) # Nodes - 1 = N-1




$$I_1 = I_2$$
$$I_1 - I_2 = 0$$

$$\begin{bmatrix} 1 & -1 & 0 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ U_1 \end{bmatrix} = \begin{bmatrix} 0 \end{bmatrix}$$
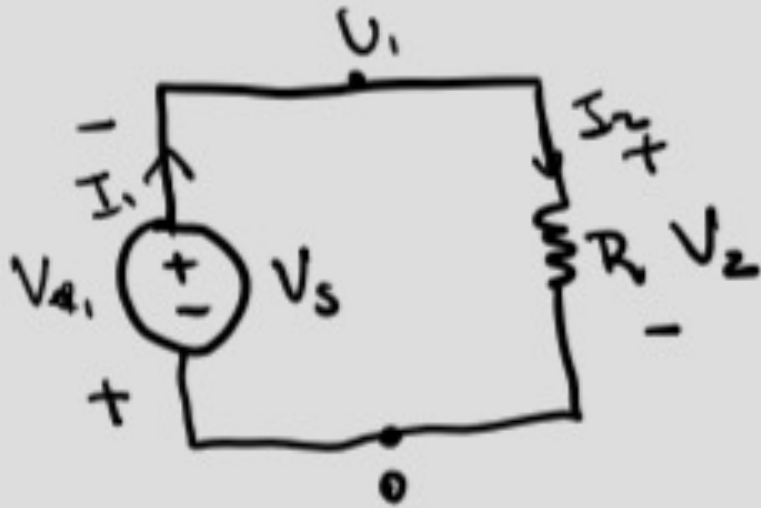
# Circuit Analysis Algorithm : step 7

Use current-voltage relationships for each element to fill the rest of the A matrix



Resistor

$$V_{el,2} = I_2 \cdot R$$
$$V_{el,2} = U_1 - 0 = U_1$$
$$U_1 = I_2 R$$
$$I_2 R - U_1 = 0 \quad \checkmark$$

Voltage element:  $V_{el,1} = -V_s$

$$V_{el,1} = 0 - U_1 = -U_1$$
$$U_1 = V_s \quad \checkmark$$

$$\begin{bmatrix} 1 & -1 & 0 \\ 0 & 0 & 1 \\ 0 & R & -1 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ U_1 \end{bmatrix} = \begin{bmatrix} 0 \\ V_s \\ 0 \end{bmatrix}$$

$$\Downarrow$$
$$U_1 = V_s$$
$$I_1 = V_s / R$$
$$I_2 = V_s / R$$