

Welcome to EECS 16A!

Designing Information Devices and Systems I

Ana Claudia Arias and Miki Lustig
Fall 2021

Module 2
Lecture 3

Power and Voltage/Current Measurements
(Note 13)



How to think about Energy and Power in circuits?

Current: flow of charges (electrons moving from point A to B inside a material) $I = \frac{dQ}{dt}$


It takes energy to move charge from A to B \Rightarrow Voltage $V_{AB} = \frac{dE}{dq}$

Power: is the rate of change of energy

$$P = \underbrace{\frac{dE}{dq}}_V \cdot \underbrace{\frac{dq}{dt}}_I = V \cdot I$$

$(V) \cdot (A) = (W)$

Energy and Power

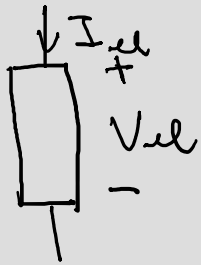

$$P_{el} = V_{el} \cdot I_{el}$$

if $el.$ is a resistor: $P = V \cdot I = R \cdot I \cdot I = RI^2 \geq 0$
↳ power dissipated is positive $\rightarrow \oplus$

$$V_{el} = R I_{el}$$


$$I_{el} = \frac{V_{el}}{R}$$

$$P = V \cdot I = V_{el} \cdot \frac{V_{el}}{R} = \frac{V_{el}^2}{R} \geq 0$$


Passive-sign convention

Energy and Power

$$P_{el} = V_{el} \cdot I_{el}$$

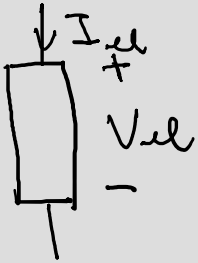


$$P_{el} = V_{el} \cdot I_{el} = 0$$

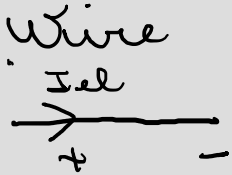

$$P_{el} = V_{el} \cdot I_{el} = 0$$

Example

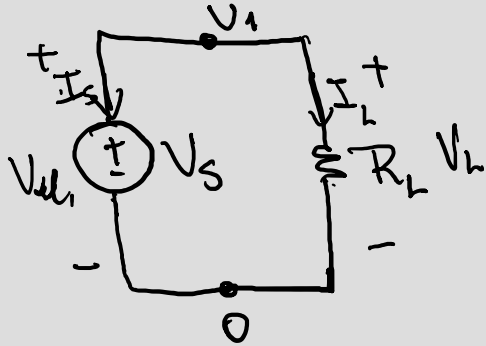

$$\text{KCL: } I_L + I_S = 0$$

$$\text{KVL: } V_1 - 0 = V_L = V_{eL}$$

$$V_{eL} = V_S \text{ (def)}$$

Power:

$$P_L = I_L \cdot V_L \text{ (def)}$$

$$P_S = I_S \cdot V_{eL} \text{ (def)}$$

$$I_L = -I_S$$

$$P_L = (-I_S) \cdot V_L$$

$$P_L = (-I_S) \cdot V_S$$

$$P_S \leq 0$$

* Conservation of Energy!



$$P_L = -P_S$$

$$P_L + P_S = 0$$

$$P_L \geq 0 \text{ (resistor)}$$

How to measure Voltage and Current?

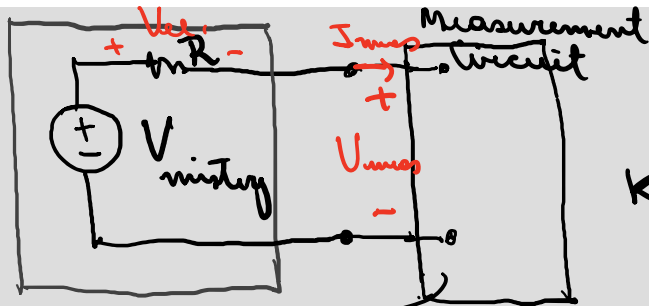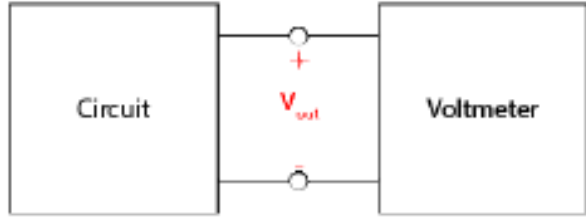Measurement should not change the energy of circuit!



Goal: $V_{\text{meas}} = V_{\text{mistry}}$

$$V_{e1} = I_{\text{meas}} \cdot R$$



KVL: $V_{\text{mistry}} = V_{\text{meas}} + V_{e1}$

$$V_{\text{mistry}} = V_{\text{meas}} + I_{\text{meas}} \cdot R$$

$$V_{\text{mistry}} = V_{\text{meas}} \quad \left| \begin{array}{l} \text{if } I_{\text{meas}} = 0 \end{array} \right.$$

V must behave as an open-circuit.

How to measure Voltage and Current?

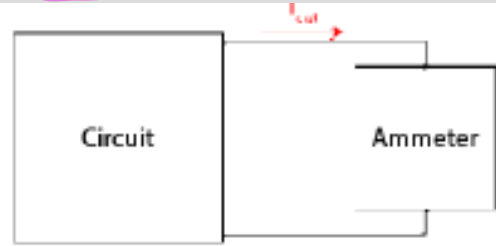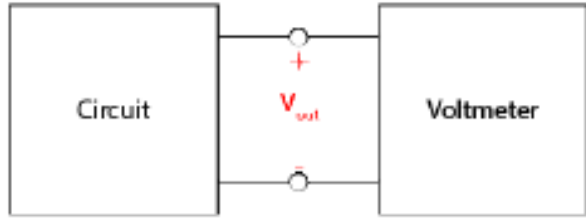

Task: measure I_{mistry}

(KCh) $I_{mistry} = I_R + I_{meas}$


$I_{mistry} = I_{meas} \quad |$

$\neq I_R = 0$

$I_R = \frac{V_{meas}}{R}$


if $V_{meas} = 0$

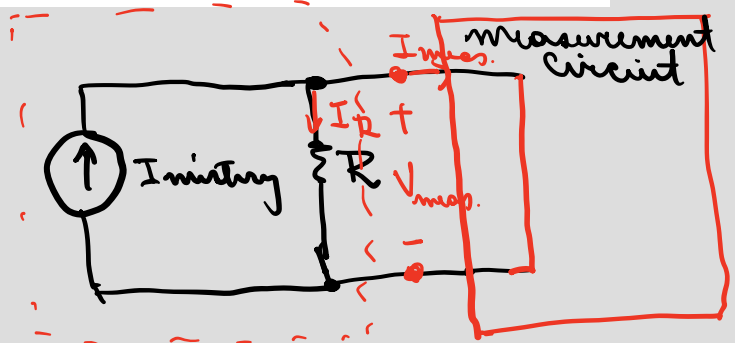by definition meas. circuit should behave as a wire



Resistance, Resistivity, Conductivity – Physics and Materials...

Material	Electrical characteristics	
	Electrical Resistivity ($\Omega \times \text{cm}$)	Electrical Conductivity ($\Omega^{-1} \times \text{cm}^{-1}$)
Cu	0.034×10^{-5}	29×10^5
Fe	32.54×10^{-5}	0.031×10^5
Ag	0.36×10^{-5}	2.8×10^5
Al	0.03×10^{-5}	33.3×10^5
Ni	0.046×10^{-5}	21.7×10^5
Cu-Fe	33.37×10^{-5}	0.030×10^5
Cu-Ag	2.71×10^{-5}	0.37×10^5
Al-Ni	0.564×10^{-5}	1.77×10^5

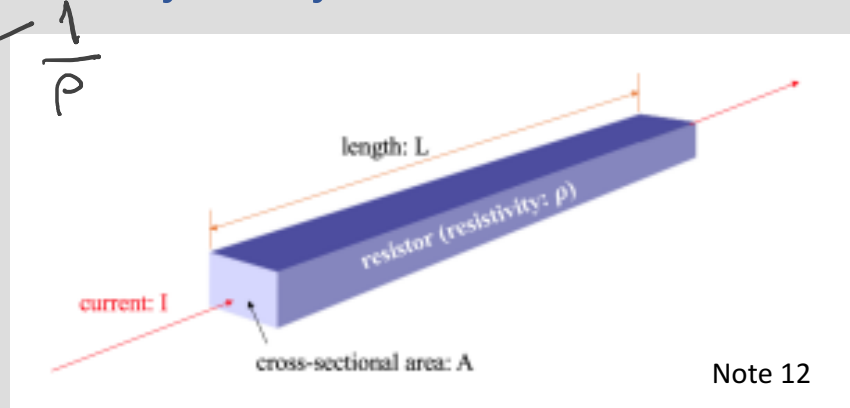

Note 12




longer the wire \rightarrow the more energy is lost.

Wide wires \rightarrow lower resistance

Wire properties depends on materials choice.


$$R = \rho \cdot \frac{L}{A}$$

Resistive Touch Screen

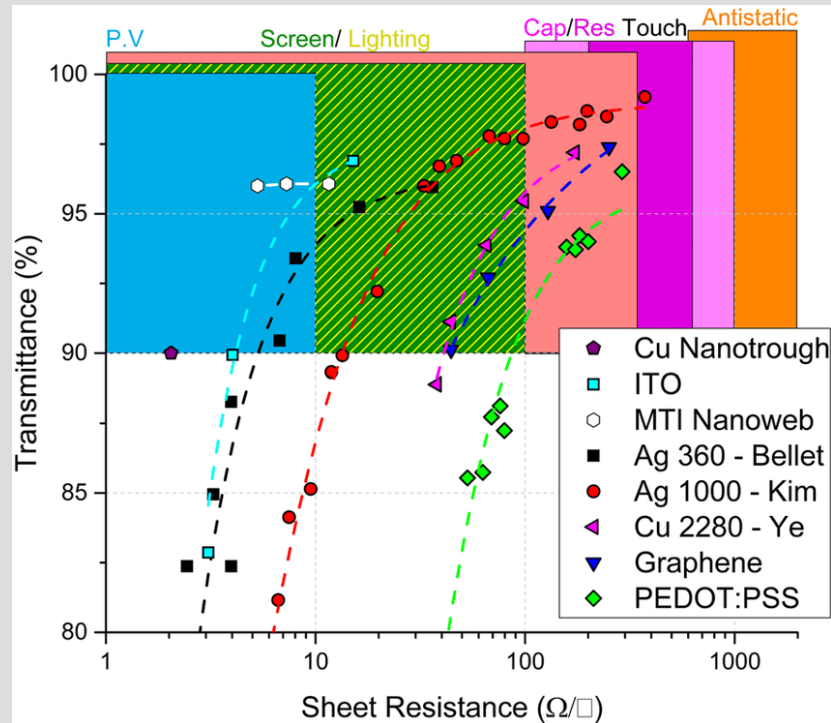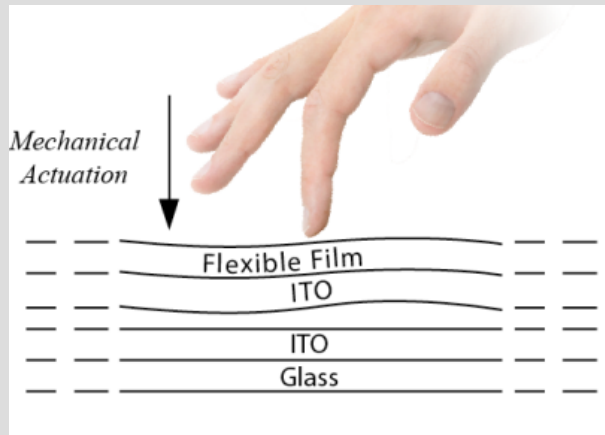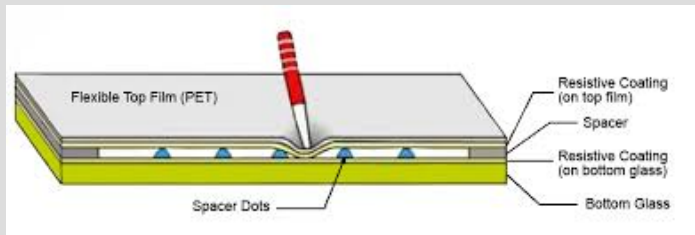

Resistive Touch Screen

Problem: To find the location of touch.

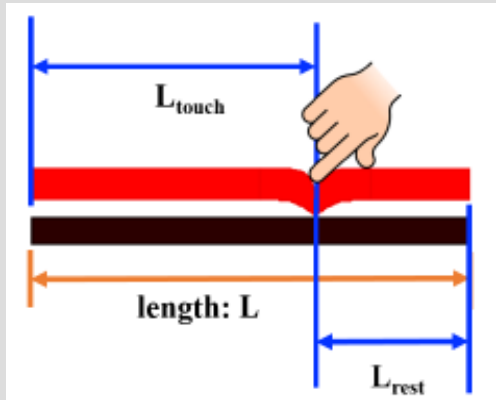


Go from mechanical to electrical quantity!


Want to measure $\frac{h_{touch}}{h}$

h_{touch} is unknown

Resistive Touch Screen – First model

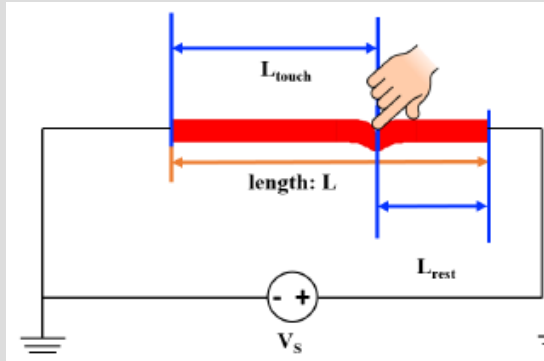

⇒

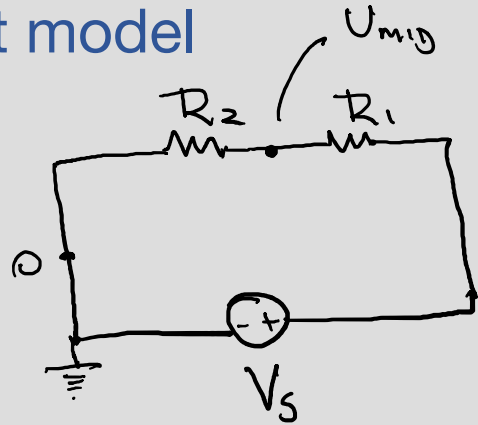

$$R_1 = \rho \cdot \frac{L_{rest}}{A} \quad (1)$$

$$R_2 = \rho \cdot \frac{L_{touch}}{A} \quad (2)$$


$$U_{mid} = \frac{L_{touch}}{L} \cdot V_s$$

$$U_{mid} = \frac{R_2}{R_2 + R_1} V_s \quad (\text{Voltage Divider})$$

$$U_{mid} = \frac{\rho \frac{L_{touch}}{A}}{\rho \frac{L_{touch}}{A} + \rho \frac{L_{rest}}{A}} \cdot V_s$$

$$L \leftarrow \frac{L_{touch}}{L_{touch} + L_{rest}} \cdot V_s$$


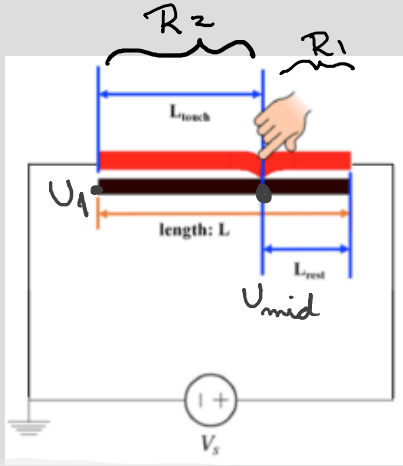
Resistive Touch Screen – More realistic model



$$R_2 = \frac{\rho L_{\text{touch}}}{A}$$

$$R_1 = \frac{\rho L_{\text{rest}}}{A}$$

⇒
Model 1

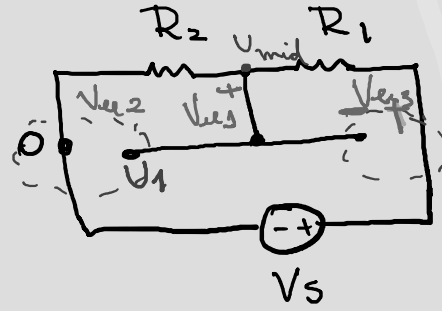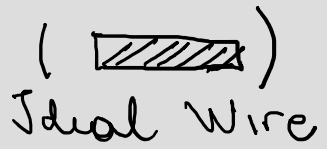

L₃ Added:

- el₁ : wire
- el₂ : open-circuit (U_{el2})
- el₃ : open-circuit (U_{el3})




Model 0

$$U_{\text{mid}} = \frac{R_2}{R_1 + R_2} \cdot V_s$$

(Voltage Divider)


Resistive Touch Screen – More realistic model

⇒
Model 1

()
Ideal Wire

↳ Added:

- el₁: wire
- el₂: open-circuit (V_{el2})
- el₃: open-circuit (V_{el3})

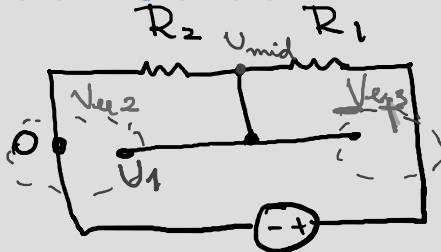

Model 0

$$U_{mid} = \frac{R_2}{R_1 + R_2} \cdot V_s$$
 (Voltage Divider)

$$R_2 = \frac{\rho L_{touch}}{A}$$

$$R_1 = \frac{\rho L_{rest}}{A}$$

V_s el 2:


$$V_{el2} = U_1 - 0 \quad (\text{definition of elem. } V)$$

el 1:

$$V_{el1} = U_{mid} - U_1$$

KVL:

$$U_{mid} - 0 = V_{el2} + V_{el1}$$

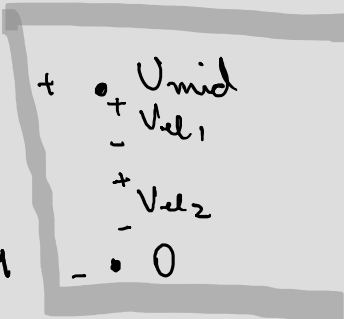

Resistive Touch Screen – More realistic model



Model 1



Ideal Wire

↳ Added:

el₁: wire

el₂: open-circuit (V_{el2})

el₃: open-circuit (V_{el3})

el₂:


$$V_{el2} = U_1 - 0 \text{ (definition of elem. V)}$$

el₁:

$$V_{el1} = U_{mid} - U_1$$

KVL:

$$U_{mid} - 0 = V_{el2} + V_{el1}$$

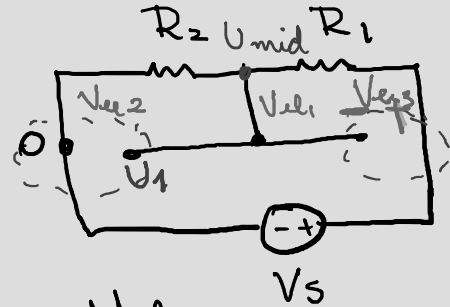

$$U_1 = V_{el2}$$

$$U_{mid} - U_1 = V_{el1}$$



$$\left. \begin{array}{l} U_{mid} - U_1 + U_1 = V_{el1} + V_{el2} \\ U_{mid} = V_{el1} + V_{el2} \end{array} \right\} +$$

el₁ is a wire: $\therefore V_{el1} = 0$

$$\underline{\underline{U_{mid} = 0 + V_{el2} = V_{el2} = U_1}}$$



* By measuring V_{el2} we get U_{mid} for any touch.

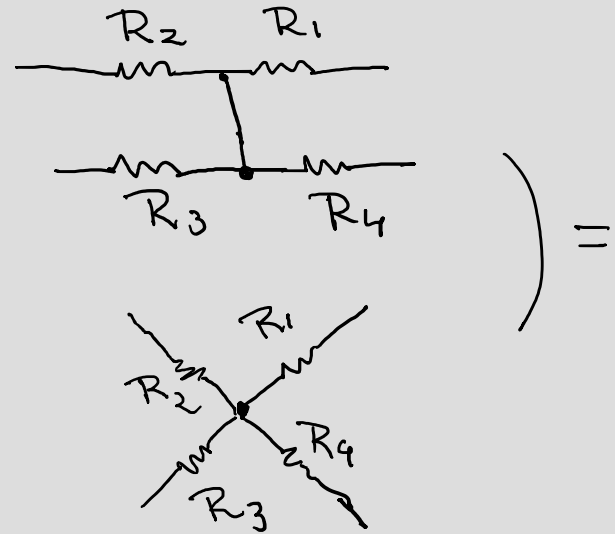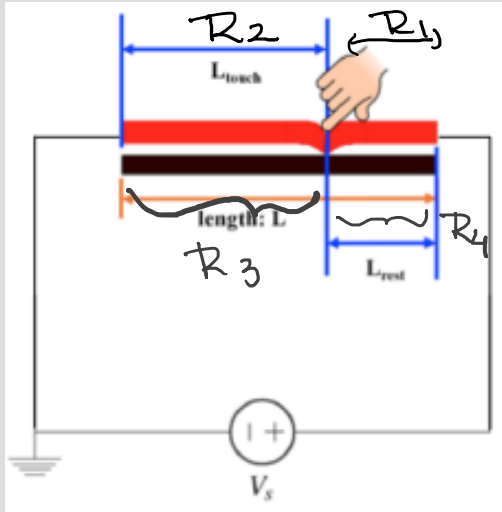Resistive Touch Screen – More realistic model



R_1 , R_2 , R_3 and R_4 are unknown.

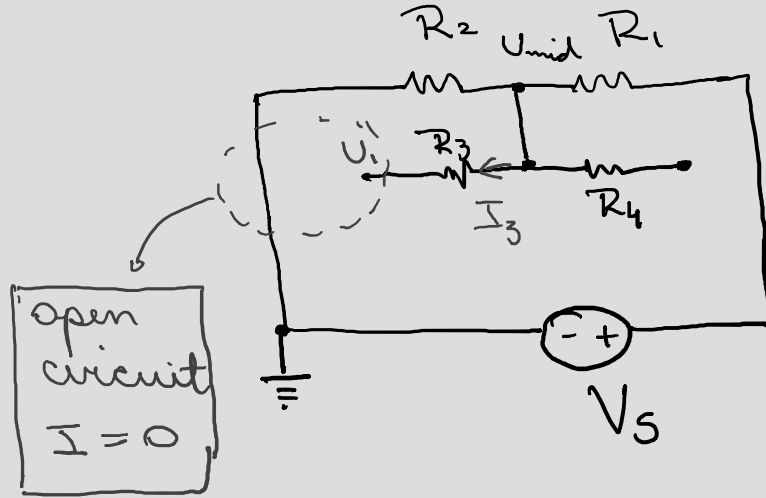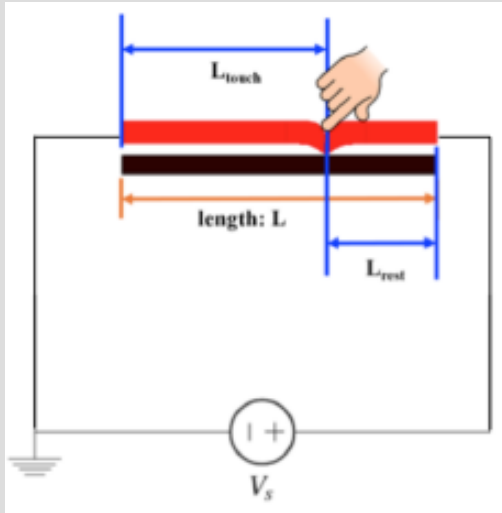Resistive Touch Screen – More realistic model





$$I_3 = 0$$

$$U_1 = 0$$

Read out is Voltage!

Resistive Touch Screen – More realistic model

Model 2 – imperfect conductor (resistor)

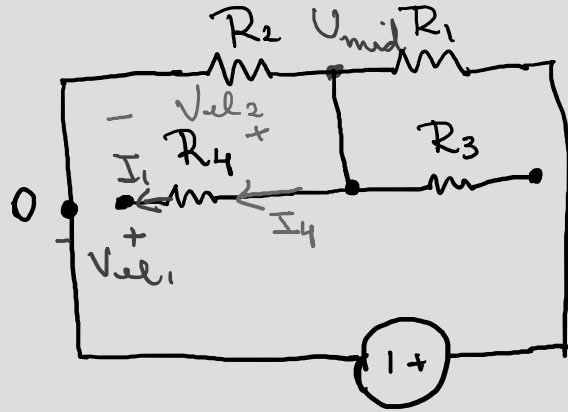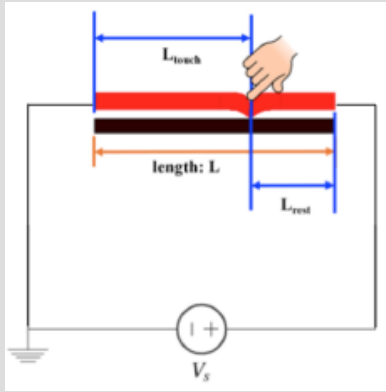

Coded

el₁: open-circuit \Rightarrow

el₂: resistor (R_4)

$$V_{el2} = R_4 \cdot I_4 \text{ (Ohm's Law)}$$


$$KCh : I_1 = I_4$$

$$I_1 = 0 \therefore I_4 = 0$$


$$U_{mid} = V_{el1} + V_{el2} = V_{el1} + R_4 \cdot I_4$$

$$U_{mid} = V_{el1}$$

Resistive Touch Screen – More realistic model

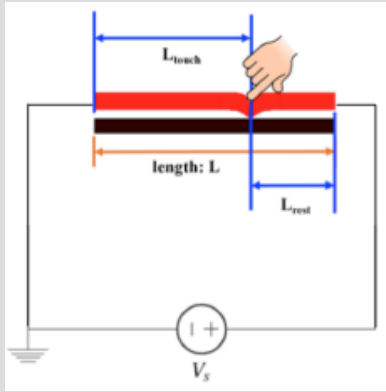

Model 2 – imperfect conductor (resistor)

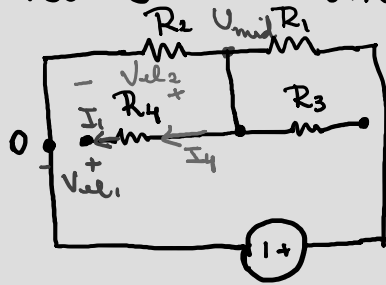


KCh : $I_1 = I_4$
 $I_1 = 0 \therefore I_4 = 0$

$U_{mid} = V_{el1} + V_{el2} = V_{el1} + R_4 I_4$

$U_{mid} = V_{el1}$

We can : measure U_{mid} at V_{el1} regardless of backplane material and value of L_{touch}

An interesting circuit

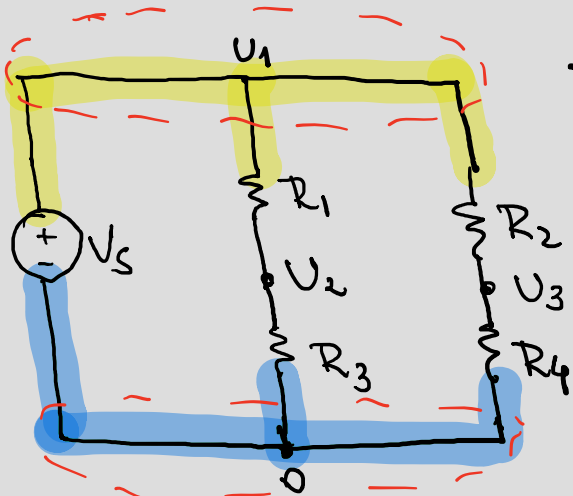

• What are U_2 and U_3 ?

$$U_2 = \frac{R_3}{R_1 + R_3} \cdot V_S$$

$$U_3 = \frac{R_4}{R_2 + R_4} \cdot V_S$$

$$V_S = U_1 - 0 \quad \Bigg| \quad U_2 - 0 = \frac{R_3}{R_1 + R_3} \cdot (U_1 - 0) \overset{V_S}{}$$

$$\Bigg| \quad U_3 - 0 = \frac{R_4}{R_2 + R_4} \cdot (U_1 - 0) \overset{V_S}{}$$

