## EECS 16A Designing Information Devices and Systems I Fall 2022 Discussion 8A

## 1. Resist the Touch

Investigate the  $N \times N$  resistive touchscreen with vertical length L and horizontal width W shown in Figure 1. The touchscreen is constructed in two layers: a flexible conductive top layer comprised of N vertically oriented strips with even spacing  $\frac{W}{N+1}$ ; and a rigid conductive bottom layer comprised of horizontally oriented strips with even spacing  $\frac{L}{N+1}$ .

The vertical and horizontal strips form a grid of detectable touch points. The upper left touch point in Figure 1(b) is position (1,1), and the upper right touch point is (N,1). All strips in top and bottom layers have equal resistivity,  $\rho$ , and cross-sectional area, A.

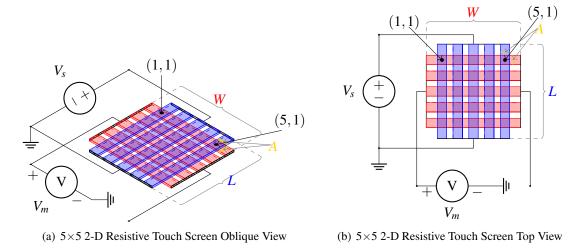


Figure 1:  $N \times N$  Resistive Touch Screen, N = 5

(a) Find the resistance  $R_y$  for a single vertical blue strip and  $R_x$  for a single horizontal red strip as a function of the screen dimensions W and L, the strip resistivity  $\rho$ , and the cross-sectional area A.

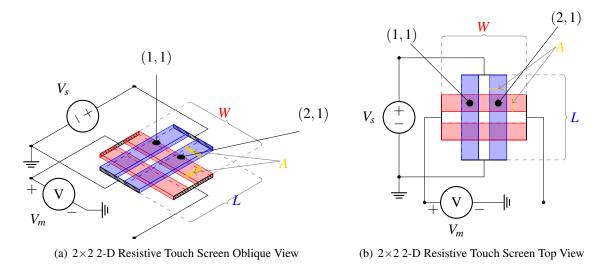


Figure 2: 2 × 2 Resistive Touch Screen

- (b) Consider a  $2 \times 2$  example for the touchscreen circuit, as shown in Figure 2.
  - Assume a voltage source  $V_s$  is connected from the top to bottom terminals of all the vertical (blue) strips, and a voltmeter  $V_m$  is connected from the left terminal of all horizontal (red) strips to the negative terminal of the voltage source.

If  $V_s = 3 \text{ V}$ ,  $R_x = 2000 \Omega$ , and  $R_y = 2000 \Omega$ , draw the equivalent circuit for when the point (2,2) is pressed and solve for the measured voltage,  $V_m$ , with respect to ground.

(c) Suppose a touch occurs at coordinates (i, j) for an arbitrary  $N \times N$  touch screen, and the voltage source and meter are connected as in the diagrams. Find an expression for  $V_m$  as a function of  $V_s$ , N, i, and j.