

Welcome to EECS 16A!





Designing Information Devices and Systems I

Ana Claudia Arias and Miki Lustig
Fall 2022

Module 2
Lecture 10
Negative Feedback
(Note 17 and 17B)



Last Lecture...

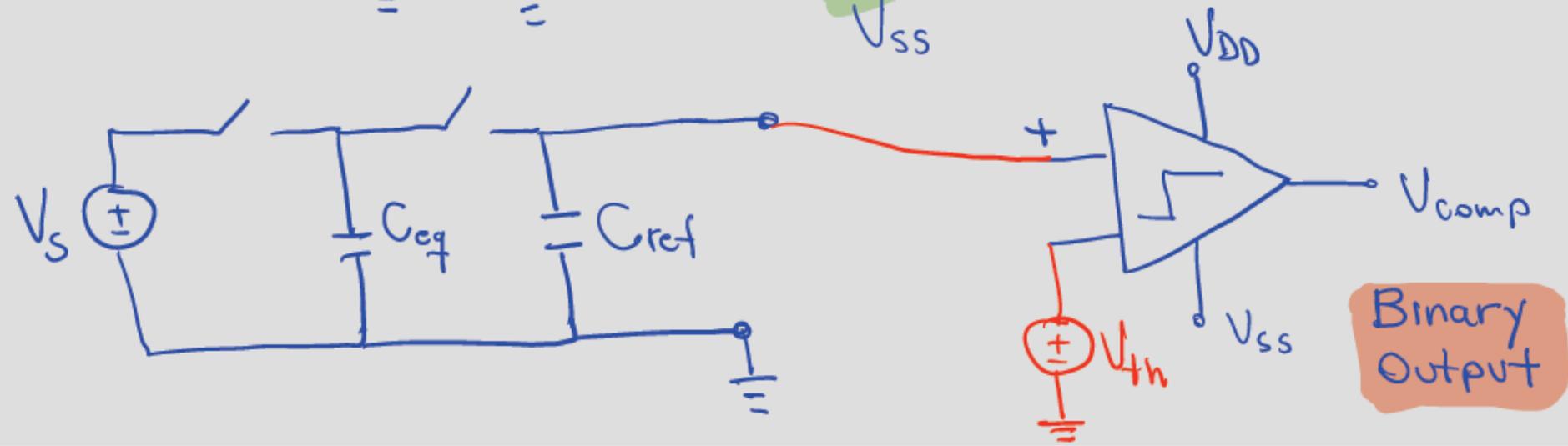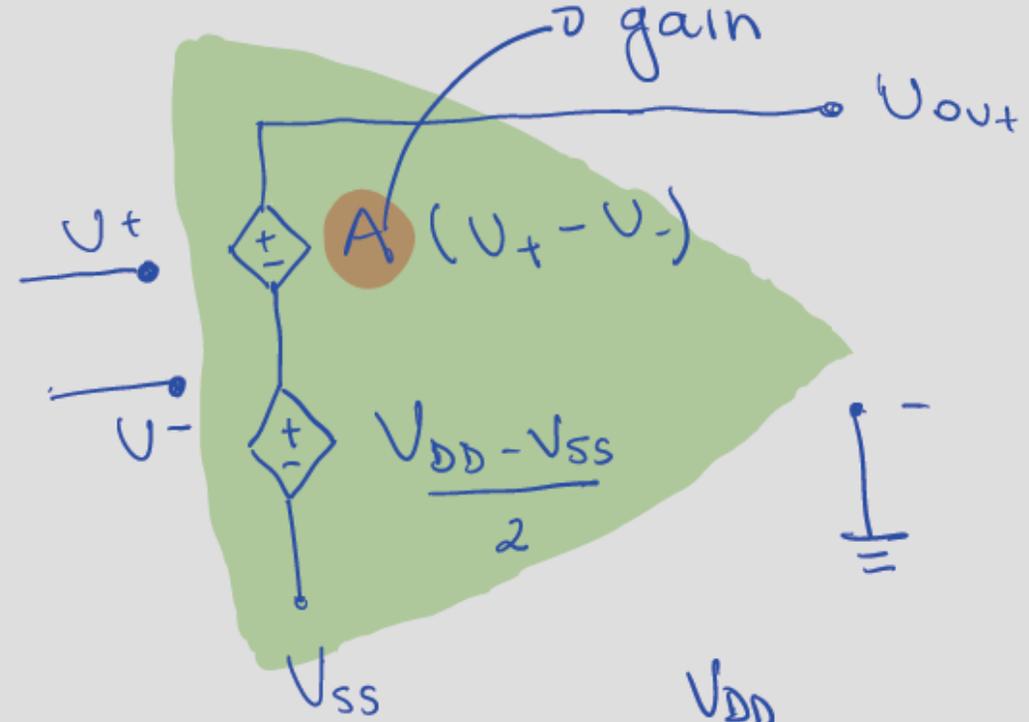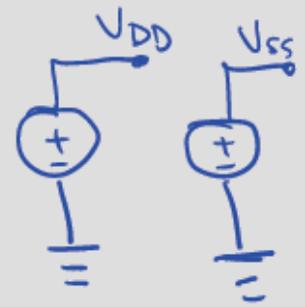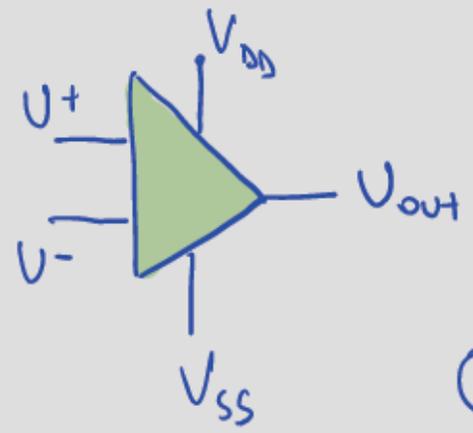

Last Lecture...

Problem

- We want to play music loud!
- Music is stored as digital signal
- Speakers are analog

Tools

- Resistors
- Capacitors
- Open-circuits
- Voltage Dividers
- Op-Amps
- Thevenin Equivalence
- Norton Equivalence
- KCL / KVL
- Element Def.


Specs

- Speaker takes 0-10V ✓
- Need to go from digital to analog. ?



New Design – Let's play music

* Want to play music LOUD

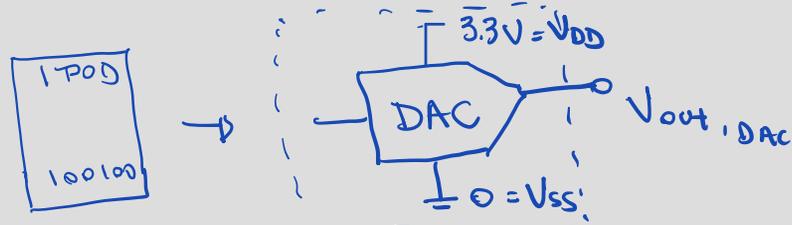↳ Music is stored as digital signal
Digital → Analog



Digital-to-analog converter



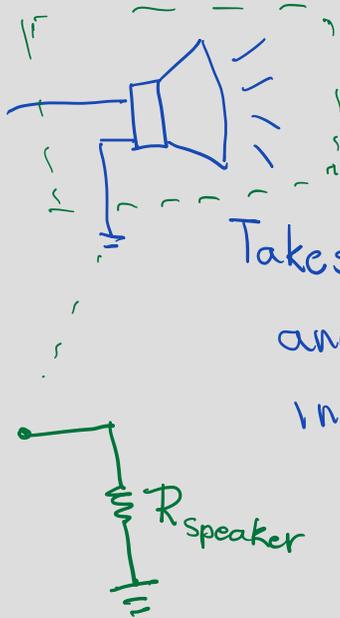
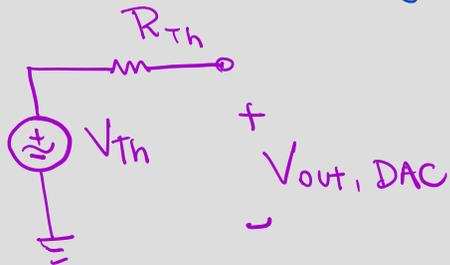


Takes Voltage and turns into sound

Dance!



Digital to Analog Converter - DAC

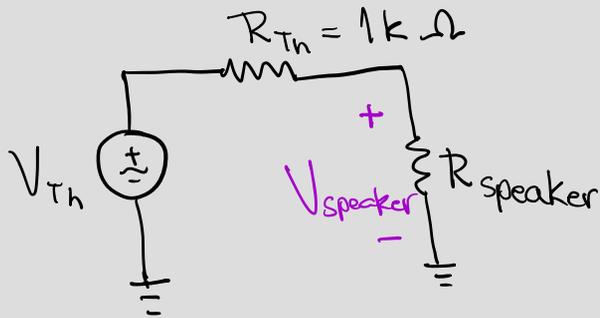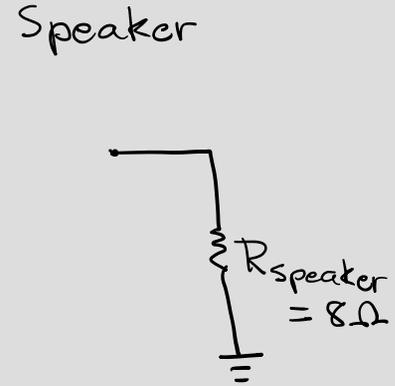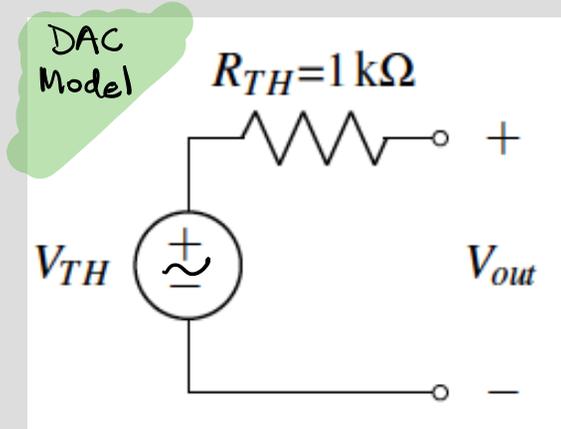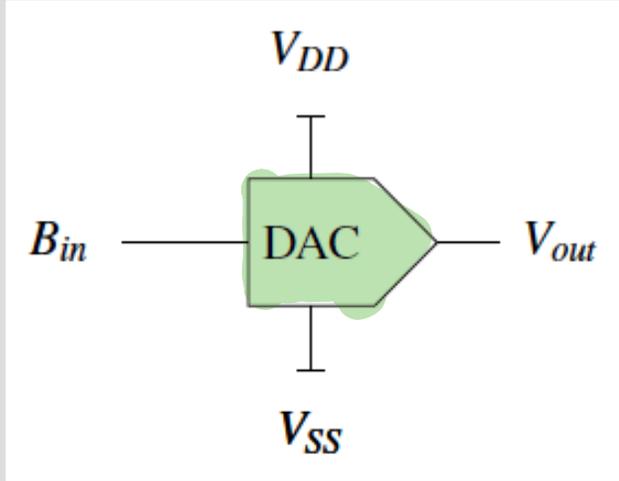

Voltage Divider

$$V_{\text{speaker}} = \frac{R_{\text{speaker}}}{R_{\text{TH}} + R_{\text{speaker}}} \cdot V_{\text{TH}}$$

(Handwritten annotations: 8Ω above R_{speaker}, 1000Ω below R_{TH}, 8Ω above R_{speaker})




$$V_{\text{speaker}} = \frac{V_{\text{TH}}}{126}$$

Not loud!
Too quiet!

Need to isolate DAC.



Digital to Analog Converter - DAC

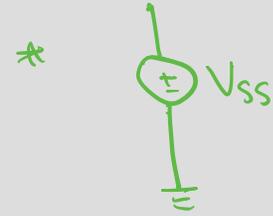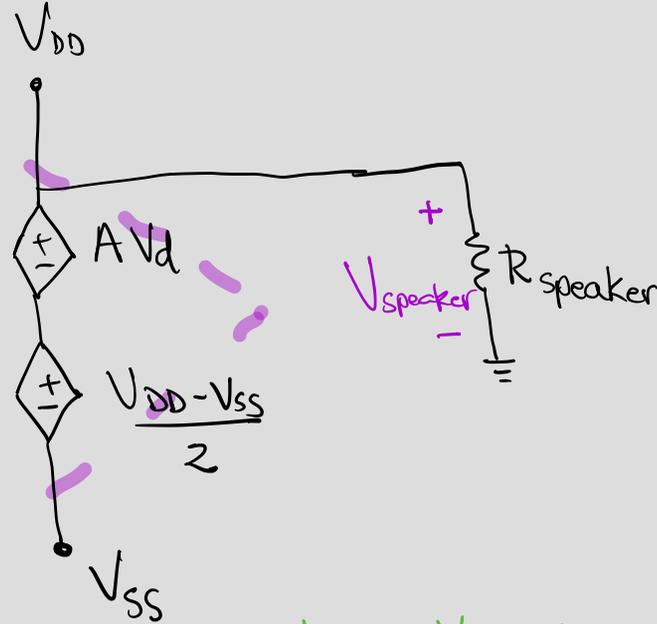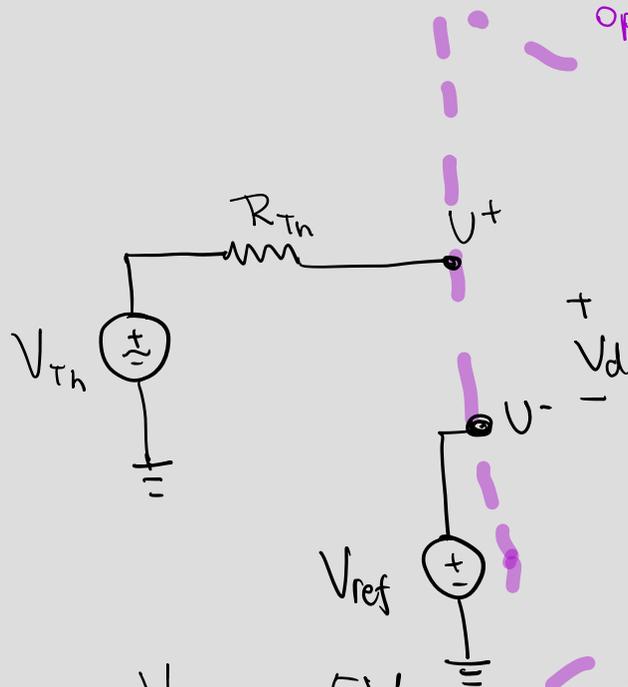

$$V_{DD} = -V_{SS} = 5V$$

10V output

(Input)

(KUL)

$$V_{speaker} = V_{SS} + \frac{V_{DD} - V_{SS}}{2} + A_{Vd} = A_{Vd}$$



$$\frac{V_{DD} + V_{SS}}{2} = 0$$

when:

$$V_{SS} < A_{Vd} < V_{DD}$$

$$V_d = U^+ - U^- = V_{Th} - V_{ref}$$

Digital to Analog Converter - DAC

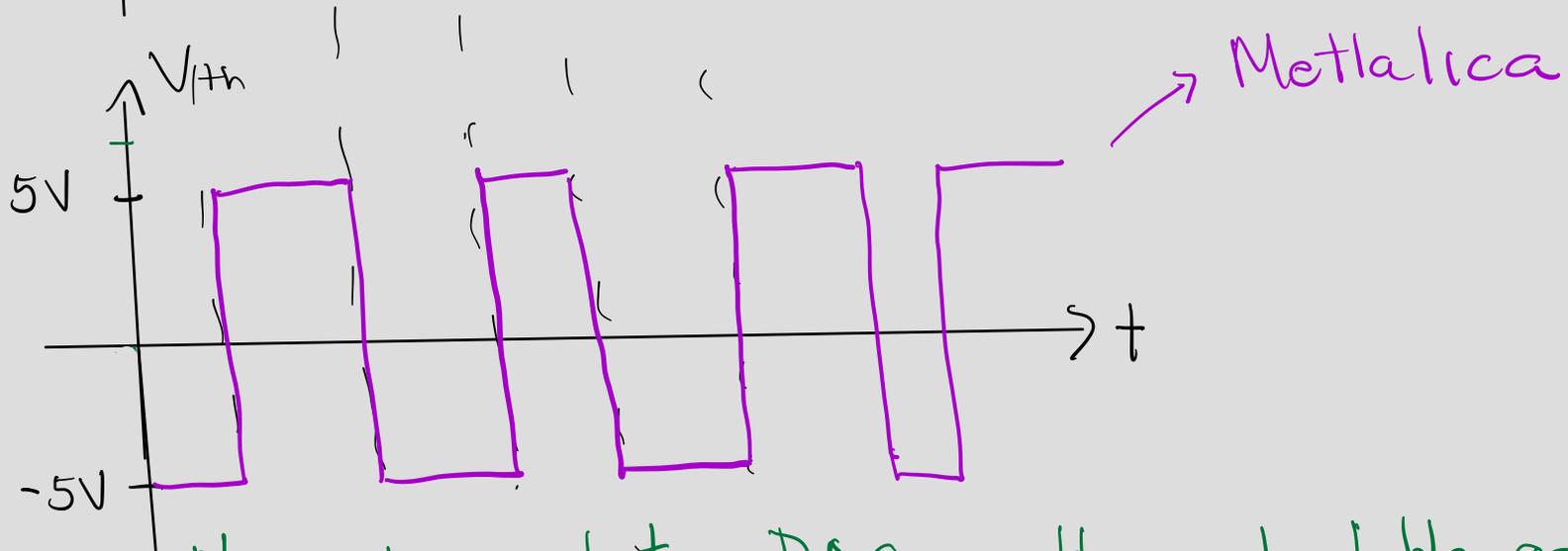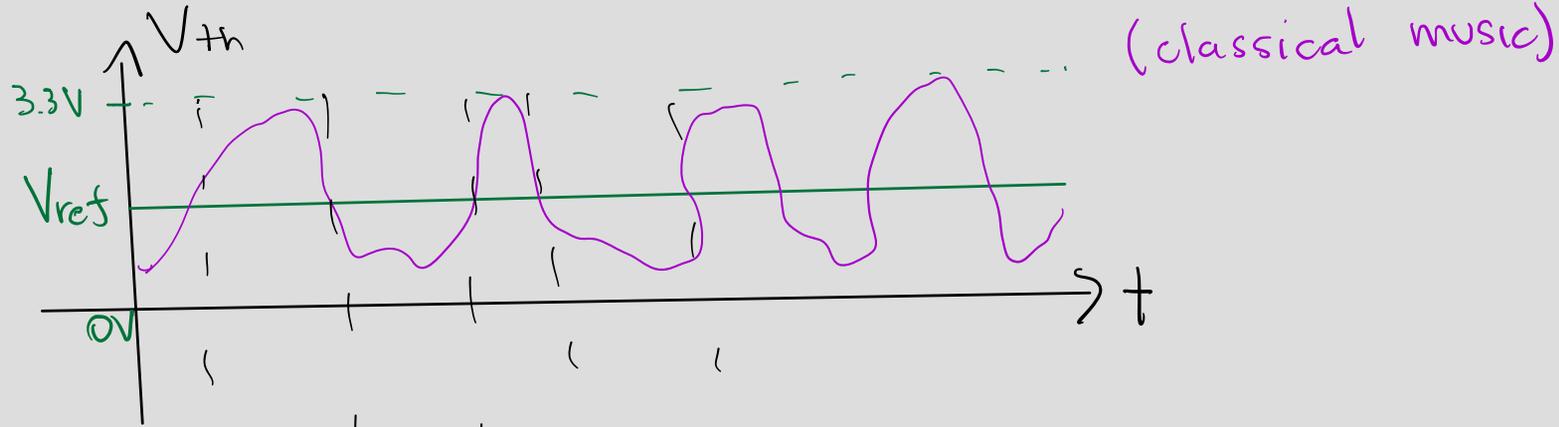

Need to isolate DAC with controllable gain!
e.g. $3\times$

Negative Feedback

$$S_{err} = S_{in} - S_{fb}$$


$$S_{out} = A \cdot S_{err}$$

$$S_{fb} = f \cdot S_{out}$$

$$\frac{S_{out}}{A} = S_{in} - S_{fb}$$

$$S_{out} \left(\frac{1}{A} + f \right) = S_{in}$$
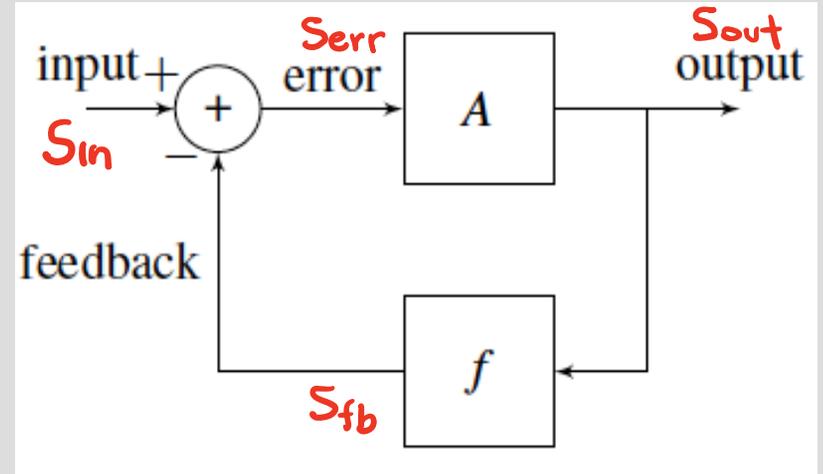
$$\frac{S_{out}}{S_{in}} = \frac{1}{\frac{1}{A} + f} = \frac{A}{1 + Af}$$



- Making small adjustments to correct output on the fly
- Basis of control theory
- Many examples in daily life:

- Biology

- Self-driving car

- Human driving car

- Hand-eye coordination

- ...

Negative Feedback

$$\frac{S_{out}}{S_{in}} = \frac{A}{1 + A f}$$

- Describes the behaviour of the system - transfer function.
- How S_{out} depends on S_{in}


$$\frac{S_{out}}{S_{in}} \underset{A \rightarrow \infty}{=} \frac{1}{f}$$

↳ We control the output via block f !


So $V_{out} = \frac{1}{f} V_{in}$ for very large gain.

↳ we can set f to get any output.
(Beautiful result) 😊

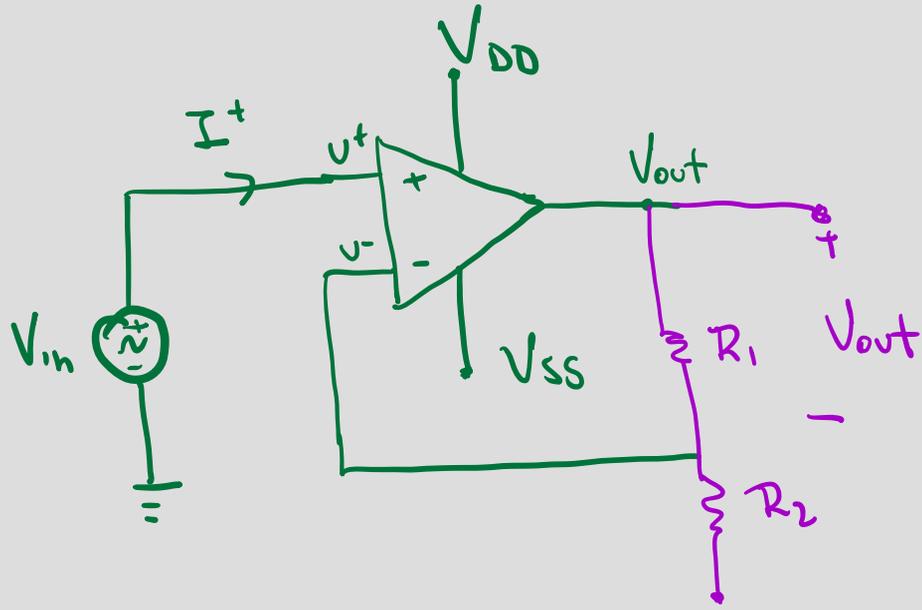Need to isolate the DAC from speaker – OP-Amp with NFB



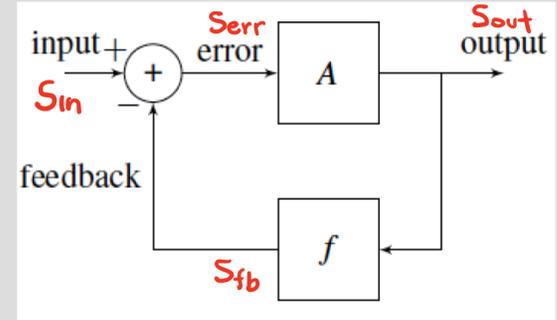- We want to measure V_{out} , take a portion of the signal and feedback as v^-



$$v^+ = S_{in}$$



$$V_{out} = S_{out}$$

$$v^- = S_{fb}$$

$$v^+ - v^- = S_{err}$$

Op-Amp in negative feedback


Non-inverting op-amp

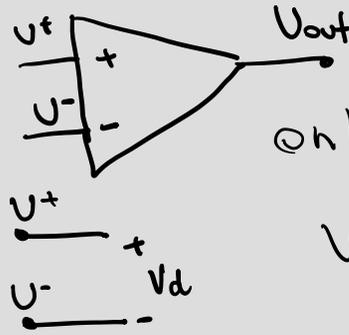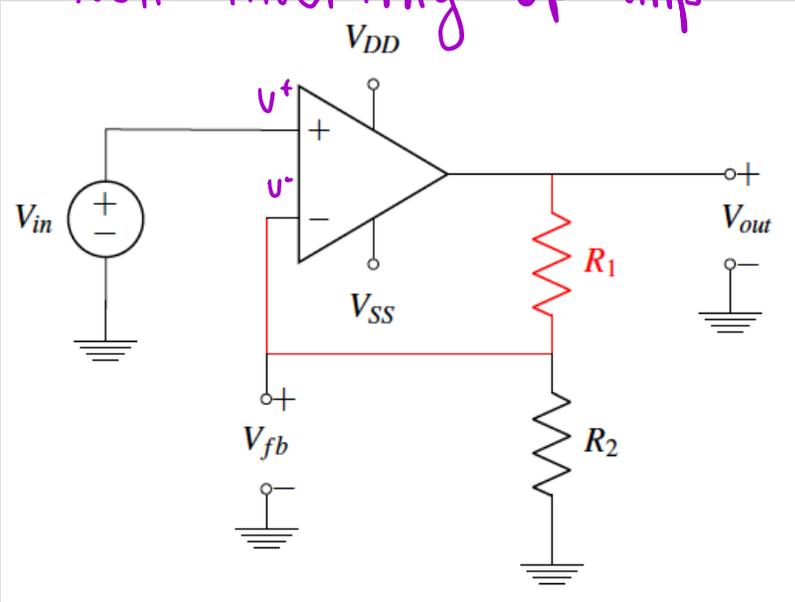

Model :

only for

$$V_{SS} < V_{out} < V_{DD}$$

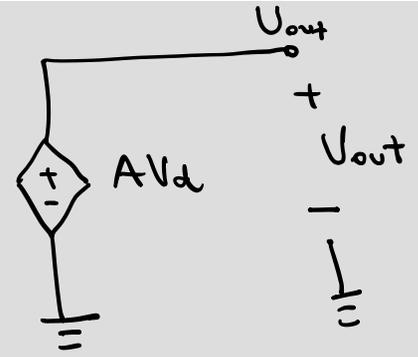

Simpler model as the second source is not "needed".

- (1) $V_d = U^+ - U^- = V_{in} - V_{fb}$
 - (2) $V_{out} = A V_d$
 - (3) $V_{fb} = \frac{R_2}{R_1 + R_2} \cdot V_{out}$
- "BUFFER circuit" $\hookrightarrow f$

$$V_{out} = A (V_{in} - f \cdot V_{out})$$

$$V_{out} (1 + Af) = A V_{in}$$

$$A_v = \text{Gain} = \frac{V_{out}}{V_{in}} = \frac{A}{1 + Af}$$

$$A_v = \frac{1}{f} \quad A \rightarrow \infty$$

$$\frac{R_1 + R_2}{R_2} = \frac{1 + \frac{R_1}{R_2}}{\frac{R_1}{R_2}}$$

Golden Rules of Op-Amps

For our design we want $A = 3$


$$V_d = \frac{V_{out}}{A} \quad \text{if } A \rightarrow \infty$$

$$V_d = \frac{1}{A} \cdot \frac{A}{1+Af} V_{in} = \frac{V_{in}}{1+Af} = 0$$


In NFB: $V^+ = V^-$ and $A \rightarrow \infty$

Rules: (Golden Rules)

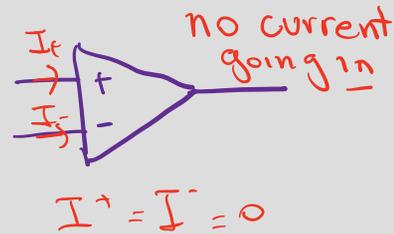
- (1) $I^+ = I^- = 0$ (always true)
- (2) $V^+ = V^-$ (only in NFB & $A \rightarrow \infty$)




Let's go back to playing music

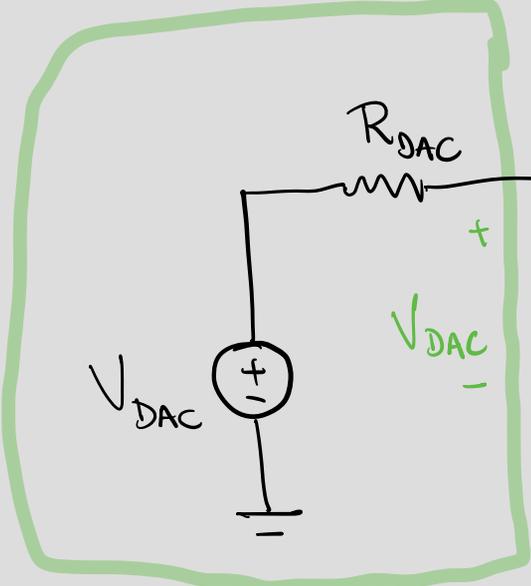

DAC

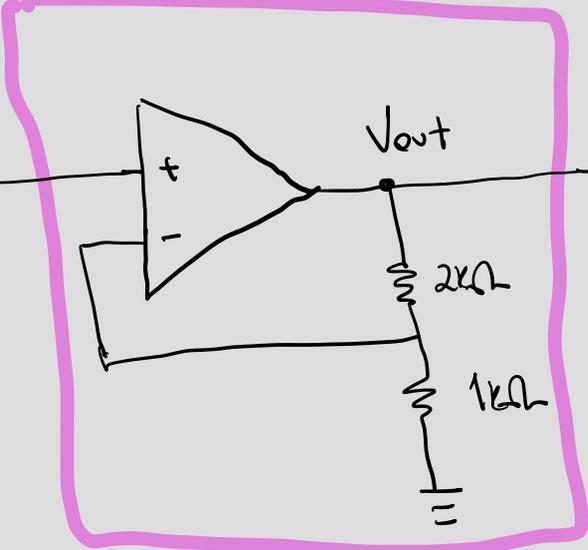

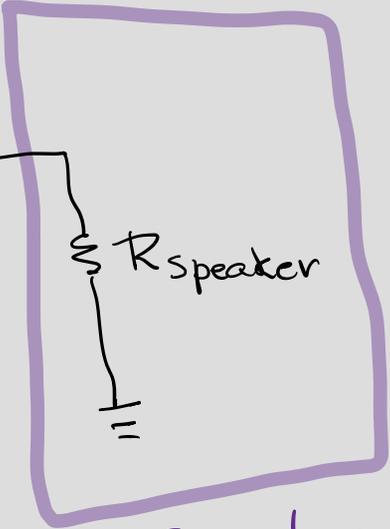Non-Inverting Amplifier
(feedback gain = 3)



Speaker

Party time!
Yay!


Checking for Negative Feedback (Determining the polarity of NFB)

Step 1 – Zero out all independent sources : replacing voltage sources with wires and current sources with open circuits as in superposition





Step 2 – Wiggle the output and check the loop – to check how the feedback loop responds to a change.

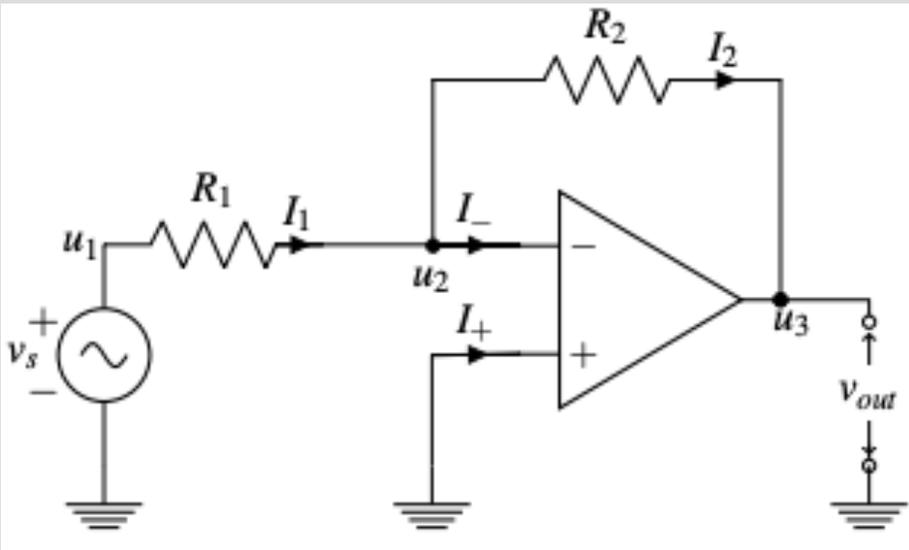- if the error signal decreases, the output must also decrease. **The circuit is in negative feedback**
- if the error signal increases, the output must also increase. **The circuit is in positive feedback**



Now lets solve it...

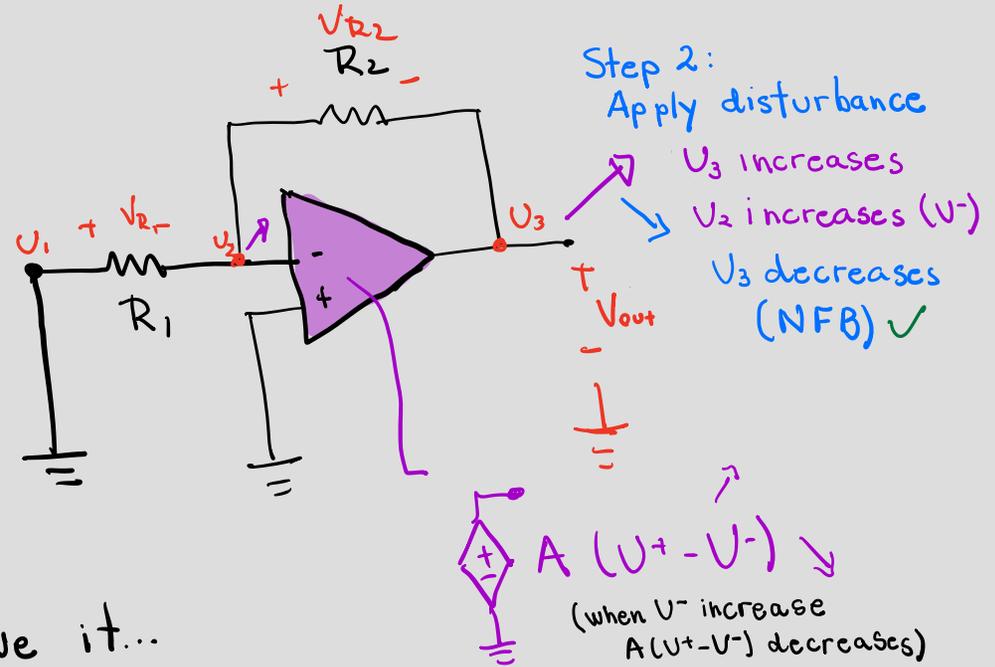

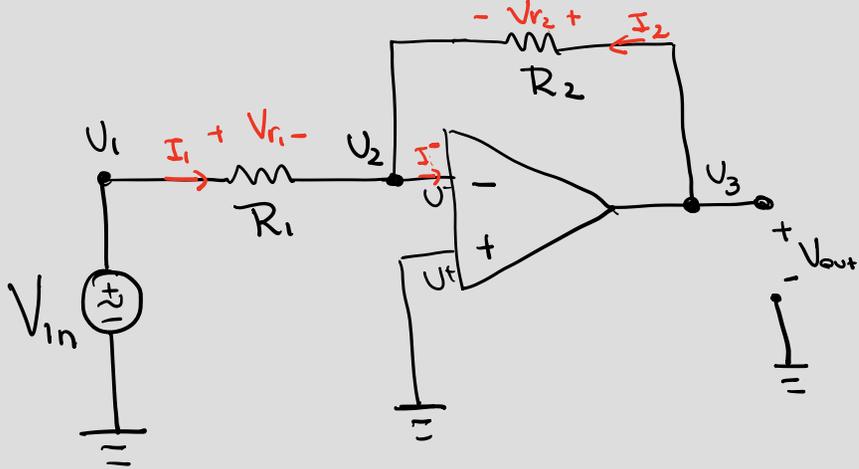

NFB \Rightarrow GR # 2 applies
 $U^+ = U^-$

- ①
- $U_1 = V_{in}$
 - $U_3 = V_{out}$
 - $U_2 = 0$ (circuit in NFB \Rightarrow GR # 2 applies $U^+ = U^-$)
 - $\hookrightarrow U_2 = U^-$ (we know $U^+ = 0 \Rightarrow U^- = 0$)
 - $U^- = U_2 \Rightarrow U_2 = 0$

- ② Element Definitions:
- $V_{R_1} = I_1 R_1$
 - $V_{R_2} = I_2 R_2$
 - Voltage Def:
 - $V_{R_1} = U_1 - U_2 = U_1 = V_{in}$
 - $V_{R_2} = U_3 - U_2 = U_3 = V_{out}$

- ③ (KCL)
- $I_1 + I_2 = I^- = 0$ (GR # 1)

Inverting Amplifier

$$V_{in} = U_1 = I_1 R_1$$

$$V_{out} = U_3 = I_2 R_2$$

$$I_1 + I_2 = 0$$


$$\frac{V_{in}}{R_1} + \frac{V_{out}}{R_2} = 0$$

$$V_{out} = R_2 \cdot \left(-\frac{V_{in}}{R_1} \right)$$

$$V_{out} = -\frac{R_2}{R_1} V_{in}$$

$$A_v = \frac{V_{out}}{V_{in}} = -\frac{R_2}{R_1}$$

A faster way...

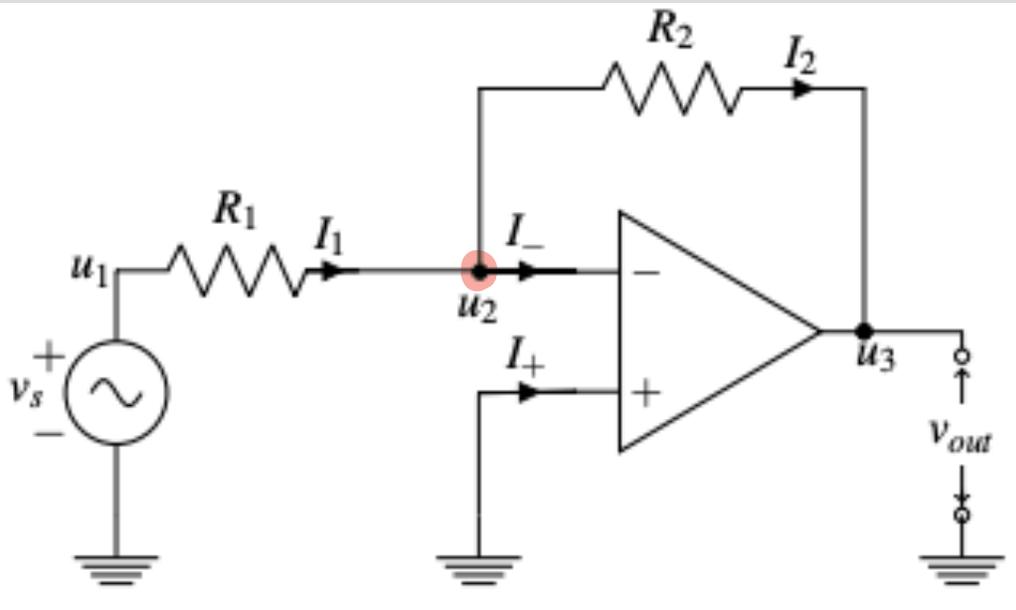

GR2: $U^+ = U^-$

$$U_2 = U^-$$

$$U^+ = 0 \Rightarrow U_2 = 0$$

GR1 + KCh ($I_1 = I_2 + I^-$)


$$\frac{U_2 - U_1}{R_1} = \frac{U_3 - U_2}{R_2} + I^-$$

$$-\frac{U_1}{R_1} = \frac{U_3}{R_2}$$


$$\frac{V_{out}}{V_{in}} = -\frac{R_2}{R_1}$$

Example circuit 2 (trans-resistance amplifier)


$$I^+ = 0 \Rightarrow U_1 = U_2$$

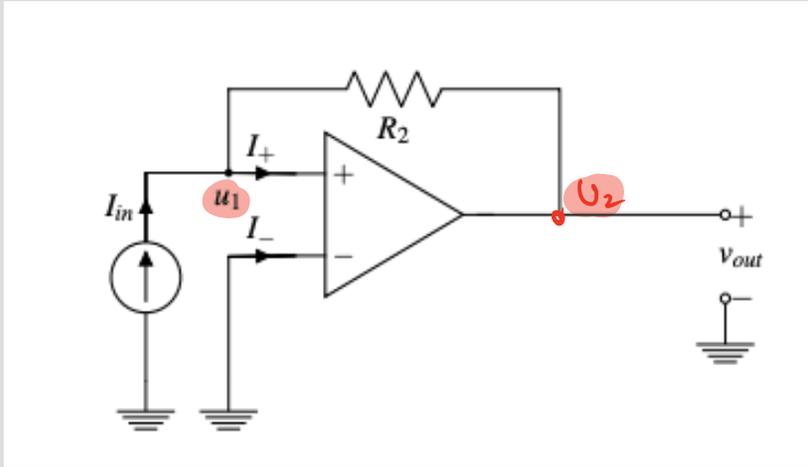

Invert polarity
⇓

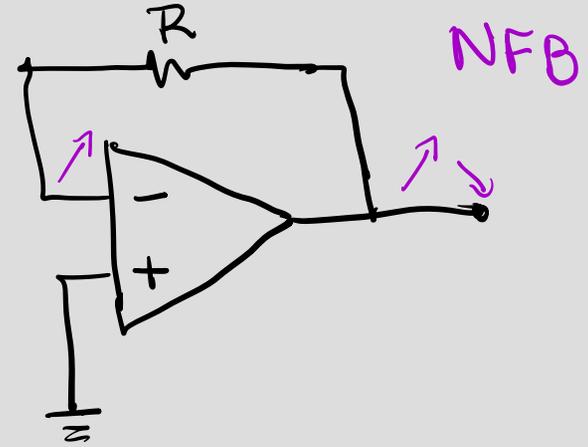


Step 1

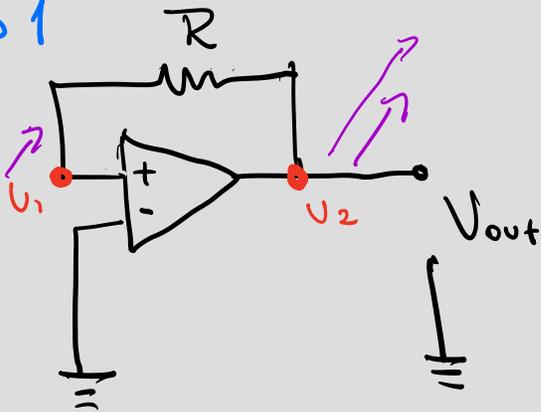

Step 2: check for NFB

Increase output →
+ moves up
output increases
by a lot

X Not in NFB

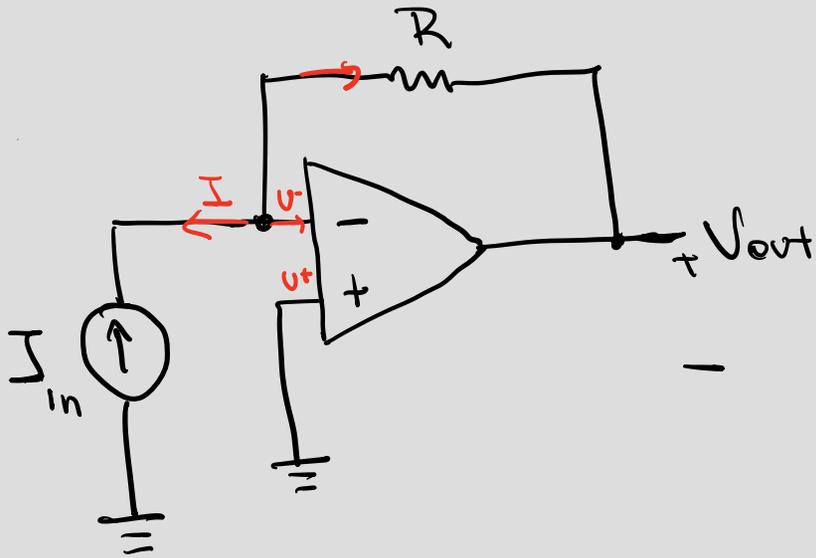

$$\text{NFB} : U^+ = U^-$$

$$U^+ = 0 \rightarrow U^- = 0$$

GR # 2

$$\frac{U^- - V_{out}}{R} + (-I_{in}) + I^- = 0$$


$$-\frac{V_{out}}{R} = I_{in}$$

$$V_{out} = -I_{in} R$$


$$\frac{V_{out}}{I_{in}} = -R$$


The input is current ; output is voltage ; we use this model in the lab for photo sensors !

Example circuit 3 -

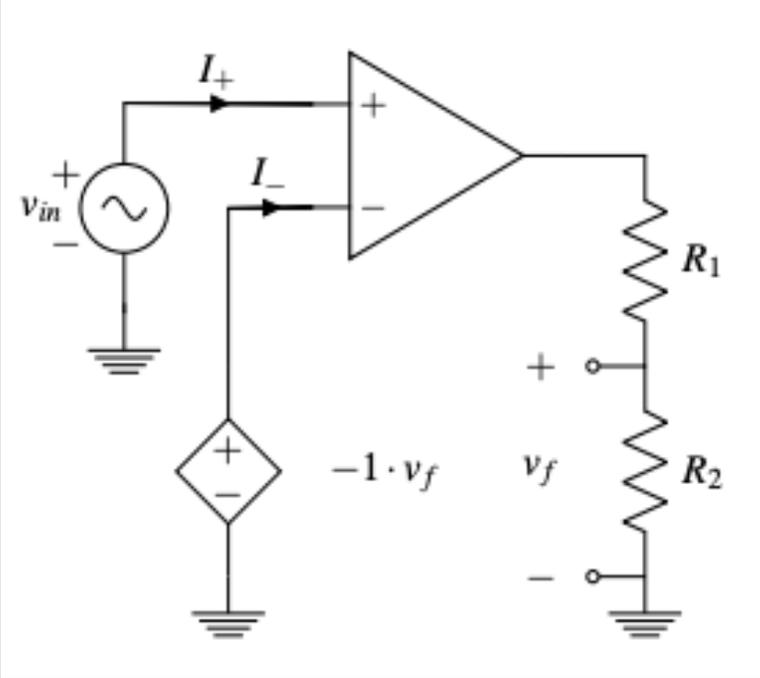

Check NFB:

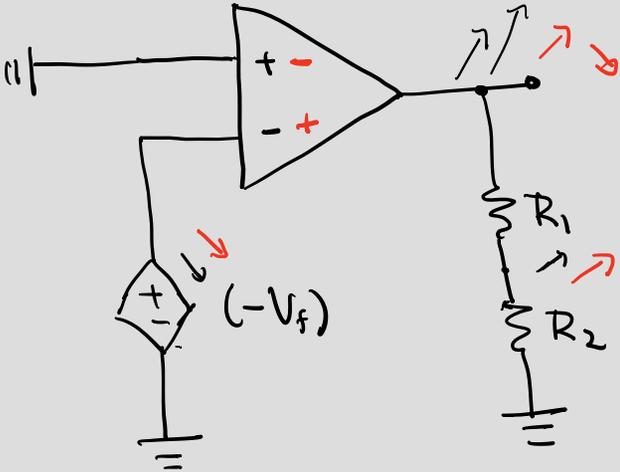

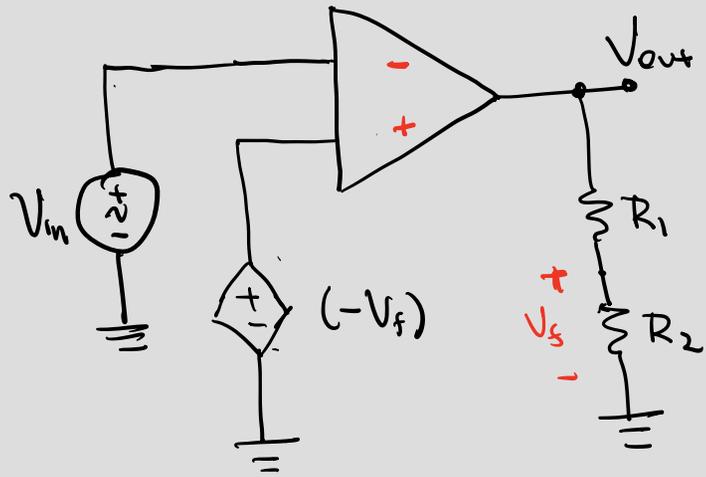

Voltage Divider

$$V_s = \frac{R_2}{R_1 + R_2} \cdot V_{out}$$

NFB (GR#2) $U^- = U^+$

$$V_{in} = -V_s$$

U^- U^+

$$V_{in} = - \frac{R_2}{R_1 + R_2} V_{out} \Rightarrow \frac{V_{in}}{V_{out}} = - \frac{R_2}{R_1 + R_2}$$


$$A_V = \frac{V_{out}}{V_{in}} = - \frac{R_1 + R_2}{R_2} = - \left(1 + \frac{R_1}{R_2} \right)$$

Artificial Neuron


(Energy Efficient Neural Networks) — Yes we can!

- Neurons in our brain are interconnected.
- The output of a single-neuron is dependent on inputs from several other neurons.
- This idea is represented with vector-vector multiplication – the output is a linear combination of several inputs.
- An artificial neuron circuit must perform addition and multiplication.
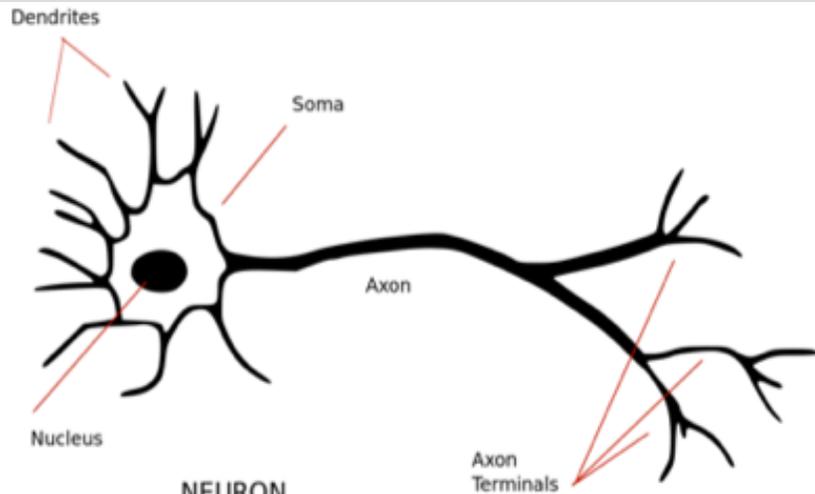
$$\begin{bmatrix} a_1 & a_2 \end{bmatrix} \cdot \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = a_1 v_1 + a_2 v_2$$



A biological Neuron

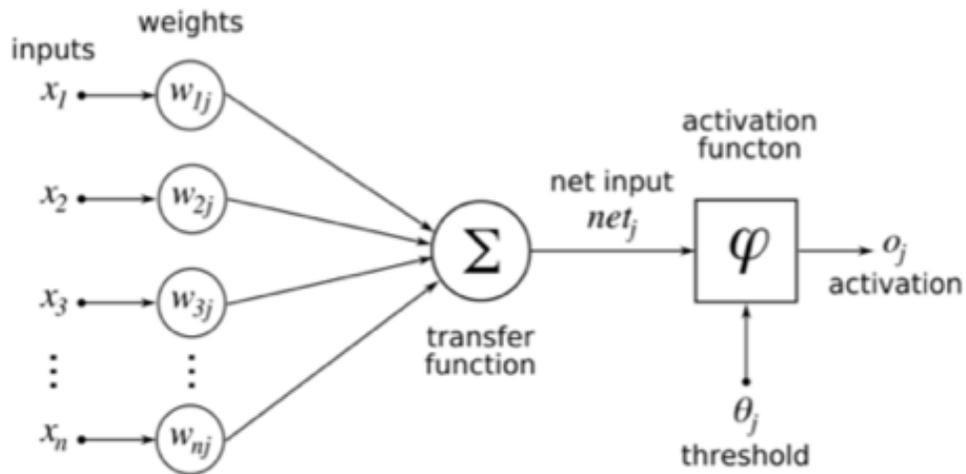


An Artificial Neuron


Artificial Neuron

- Neurons in our brain are interconnected.
- The output of a single-neuron is dependent on inputs from several other neurons.
- This idea is represented with vector-vector multiplication – the output is a linear combination of several inputs.
- An artificial neuron circuit must perform addition and multiplication.

Inverting summer $V_3 = V_{out} - V^-$

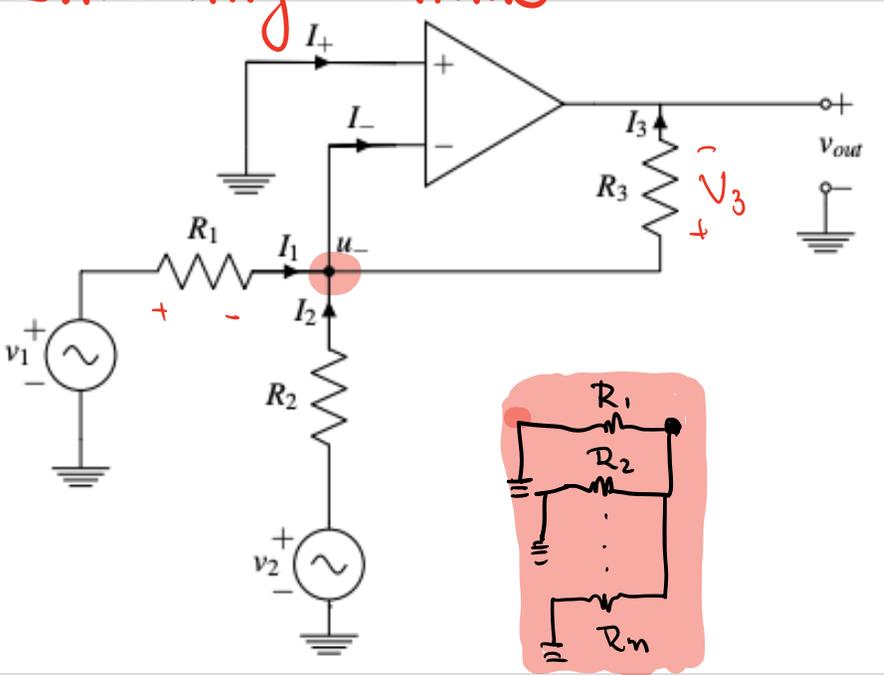

Check for NFB:

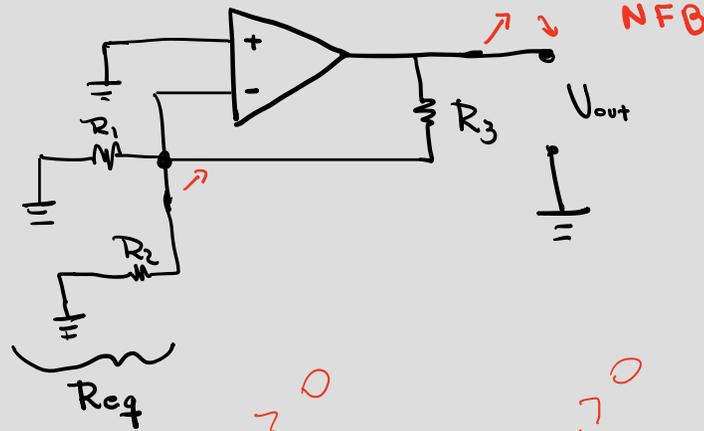

$$V^+ = V^- : \text{GRZ}$$

$$V^+ = 0 \Rightarrow V^- = 0$$

$$\text{KCL} : \frac{V^- - V_1}{R_1} + \frac{V^- - V_2}{R_2} = I^- + \frac{V_{out} - V^-}{R_3}$$

$$-\frac{V_1}{R_1} - \frac{V_2}{R_2} = \frac{V_{out}}{R_3}$$

$$V_{out} = -\frac{R_3}{R_1} V_1 + \left(-\frac{R_3}{R_2} V_2\right) + \dots + \left(-\frac{R_3}{R_N} V_N\right)$$


only negative
coef.

Weights
 $a_{11} V_1$ $a_{12} V_2$

a_{1N} V_N

All weights are negative: How can we make a_1 and a_2 positive?

Add another inverting amplifier circuit.

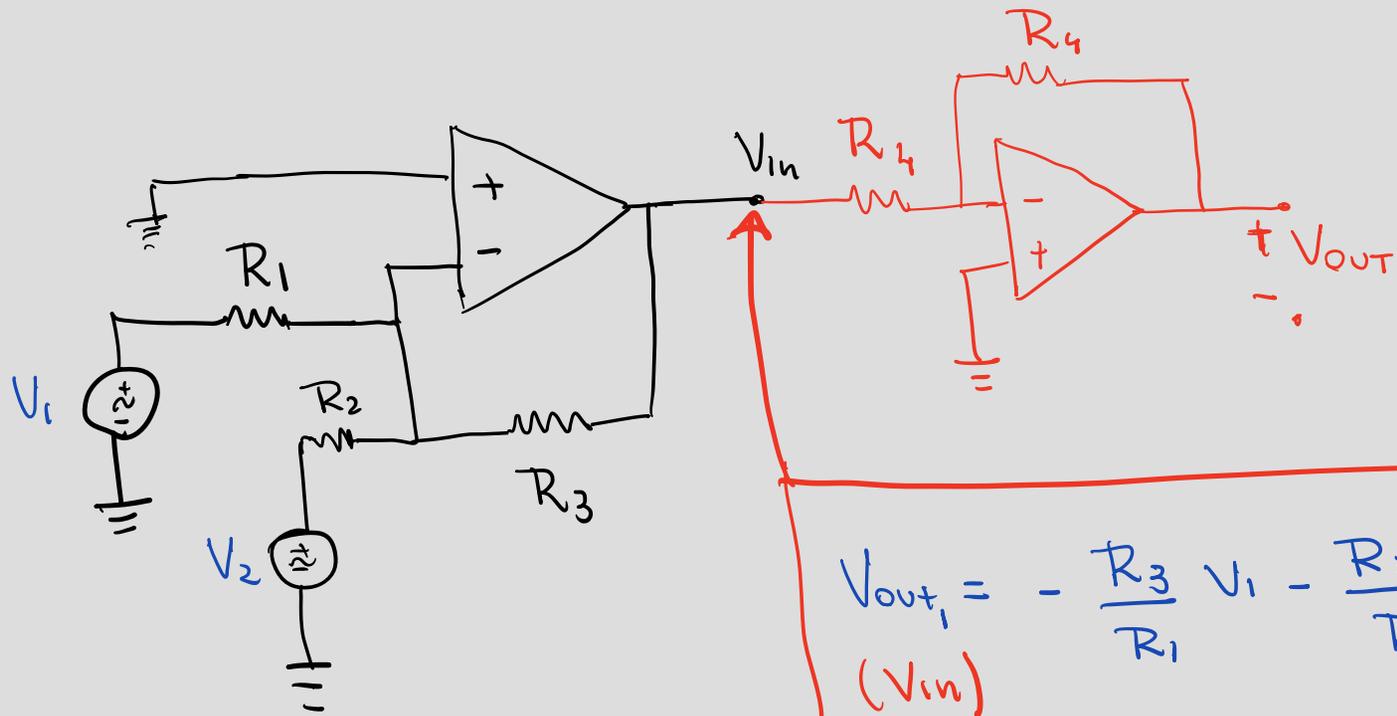

$$V_{out_1} = - \frac{R_3}{R_1} V_1 - \frac{R_3}{R_2} V_2$$

(V_{in})

$$\frac{V_{out}}{V_{in}} = - \frac{R_2}{R_1}$$


↳ result from inverting amplifier

$$V_{out} = - \frac{R_2}{R_1} V_{in}$$

$V_{out} \approx - V_{in}$ (when R_1 and R_2 are the same)

Unity Gain Buffer

↳ Allows us to isolate circuits

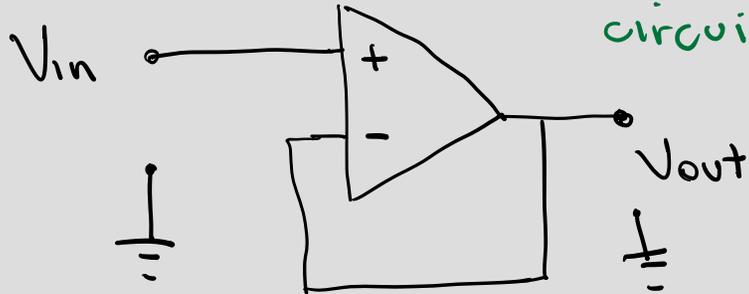

$$U^+ = V_{in}$$


$$U^- = V_{out}$$

GR2

$$U^+ = U^-$$


$$V_{in} = V_{out}$$

Speaker Design

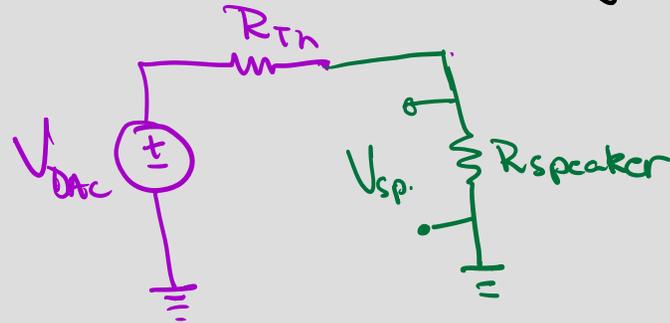

$$V_{speaker} = \frac{V_{DAC}}{126}$$

loading

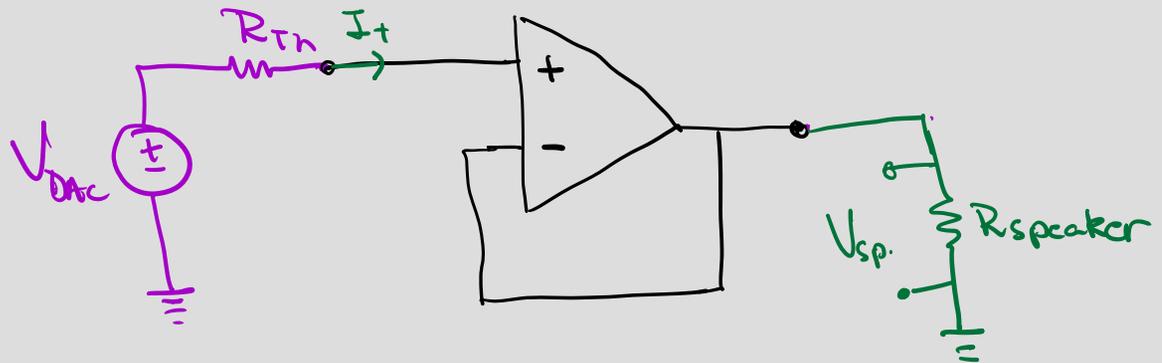

$$I^+ = 0 \Rightarrow U^+ = V_{DAC}$$

$$V_{out} = V_{speaker} = U^- \Rightarrow U^+ = U^-$$

$$V_{DAC} = V_{speaker}$$