





Welcome to EECS 16A!

Designing Information Devices and Systems I



Ana Claudia Arias and Miki Lustig Fall 2022

Module 2 Lecture 1 Introduction to Circuit Analysis (Note 11)



Designing Information Devices and Systems



Analog World S

Sensor

Processing

Actuation







System Example - Electromyography

- Monitors muscle activity
- Used in gesture recognition
- Impact in rehabilitation

- X Bulky electrodes
- X Poor accuracy low resolution
- X Computation performed on external devices





System Example - Electromyography



In Module 2 we will learn how to analyze circuits



We need to be able to go from a real-world circuit, to a circuit model, and vice versa.

In Module 2 we will learn how to analyze circuits



We need to be able to go from a real-world circuit, to a circuit model, and vice versa.



Then we need to know how to solve the model...

Note: the tool used by computers to analyze circuits is *linear algebra*!

First: Science Review

actinides



post-transition metals metalloids

reactive nonmetals noble gases

First: Science Review



First: Science Review







| Element | Symbol | E | |
|-----------|--------|---|--|
| Scandium | Sc | 1 | |
| Titanium | Ti | 1 | |
| Vanadium | v | 1 | |
| Chromium | Cr | 1 | |
| Manganese | Mn | 1 | |
| Iron | Fe | 1 | |
| Cobalt | Co | 1 | |
| Nickel | Ni | 1 | |
| Copper | Cu | 1 | |
| Zinc | Zn | | |

| Electronic Configuration | |
|---|--|
| 1s2 2s2 2p6 3s2 3p6 3d1 4s2 | |
| 1s ² 2s ² 2p ⁶ 3s ² 3p ⁶ 3d ² 4s ² | |
| $1s^2 2s^2 2p^6 3s^2 3p^6 3d^3 4s^2$ | |
| 1s ² 2s ² 2p ⁶ 3s ² 3p ⁶ 3d ⁵ 4s ¹ | |
| 1s ² 2s ² 2p ⁶ 3s ² 3p ⁶ 3d ⁸ 4s ² | |
| 1s ² 2s ² 2p ⁶ 3s ² 3p ⁶ 3d ⁶ 4s ² | |
| 1s ² 2s ² 2p ⁶ 3s ² 3p ⁶ 3d ⁷ 4s ² | |
| $1s^2 2s^2 2p^6 3s^2 3p^6 3d^8 4s^2$ | |
| $1s^2 2s^2 2p^6 3s^2 3p^6 3d^{10} 4s^1$ | |
| 1s2 2s2 2p6 3s2 3p6 3d10 4s2 | |

Second: a tiny bit of Solid-State Physics



Electronic Devices depend on movement of charges

Electrical Quantities

| Quantities | Analytical Symbol | Units |
|------------|-------------------|-------------|
| Current | I | Amperes (A) |
| Voltage | V | Volts (V) |
| Resistance | R | Ohms (IL) |



In the lab



In the lab









Definitions needed to analyze a circuit : Circuit Diagram

Collection of elements, where each element has some voltage across it and some current through it



Key circuit elements: Wire





Key circuit elements: Resistor







Key circuit elements: Open circuit

+

Velem









Key circuit elements: Current Source Iclem Iclem = Is Velem = ? (V is set by external circuit) I clem can be positive or negative Velem and

Definitions needed to analyze a circuit : Circuit Diagram

Collection of elements, where each element has some voltage across it and some current through it





Circuit Analysis Algorithm

Voltage = difference of two potential

Find: currents through elements and potentials of inputs/outputs of each element (junctions)



Electronic Devices depend on movement of charges



We always need to define a reference for potentials. Ground = 0

 V_2, V_3 potentials $V_1 = U_1 - U_2$ $V_2 = U_2 - U_3$ $= V_1 + V_2$

Rules for circuit analysis: Kirchoff's Voltage Law (KVL)

Sum of Voltages across the elements in a loop equal zero

$$+ V_{elc} - V_{el} - V_{el}$$

Rules for circuit analysis: Kirchoff's Current Law (KCL)

The current flowing into any junction must equal the current flowing out



Iel, = Iclz Jolz = Jolz Ida = Ida Joly = John

Iels + Iak = Iel:

Rules for circuit analysis: KCL within the element

The current flowing into any junction must equal the current flowing out

