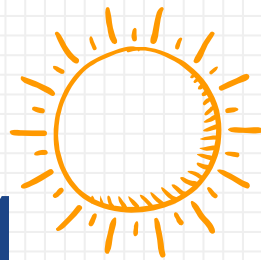


EECS16A Imaging 1



TA, ASE, ASE, ASE

Please sit in front of a lab station with a partner! You need to use the towers!



IMPORTANT: ROOM CAPACITY

- We can't have more than 49 people in this room
- If lab is full, we will first kick out **all** waitlisted folks
- If you **lie** about being enrolled in this section, you will be **REMOVED** from the course
 - Please be ready to show either CalCentral enrollment or an email confirming a switch.

Semester Outline



Imaging
Module




Touchscreen
Module





Locationing
Module

Why Imaging?

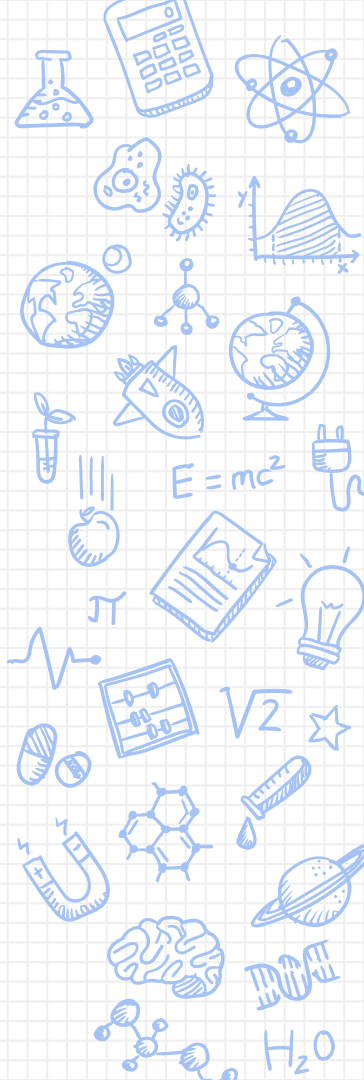- Use linear algebra techniques to capture real world images with limited sensors
- Today:
 - Finding a link between physical quantities and voltage
 - If you can digitize it, you can do anything (IOT devices, internet, code, processing)




Our circuit

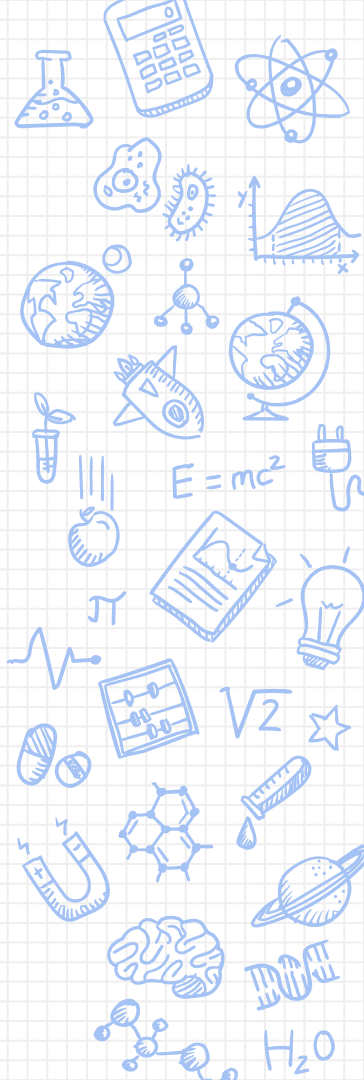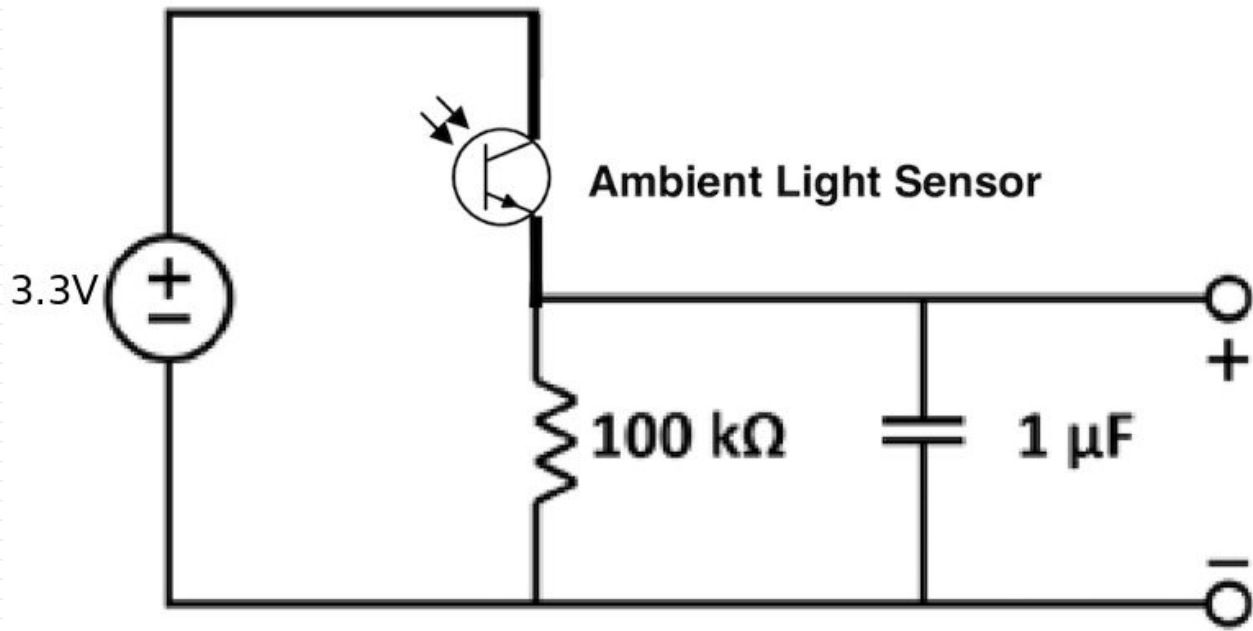

A Little Physics: Voltage, Current, and Resistors

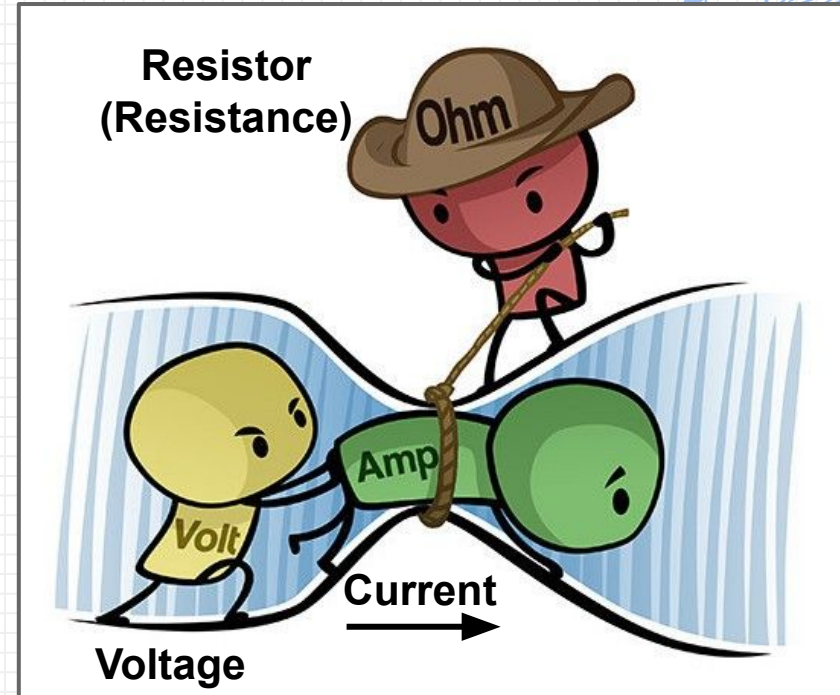- **Voltage [Volts]** - pushes charge through circuit
- **Current [Amps]** - flow of charge through circuit
 - 1 Amp = 1 charge per second
- **Resistor [Ohms]** - circuit component that resists the flow of charge through circuit







Simple Circuit: The Tools™

- Components
 - Resistors
 - Capacitors
 - Voltage Source
- Wires / Jumpers [male-to-male vs male-to-female]



What's in your circuit? : Resistors

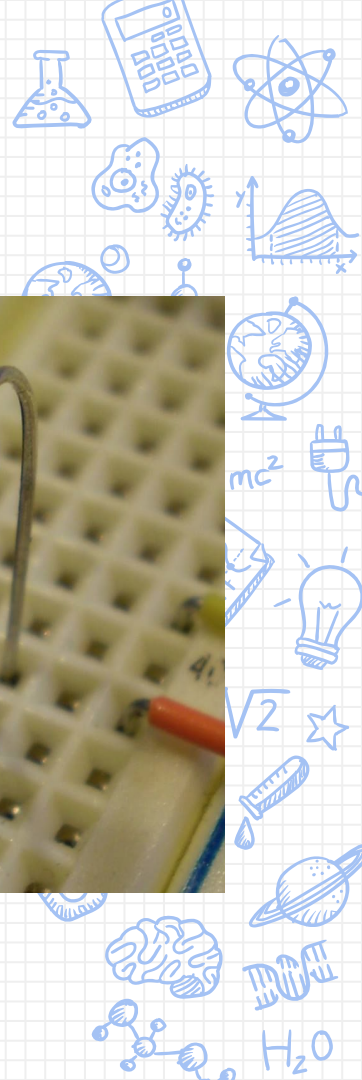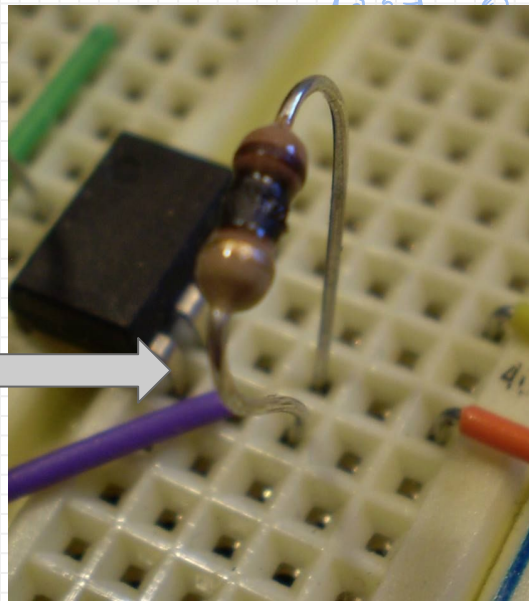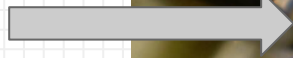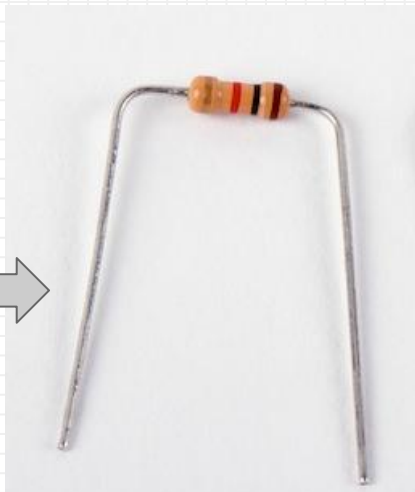


What's on your circuit? : Resistors



4 Band Resistor Color Coding




COLOR	1ST BAND	2ND BAND	MULTIPLIER	TOLERANCE
BLACK	0	0	x1 Ω	
BROWN	1	1	x10 Ω	$\pm 1\%$
RED	2	2	x100 Ω	$\pm 2\%$
ORANGE	3	3	x1000 Ω	
YELLOW	4	4	x10000 Ω	
GREEN	5	5	x100000 Ω	$\pm 0.5\%$
BLUE	6	6	x1000000 Ω	± 0.25
VIOLET	7	7	x10000000 Ω	± 0.10
GREY	8	8		± 0.05
WHITE	9	9		
GOLD			0.1	$\pm 5\%$
SILVER			0.01	$\pm 10\%$

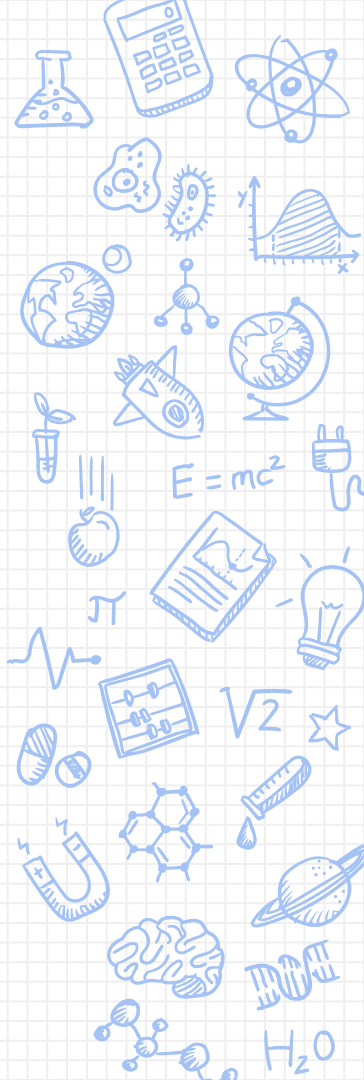

A diagram showing a wheel of radius R on a horizontal surface. A horizontal force F is applied at the center of the wheel, pointing to the right. A friction force f is shown at the point of contact between the wheel and the surface, pointing to the left. The weight of the wheel acts vertically downwards from the center.


Equipment for Today: Capacitors

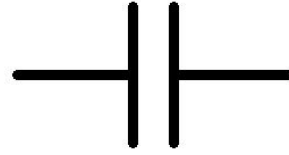


They store your charge!
Called capacitors because they
have a set capacity (in Farads)



Equipment for Today: Wires/Jumpers

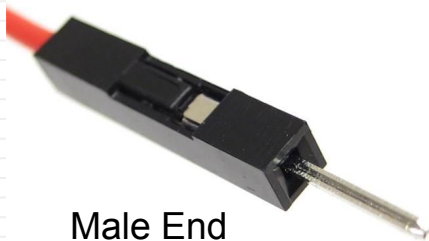

Male End


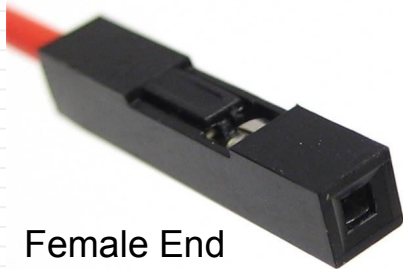


Female End




Equipment for Today: Voltage Source

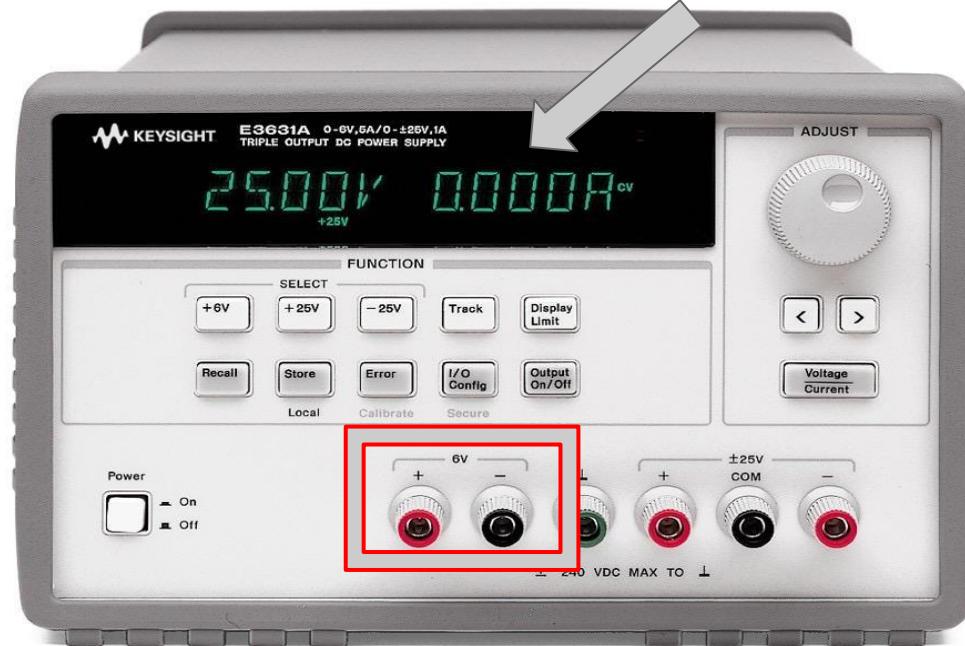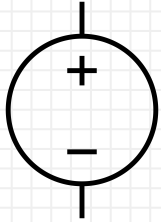**IMPORTANT: Always keep
current limited @ 0.1 A limit**




PSU cables
are hanging
on back wall

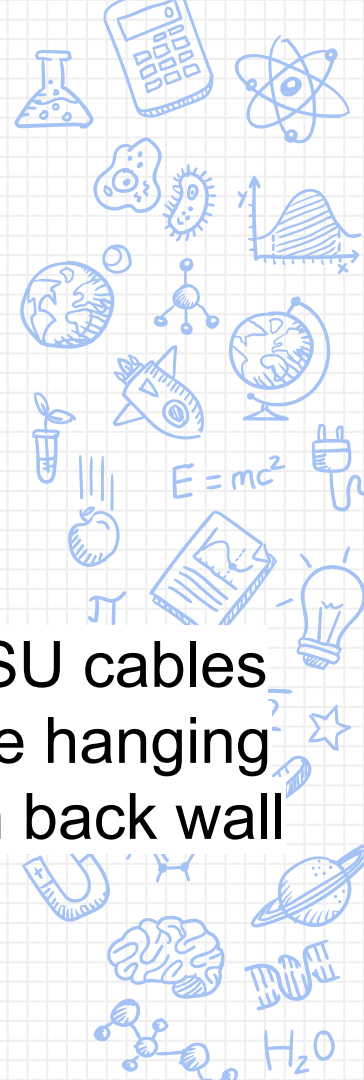

Simple Circuit: The Theory™

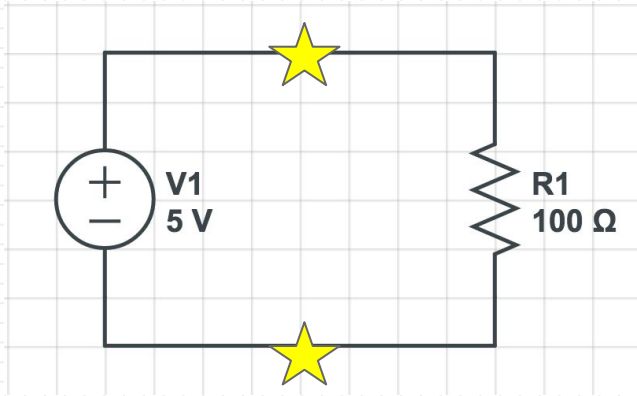- Components (Resistors, LEDs, Capacitors)
- Nodes
 - Point in circuit where circuit elements meet
 - Wire between components are considered part of one node



What components?

Voltage source, resistor


How many nodes? **2**

Where are these nodes?



Simple Circuit: The Theory™

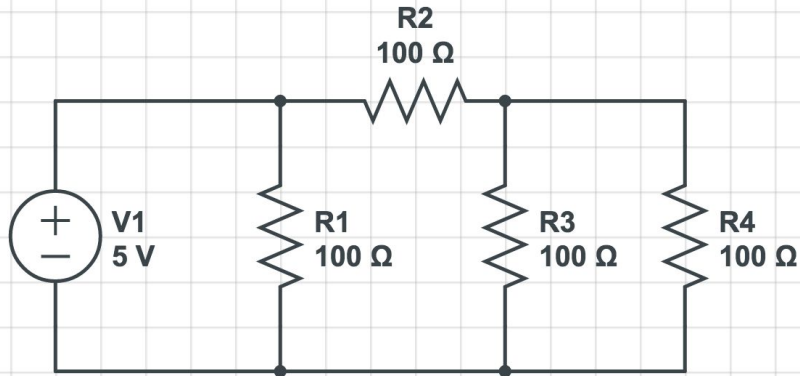- Components (Resistors, LEDs, Capacitors)
- Nodes
 - Point in circuit where circuit elements meet
 - Wire between components are considered part of one node



What components?

How many nodes?



Where are these nodes?







Breadboard Do's and Don't's

How do we make this circuit? →

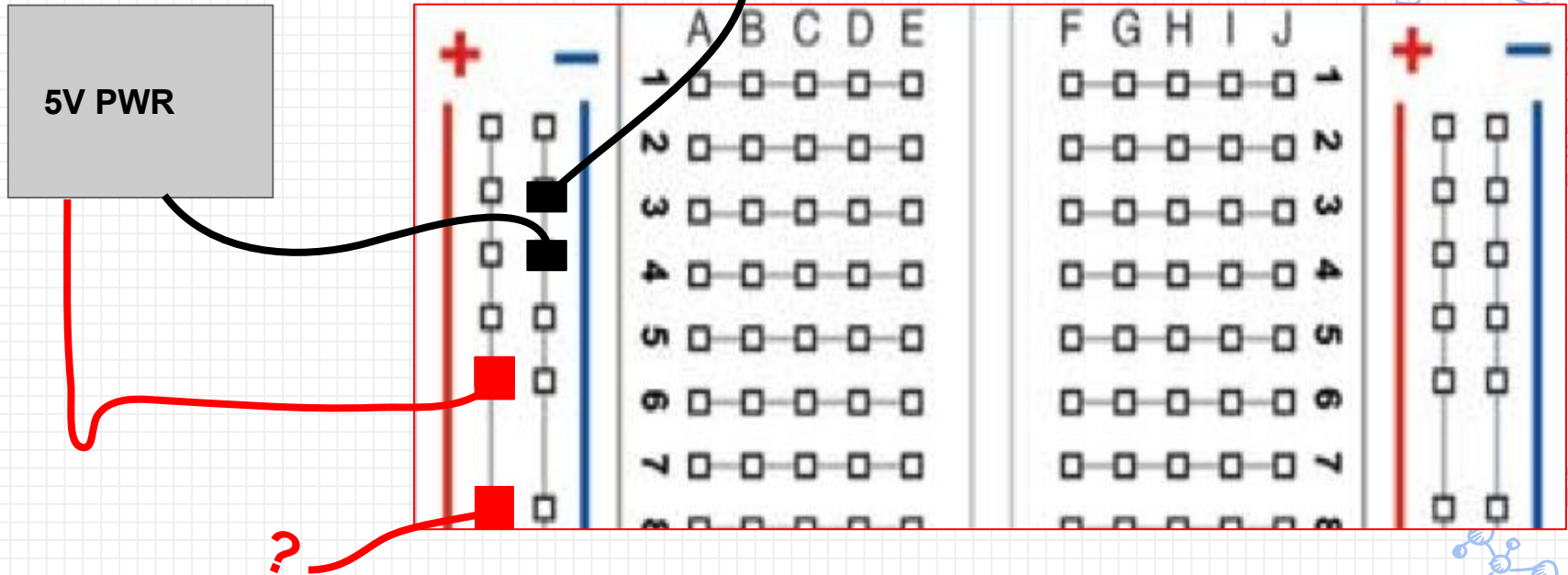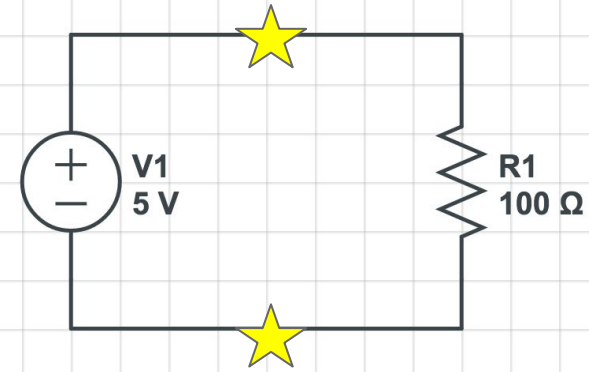



Breadboard Do's and Don't's

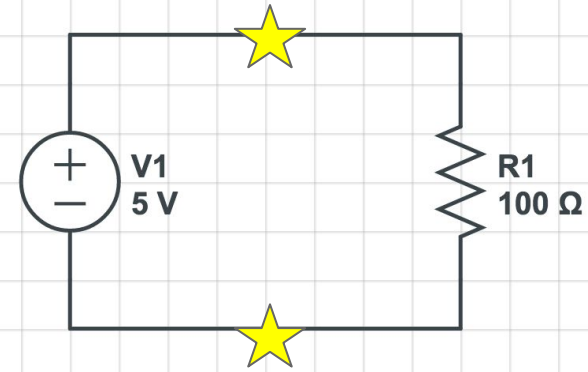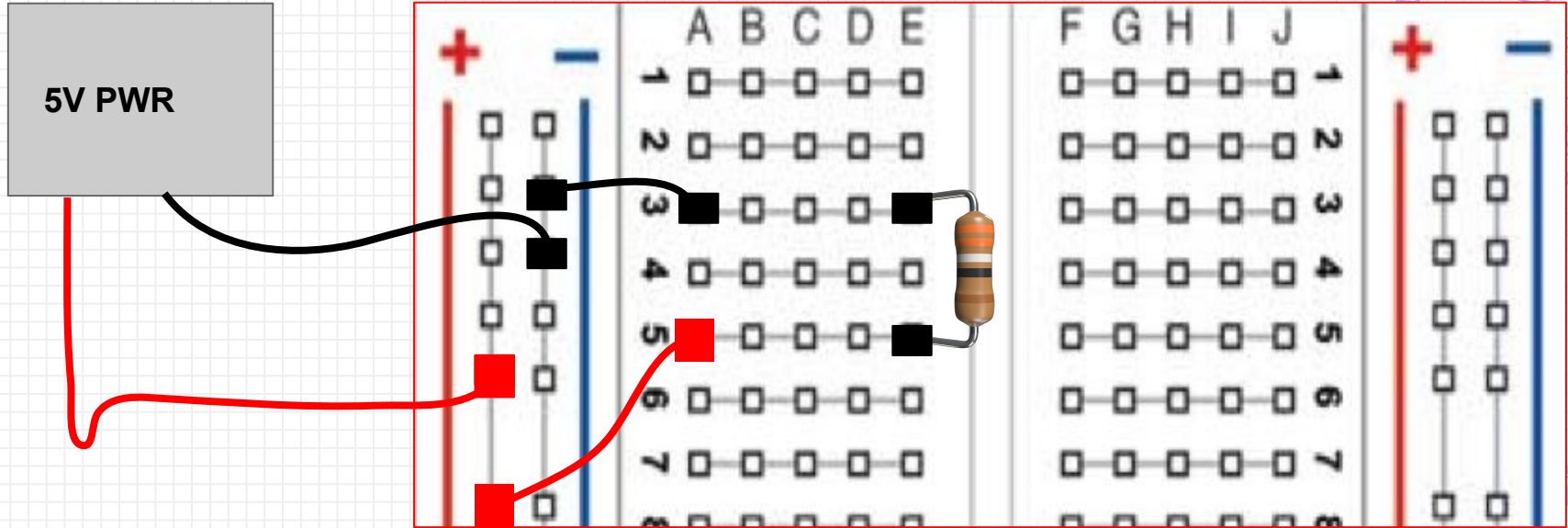- ✓ **Do** plug component's ends into two different rows - separate nodes





Breadboard Do's and Don't's

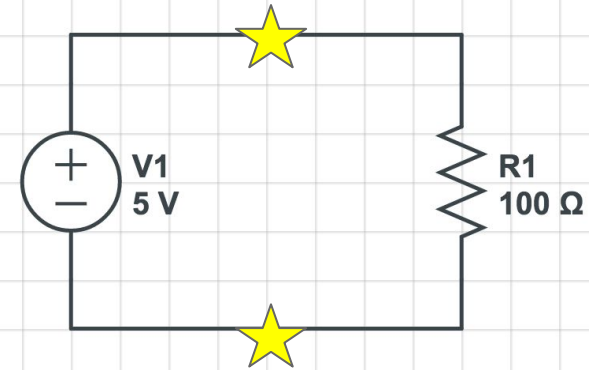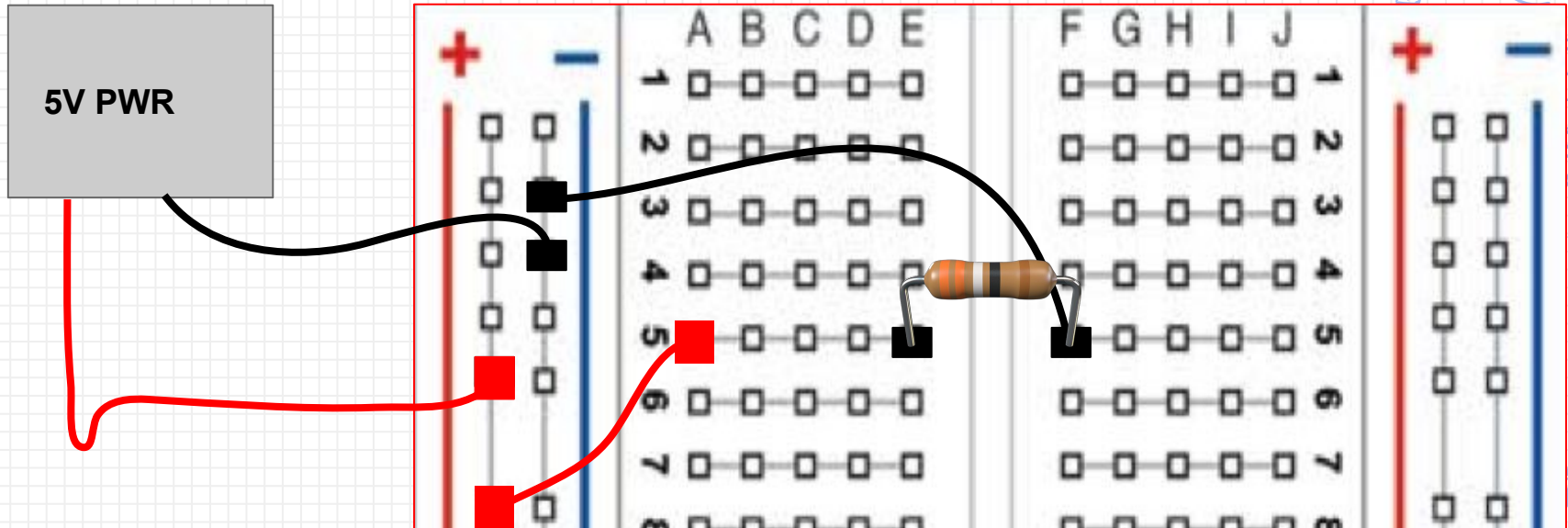- ✓ **Do** plug components across the gap in your breadboard - A-E and F-J are separate




Breadboard Do's and Don't's

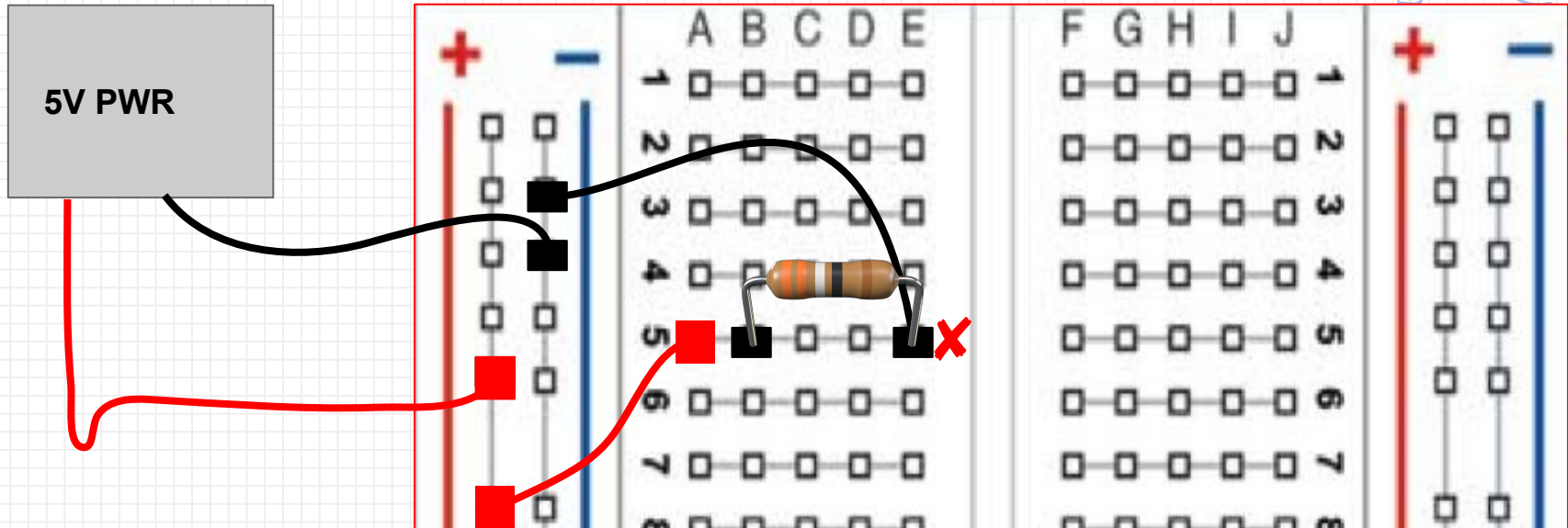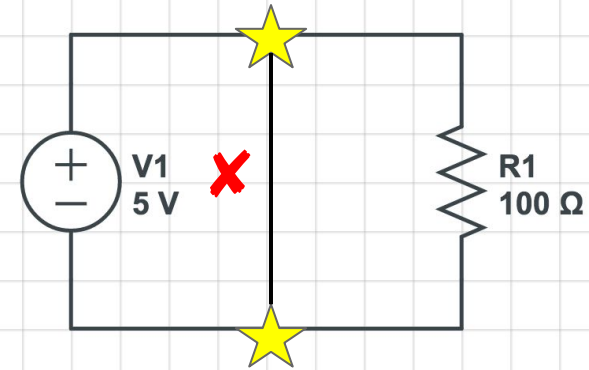✗ **Do not** plug both ends of component into the same row! This creates a short



Light-detecting Circuit

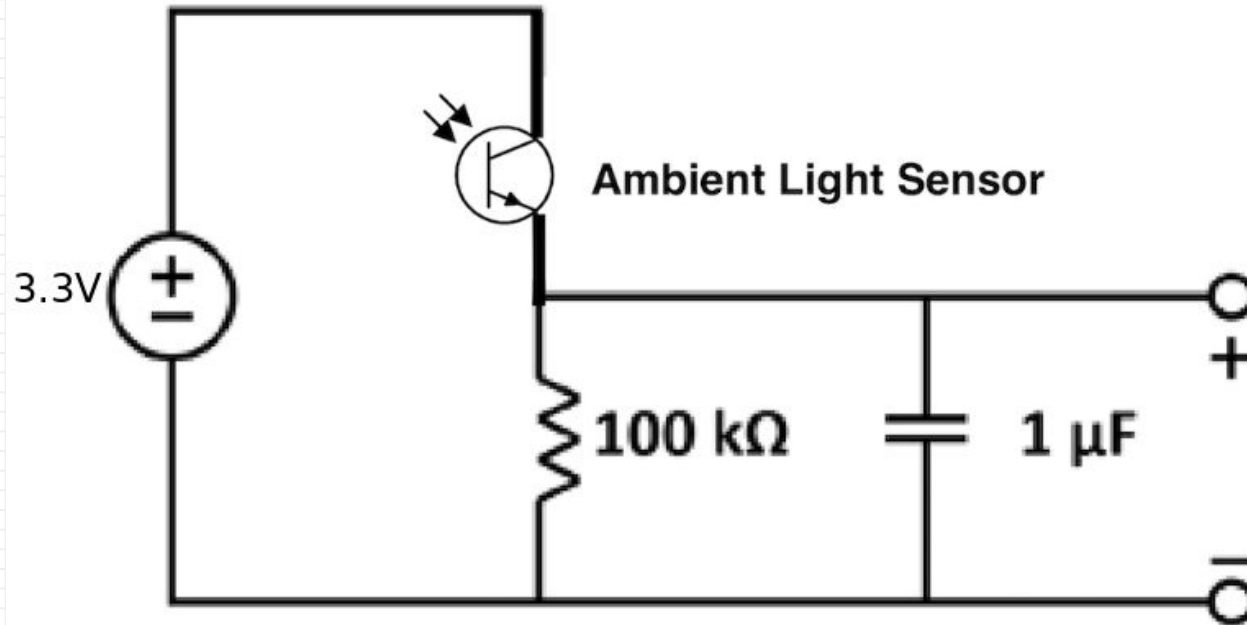

How to get your lab kit (1 per student)

- After finishing ~20% of the lab you will reach the end of the “Obtaining a Lab Kit” section
- Call over a lab staff member and: (also described in lab notebook)
 - Show answers to PSU, Oscilloscope, and lab kit questions
 - Demonstrate how to use the equipment
 - Be able to name components in the lab kit
- Everything in kit (bag+Launchpad) is yours to keep but **EACH STUDENT HAS TO BRING THEM BACK TO EVERY LAB**



-

EE16A Spring 2016					
Schedule Homework Staff Resources Policies					
Calendar					
Wk	Date	Lecture Topic	Section	Lab	Homework
1	01/19 Tu	Introduction to Class: Welcome to EE16A! (Slides)	Section 0A	Installation Get Started: iPython + NumPy	Homework 0
	01/21 Th	Intro to Imaging/Tomography (Slides) (Notes)	Section 0B: dis0B.pdf		
2	01/26 Tu	Vectors and Systems of Equations (Notes)	Section 1A: TBA	Get Started: Lab Equipment	Homework 1
	01/28 Th	Linear Dependence	Section 1B: TBA		
3	02/02 Tu	Matrices and Transformations	Section 2A: TBA	Imaging Lab 1: Building a Light Sensor	Homework 2
	02/04 Th	Rank and Inverses	Section 2B: TBA		
4	02/09 Tu	Vector Spaces	Section 3A: TBA	Imaging Lab 2: Single Pixel Scanning	Homework 3
	02/11 Th	Nullspaces and Flows	Section 3B: TBA		
5	02/16 Tu	Special	Section 4A: Midterm review (no worksheet)	Buffer Week	Homework 4
Midterm					

X BEFORE LEAVING, PLEASE RETURN THE WIRES, POWER OFF YOUR MACHINES, AND SIGN OUT OF THE COMPUTERS

- **EXTRACT (unzip) the downloaded file before doing anything - ask us if you have questions**
- **SHIFT+RIGHT CLICK** on a folder window to open in **CMD**
 - Select 'open powershell window here'
 - **'ipython notebook'** to open notebook inside prompt
 - Let us know **IMMEDIATELY** if you're having trouble with this
- Keep output of the voltage source **off** while you are building things
- Probes are in the back
- **Make sure you are using the right resistor (Brown Black Gold) - get at TA desk**
- **Make sure your ambient light sensor is in the right direction**
- **DO NOT PIP INSTALL ANYTHING, keep the install as is**
- Complete the lab in **PAIRS**, do ONE setup per group
- Make sure current limit of power supply is set to **0.1A**
- **DON'T LEAVE/CLEAN UP WITHOUT BEING CHECKED OFF FIRST**

