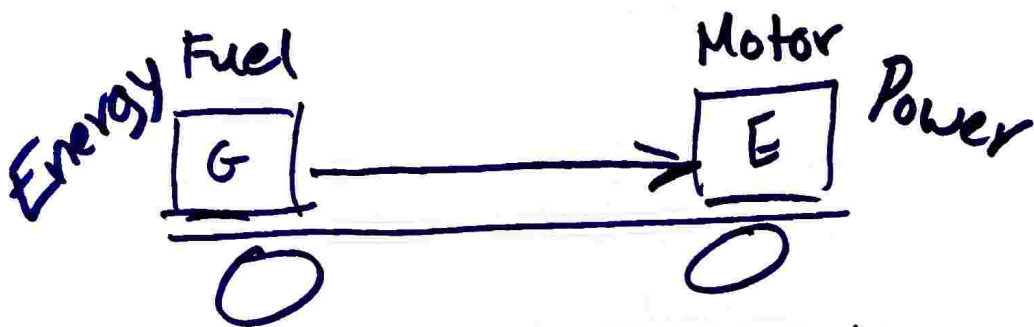


EECS 16A

Module 2, Lecture 3

- Energy & Power
- 2D Resistive Touchscreen



$$P = \frac{\Delta E}{\Delta t} = \frac{dE}{dt}$$

$$E = P \cdot \Delta t = \int_0^{\Delta t} P(t) dt$$

Power P [W]

Energy E [J] = [W · s]

Light Bulb Ex.

$$10 \text{ W}, 1 \text{ hr} = 10 \text{ W}\cdot\text{h}$$

$$\begin{aligned} E &= 10 \text{ W}\cdot 1 \text{ hr} \\ &= 10 \text{ W}\cdot 3600 \text{ s} \\ &= 36,000 \text{ W}\cdot\text{s} \\ &= 36,000 \text{ J} \\ &= 36 \text{ kJ} \end{aligned}$$

$$E = 10 \text{ W}\cdot 10 \text{ h} = 100 \text{ Wh}$$

PG&E:
\$0.19/kWh

Battery : stores energy

"Energy" \rightarrow

$$2000 \text{ [mAh]} = C_{\text{bat}}$$

"AA" battery $V = 1.5\text{V}$

$$\text{Energy} = V \cdot C_{\text{bat}}$$

$$= 1.5\text{V} \times 2000 \text{ mAh}$$

$$= 3 \text{ kV} \cdot \text{mAh}$$


$$= 3 \text{ VAh}$$

$$= 3 \text{ Wh}$$


Battery (cont')

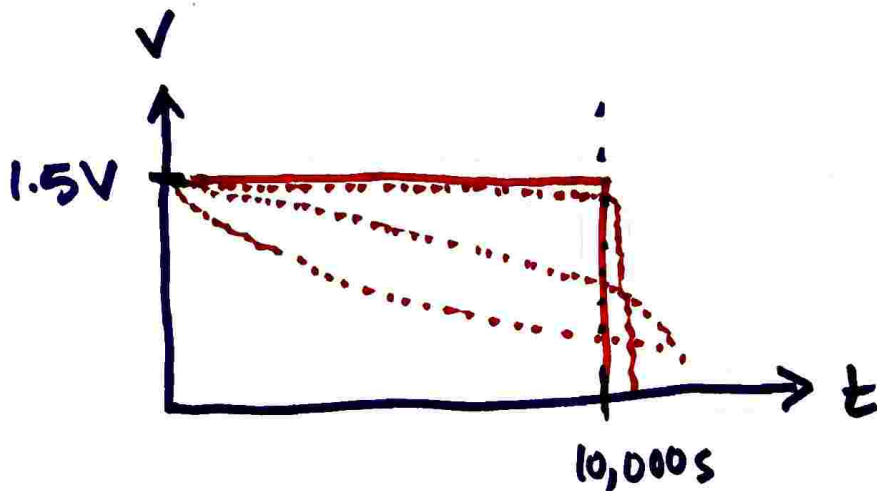2.3.3.a

$$3 \text{ Wh} = 3 \cdot 3600 \text{ W}\cdot\text{s}$$
$$= 10,000 \text{ Ws}$$



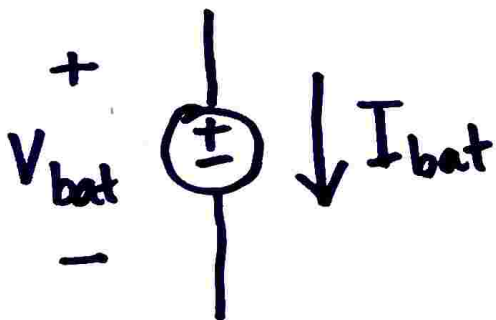1 Ah
@ 250 mA \Rightarrow 4 hr
@ 2 A \Rightarrow 30 min



P.S.C.

$$E, P \rightarrow V, I$$

Define:

$$V_{ab} = \frac{dE_{ab}}{dQ} = [V]$$

↑
charge

Charge $Q \equiv$ electrons $[C]$

Current: $I = \frac{\Delta Q}{\Delta t} = \frac{dQ}{dt} [A]$


$$1 A = \frac{1 C}{1 S}$$

$$1 C = 6.2 \times 10^{18} \text{ electrons}$$

$\sim 10^9$ people

$$P = \frac{dE}{dt} = \underbrace{\frac{dE}{dq}}_V \cdot \underbrace{\frac{dq}{dt}}_I = V \cdot I$$

Passive Sign Convention (P.S.C.)

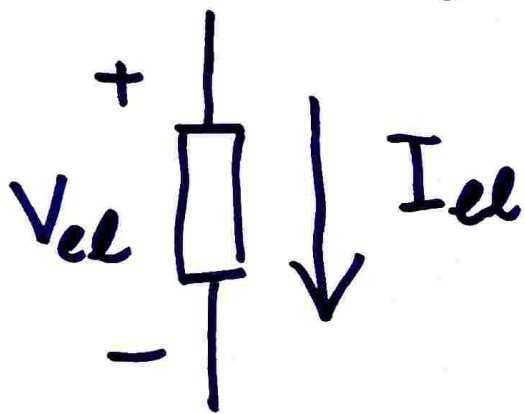


e.g.
(resistor)

$$P_{\text{dissipation}} = V_{el} \cdot I_{el}$$

\uparrow
 $P_{\text{delivered}}$

Power Example 1

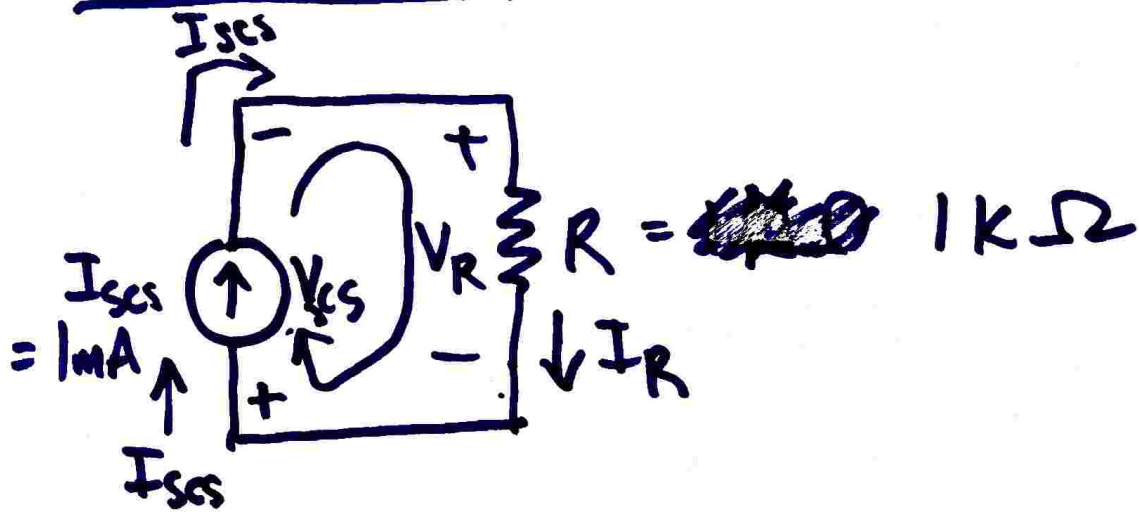

$$I_R = I_{cs}$$

$$\begin{aligned} V_R &= I_R R \\ &= (1\text{mA})(1\text{k}\Omega) \\ &= 1\text{V} \end{aligned}$$

Resistor

Power:

$$\begin{aligned} P_R &= I_R \cdot V_R \\ &= (1\text{mA})(1\text{V}) \\ &= 1\text{mW} \Rightarrow \text{dissipated!} \end{aligned}$$

Apply KVL:

$$V_{scs} + V_R = 0$$

$$V_{scs} = -V_R = -1V$$

Current Source

$$P_{scs} = I_{sc} \cdot V_{scs}$$

$$= (1mA) \cdot (-1V)$$


$$= -1mW \Rightarrow \text{delivered!}$$

Energy is conserved, so :


$$P_R + P_{scs} = 0$$

$$1mW + (-1mW) = 0 \quad \checkmark$$

Short Circuit

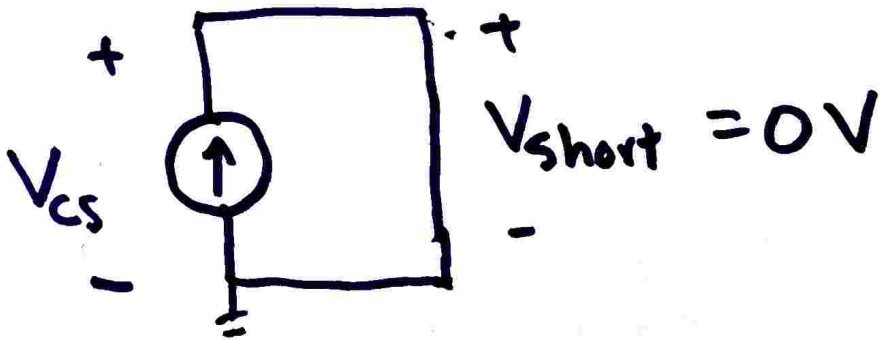
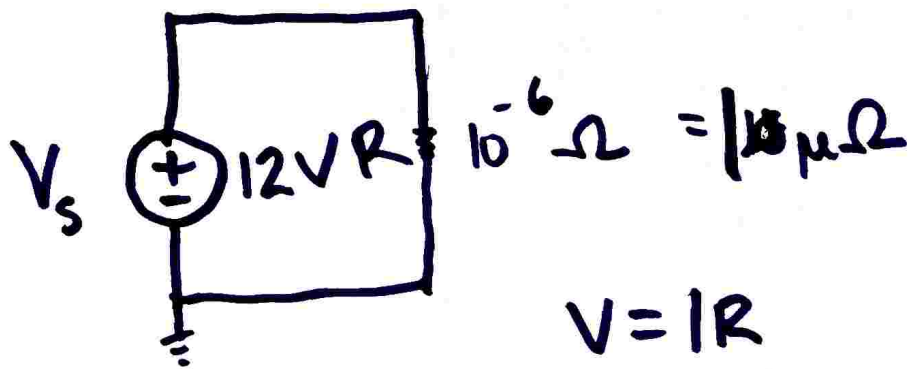
$$P_{cs} = V_{cs} \cdot I_{cs} = 0 \cdot I_{sc} = 0$$








$$V = IR$$


$$I = \frac{V_s}{R} = \frac{12V}{10 \mu\Omega} = 12,000,000 A$$

12 MA

1D Touchscreen → 2D Touchscreen

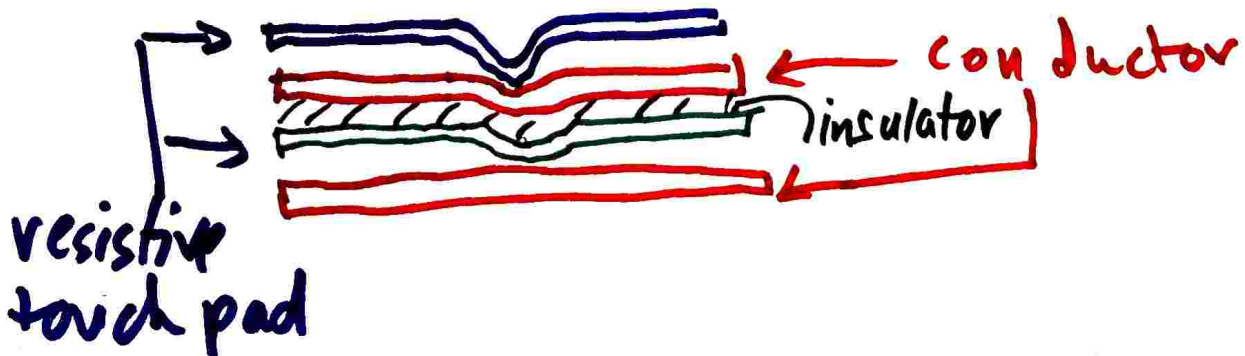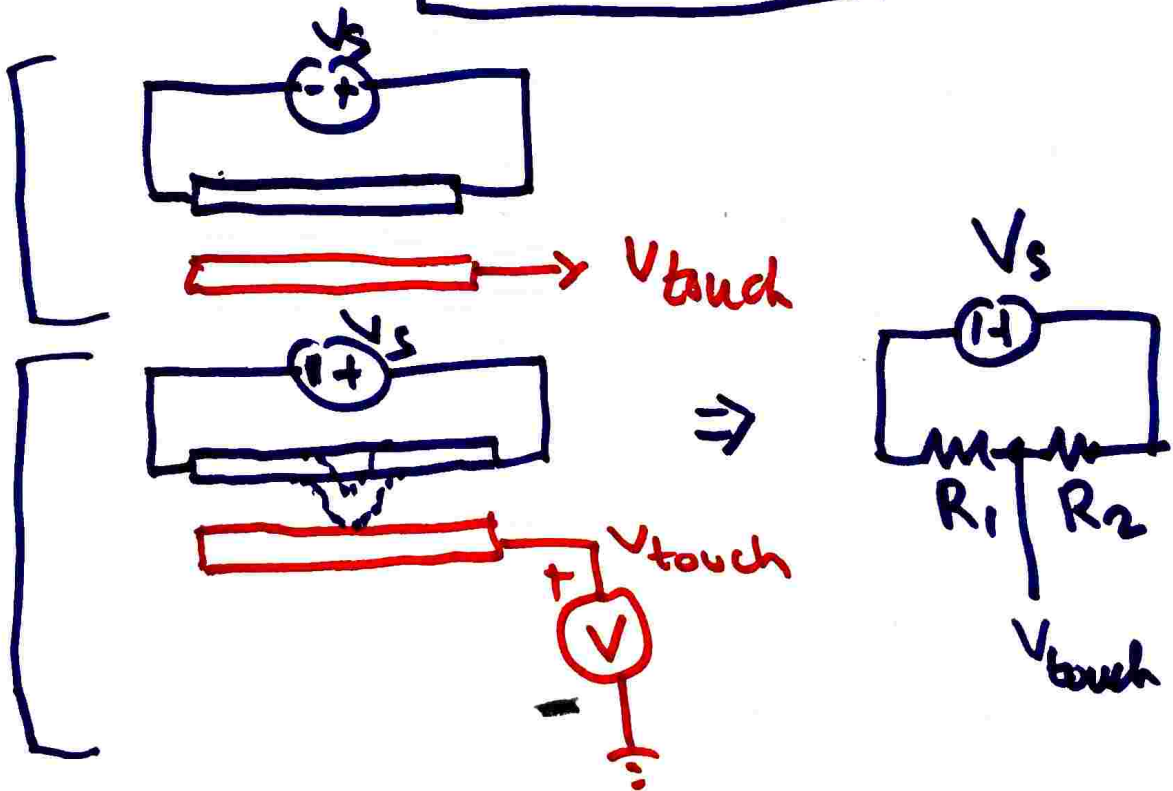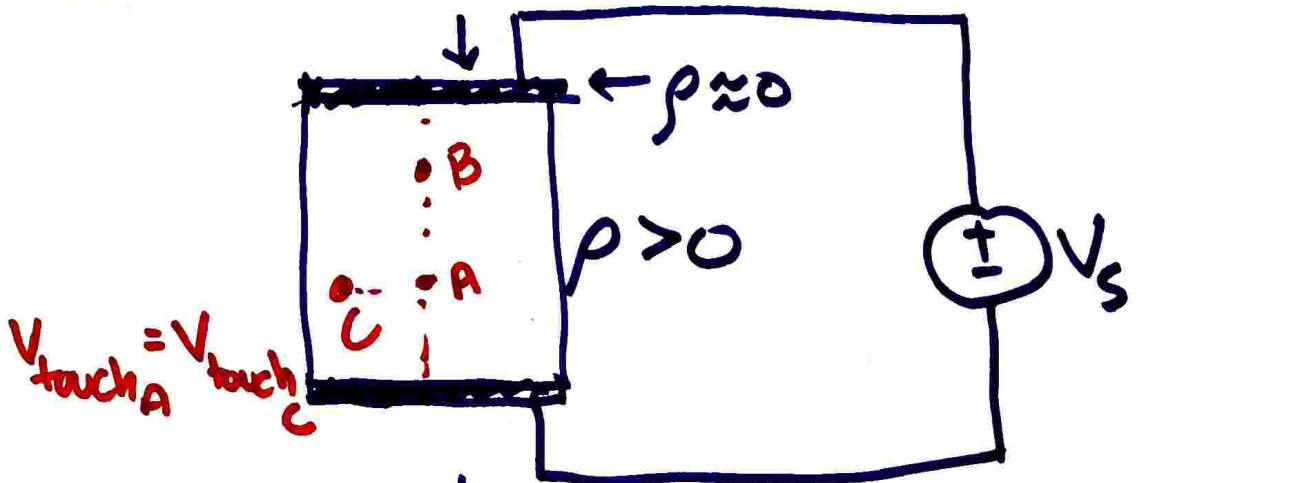

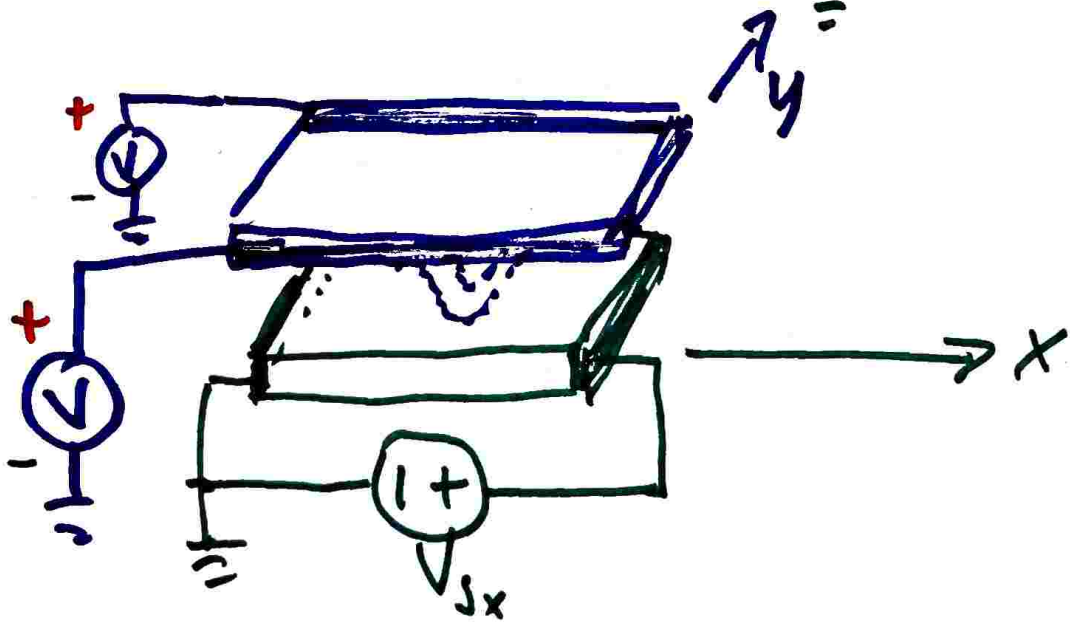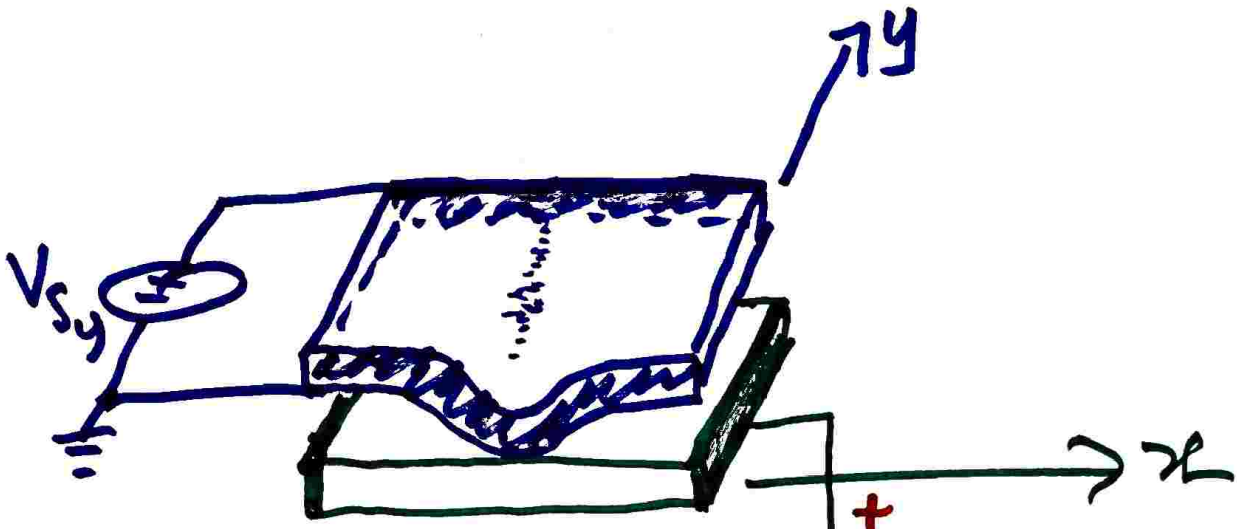

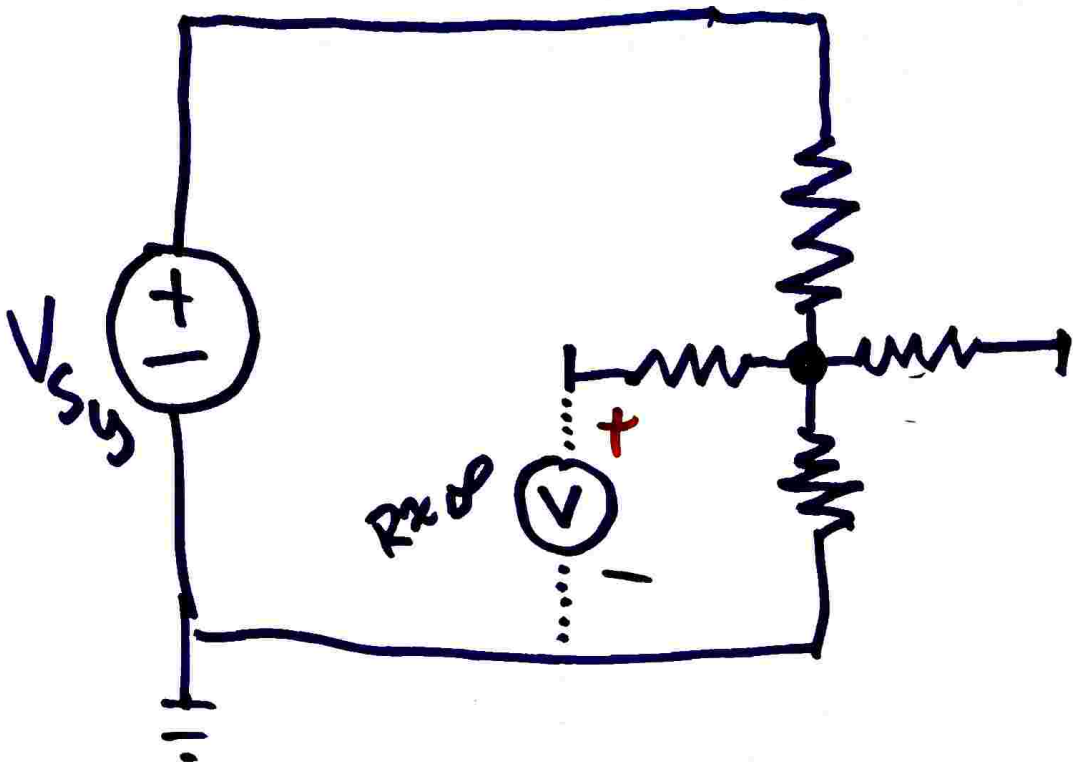

2.3.12

