
EECS 16A Designing Information Devices and Systems I Discussion 7A

1. Material Resistivity

- (a) Recall the 1D resistive touch screen model introduced in class. In this model, the top layer can be thought of as a resistor, while the bottom layer can be thought of as a wire. When the top layer is touched, it flexes at the touch point and makes contact with the bottom layer. This results in a voltage divider.

| Material | Resistivity ρ ($\Omega \text{ cm}$) | Conductivity $1/\rho$ ($\Omega^{-1} \text{ cm}^{-1}$) |
|-------------------|---|--|
| Silver | 1.6×10^{-5} | 6.3×10^4 |
| Aluminum | 2.7×10^{-5} | 3.7×10^4 |
| Carbon (graphite) | 10×10^{-2} | 10 |
| Rubber | 100×10^{12} | 1×10^{-14} |

Given the following list of materials and their resistivity/conductivity, which materials would be good to use as a top layer, and which would be good to use as a bottom layer? Why?

- (b) Let's say you want to make your own **10 cm** long resistor out of **graphite**. You need the resistance to be **1 Ω** . Recall the equation for resistance: $R = \rho \frac{L}{A} = \rho \frac{L}{W \cdot H}$
- What are some possible widths and heights of your resistor?
 - Can you think of advantages of having a wide and thin resistor? How about advantages of a narrow and thick resistor?

2. More Node Voltage Analysis!

Given $I_s = 1\text{ A}$, $R_1 = 4\ \Omega$, $R_2 = 2\ \Omega$, $R_3 = 3\ \Omega$, and $R_4 = 10\ \Omega$, find the voltage across and the current through each of the resistors in the circuit below:

