

---

# EECS 16A    Designing Information Devices and Systems I

## Spring 2022    Homework 8

---

**This homework is due Friday, March 18, 2022 at 23:59. Self-grades are due Monday, March 21, 2022, at 23:59.**

### Submission Format

Your homework submission should consist of **one** file.

- `hw8.pdf`: A single PDF file that contains all of your answers (any handwritten answers should be scanned).

Submit the file to the appropriate assignment on Gradescope.

### 1. Mid-semester Class Survey

Please fill out the EECS16A Mid-semester Class Survey ([click here](#)). We appreciate your feedback towards improving this class — this really helps us improve future semesters as well as latter parts of this class. This survey is completely anonymous.

An incentive to do this: If more than 70% of the class fills out this survey in full, we will add 1 point to everyone's MT1 score. If more than 80% of the class fills out this survey in full, we will add 2 point to everyone's MT1 score. Please note that EECS 47D students are not required to fill out the survey.


### 2. Reading Assignment

For this homework, please read Note 15. Note 15 covers superposition and equivalence, two very helpful techniques to help simplify circuit analysis.


### 3. Equivalent Resistance

**Learning Goal:** *The objective of this problem is to practice finding the equivalent to a series/parallel combination of resistors.*

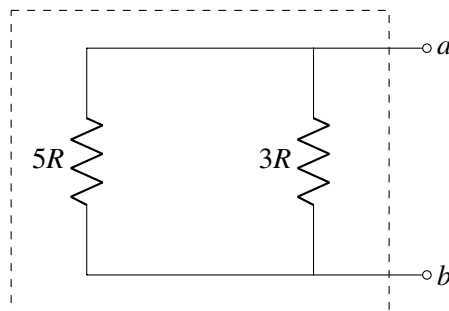
- (a) Find the equivalent resistance looking in from points  $a$  and  $b$ . In other words, express the resistive network in the dashed box as one resistor.



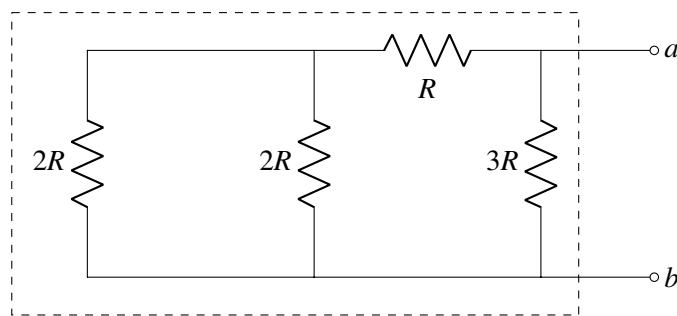
- (b) Find the equivalent resistance looking in from points  $a$  and  $b$ . In other words, express the resistive network in the dashed box as one resistor.



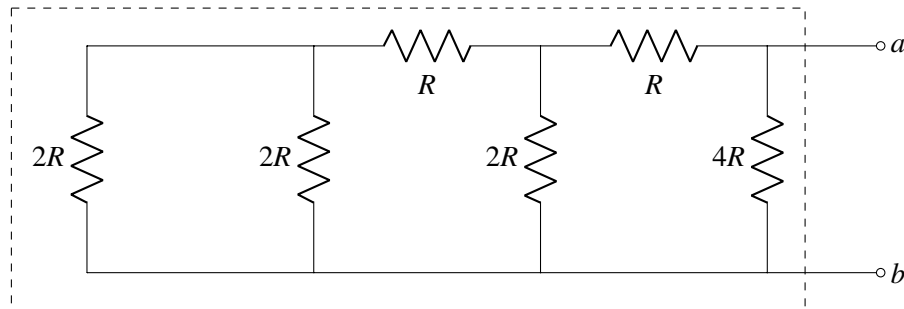
(c) Find the equivalent resistance looking in from points  $a$  and  $b$ . In other words, express the resistive network in the dashed box as one resistor.



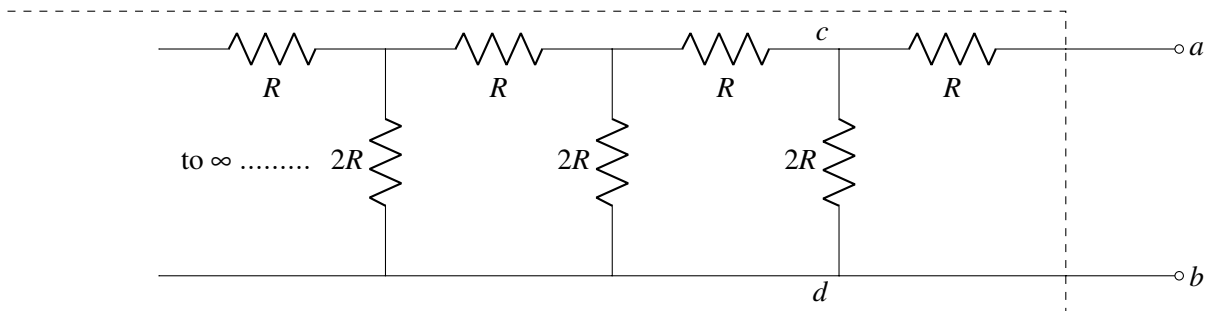(d) **(OPTIONAL, CHALLENGE)** Find the equivalent resistance for the infinite ladder looking in from points  $a$  and  $b$ . In other words, express the resistive network in the dashed region as one resistor. (Hint: Let's call the resistance looking in from  $a$  and  $b$  as  $R_{in}$ , and the resistance looking to the left from points  $c$  and  $d$  as  $R_{in1}$ . Replace the entire circuit to the left of points  $c$  and  $d$  with a resistor whose value is given by  $R_{in1}$ . Find the relationship between  $R_{in}$  and  $R_{in1}$  using this circuit. Find another relationship between  $R_{in}$  and  $R_{in1}$  using the fact that the ladder is infinite. For an infinite ladder, adding another branch does not change the equivalent resistance. Think of this as a convergent infinite series.)




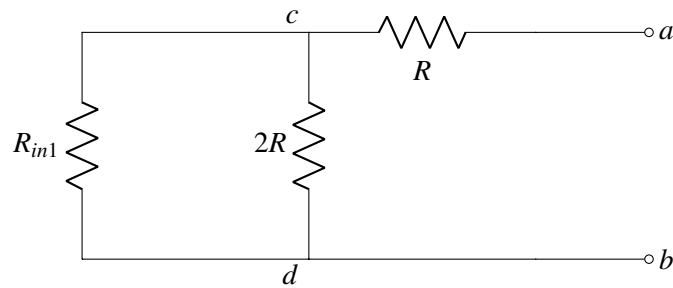As a first step you can replace the circuit looking to the left from  $c$  and  $d$  by  $R_{in1}$ .





#### 4. Why Bother With Thévenin Anyway?

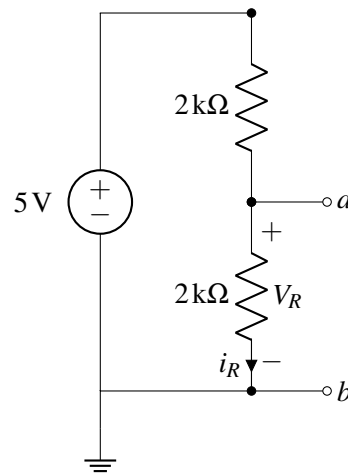- (a) Find a Thévenin equivalent for the circuit shown below looking from the terminals  $a$  and  $b$ . (Hint: That is, find the open circuit voltage  $V_R$  across the terminals  $a$  and  $b$ . Also, find the equivalent resistance looking from the terminals  $a$  and  $b$  when the input voltage source is zeroed.)




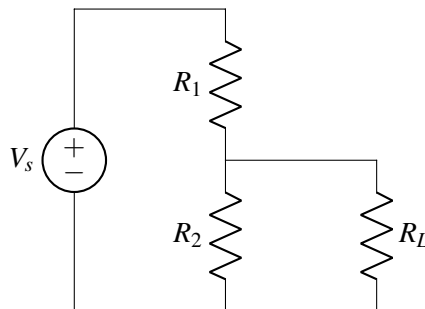- (b) Now consider the circuit shown below where a load resistor of resistance  $R_L$  is attached across the terminals  $a$  and  $b$ . Compute the voltage drop  $V_R$  across the terminals  $a$  and  $b$  in this new circuit with the attached load. Express your answer in terms of  $R_L$ . (Hint: We have already computed the Thévenin equivalent of the unloaded circuit in part (a). To analyze the new circuit, attach  $R_L$  as the load resistance across the Thévenin equivalent computed in part (a), as shown in the figure below. One of the main advantages of using Thévenin (and Norton) equivalents is to avoid re-analyzing different circuits which differ only by the amount of loading.)




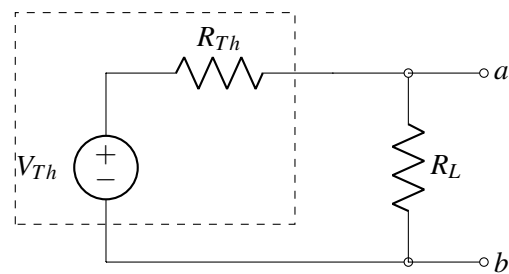


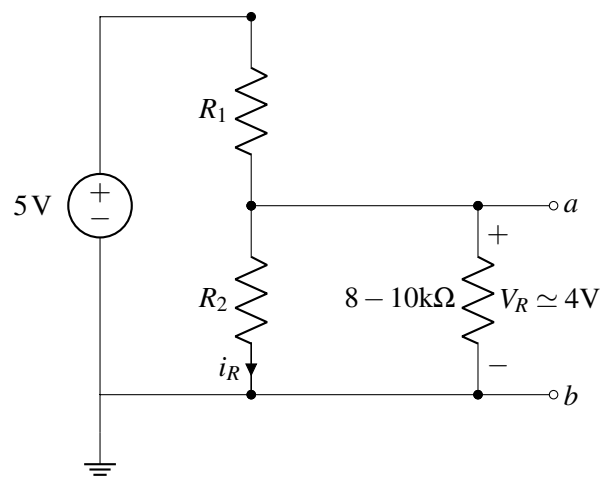- (c) Now compute the voltage drop  $V_R$  for three different values of  $R_L$  equal to  $8/3 \text{ k}\Omega$ ,  $8 \text{ k}\Omega$ ,  $80 \text{ k}\Omega$ ? What can you comment on the value of  $R_L$  needed to ensure that the loading does not reduce the voltage drop  $V_R$  compared to the unloaded voltage  $V_R$  computed in part (a)?
- (d) Say that we want to support loads in the range of  $8 \text{ k}\Omega$  to  $10 \text{ k}\Omega$ . We would like to maintain  $4 \text{ V}$  across these loads. How can we approximately achieve this by setting  $R_1$  and  $R_2$  in the following circuit?



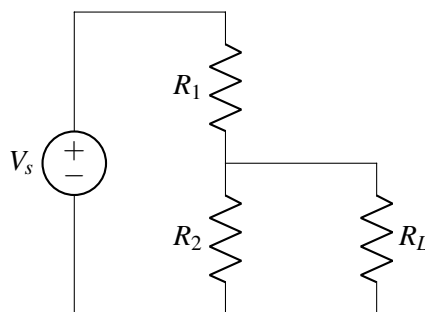
- (e) Thus far, we have seen how to use Thevenin equivalents to compute the voltage drop across a load without re-analyzing the entire circuit. We would like to see if we can use the Thevenin equivalent for power computations. Consider the case where the load resistance  $R_L = 8 \text{ k}\Omega$ ,  $V_S = 5 \text{ V}$ ,  $R_1 = R_2 = 2 \text{ k}\Omega$ . Compute the power dissipated across the load resistor  $R_L$  both using the original circuit and the Thevenin equivalent. Are they equal? Now, compute the power dissipated by the voltage source  $V_S$  in the original circuit. Also, compute the power dissipated by the Thevenin voltage source  $V_{Th}$  in the Thevenin equivalent circuit. Is the power dissipated by the two sources equal?



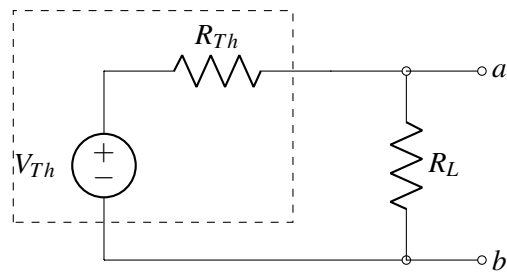

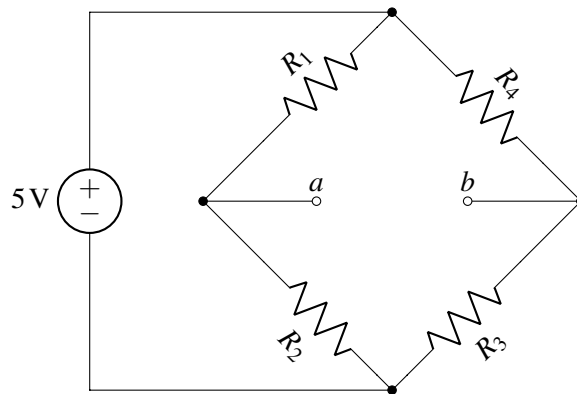
## 5. Wheatstone Bridge

Thévenin equivalence is a powerful technique we can use to analyze the Wheatstone bridge circuit shown below. This circuit is used in many sensor applications where resistors  $R_1, R_2, R_3, R_4$  are varying with respect to some external actuation. For example, it can be used to build a strain gauge or a scale (remember Fruity Fred from HW 7). In that case the resistors  $R_1, R_2, R_3, R_4$  would vary with respect to a strain caused by a force, and the Wheatstone Bridge circuit would translate that variation into a voltage difference across the “bridge” terminals  $a$  and  $b$ . Assume that  $R_1 = 2\text{ k}\Omega$ ,  $R_2 = 2\text{ k}\Omega$ ,  $R_3 = 1\text{ k}\Omega$ ,  $R_4 = 4\text{ k}\Omega$



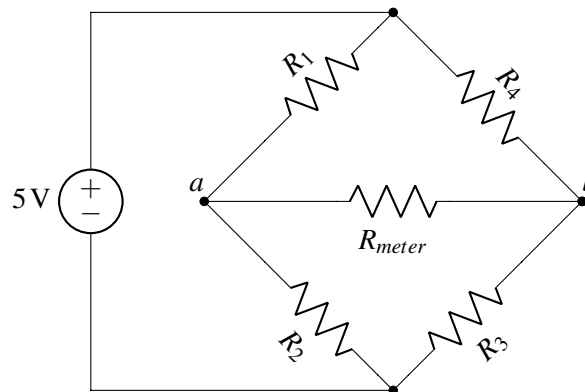- Calculate the voltage  $V_{ab}$  between the two terminals  $a$  and  $b$ .
- Next, draw the Thévenin equivalent of the Wheatstone bridge circuit.
- Now assume that you are trying to measure the voltage  $V_{ab}$  using a voltmeter, whose resistance is  $R_{meter}$ , so you end up with the circuit below.




Unfortunately, your voltmeter is far from ideal, so  $R_{meter} = 4k\Omega$ . Is the voltage  $V_{ab}$  you found in part (a) equal to the new voltage  $V_{R_{meter}}$  across the voltmeter resistor? Why or why not? Calculate the current  $I_{R_{meter}}$  through the voltmeter resistor and the voltage  $V_{R_{meter}}$  across the meter resistor.
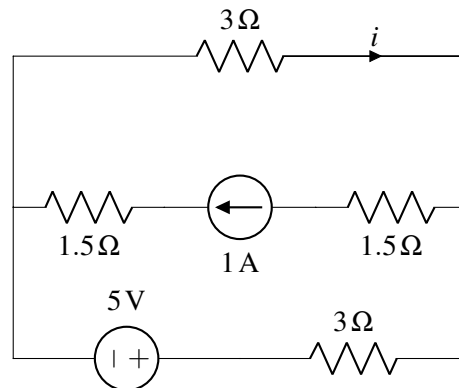
## 6. Superposition

**Learning Goal:** The objective of this problem is to help you practice solving circuits using the principles of superposition.

Find the current  $i$  indicated in the circuit diagram below using superposition.



## 7. Homework Process and Study Group

Who did you work with on this homework? List names and student ID's. (In case you met people at homework party or in office hours, you can also just describe the group.) How did you work on this homework? If you worked in your study group, explain what role each student played for the meetings this week.