

Welcome to EECS 16A!

Designing Information Devices and Systems I

Ana Arias and Miki Lustig



2022



Lecture 10A
Op-amp circuit analysis



Last Lecture...

Toolbox

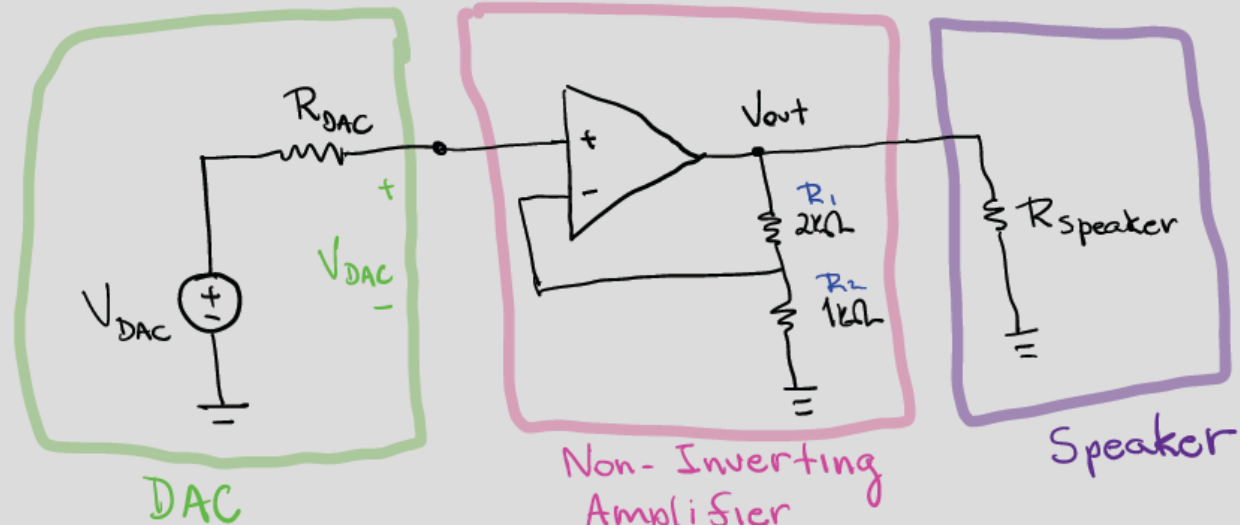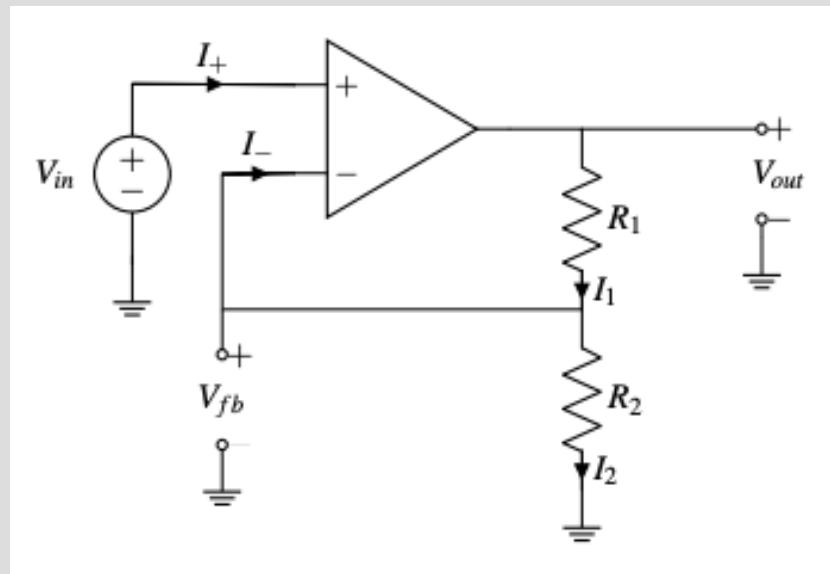- Resistors
- Capacitors
- Open-circuits
- Voltage Dividers/Summers
- Op-Amps
- Thevenin and Norton Equivalence
- KCL/KVL
- Element Definitions
- DAC
- Negative Feedback
- Op-Amp in Negative Feedback
- "Golden Rules" for Op-Amps



GR #1: $I_+ = 0$, $I_- = 0$ no current into OpAmp


GR #2: in negative feedback: $U^+ = U^-$

Non-Inverting Amplifier
(feedback gain = 3)
$$\text{Gain} = 1 + \frac{R_1}{R_2}$$

Party time!
Yay!


Today

Voltage Divider

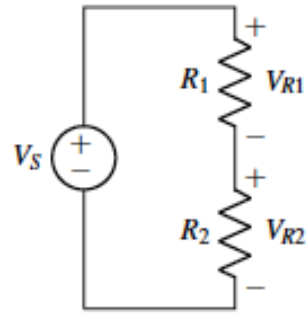


$$V_{R2} = V_S \left(\frac{R_2}{R_1 + R_2} \right)$$

Voltage Summer

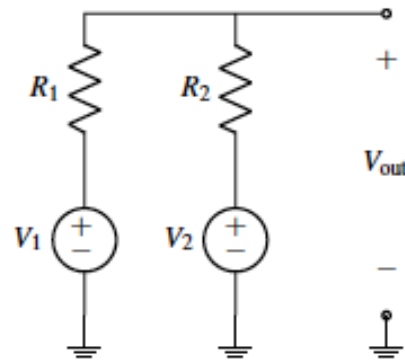


$$V_{out} = V_1 \left(\frac{R_2}{R_1 + R_2} \right) + V_2 \left(\frac{R_1}{R_1 + R_2} \right)$$

Unity Gain Buffer

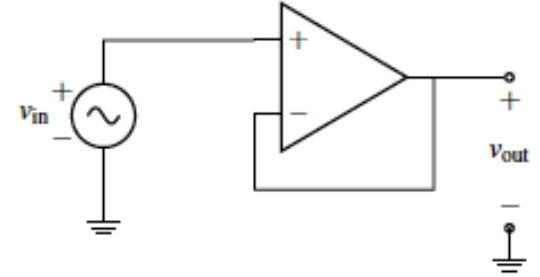


$$\frac{v_{out}}{v_{in}} = 1$$

Inverting Amplifier

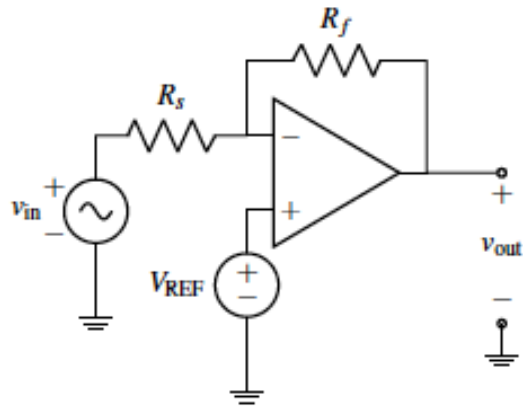


$$v_{out} = v_{in} \left(-\frac{R_f}{R_s} \right) + V_{REF} \left(\frac{R_f}{R_s} + 1 \right)$$

Non-inverting Amplifier

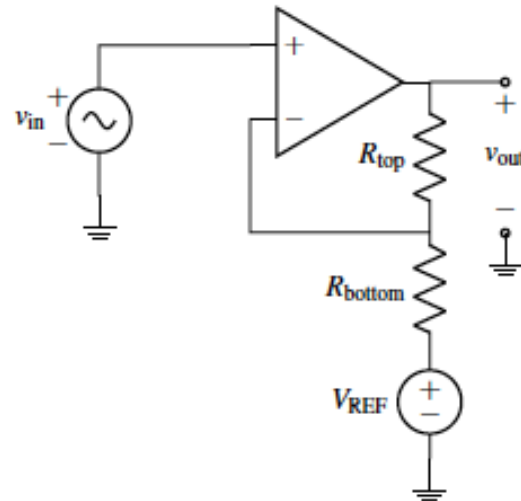

$$v_{out} = v_{in} \left(1 + \frac{R_{top}}{R_{bottom}} \right) - V_{REF} \left(\frac{R_{top}}{R_{bottom}} \right)$$

Transresistance Amplifier

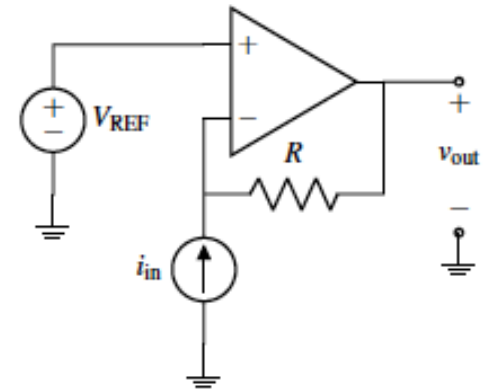

$$v_{out} = i_{in} (-R) + V_{REF}$$


Checking for Negative Feedback

Step 1 – Zero out all independent sources

- replacing voltage sources with wires
- current sources with open circuits as in superposition

Step 2 – Wiggle the output and check the loop – to check how the feedback loop responds to a change.

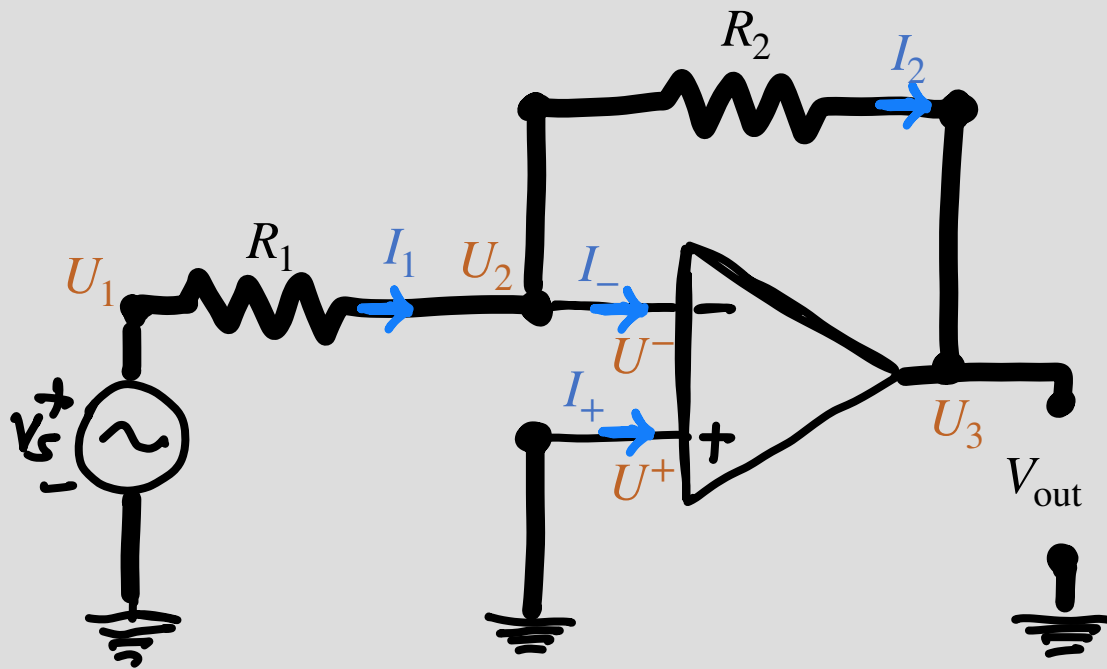- if the $(U^+ - U^-)$ decreases, the output $A(U^+ - U^-)$ must also decrease. **The circuit is in negative feedback**
- if the $(U^+ - U^-)$ increases, the output $A(U^+ - U^-)$ must also increase. **The circuit is in positive feedback**





Checking for Negative Feedback

Step 1 – Zero out all independent sources

- replacing voltage sources with wires
- current sources with open circuits as in superposition

Step 2 – Wiggle the output and check the loop – to check how the feedback loop responds to a change.

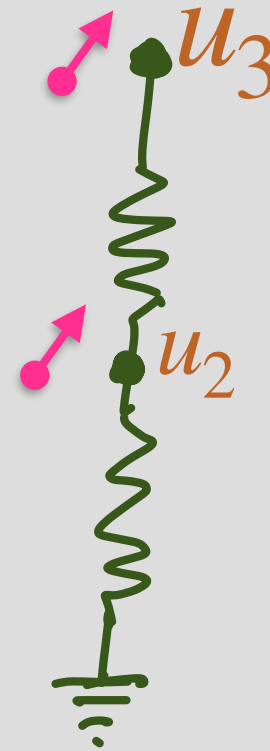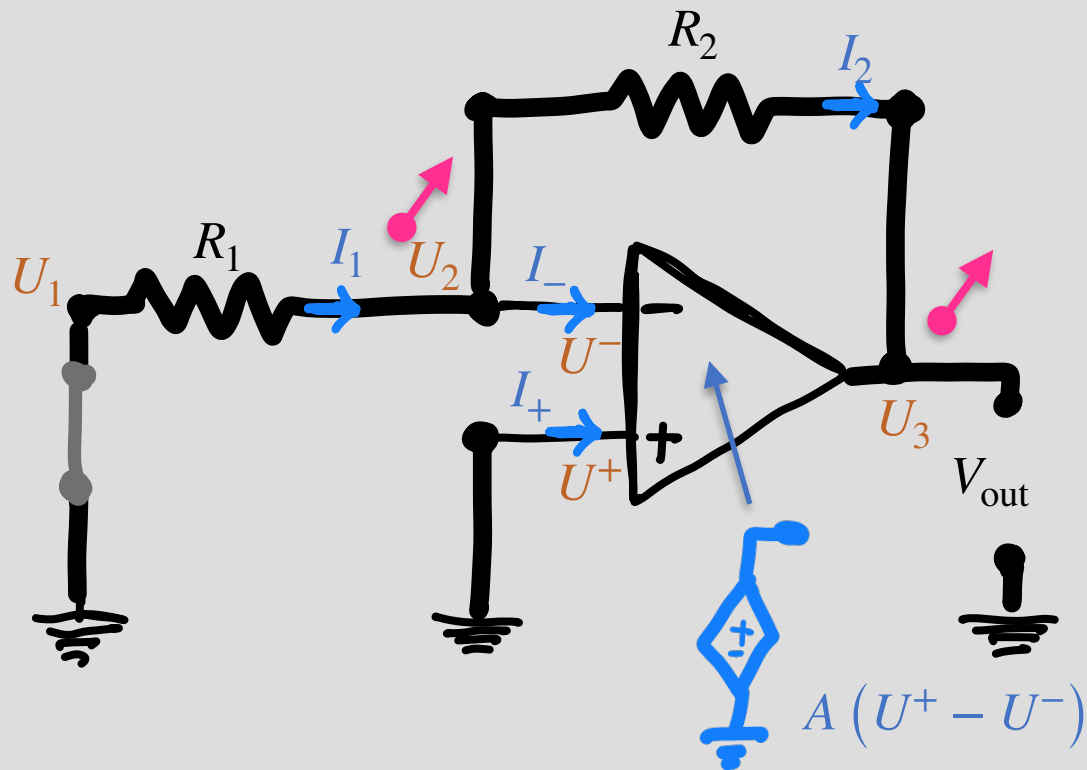
- if the $(U^+ - U^-)$ decreases, the output $A(U^+ - U^-)$ must also decrease. **The circuit is in negative feedback**
- if the $(U^+ - U^-)$ increases, the output $A(U^+ - U^-)$ must also increase. **The circuit is in positive feedback**



$$A (U^+ - U^-) \searrow$$

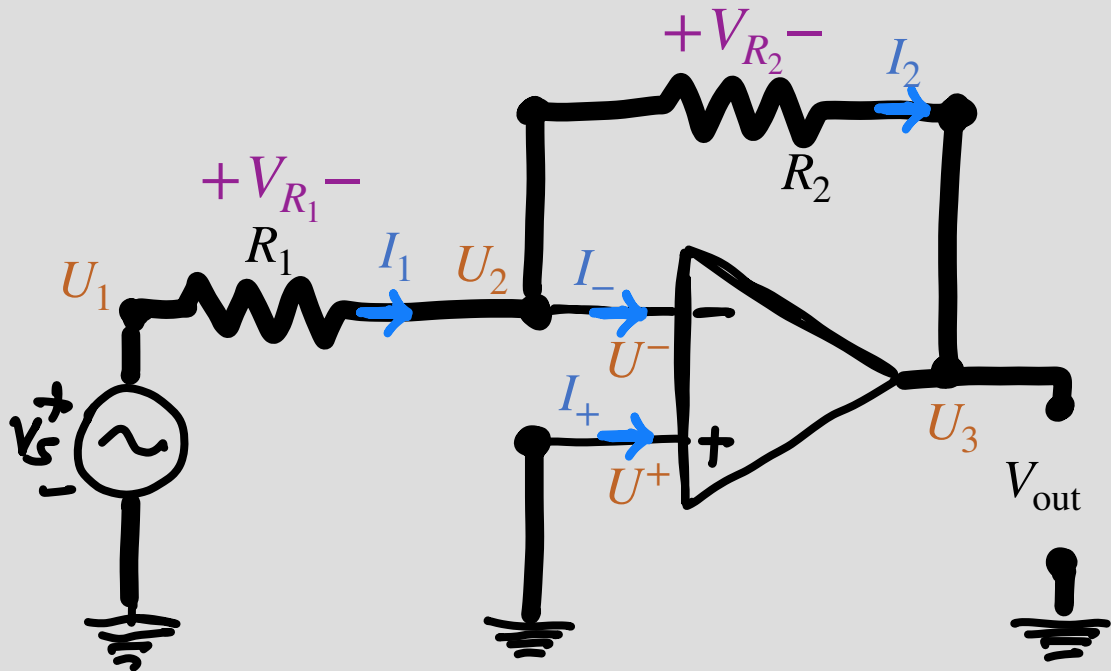Negative feedback
Golden Rule #2 applies!





NFB \Rightarrow Golden Rule #2 $\Rightarrow U^- = U^+$

①

$$U_1 = V_{\text{in}}$$

$$U_3 = V_{\text{out}}$$

$$U_2 = 0$$

$$U_2 = U^- \Rightarrow \text{NFB} \Rightarrow U^- = U^+ = 0$$

②


Element Definitions:

$$V_{R_1} = I_1 R_1$$

$$V_{R_2} = I_2 R_2$$

$$V_{R_1} = U_1 - \cancel{U_2} = V_{\text{in}}$$
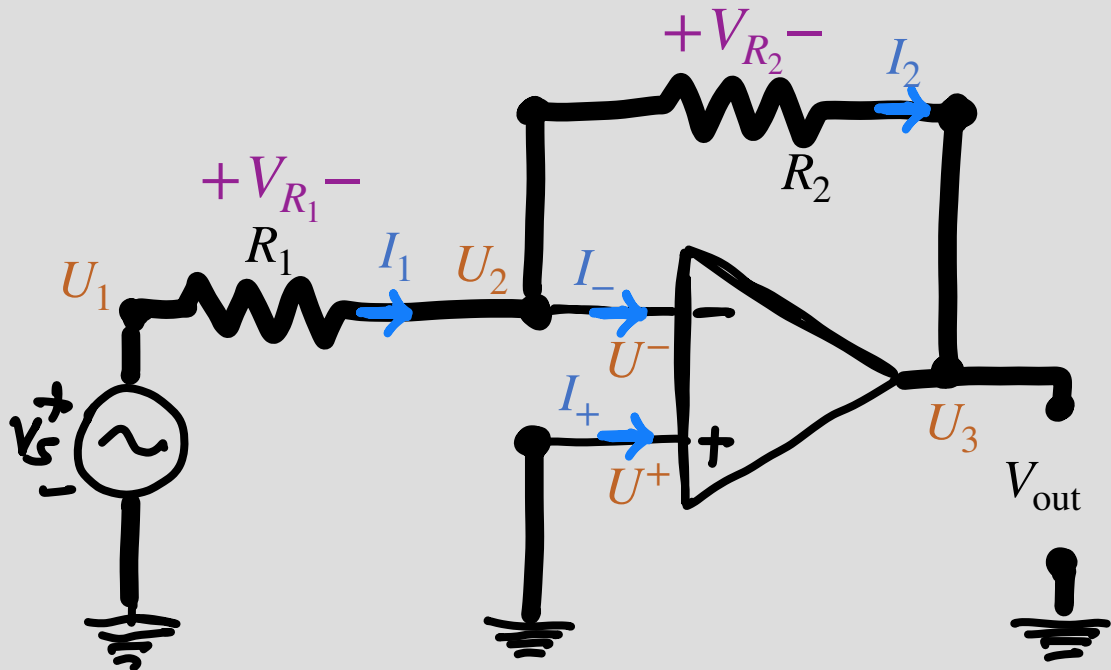
$$V_{R_2} = \cancel{U_2} - U_3 = -V_{\text{out}}$$



NFB \Rightarrow Golden Rule #2 $\Rightarrow U^- = U^+$

①

$$U_1 = V_{in}$$

$$U_3 = V_{out}$$

$$U_2 = 0$$

$$U_2 = U^- \Rightarrow \text{NFB} \Rightarrow U^- = U^+ = 0$$

②

Element Definitions:

$$V_{R_1} = I_1 R_1$$

$$V_{R_2} = I_2 R_2$$


$$V_{R_1} = U_1 - \cancel{U_2} = V_{in}$$

$$V_{R_2} = \cancel{U_2} - U_3 = -V_{out}$$

③

(KCL)
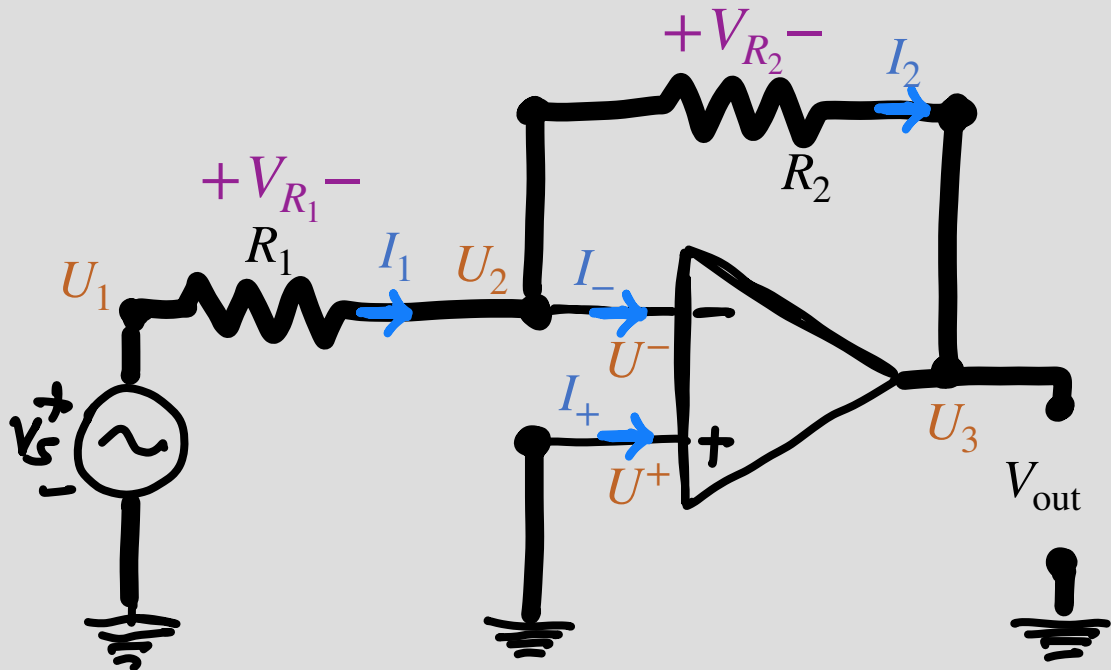
$$I_1 = I_2 + \cancel{I_-} \quad (\text{GR\#1})$$



NFB \Rightarrow Golden Rule #2 $\Rightarrow U^- = U^+$

①

$$U_1 = V_{in}$$

$$U_3 = V_{out}$$

$$U_2 = 0$$

$$U_2 = U^- \Rightarrow \text{NFB} \Rightarrow U^- = U^+ = 0$$

②

Element Definitions:

$$V_{R_1} = I_1 R_1$$

$$V_{R_2} = I_1 R_2$$

$$V_{R_1} = U_1 - \cancel{U_2} = V_{in}$$

$$V_{R_2} = \cancel{U_2} - U_3 = -V_{out}$$

③

(KCL)

$$I_1 = I_2 + \cancel{I_-} \quad (\text{GR\#1})$$

$$V_{in} = I_1 R_1$$

$$V_{out} = -I_2 R_2$$

$$I_2 = I_1$$

$$\frac{V_{out}}{R_2} = \frac{V_{in}}{R_1}$$

$$V_{out} = -\frac{R_2 V_{in}}{R_1}$$

$$A_v = \frac{V_{out}}{V_{in}} = -\frac{R_2}{R_1}$$

Inverting Amplifier!

A faster way...

NFB \Rightarrow Golden Rule #2 $\Rightarrow U^- = U^+$


$$U^+ = 0 \Rightarrow U^- = 0 \Rightarrow U_2 = 0$$

GR #1 + KCL $I_1 = I_2 + I_-$


$$\frac{U_1 - U_2}{R_1} = \frac{U_2 - U_3}{R_2}$$

$$\frac{V_{in}}{R_1} = -\frac{V_{out}}{R_2}$$
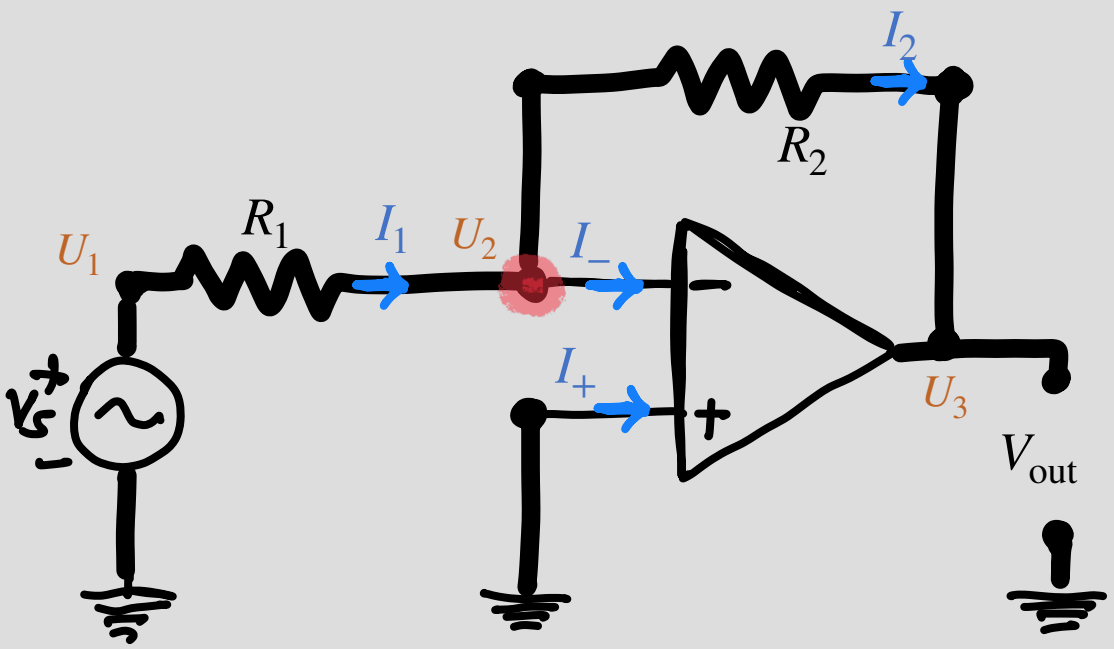
$$\frac{V_{out}}{V_{in}} = -\frac{R_2}{R_1}$$




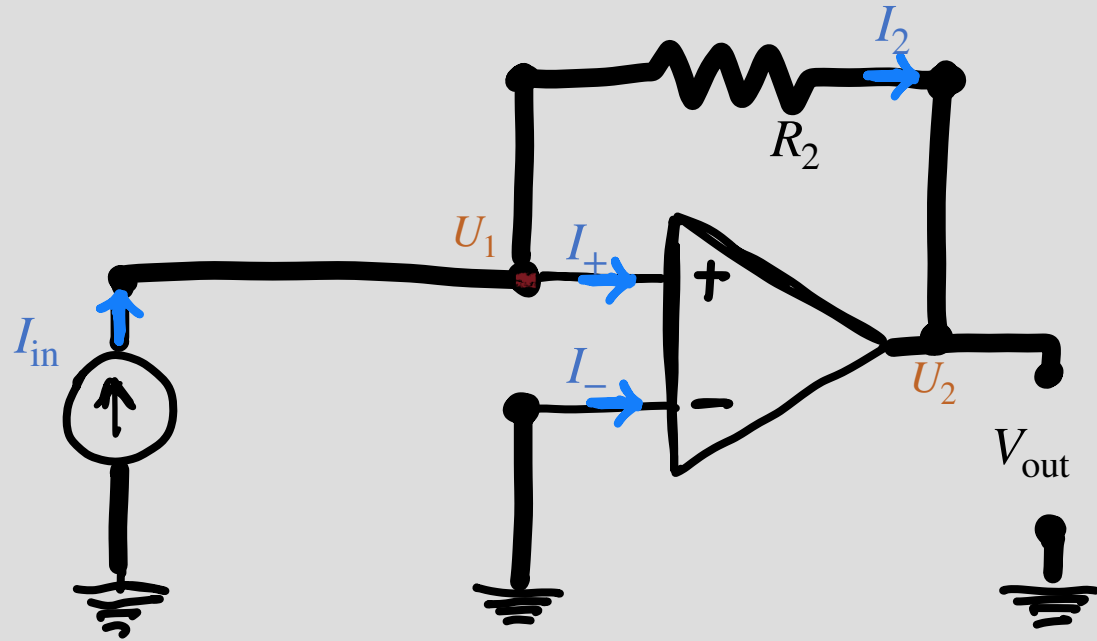Example circuit 2 (trans-resistance amplifier)



① Zero-out independent sources

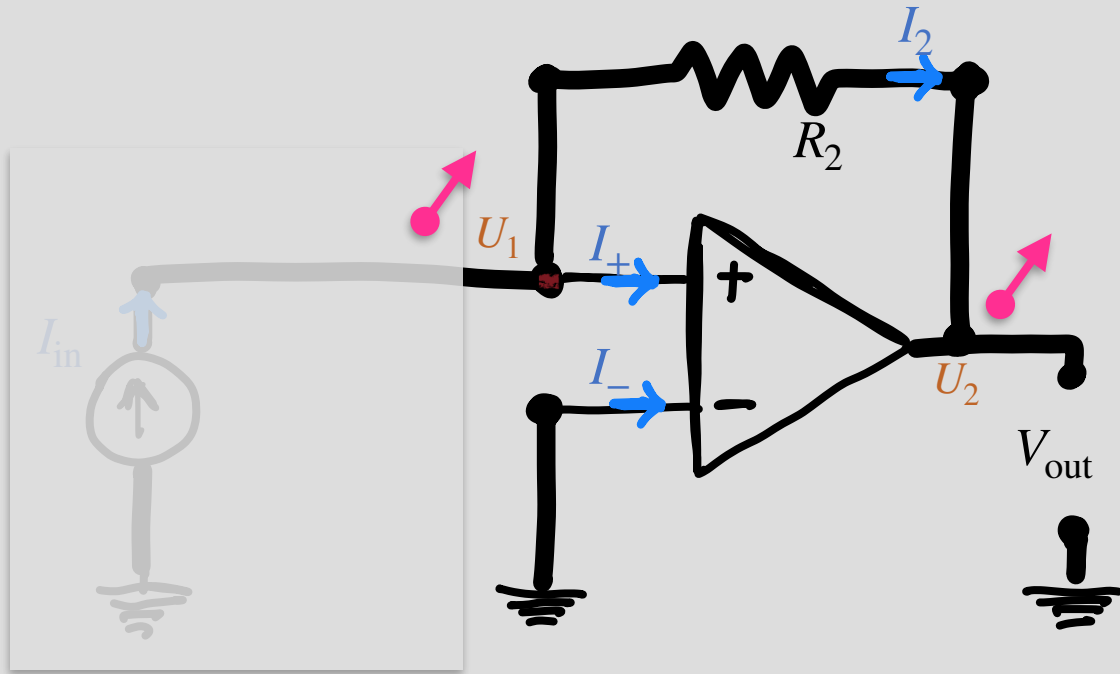Example circuit 2 (trans-resistance amplifier)



① Zero-out independent sources

$$\begin{aligned} \text{From GR \#1: } I_+ = 0 &\Rightarrow I_2 = 0 \\ &\Rightarrow U_2 = U_1 \end{aligned}$$

② Check for negative feedback


$$A (U^+ - U^-)$$

Increasing output, increases U^+ , increases output

Not in Negative feedback



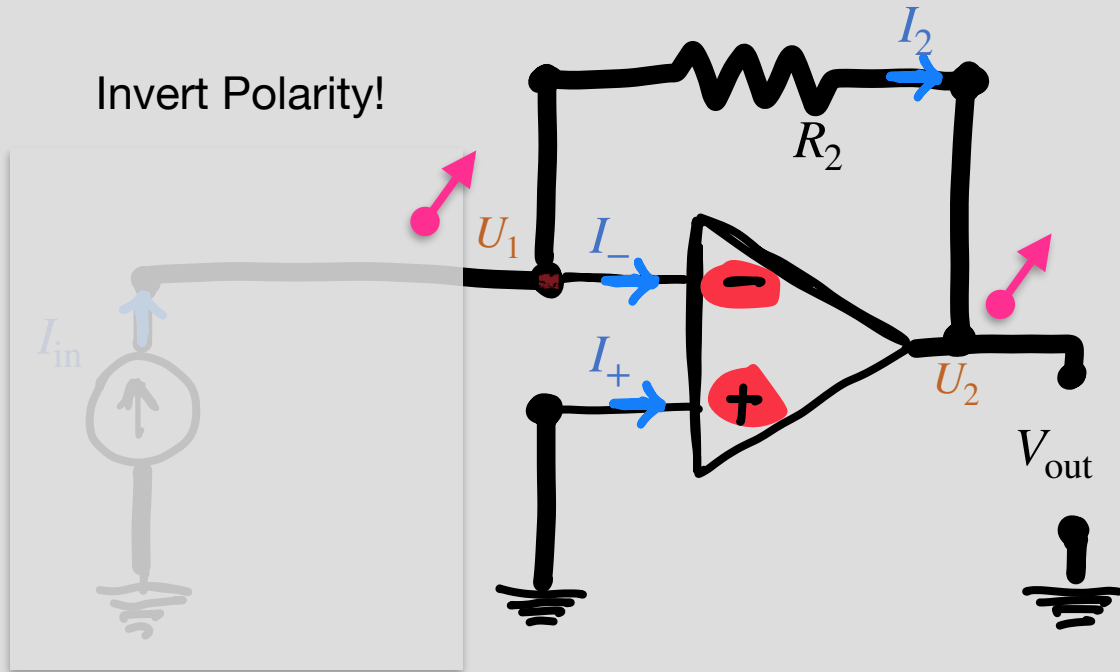Example circuit 2 (trans-resistance amplifier)



① Zero-out independent sources

$$\begin{aligned} \text{From GR \#1: } I_- = 0 &\Rightarrow I_2 = 0 \\ &\Rightarrow U_2 = U_1 \end{aligned}$$

② Check for negative feedback


$$A (U^+ - U^-)$$

Increasing output, increases U^- , decreases output

in Negative feedback



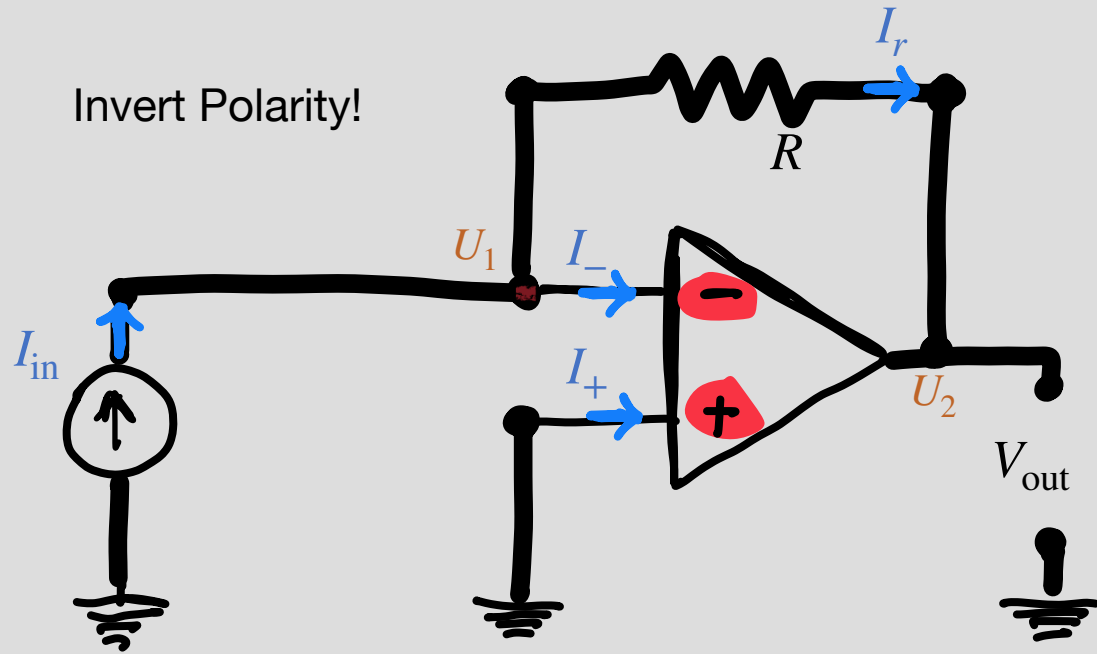Example circuit 2 (trans-resistance amplifier)



NFB \Rightarrow Golden Rule #2 $\Rightarrow U^- = U^+$


$U^+ = 0 \Rightarrow U^- = 0 \Rightarrow U_1 = 0$

Golden Rule #1 & KCL $I_{in} = I_r + I_-$

$$I_{in} = \frac{U_1 - U_2}{R_1}$$


$$V_{out} = -R_1 I_{in}$$

Input current, output is voltage!

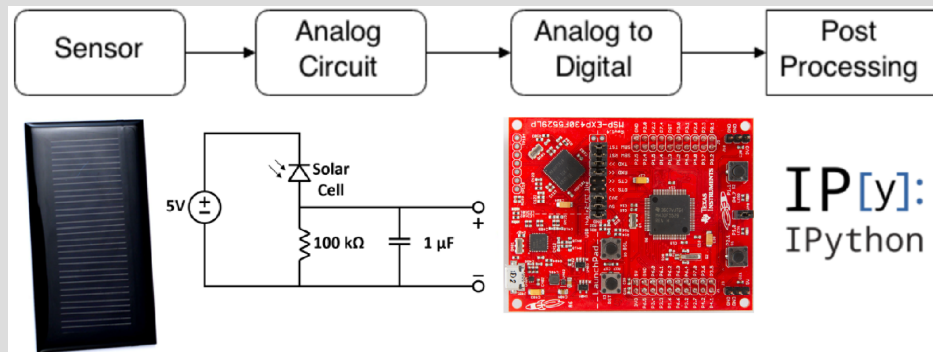


$$\frac{V_{out}}{I_{in}} = -R$$

Example circuit 3 -

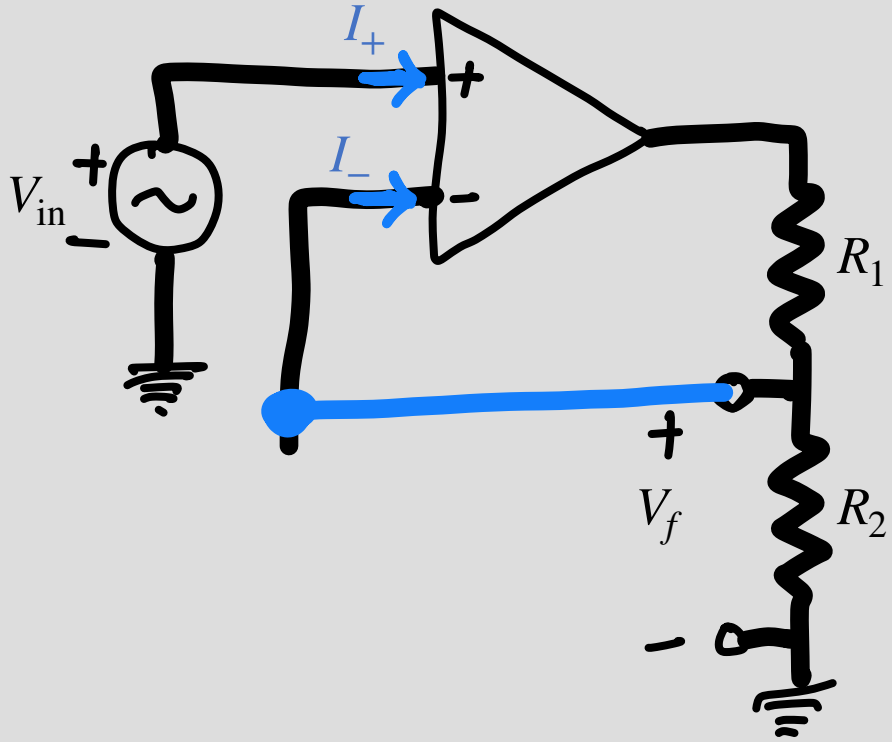


Example circuit 3 -

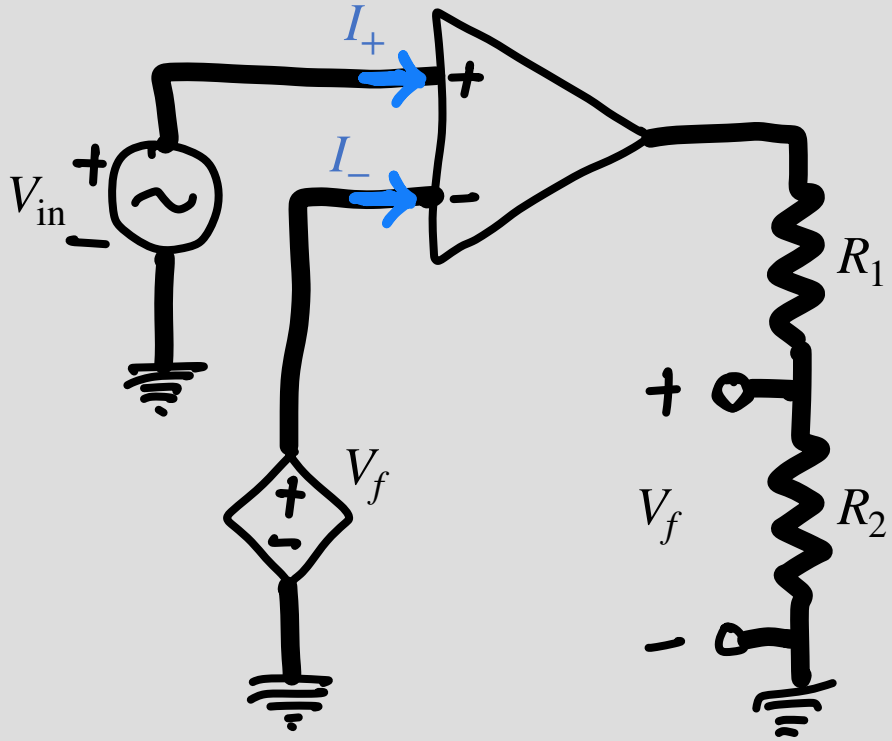


Example circuit 3 -

① Zero-out independent sources

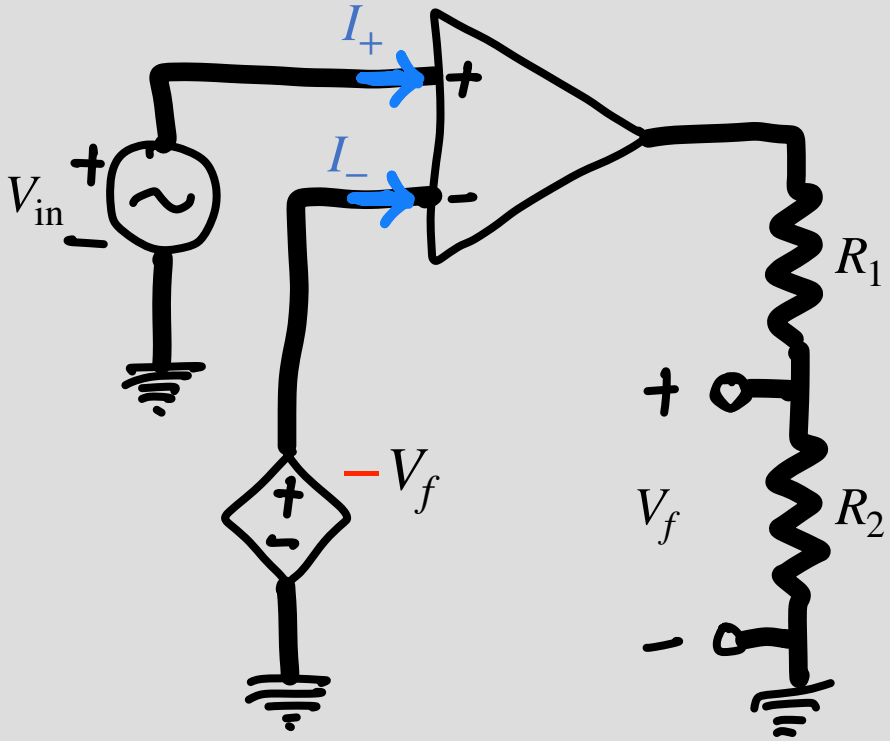

Example circuit 3 -

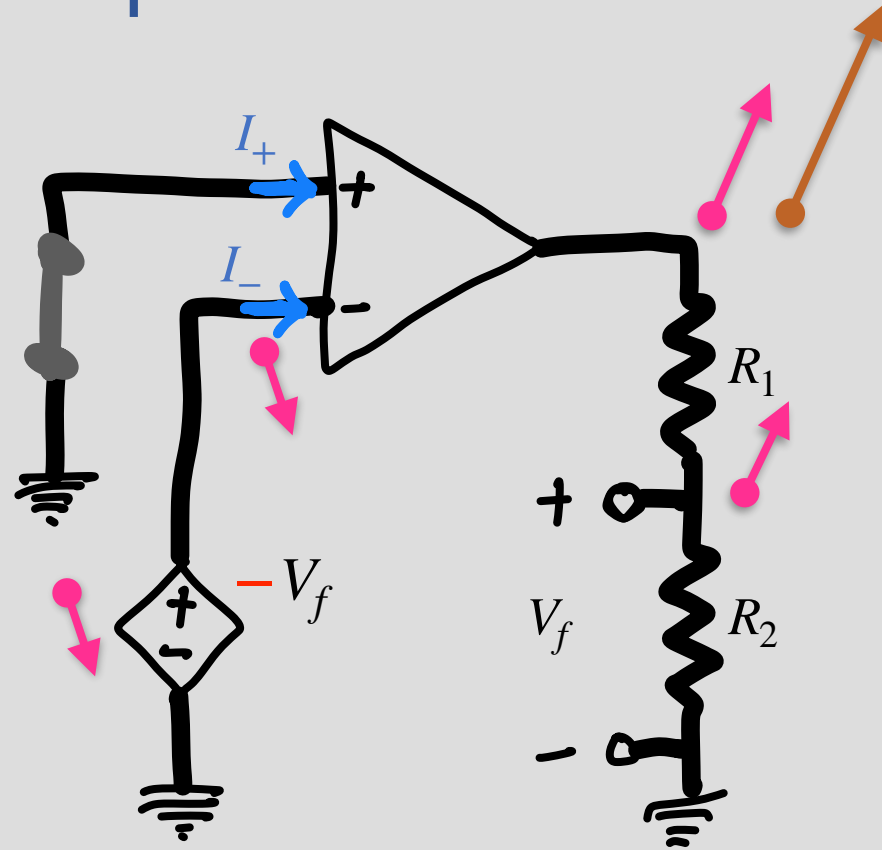

- ① Zero-out independent sources
- ② Check for negative feedback


$$A (U^+ - U^-)$$

Increasing output, decreases U^- , increases output

Not in Negative feedback



Example circuit 3 -

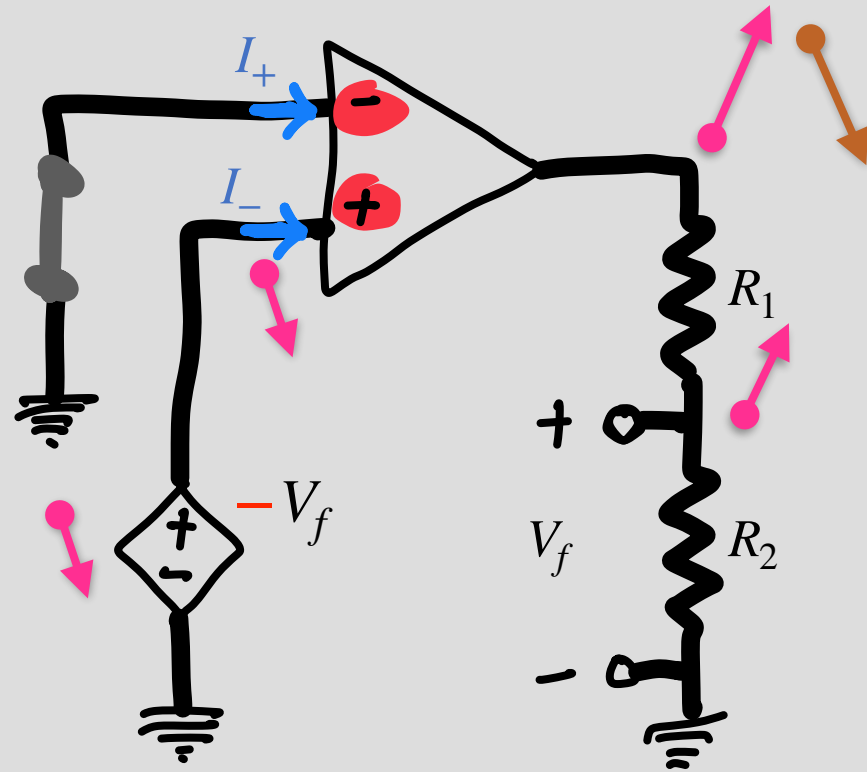

- ① Zero-out independent sources
- ② Check for negative feedback


$$A (U^+ - U^-)$$

Increasing output, decreases U^+ , decreases output

in Negative feedback



Example circuit 3 -

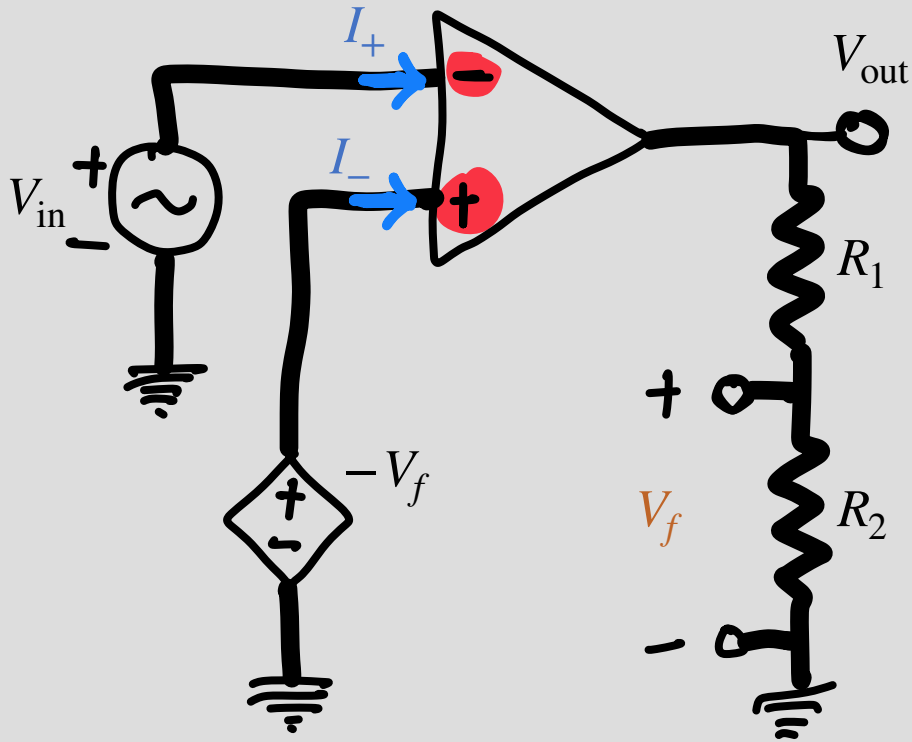

NFB \Rightarrow Golden Rule #2 $\Rightarrow U^- = U^+$

$$\Rightarrow V_{in} = -V_f$$

Voltage divider:

$$V_f = \frac{R_2}{R_1 + R_2} V_{out}$$



$$V_{in} = -\frac{R_2}{R_1 + R_2} V_{out}$$

$$A_v = \frac{V_{out}}{V_{in}} = -\frac{R_1 + R_2}{R_2} = -\left(1 + \frac{R_1}{R_2}\right)$$

Artificial Neuron


- Neurons in our brain are interconnected.
- The output of a single-neuron is dependent on inputs from several other neurons.
- This idea is represented with vector-vector multiplication – the output is a linear combination of several inputs.
- An artificial neuron circuit must perform addition and multiplication.
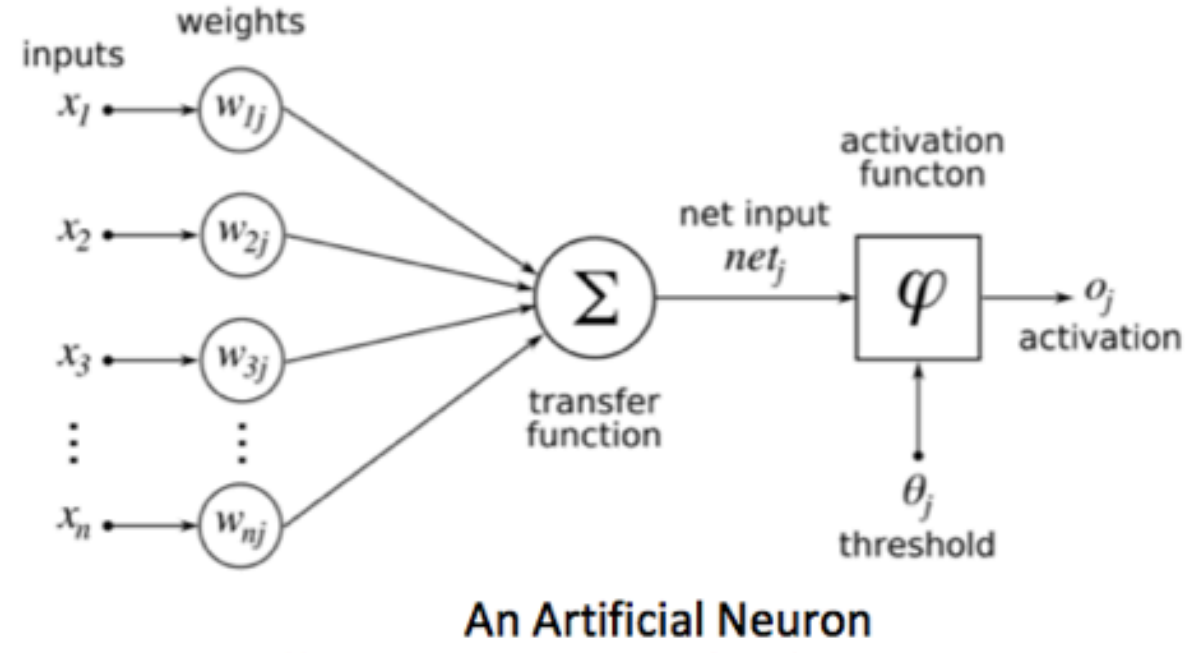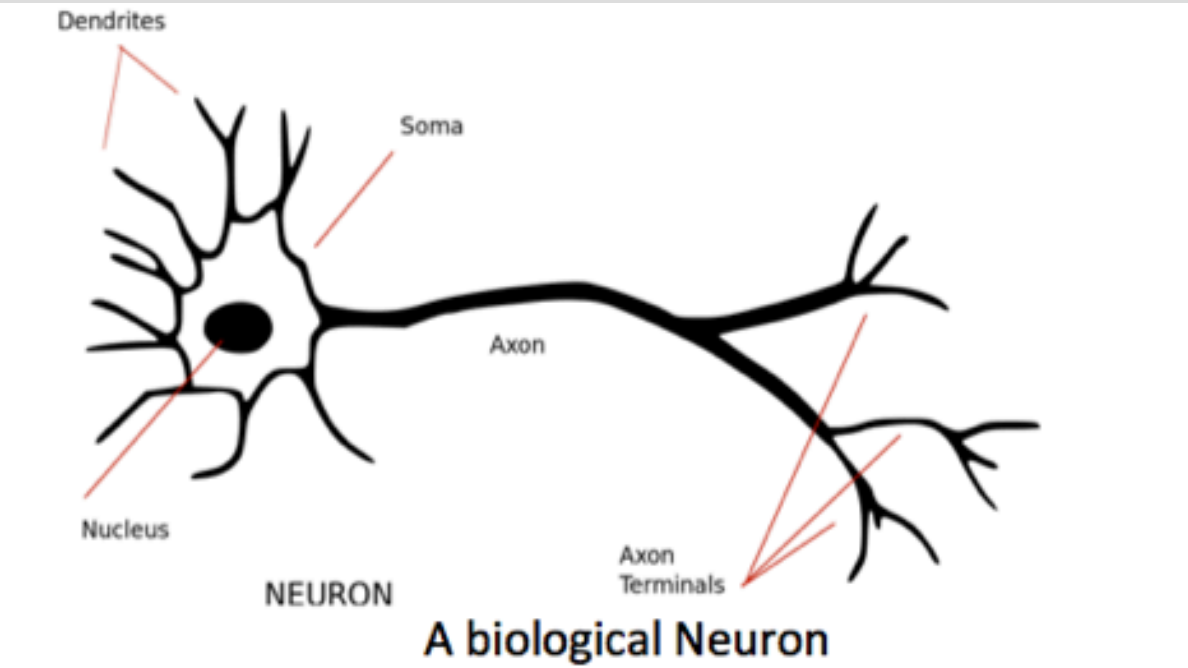
$$\begin{bmatrix} w_{1j} & w_{2j} & \cdots & w_{nj} \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \\ \vdots \\ x_n \end{bmatrix} = \sum_{i=1}^n w_{ij} x_i$$



Artificial Neuron

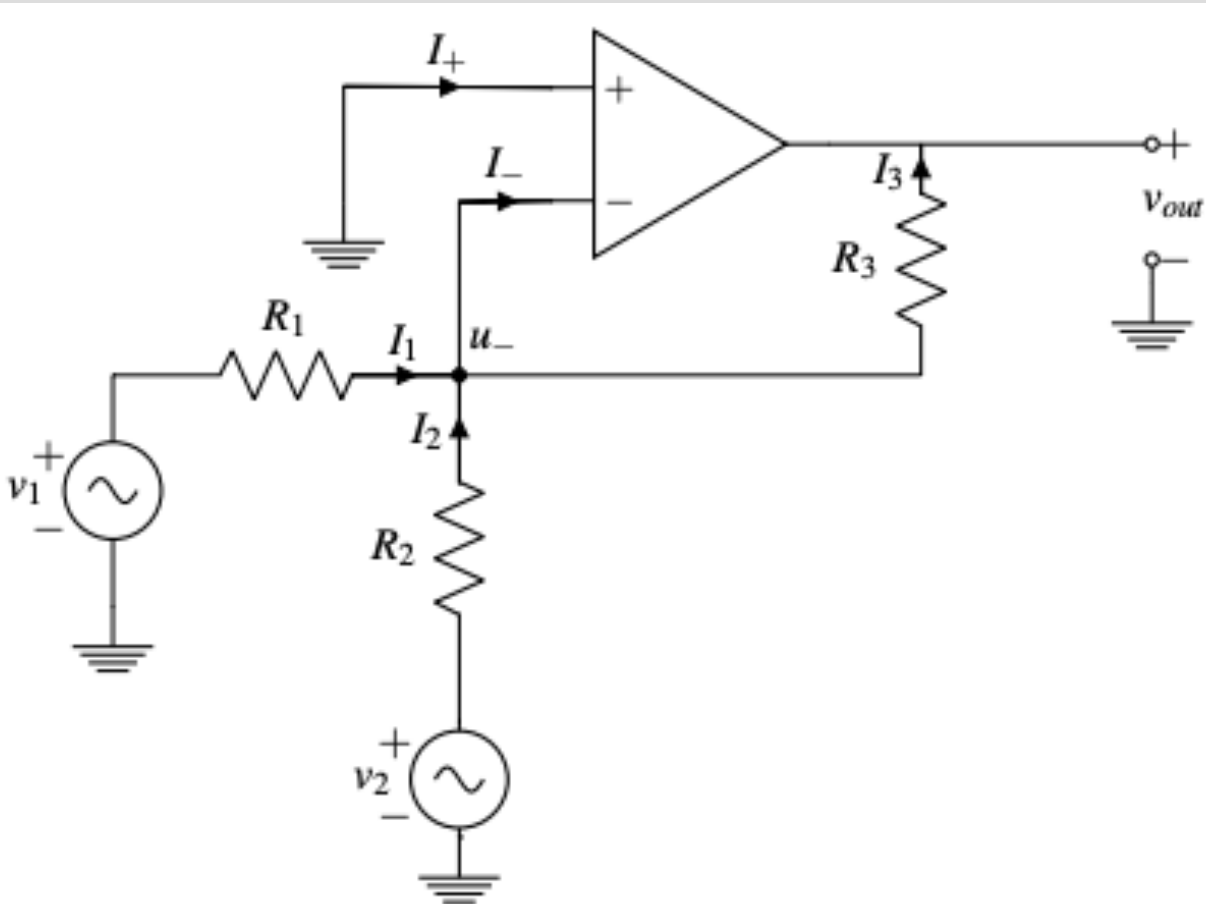
- Neurons in our brain are interconnected.
- The output of a single-neuron is dependent on inputs from several other neurons.
- This idea is represented with vector-vector multiplication – the output is a linear combination of several inputs.
- An artificial neuron circuit must perform addition and multiplication.



① Zero-out independent sources

Artificial Neuron

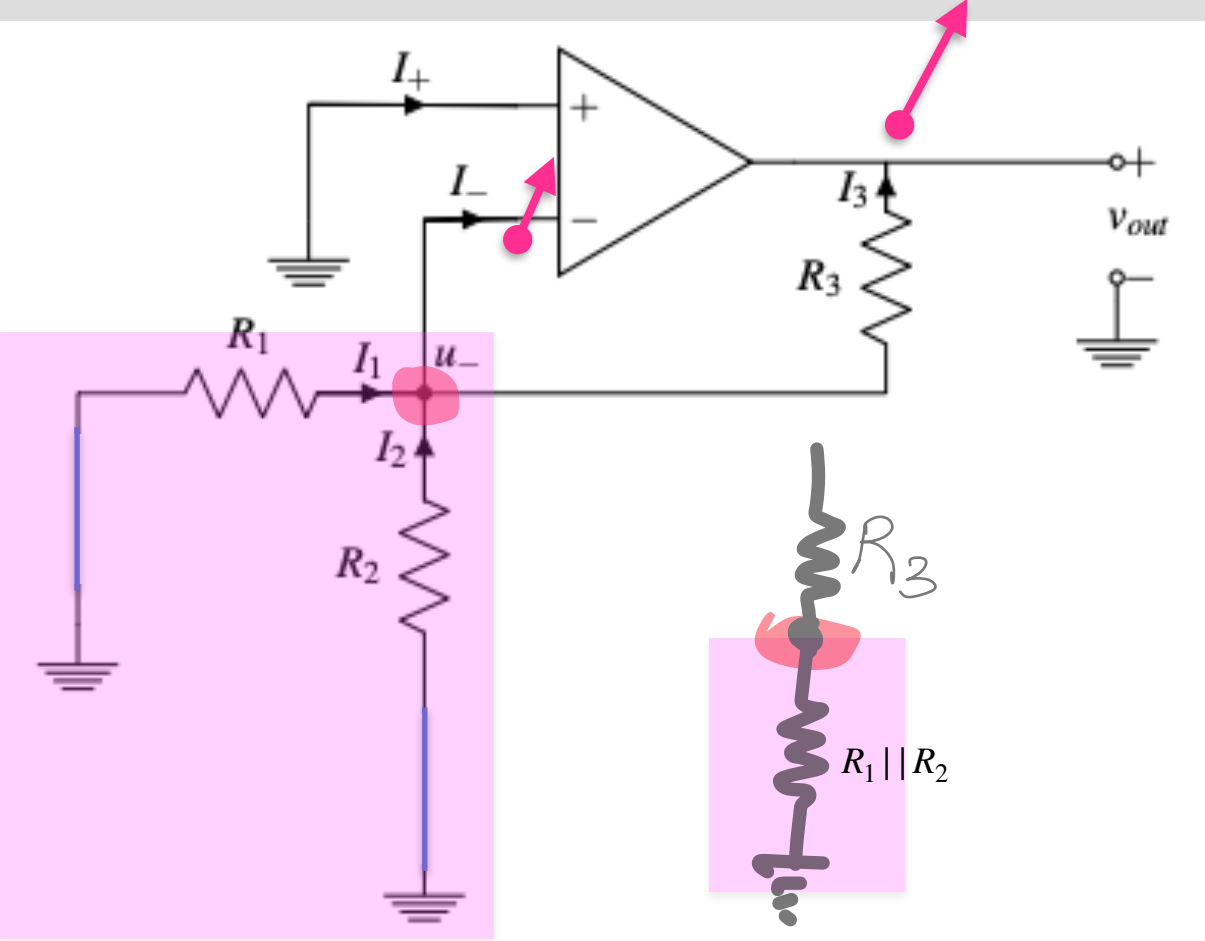- Neurons in our brain are interconnected.
- The output of a single-neuron is dependent on inputs from several other neurons.
- This idea is represented with vector-vector multiplication – the output is a linear combination of several inputs.
- An artificial neuron circuit must perform addition and multiplication.



- ① Zero-out independent sources
- ② Check for negative feedback

$$A (U^+ - U^-)$$


Increasing output, increases U^- , decreases output

in Negative feedback



Artificial Neuron

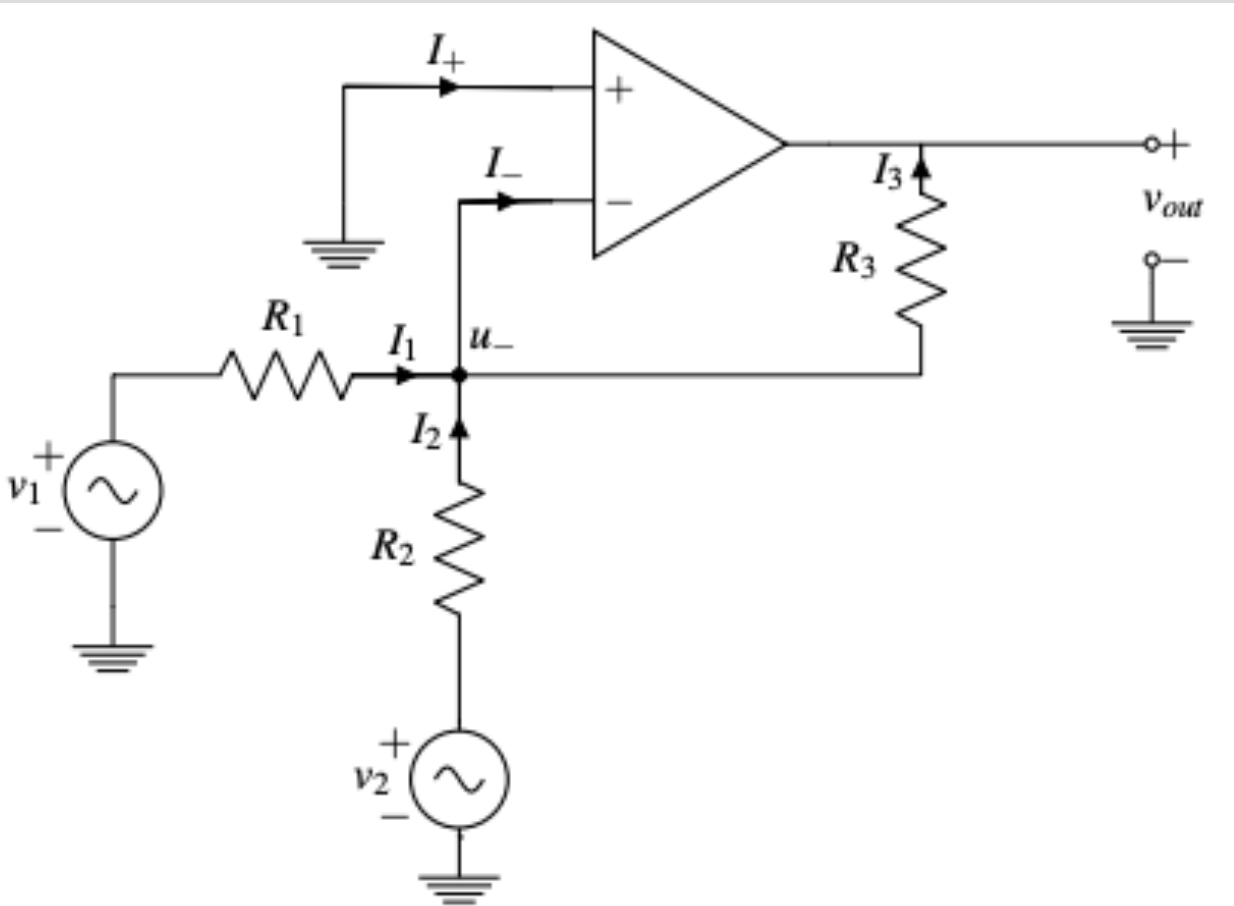- Neurons in our brain are interconnected.
- The output of a single-neuron is dependent on inputs from several other neurons.
- This idea is represented with vector-vector multiplication – the output is a linear combination of several inputs.
- An artificial neuron circuit must perform addition and multiplication.



NFB \Rightarrow Golden Rule #2 $\Rightarrow U^- = U^+$

$U^+ = 0 \Rightarrow U^- = 0$

KCL: $I_1 + I_2 = I_3 + I_-$

$$\frac{\cancel{U^-} - V_1}{R_1} + \frac{\cancel{U^-} - V_2}{R_2} = \frac{V_{out} - \cancel{U^-}}{R_3}$$

$$-\frac{V_1}{R_1} - \frac{V_2}{R_2} = \frac{V_{out}}{R_3}$$

$$V_{out} = -\frac{R_3}{R_1}V_1 - \frac{R_3}{R_2}V_2 \dots - \frac{R_3}{R_i}V_i \dots$$


Artificial Neuron

$$V_{out} = -\frac{R_3}{R_1}V_1 - \frac{R_3}{R_2}V_2 \cdots - \frac{R_3}{R_i}V_i \cdots$$

ω_1 ω_2 ω_i

Q: All weights are negative. How can we change sign?

A: Add an inverting amp circuit?

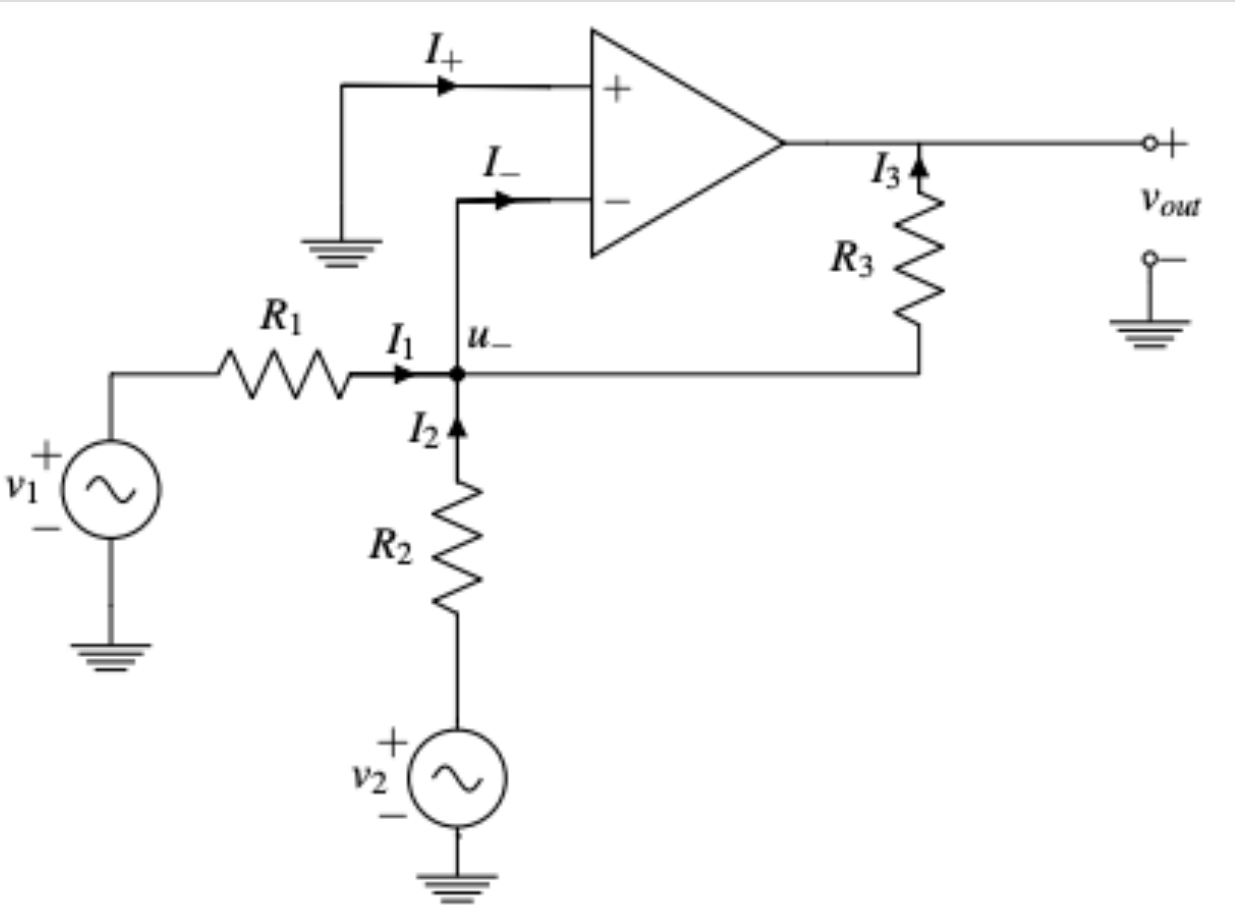


Artificial Neuron

$$V_{out} = -\underbrace{\frac{R_3}{R_1}}_{w_1} V_1 - \underbrace{\frac{R_3}{R_2}}_{w_2} V_2 \dots - \underbrace{\frac{R_3}{R_i}}_{w_i} V_i \dots$$

Q: All weights are negative. How can we change sign?

Q: Can we invert amp circuit?


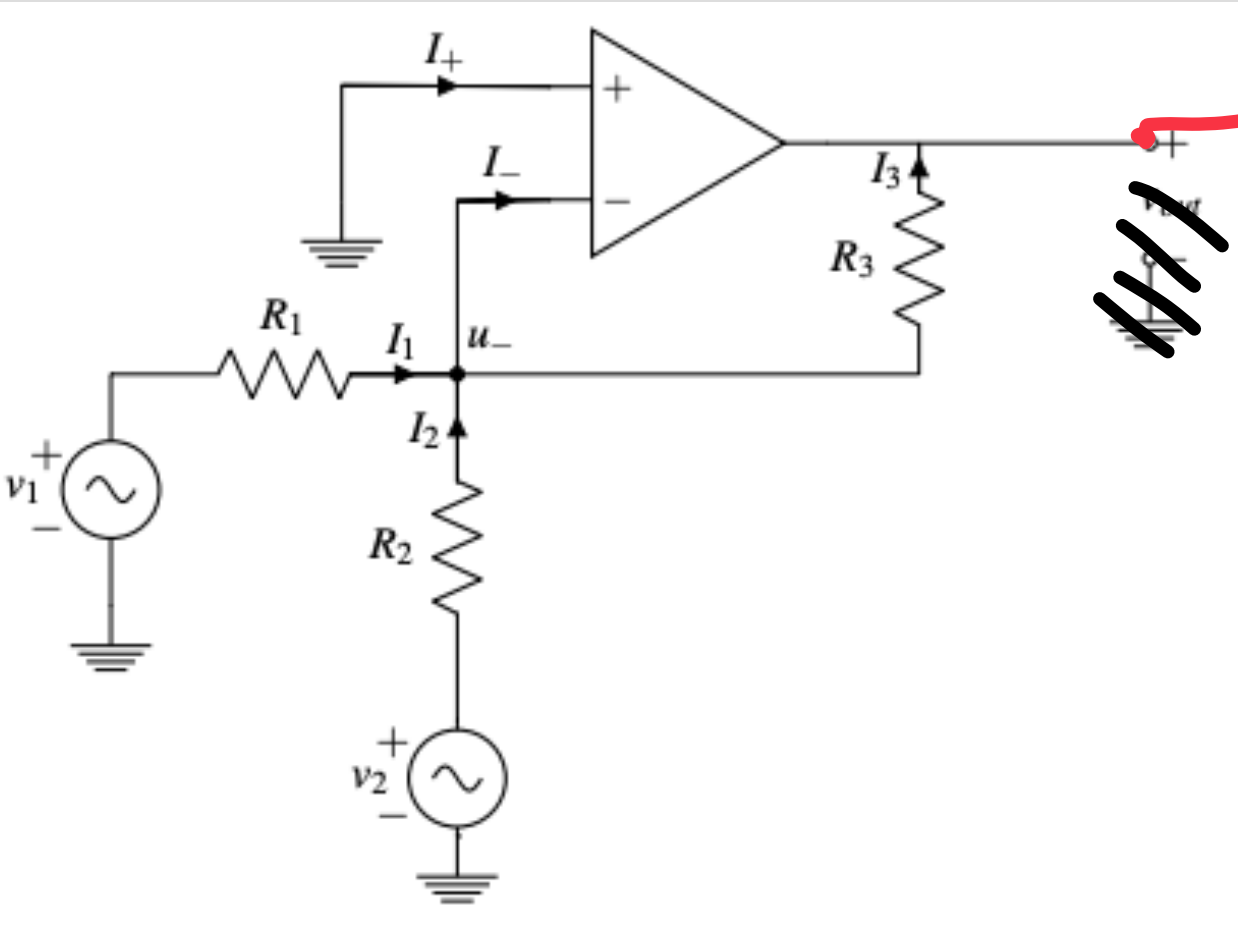


Artificial Neuron

$$V_{out} = - \underbrace{\frac{R_3}{R_1}}_{w_1} V_1 - \underbrace{\frac{R_3}{R_2}}_{w_2} V_2 \dots - \underbrace{\frac{R_3}{R_i}}_{w_i} V_i \dots$$

Q: All weights are negative. How can we change sign?

Q: Can we add an inverting amp circuit?

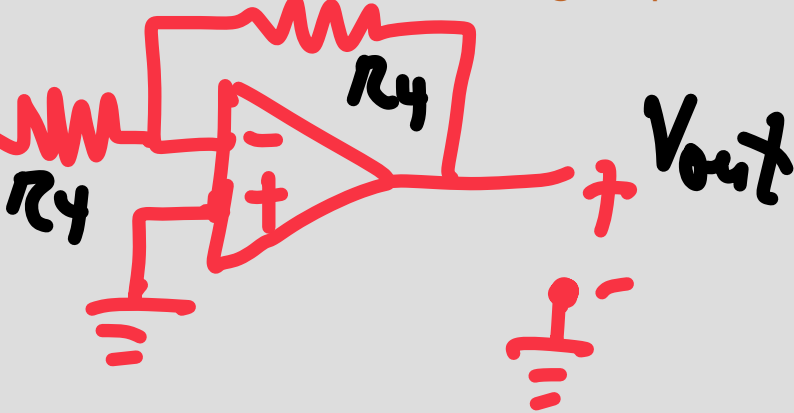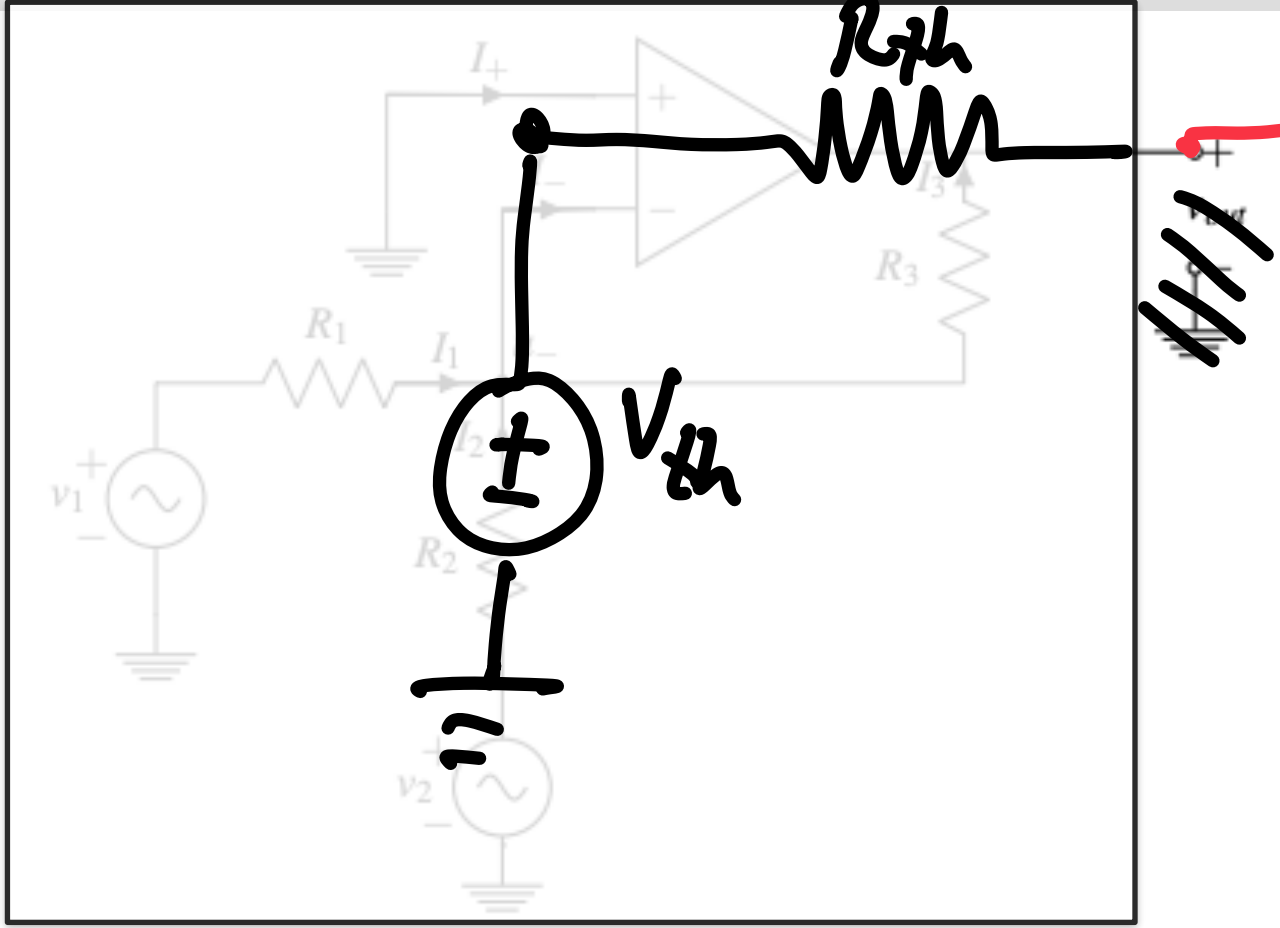

A: Not always.... But perhaps here is OK.

Q: What's the requirement on Rth?


A: Rth = 0?

Artificial Neuron

$$V_{out} = - \underbrace{\frac{R_3}{R_1}}_{w_1} V_1 - \underbrace{\frac{R_3}{R_2}}_{w_2} V_2 \dots - \underbrace{\frac{R_3}{R_i}}_{w_i} V_i \dots$$

Q: All weights are negative. How can we change sign?

Q: Can we add an inverting amp circuit?

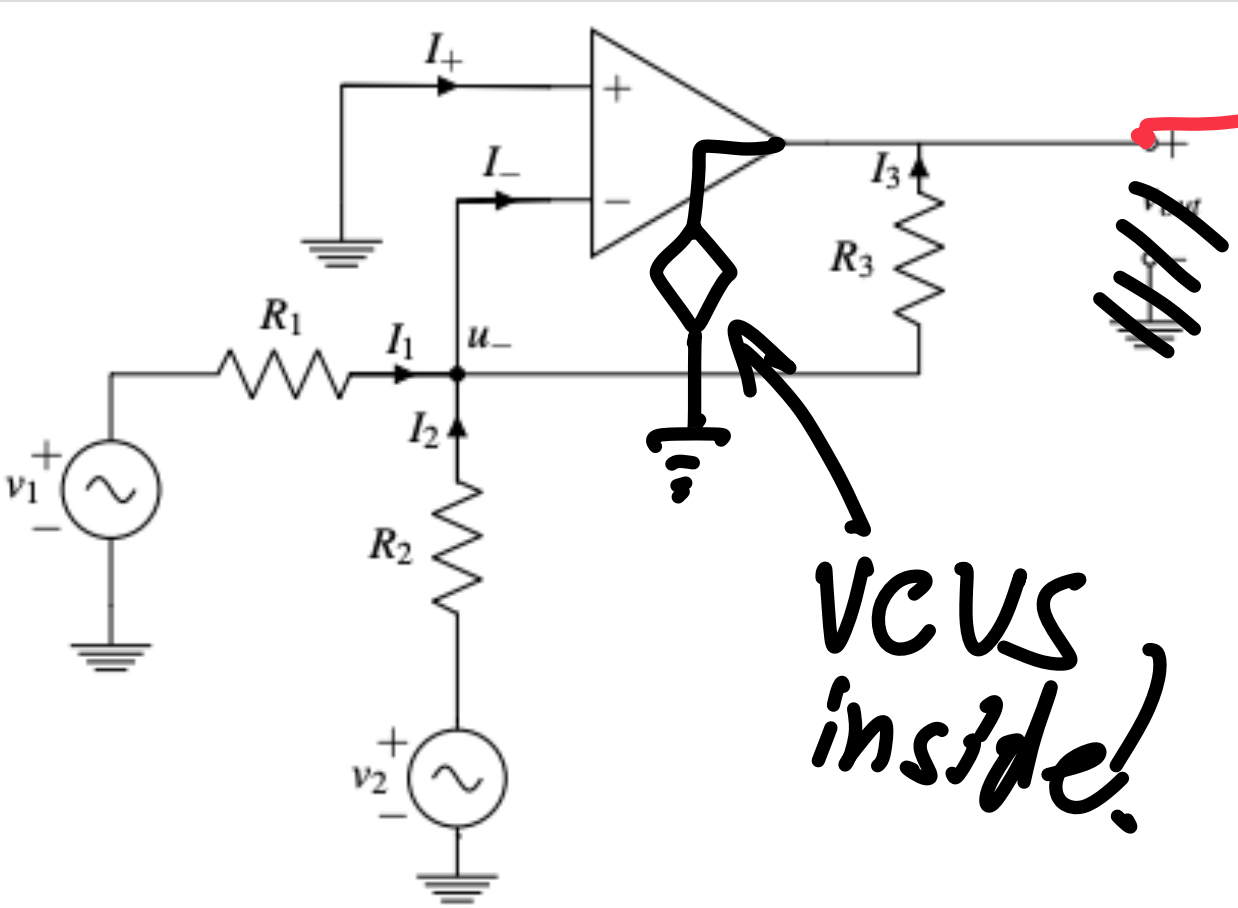

VCVS inside!




A: Not always.... But perhaps here is OK.

Q: What's the requirement on Rth?

A: Rth = 0?


Unity Gain Buffer

- Safely cascading circuit modules

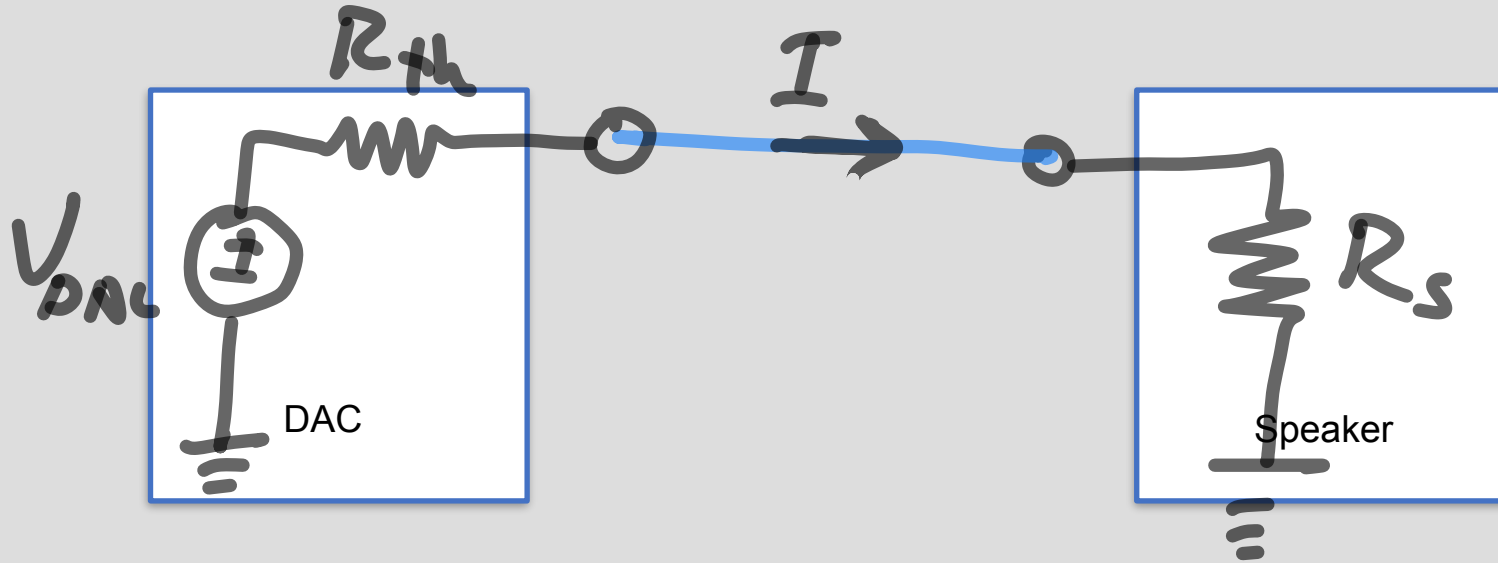



Unity Gain Buffer

- Safely cascading circuit modules

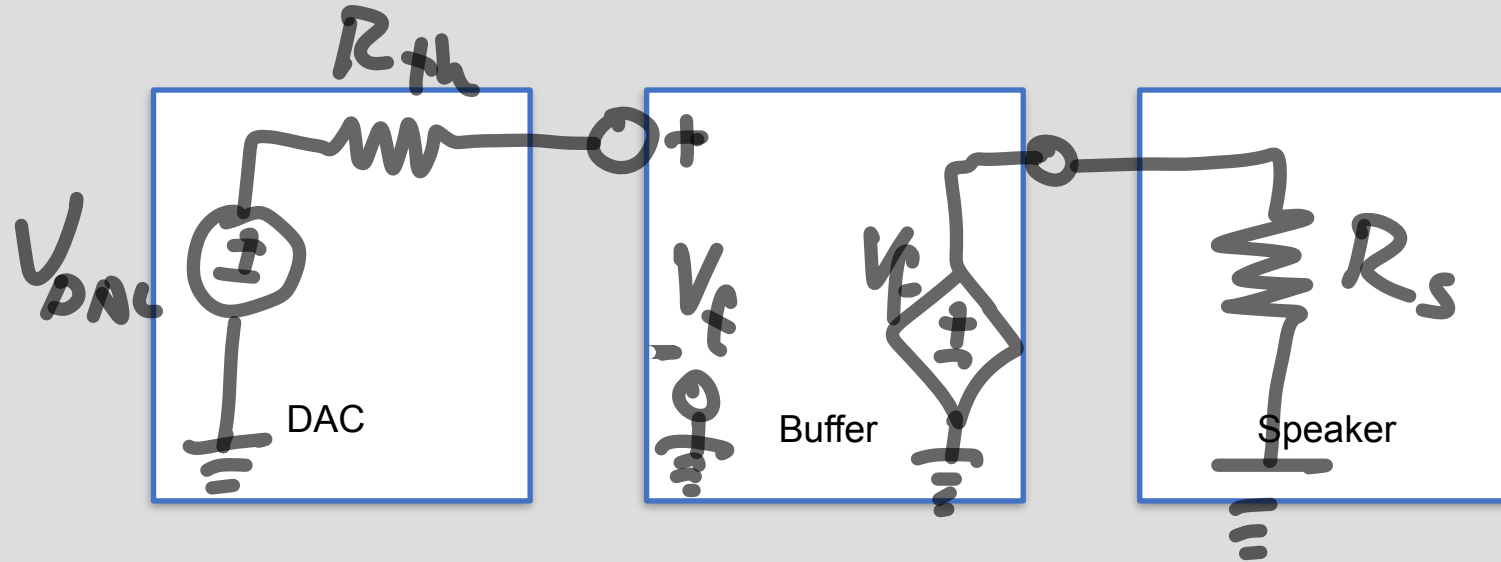

Unity Gain Buffer

- Safely cascading circuit modules

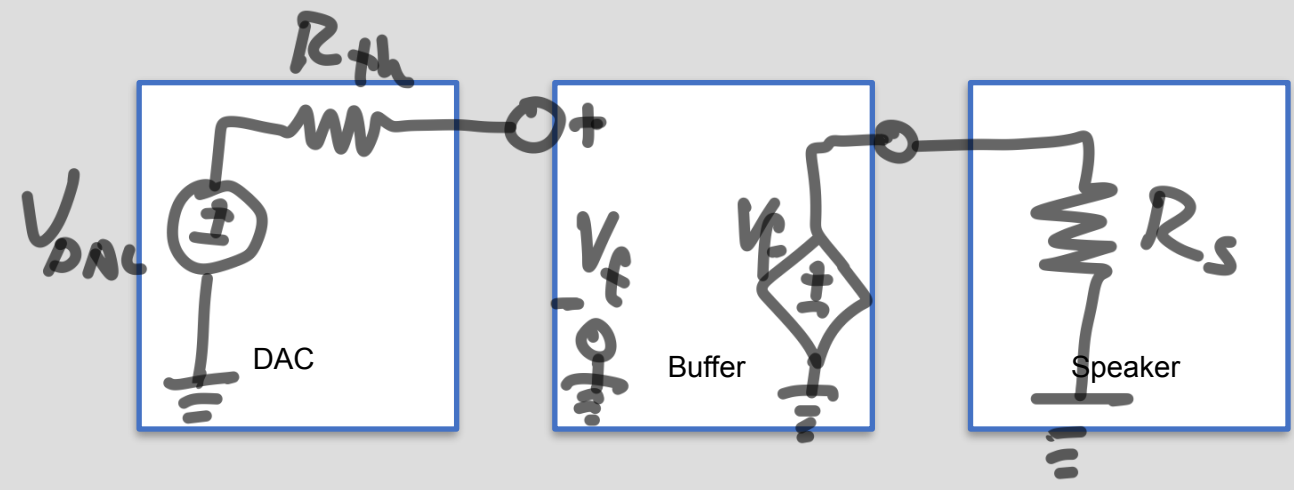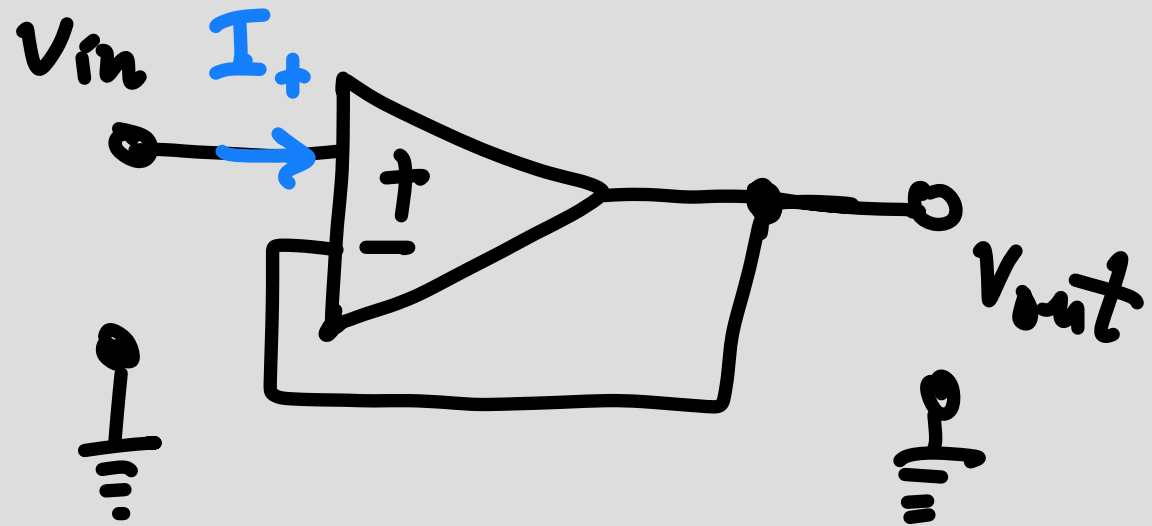

$$U^+ = V_{in}$$

$$U^- = V_{out}$$

NFB \Rightarrow Golden Rule #2 $\Rightarrow U^- = U^+$

$$V_{in} = V_{out}$$